

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascade Amplifier Design

Design 1

Design a two stage RC coupled JFET amplifier to meet the following specifications $|A_V| \geq 160$, $V_{rms} = 3V$, $R_i \geq 1M\Omega$.

Solution:

1) Selection of JFET:

For above requirement, we can select JFET BFW 11 transistor from the data sheet with the following specifications:

$$V_P = -2.5V, r_d = 50\Omega, I_{DSS} = 7mA \text{ \& } g_{mo} = 5600\mu S$$

 


Figure 1: Circuit for Design 1

2) Selection of voltage gain:

$$A_V \geq 160 \quad (\text{Given})$$

$$\text{Let } A_V = 180$$

$$\text{Also let } A_{V_1} = 0.6A_{V_2}$$

$$A_V = A_{V_1} \times A_{V_2}$$

$$180 = 0.6A_{V_2}^2$$

$$A_{V_2} = \frac{180}{0.6}$$

$$A_{V_2} = 17.32$$

$$A_{V_1} = 0.6 \times A_{V_2}$$

$$A_{V_1} = 10.39$$

$$\text{Gain of 2nd Stage: } A_{V_2} = 18$$

$$\text{Gain of 1st Stage: } A_{V_2} = 11$$

3) Calculation of V_{GS} & I_D :

Using mid point biasing technique:

i) Calculation of I_D

$$\text{For mid point biasing, } I_D = \frac{I_{DSS}}{2}$$

$$\text{i.e. } I_D = \frac{7mA}{2}$$

$$\therefore I_D = 3.5mA$$

ii) Calculation of V_{GS}

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\text{i.e. } V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) = -2.5 \left(1 - \sqrt{\frac{3.5}{7}}\right)$$

$$V_{GS} = -0.732V$$

iii) Calculation of g_m

$$g_m = g_{m1} = g_{m2} = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right) = 5600 \times 10^{-6} \left(1 - \frac{(-0.732)}{(-2.5)}\right)$$

$$\therefore g_m = 3.9603m\Omega$$

4) Selection of R_{D2} :

$$|A_V| = g_{m2}(r_{d2} \parallel R_{D2})$$

.....(1)

$$r_{d1} = r_{d2} = r_d = 50k\Omega$$

$$g_m = g_{m1} = g_{m2} = 3.9603m\Omega$$

From (1) we get,

$$\frac{18}{3.9603m} = \frac{R_{D2} \times 50k}{R_{D2} + 50k}$$

$$R_{D2} = 4.995k \approx 5k$$

Select $R_{D2} = 5.1k\Omega_{(std)}, 1/4W \dots (HSV)$

5) Calculation of R_{S2} :

$$V_{GSQ} = -I_{DQ}R_{S_2}$$

$$R_{S_2} = \frac{-V_{GSQ}}{I_{DQ}} = \frac{-(-0.732)}{3.5mA}$$

$$\therefore R_{S_2} = 209\Omega$$

Select $R_{S_2} = 180\Omega_{(std)}, 1/4W.....(LSV)$

6) Selection of R_{G_2} :

To prevent loading for the 1st Stage

Select $R_G = 1M\Omega_{(std)}, 1/4W$

7) Selection of V_{DD} :

$$V_{DSQ} \geq V_{o_{peak}} + |V_P|.....(\text{Condition for undistorted output})$$

$$V_{DSQ_2} = 1.5(V_{o_{peak}} + |V_P|)$$

$$V_{DSQ_2} = 1.5(V_{o_{peak}} + 2.5)$$

The value is multiplied by 1.5 to take care of saturation voltages, tolerance in resistance value, variation in supply voltage and device parameter variation.

$$V_{rms} = 3V$$

$$\therefore V_{o_{peak}} = 3\sqrt{2}$$

$$\text{i.e. } V_{DSQ_2} = 1.5(2.5\sqrt{2} + 2.5) = 10.05V \approx 10.1V$$

Applying KVL to the JFET-2 D-S loop we get,

$$V_{DD} - I_{DQ_2}R_{D_2} - V_{DSQ_2} - I_{DQ_2}R_{S_2} = 0$$

$$V_{DD} = V_{DSQ_2} + I_{DQ_2}(R_{D_2} + R_{S_2})$$

$$V_{DD} = 10.1 + 3.5 \times 10^{-3}(0.18k + 5.1k)$$

$$\therefore V_{DD} = 28.58V$$

Select $V_{DD} = 30V$

8) Selection of R_{D_1} :

$$|A_{V_2}| = g_{m_2}(r_{d_2} \parallel R_{D_2})$$

$$|A_{V_2}| = 3.9603 \times 10^{-3}(50k \parallel 5.1k)$$

$$|A_{V_2}| = 18.3281$$

$$|A_{V_1}| = \frac{A_V}{|A_{V_2}|} = \frac{180}{18.3281}$$

$$|A_{V_1}| = 9.82$$

$$\text{let } |A_{V_1}| = 10$$

$$|A_{V_1}| = g_{m_1}(r_{d_1} \parallel R_{D_1} \parallel R_{G_2})$$

$$10 = 3.9603 \times 10^{-3}(50k \parallel R_{D_1} \parallel 1M)$$

$$R_{D_1} = 2.665k\Omega$$

Select $R_{D_1} = 3.3k\Omega_{(std)}, 1/4W.....(HSV)$

9) Calculation of R_{S_1} :

$$V_{GSQ} = -I_{DQ}R_{S_1}$$

$$R_{S_1} = \frac{-V_{GSQ}}{I_{DQ}} = \frac{-(-0.732)}{3.5mA}$$

$$\therefore R_{S_1} = 209\Omega$$

Select $R_{S_1} = 180\Omega_{(std)}, 1/4W.....(LSV)$

10) Selection of C_{C_1} :

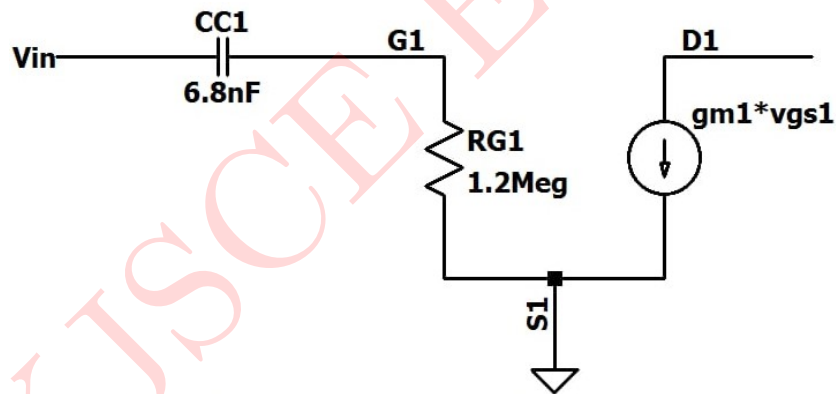


Figure 2: Small Signal Equivalent Circuit for C_{C_1}

$$C_{C_1} = \frac{1}{2\pi f_{L_{C_{C_1}}} R_{eq}}$$

$$f_{C_{C_1}} = f_L = 20Hz$$

$$R_{eq} = R_{G_1} = 1.2M\Omega$$

$$C_{C_1} = \frac{1}{2\pi \times 20 \times 1.2M\Omega} = 6.63nF$$

Select $C_{C_1} = 6.8nF/60V....(H.S.V)$

11) Selection of C_{C_2} :

$$C_{C_2} = \frac{1}{2\pi f_{L_{C_{C_2}}} R_{eq}}$$

$$f_{L_{C_{C_2}}} = f_L = 20Hz$$

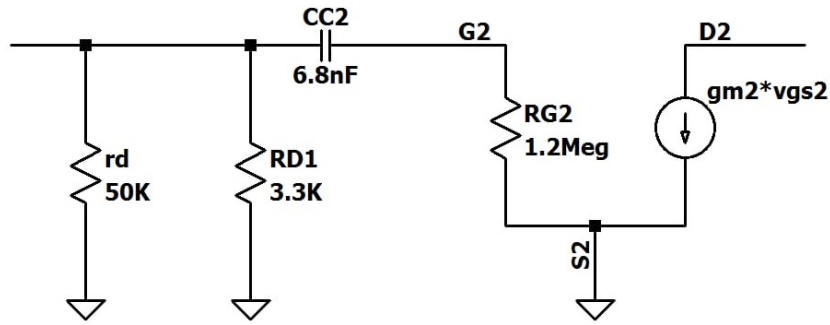


Figure 3: Small Signal Equivalent Circuit for C_{C2}

$$R_{eq} = r_{d1} || R_{D1} + R_{G2}$$

$$R_{eq} = 50k || 4.7k + 1M\Omega$$

$$R_{eq} = 4.296k + 1M\Omega = 1.0043M\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 20 \times 1.0043M\Omega}$$

$$C_{C2} = 7.92nF$$

Select $C_{C2} = 8.2nF/60V.....(H.S.V)$

12) Selection of C_{C3} :

 


Figure 4: Small Signal Equivalent Circuit for C_{C3}

$$C_{C3} = \frac{1}{2\pi f_{L_{CC3}} R_{eq}}$$

$$f_{L_{CC3}} = f_L = 20Hz$$

$$R_{eq} = r_{d2} || R_{D2}$$

$$R_{eq} = 50k || 5.1k$$

$$R_{eq} = 4.6279k\Omega$$

$$C_{C3} = \frac{1}{2\pi \times 20 \times 4.6279k\Omega}$$

$$C_{C3} = 1.7195\mu F$$

Select $C_{C3} = 1.87\mu F/60V.....(H.S.V)$

12) Selection of Bypass capacitor:

$$C_{S1} = C_{S2} = \frac{1}{2\pi f_L R_{eq}}$$

$$f_L = 20Hz$$

$$R_{eq} = \frac{1}{g_m} \parallel R_S$$

$$R_{eq} = 252.51 \parallel 180$$

$$R_{eq} = 0.105k\Omega$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 20 \times 0.105k\Omega}$$

$$C_{S1} = C_{S2} = 75.7250\mu F$$

Select $C_{S1} = C_{S2} = 100\mu F/60V.....(H.S.V)$

13) Designed circuit:

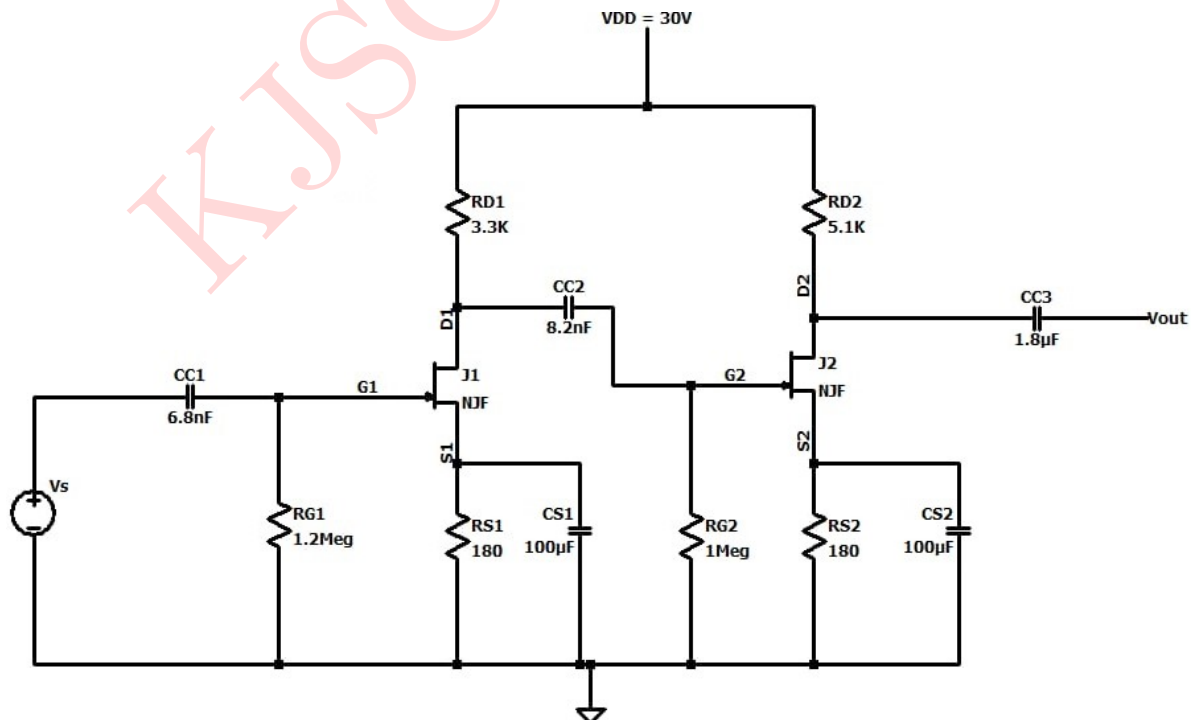


Figure 5: Designed JFET Amplifier Circuit using Mid-Point Biasing Technique

Calculation of Z_i & Z_o

From figure 2 we get,

$$Z_i = R_{G_1}$$

$$\mathbf{Z_i = 1.2M\Omega}$$

$$Z_o = r_{d_2} \parallel R_{D_2} = 50k \parallel 5.1k$$

$$\mathbf{Z_o = 4.679k\Omega}$$

Calculation of overall voltage gain:

$$g_{m_1} = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$g_{m_1} = \frac{2 \times 7mA}{2.5V} \left(1 - \frac{0.732}{2.5}\right)$$

$$g_m = g_{m_1} = g_{m_2} = 3.96mA/V$$

$$A_{V_1} = -g_m(r_{d_1} \parallel R_{D_1} \parallel R_{G_2})$$

$$A_{V_1} = -3.96mA/V \times (50k \parallel 3.3k \parallel 1M)$$

$$\mathbf{A_{V_1} = -12.22}$$

$$A_{V_2} = -g_m(r_{d_2} \parallel R_{D_2})$$

$$A_{V_2} = -3.96mA/V(50k \parallel 5.1k)$$

$$\mathbf{A_{V_2} = -18.326}$$

$$A_{V_T} = A_{V_1} \times A_{V_2}$$

$$A_{V_T} = -12.22 \times -18.326 = 223.94$$

$$|A_{V_T}|(dB) = 20\log_{10}(A_{V_T}) = 20\log_{10}(223.94)$$

$$\mathbf{|A_{V_T}|(dB) = 47dB}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

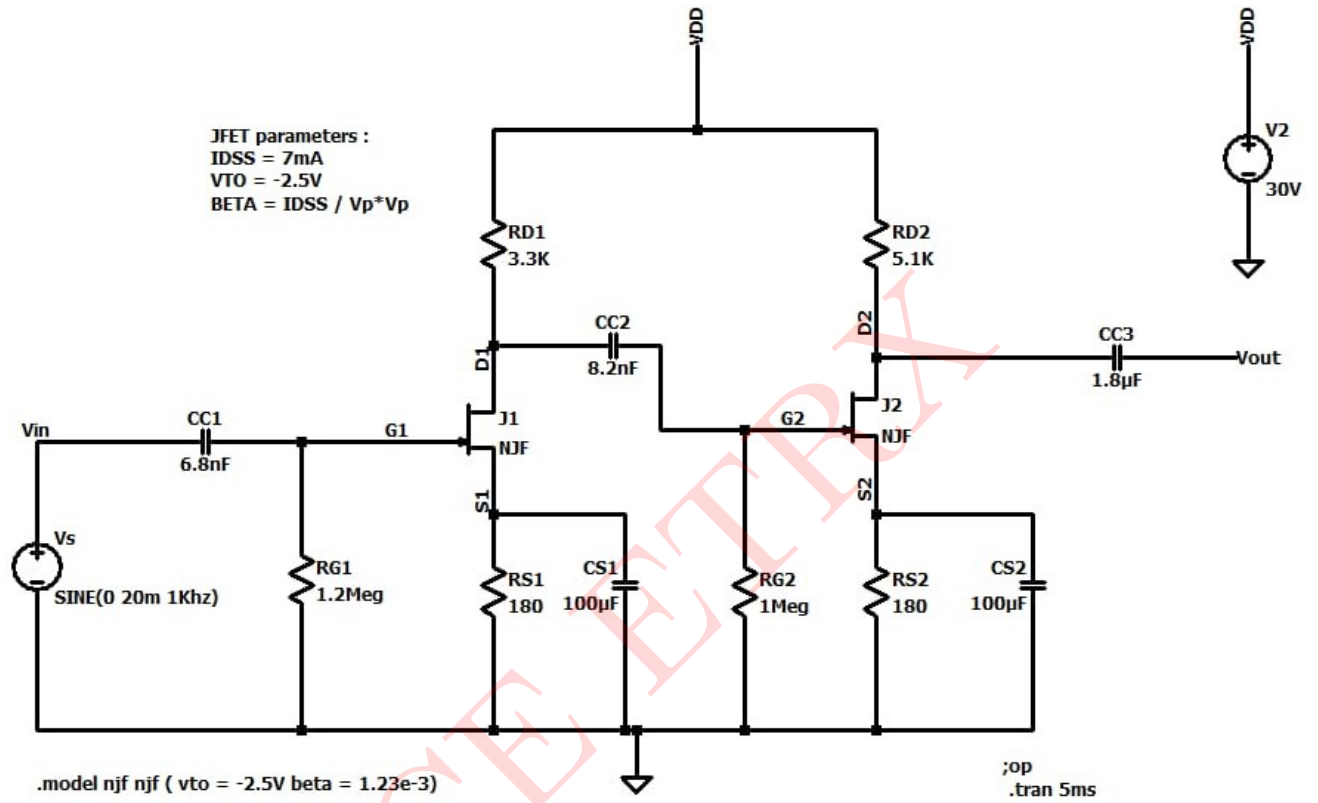


Figure 6: Circuit Schematic: Results

Output Waveforms:

The input and output waveforms are shown in figure 4 and figure 5

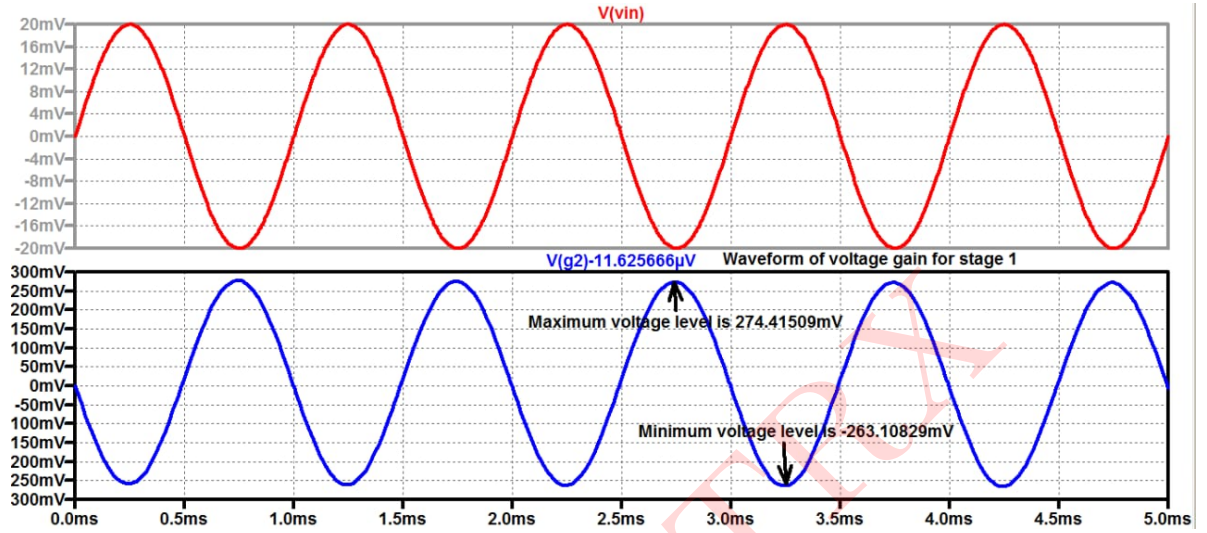


Figure 7: Input and Output Waveforms for 1st Stage

 


Figure 8: Input and Output Waveforms 2nd Stage

Comparison between theoretical and simulated values is given below:

| Parameters | Simulated Values | Theoretical Values |
|--|------------------|--------------------|
| Stage 1: I_{D_1} | $3.6mA$ | $3.5mA$ |
| Stage 1: V_{GS_1} | $-0.7318V$ | $-0.732V$ |
| Stage 2: I_{D_2} | $3.6mA$ | $3.5mA$ |
| Stage 2: V_{GS_1} | $-0.7318V$ | $-0.732V$ |
| Voltage gain of first stage $ A_{V_1} $ | 13.443 | > 11 |
| Voltage gain of second stage $ A_{V_2} $ | 20.84 | > 18 |
| Overall voltage gain $A_V(\text{dB})$ | 48.96 | 47 |
| Input Impedance Z_i | — | $1.2M\Omega$ |
| Output Impedance Z_o | — | $4.6279k\Omega$ |

Table 1: Design 1

Design 2

Design a two stage RC coupled amplifier to meet the following specifications $A_V \geq 650$, $V_{CC} = 18V$, $S \leq 10$, $R_i \geq 1M\Omega$.

Solution:

Above requirements can be fulfilled by CS-CE stage.

Selecting CS as 1st stage since $R_i \geq 1M\Omega$

1) Circuit Diagram:

Select: BC147B

$h_{fe}(typ) = 330$, $h_{FE}(typ) = 290$, $h_{ie} = 4.5k\Omega$, $V_{CEsat} = 0.25V$

Select BFW11:

$V_P = -2.5V$, $r_d = 50\Omega$, $I_{DSS} = 7mA$ & $g_{mo} = 5600\mu S$

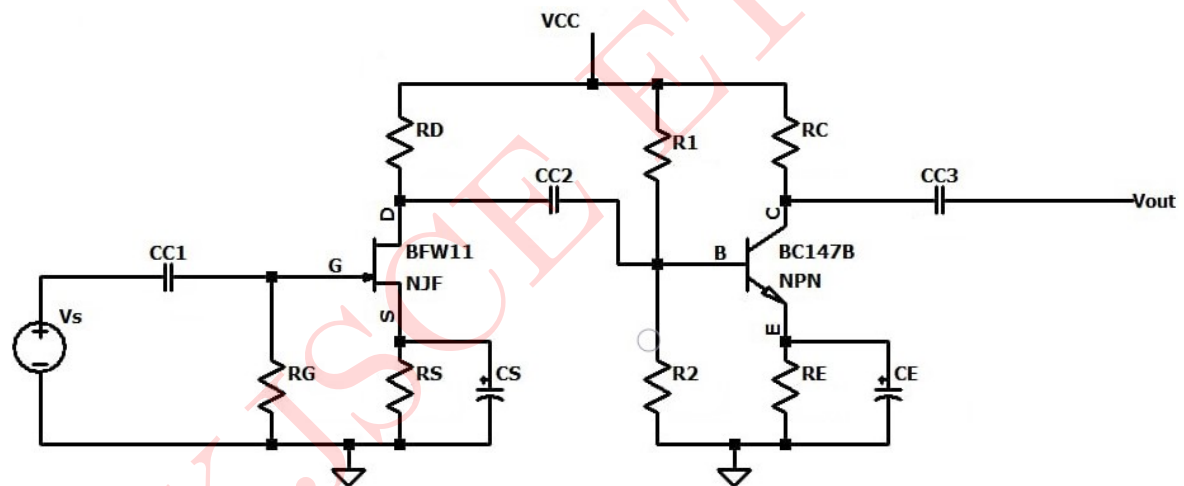


Figure 9: Circuit for Design 2

2) Selection of voltage gains:

$A_V \geq 650$ (Given)

let $A_{V_1} = 4$ (Since JFET amplifier gain is less)

$$A_{V_2} = \frac{650}{4}$$

$$A_{V_2} = 162.5$$

let $A_{V_2} = 170$

Design of 2nd stage

3) Selection of R_C:

$$|A_{V_2}| = \frac{h_{fe}(typ) \times R_C}{h_{ie}}$$

$$170 = \frac{330 \times R_C}{4.5k}$$

$$R_C = 2.3k\Omega$$

Select **R_C = 2.4k Ω _(std), 1/4W.....(HSV)**

4) Selection of Q-Point:

$$V_{CC} = 18V$$

$$\text{let } V_{CEQ} = \frac{V_{CC}}{2} = \frac{18}{2}$$

$$\mathbf{V_{CEQ} = 9V}$$

$$V_{RE} = 0.1 \times V_{CC} = 0.1 \times 18$$

$$\mathbf{V_{RE} = 1.8V}$$

Applying KVL to the C-E loop of BJT

$$V_{CC} - V_{R_C} - V_{CEQ} - V_{R_E} = 0$$

$$V_{R_C} = V_{CC} - V_{CEQ} - V_{R_E} = 18 - 9 - 1.8$$

$$\mathbf{V_{R_C} = 7.2V}$$

$$I_{CQ}R_C = V_{R_C} = 7.2$$

$$I_{CQ} = \frac{V_{R_E}}{R_C} = \frac{7.2}{2.4k}$$

$$\mathbf{I_{CQ} = 3mA}$$

5) Selection of R_E:

$$I_{CQ}R_E = V_{R_E} = 1.8V$$

$$R_E = \frac{V_{R_E}}{I_{CQ}} = \frac{1.8}{3mA}$$

$$\mathbf{R_E = 0.6k\Omega}$$

Select **R_E = 560 Ω _(std), 1/4W.....(LSV)**

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{3mA}{290}$$

$$\mathbf{I_{BQ} = 10.34\mu A}$$

$$I_E = I_B + I_C = 3 + 0.010$$

$$\mathbf{I_E = 3.01mA}$$

6) Selection of biasing resistors:

$$S \leq 10$$

$$\beta = 290$$

$$\text{let } S = 10$$

$$S = \frac{1 + \beta}{1 + \beta \times \left[\frac{R_E}{R_B + R_E} \right]}$$

$$10 = \frac{1 + 290}{1 + 290 \left[\frac{560}{560 + R_B} \right]}$$

$$\mathbf{R_B = 5.219k\Omega}$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = 5.219k\Omega \quad \text{.....(1)}$$

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \text{.....(2)}$$

Applying KVL at BE loop of BJT,

$$V_B - I_{BQ}R_B - V_{BE} - I_{EQ}R_E = 0$$

$$V_B = \frac{I_C}{\beta} \times R_B + V_{BE} + I_{CQ}R_E$$

$$V_B = \frac{3mA}{290} \times 5.219k + 0.7 + 3mA \times 560$$

$$\mathbf{V_B = 2.434V}$$

From (2) we get,

$$V_B = 2.434 = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$V_B = 2.434 = \frac{R_2}{R_1 + R_2} \times 18V$$

$$\frac{R_2}{R_1 + R_2} = 0.1352 \quad \text{.....(3)}$$

$$V_E = I_E R_E = 3.01mA \times 560$$

$$\mathbf{V_E = 1.6856V}$$

Substituting (3) in (1) we get,

$$R_1 \times (0.1352) = 5.219k$$

$$R_1 = 38.60k\Omega$$

Select $R_1 = 39k\Omega_{(std)}, 1/4W.....(HSV)$

From (3) $\frac{R_2}{R_1 + R_2} = 0.1352$

$$\frac{R_2}{39k + R_2} = 0.1352$$

$$R_2 = 6k\Omega \quad (\text{Select HSV only for CS-CE})$$

Select $R_2 = 6.2k\Omega_{(std)}, 1/4W.....(HSV)$

7) Calculation of Q-Point:

Using mid point biasing technique:

i) Calculation of I_D

For mid point biasing, $I_D = \frac{I_{DSS}}{2}$

i.e. $I_D = \frac{7mA}{2}$

$\therefore I_D = 3.5mA$

ii) Calculation of V_{GS}

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

i.e. $V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) = -2.5 \left(1 - \sqrt{\frac{3.5}{7}}\right)$

$V_{GS} = -0.732V$

iii) Calculation of g_m

$$g_m = g_{m1} = g_{m2} = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right) = 5600 \times 10^{-6} \left(1 - \frac{(-0.732)}{(-2.5)}\right)$$

$\therefore g_m = 3.9603m\Omega$

4) Selection of R_D :

$$|A_{V_2}| = \frac{h_{fe}(typ) \times R_C}{h_{ie}}$$

$$|A_{V_2}| = \frac{330 \times 2.4k}{4.5k}$$

$$|A_{V_2}| = 176$$

$$|A_{V_1}| = \frac{A_V}{|A_{V_2}|} = \frac{650}{176} = 3.69$$

$$|A_{V_1}| = g_{m1} [R_D \parallel r_d \parallel R_1 \parallel R_2 \parallel h_{ie}]$$

$$R_{L_1} = r_d \parallel R_1 \parallel R_2 \parallel h_{ie} = 50k \parallel 39k \parallel 6.2k \parallel 4.5k$$

$$R_{L_1} = 2.397k\Omega$$

$$|A_{V_1}| = 3.69 = g_{m_1}[R_D \parallel 2.397k]$$

$$\mathbf{R_D = 1.5k\Omega_{(std)}, 1/4W}$$

9) Calculation of R_S :

$$V_{GSQ} = -I_{DQ}R_S$$

$$R_S = \frac{-V_{GSQ}}{I_{DQ}} = \frac{-(-0.732)}{3.5mA}$$

$$\therefore R_S = 209\Omega$$

$$\text{Select } \mathbf{R_S = 180\Omega_{(std)}, 1/4W.....(LSV)}$$

10) Selection of R_G :

Since $R_1 = 1M\Omega$, to prevent loading we take $R_G > 1M\Omega$

$$\text{Select } \mathbf{R_G = 1.2M\Omega_{(std)}, 1/4W}$$

11) Selection of C_{C1} :

 


Figure 10: Low Frequency Equivalent Circuit for C_{C1}

$$C_{C1} = \frac{1}{2\pi f_{LC_{C1}} R_{eq}}$$

$$f_{C_{C1}} = f_L = 20Hz \quad (\text{Assume } f_L = 20Hz)$$

$$R_{eq} = R_{G_1} = 1.2M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1.2M\Omega} = 6.63nF$$

$$\text{Select } \mathbf{C_{C1} = 6.8nF/50V....(H.S.V)}$$

11) Selection of C_{C2} :

 


Figure 11: Low Frequency Equivalent Circuit for C_{C2}

$$C_{C2} = \frac{1}{2\pi f_{L_{CC2}} R_{eq}}$$

$$f_{L_{CC2}} = f_L = 20Hz$$

$$R_{eq} = r_{d1} || R_{D1} + R_1 || R_2 || h_{ie}$$

$$R_{eq} = 50k || 1.5k + 39k || 6.2k || 4.5k\Omega$$

$$R_{eq} = 1.456k + 2.446k\Omega = 3.902k\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 20 \times 3.902k\Omega}$$

$$C_{C2} = 2.060\mu F$$

Select $C_{C2} = 2.2\mu F/50V.....(H.S.V)$

12) Selection of C_{C3} :

 


Figure 12: Low Frequency Equivalent Circuit for C_{C3}

$$C_{C3} = \frac{1}{2\pi f_{L_{CC3}} R_{eq}}$$

$$f_{L_{C3}} = f_L = 20Hz$$

$$R_{eq} = R_C$$

$$R_{eq} = 2.4k\Omega$$

$$C_{C3} = \frac{1}{2\pi \times 20 \times 2.4k\Omega}$$

$$C_{C3} = 3.31\mu F$$

Select $C_{C3} = 3.9\mu F/50V.....(H.S.V)$

12) Selection of Bypass capacitor:

$$C_{S1} = C_{S2} = \frac{1}{2\pi f_L R_{eq}}$$

$$f_L = 20Hz$$

$$R_{eq} = \frac{1}{g_m} \parallel R_S$$

$$R_{eq} = 252.51 \parallel 180$$

$$R_{eq} = 105.09\Omega$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 20 \times 105.09\Omega}$$

$$C_{S1} = C_{S2} = 75.7250\mu F$$

Select $C_{S1} = C_{S2} = 82\mu F/50V.....(H.S.V)$

$$X_{CE} = 0.1R_E \quad (\text{Ensures complete bypass of } R_E)$$

$$C_E = \frac{1}{2\pi \times f_L \times 0.1R_E}$$

$$C_E = \frac{1}{2\pi \times 20 \times 0.1}$$

$$C_E = 284.34\mu F$$

Select $C_E = 330\mu F/50V.....(HSV)$

12) Small Signal Analysis:

 


Figure 13: Small Signal Equivalent Circuit

Calculation of Z_i & Z_o

From figure 2 we get,

$$Z_i = R_G$$

$$Z_i = 1.2M\Omega$$

$$Z_o = R_C$$

$$Z_o = 2.4k\Omega$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{3mA}{26mV}$$

$$g_{m2} = 115.384mA/V$$

Calculation of A_{V2} :

$$A_{V2} = \frac{V_{out}}{V_1} = \frac{-g_{m2}V_{\pi}R_C}{V_{\pi}} = -g_{m2}R_C$$

$$A_{V2} = -115.384mA/V \times 2.4k$$

$$A_{V2} = -276.92$$

Calculation of A_{V1} :

$$A_{V1} = \frac{V_1}{V_{in}} = g_{m1}V_{gs}(r_d \parallel R_D \parallel R_{th} \parallel r_{\pi})$$

$$r_{\pi} = \frac{\beta \times V_T}{I_C} = \frac{290 \times 26mV}{3}$$

$$r_{\pi} = 2.513k\Omega$$

$$A_{V1} = -3.96 \times 10^{-3}(50k \parallel 1.5k \parallel 5.34k \parallel 2.513k)$$

$$A_{V1} = -3.113$$

Calculation of overall voltage gain:

$$A_{V_T} = A_{V_1} \times A_{V_2} = (-276.92) \times (-3.113)$$

$$A_{V_T} = 862.05$$

$$A_{V_T}(dB) = 20 \log_{10}(A_{V_T}) = 20 \log_{10}(862.05)$$

$$A_{V_T}(dB) = 58.71dB$$

13) Designed circuit:

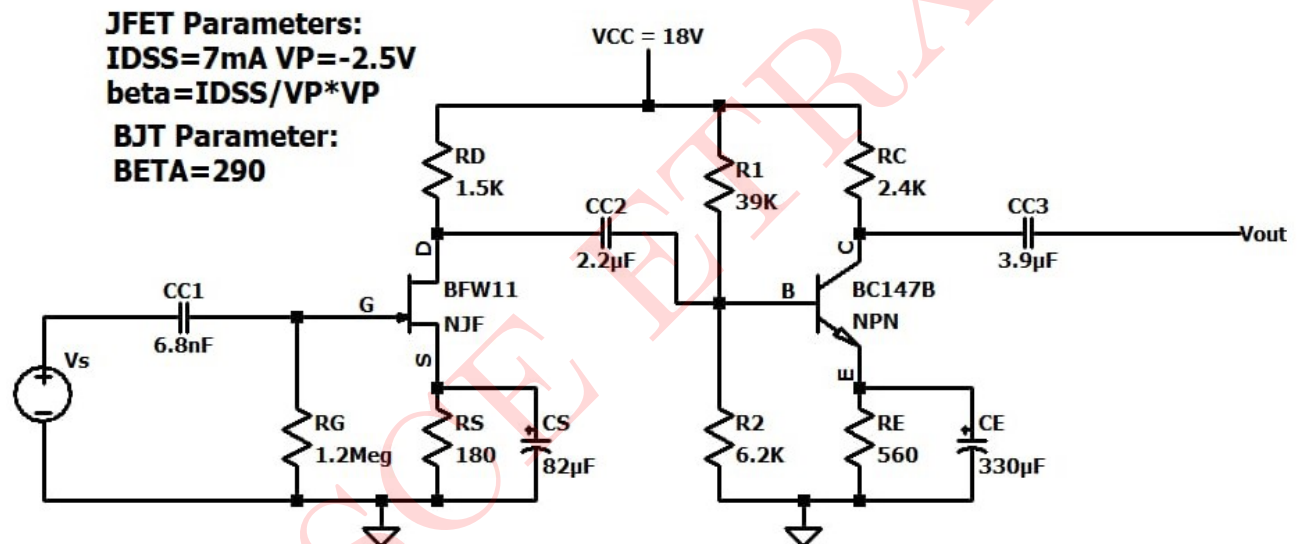


Figure 14: Designed Circuit

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

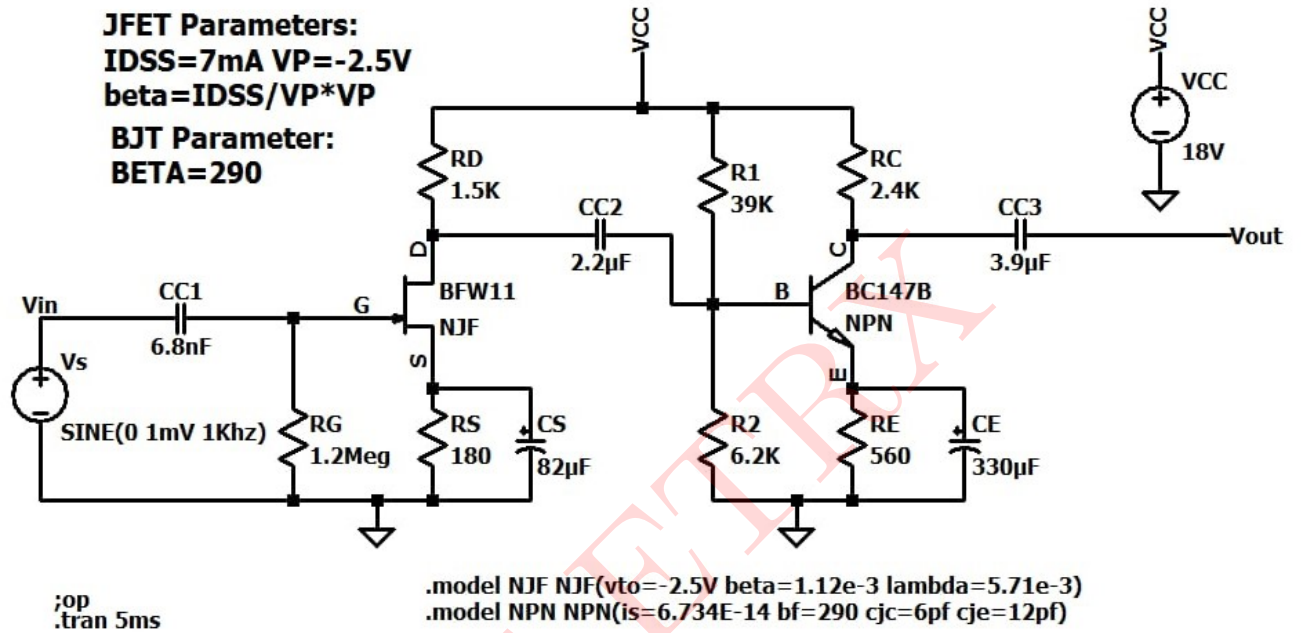


Figure 15: Circuit Schematic: Results

The input and output waveforms are shown in figure 8 and figure 9

 


Figure 16: Input and Output Waveforms for 1st Stage

 


Figure 17: Input and Output Waveforms 2nd Stage

Comparison between theoretical and simulated values is given below:

| Parameters | Simulated Values | Theoretical Values |
|--|------------------|--------------------|
| Stage 1: I_{DQ} | 3.87mA | 3.5mA |
| Stage 1: V_{GSQ} | -0.691V | -0.732V |
| Stage 2: I_B | 10.89 μ A | 10.34 μ A |
| Stage 2: I_C | 3.1mA | 3mA |
| Stage 2: I_E | 3.1mA | 3.01mA |
| Stage 2: V_E | 1.77V | 1.68V |
| Stage 2: V_B | 2.41V | 2.434V |
| Voltage gain of first stage A_{V_1} | -3.41 | -3.113 |
| Voltage gain of second stage A_{V_2} | -290.1 | -276.92 |
| Overall voltage gain A_V (dB) | 59.9dB | 58.71dB |
| Input Impedance Z_i | — | 1.2M Ω |
| Output Impedance Z_o | — | 2.4k Ω |

Table 2: Design 2
