

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**

**Low & high frequency response of single-stage amplifier**

11<sup>th</sup> July, 2020

**Numerical 1:**

The parameters of the transistor in the circuit shown in figure 1 are:  $V_{BE(ON)} = 0.7V$ ,  $\beta = 100$ ,  $V_A = \infty$

- Determine the quiescent and small signal parameters of the transistor.
- Determine lower cut-off frequency due to  $C_{C1}$  and  $C_{C2}$
- Find the midband voltage gain in dB.

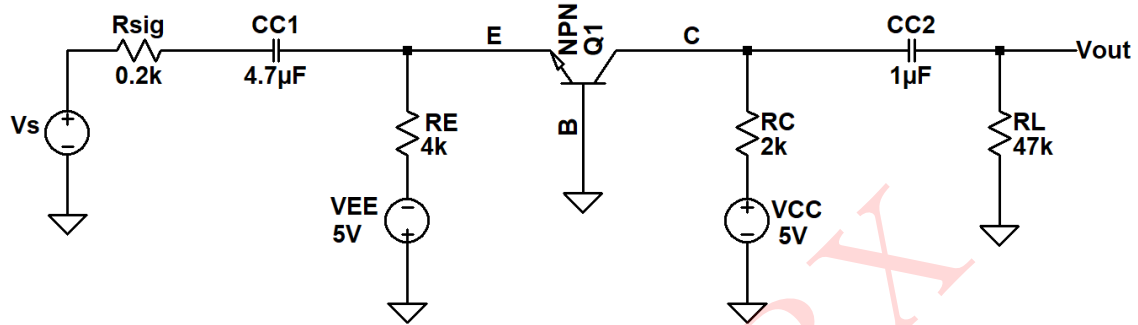


Figure 1: Circuit Diagram

**Solution:** The circuit shown in figure 1 is common base BJT amplifier.

- DC analysis: All capacitors are open-circuited and DC equivalent circuit is shown in figure 2.

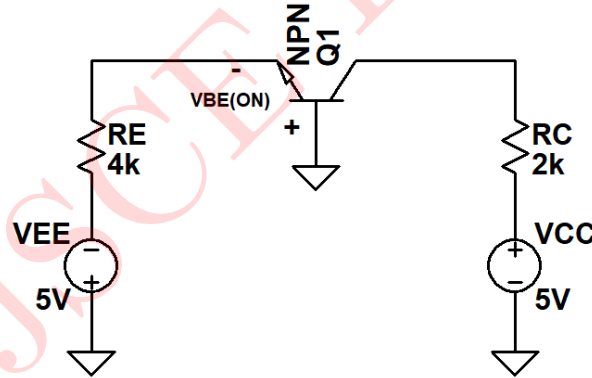


Figure 2: DC equivalent circuit

Applying KVL to B-E loop:

$$-V_{BE(ON)} - I_E R_E + 5 = 0$$

$$\therefore I_E = \frac{5 - 0.7}{4k\Omega} = 1.075mA$$

$$\therefore I_B = \frac{I_E}{1 + \beta} = \frac{1.075mA}{101}$$

$$\therefore I_B = 10.6435\mu A$$

$$I_C = \beta I_B$$

$$\therefore I_C = 100 \times 10.6435 \mu A = \mathbf{1.0644 mA}$$

Small signal parameters:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26 mV}{1.0664 mA} = \mathbf{2.4427 k\Omega}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.0664 mA}{26 mV} = \mathbf{40.9385 mA/V}$$

b. Small signal low frequency equivalent circuit for  $C_{C1}$  alone is shown in figure 3:

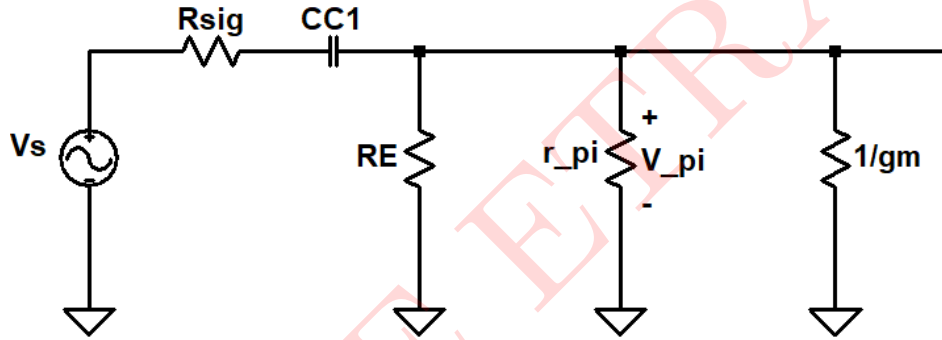


Figure 3: Small signal low frequency equivalent circuit for  $C_{C1}$  alone

Looking from  $C_{C1}$ , the equivalent resistance will be:

$$R_{eq} = R_{sig} + R_E \parallel r_\pi \parallel \frac{1}{g_m}$$

$$f_{LCC1} = \frac{1}{2\pi R_{eq} C_{C1}}$$

$$\therefore f_{LCC1} = \frac{1}{2\pi [R_{sig} + R_E \parallel r_\pi \parallel 1/g_m] C_{C1}}$$

$$\therefore f_{LCC1} = \frac{1}{2\pi [0.2 k\Omega + 4 k\Omega \parallel 2.4427 k\Omega \parallel 0.024427 k\Omega] 4.7 \mu F}$$

$$\therefore \mathbf{f_{LCC1} = 151.1450 Hz}$$

Small signal low frequency equivalent circuit for  $C_{C2}$  alone is shown in figure 3:

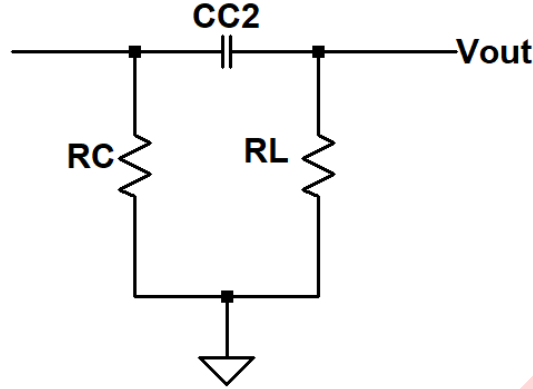


Figure 4: Small signal low frequency equivalent circuit for  $C_{C1}$  alone

Looking from  $C_{C2}$ , the equivalent resistance will be:

$$R_{eq} = R_C + R_L$$

$$\therefore f_{LCC2} = \frac{1}{2\pi R_{eq} C_{C2}}$$

$$\therefore f_{LCC2} = \frac{1}{2\pi [R_C + R_L] C_{C2}} = \frac{1}{2\pi [2k\Omega + 47k\Omega] 10^{-6}}$$

$$\therefore f_{LCC2} = \mathbf{3.2481Hz}$$

Lower cut-off frequency is the highest among  $f_{LCC1}$  and  $f_{LCC2}$  which is 151.1460Hz  
This is the more dominant  $-3dB$  frequency

$$\therefore f_L \text{ of the amplifier is } \mathbf{151.1460Hz}$$

c. Small signal mid-frequency equivalent circuit is shown in figure 5:

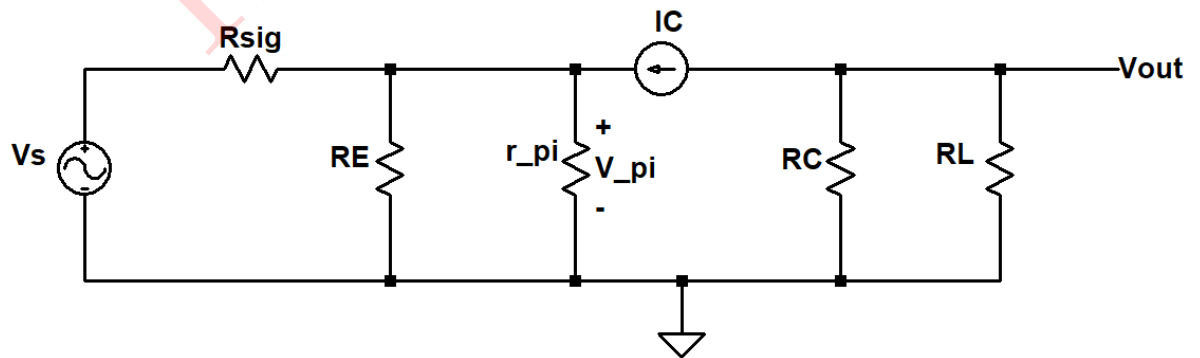


Figure 5: Small signal mid-frequency equivalent circuit

All the capacitors are short-circuited.

Voltage gain is:

$$A_V = \frac{V_{out}}{V_s} \quad \dots(1)$$

$$V_{out} = -g_m V_\pi (R_C \parallel R_L) \quad \dots(2)$$

$$V_{in} = \frac{R_E \parallel r_\pi \parallel 1/g_m}{R_{sig} + [R_E \parallel r_\pi \parallel 1/g_m]} \times V_s$$

$$\therefore \frac{1}{V_s} = \frac{R_E \parallel r_\pi \parallel 1/g_m}{R_{sig} + [R_E \parallel r_\pi \parallel 1/g_m]} \times \frac{1}{V_{in}}$$

$$\therefore \frac{1}{V_s} = \frac{R_E \parallel r_\pi \parallel 1/g_m}{R_{sig} + [R_E \parallel r_\pi \parallel 1/g_m]} \times \frac{1}{V_\pi} \quad \dots(\because V_{in} = V_{pi}) \quad \dots(3)$$

$\therefore$  From (1), (2) & (3) :

$$A_V = \frac{-g_m (R_C \parallel R_L) [R_E \parallel r_\pi \parallel 1/g_m]}{R_{sig} + [R_E \parallel r_\pi \parallel 1/g_m]}$$

$$\therefore A_V = \frac{-(40.9385 \times 10^{-3})(2k\Omega \parallel 47k\Omega)[4k\Omega \parallel 2.4427k\Omega \parallel 1/(40.9385 \times 10^{-3})]}{0.2k\Omega + [4k\Omega \parallel 2.4427k\Omega \parallel 1/(40.9385 \times 10^{-3})]}$$

$$A_V = -8.4271$$

$$\therefore A_V = 18.5136\text{dB}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

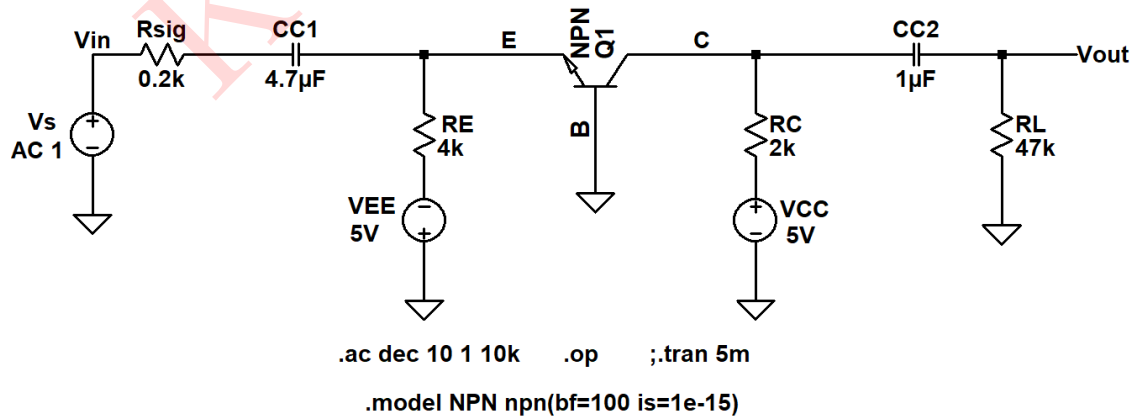


Figure 6: Circuit Schematic: Results

The frequency plots are shown in figures below:

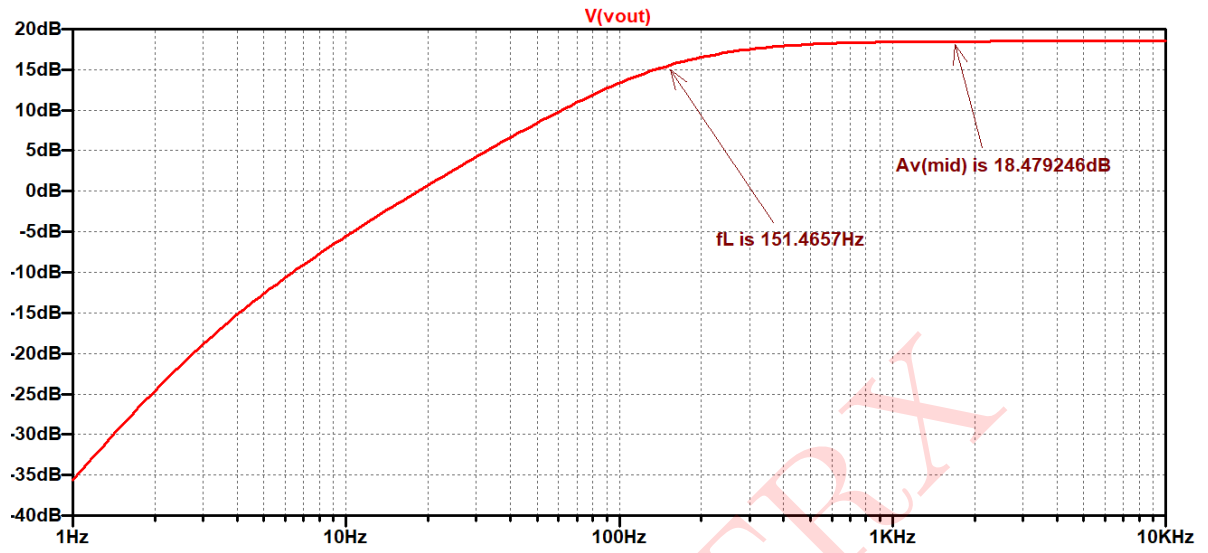


Figure 7: Low frequency response for circuit

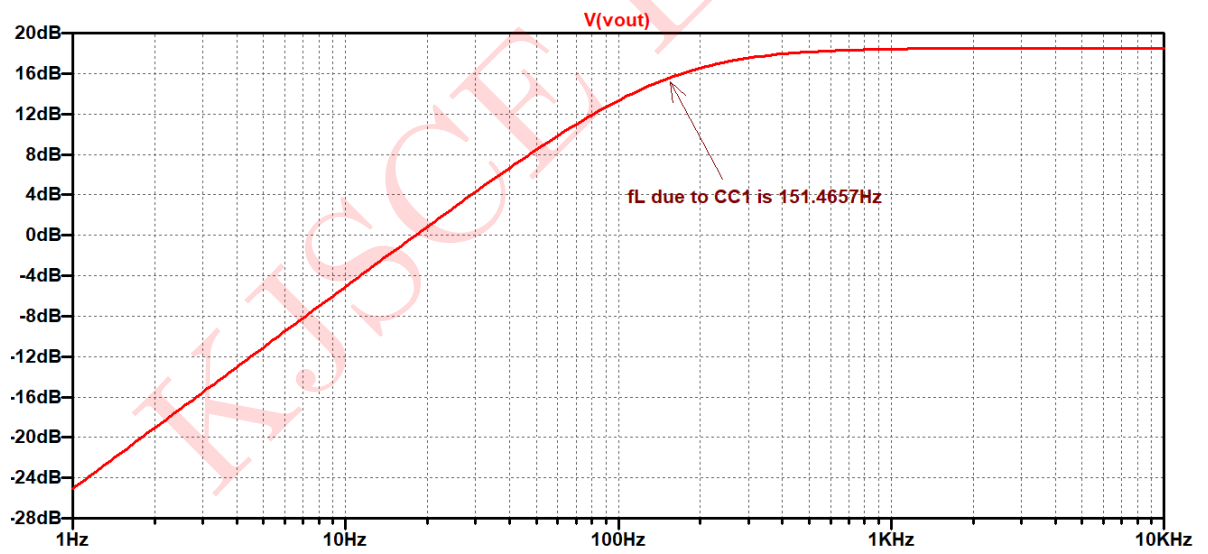


Figure 8: Low frequency response for  $C_{C1}$

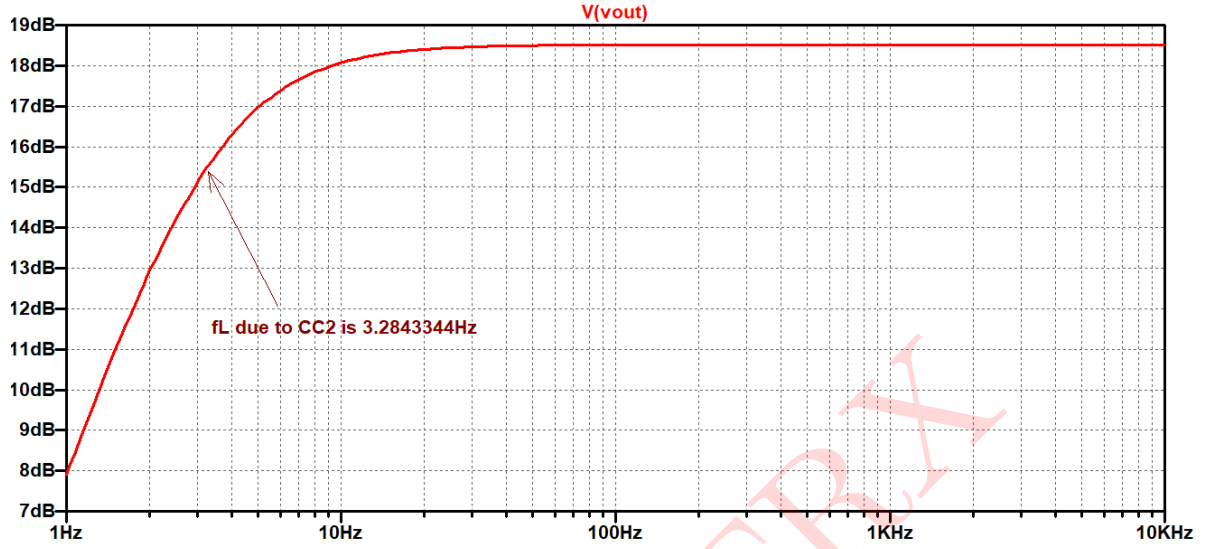


Figure 9: Low frequency response for  $C_{C2}$

Comparison between theoretical and simulated values:

Parameter	Theoretical value	Simulated value
$I_{CQ}$	1.0644mA	1.0604mA
Lower cutoff frequency due to $C_{C1}$	151.1460Hz	151.9911Hz
Lower cutoff frequency due to $C_{C2}$	3.2481Hz	3.2740Hz
Overall cutoff frequency $f_L$	151.1460Hz	151.8880Hz
Midband voltage gain $A_{V(mid)}$	18.5136 dB	18.3779 dB

Table 1: Design 1

**Numerical 2:**

For the network shown in figure 10:

- Determine  $V_{GSQ}$  and  $I_{DQ}$
  - Find  $g_{mo}$  &  $g_m$
  - Calculate midband gain  $A_V = \frac{V_o}{V_i}$
  - Determine  $Z_i$
  - Calculate  $A_{V_s} = \frac{V_o}{V_s}$
  - Determine  $f_{LCC1}$ ,  $f_{LCC2}$  and  $f_{LCE}$
  - Determine the lower cut-off frequency
- Given:  $I_{DSS} = 6mA$ ,  $r_d = \infty$  &  $V_P = -6V$

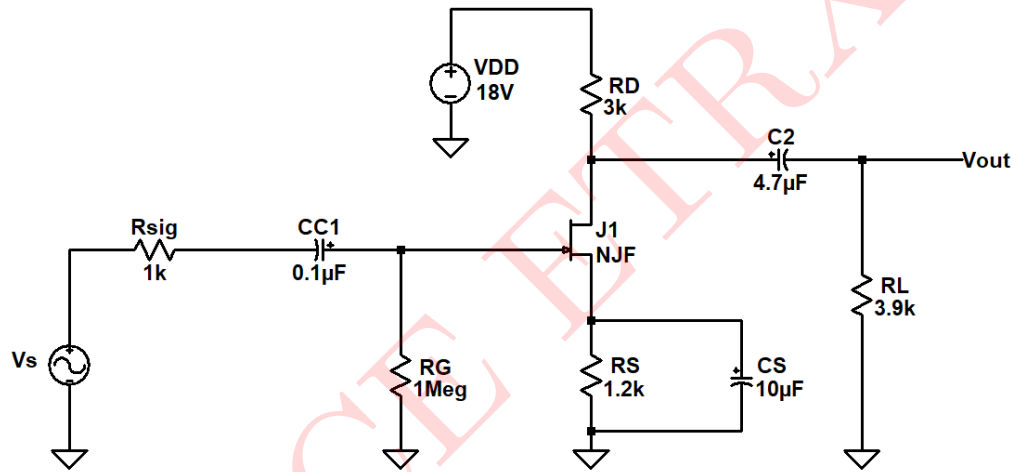


Figure 10: Circuit Diagram

**Solution:** Figure 10 is a common-source JFET amplifier.

- DC analysis: All capacitors are open-circuited and DC equivalent circuit is shown in figure 11.

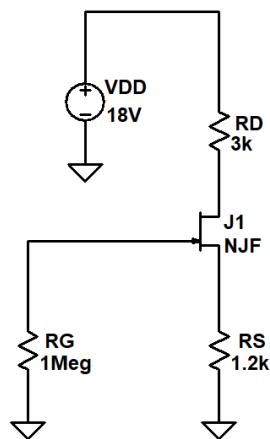


Figure 11: DC equivalent circuit

Applying KVL to G-S loop:

$$V_G - V_{GSQ} - I_S R_S = 0$$

$$\therefore V_{GSQ} - I_D R_S = 0 \quad \dots (\because I_D = I_S)$$

$$\therefore -V_{GSQ} = -I_D R_S$$

$$\therefore I_{DQ} = \frac{-V_{GSQ}}{R_S} = \frac{-V_{GSQ}}{1.2k\Omega} \quad \dots (1)$$

$$\text{In saturation, } I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$\therefore \frac{-V_{GS}}{1.2k\Omega} = (6mA) \left[ 1 + \frac{V_{GS}}{6} \right]^2 \quad \dots (\text{from (1)})$$

$$-V_{GS} = 7.2 \left[ 1 + \frac{V_{GS}^2}{36} + \frac{V_{GS}}{3} \right]$$

$$-V_{GS} = 7.2 + 0.2V_{GS}^2 + 2.4V_{GS}$$

$$\therefore 0.2V_{GS}^2 + 3.4V_{GS} + 7.2 = 0$$

$$\therefore V_{GS} = -2.4792V, -14.5208V$$

$$\text{Since } V_{GS} > V_P \quad \therefore \mathbf{V_{GSQ} = -2.4792V}$$

$$\therefore I_{DQ} = \frac{-(-2.4792V)}{1.2k\Omega} = \mathbf{2.0660mA}$$

$$\text{b. } g_{mo} = \frac{2I_{DSS}}{|V_P|} = \frac{2 \times 6mA}{6V}$$

$$\therefore \mathbf{g_{mo} = 2mA/V}$$

$$g_m = g_{mo} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$$\therefore g_m = (2mA) \left[ 1 - \frac{2.4792}{6} \right]$$

$$\therefore \mathbf{g_m = 1.1736mA/V}$$



c. Small signal equivalent circuit is shown in figure 12:

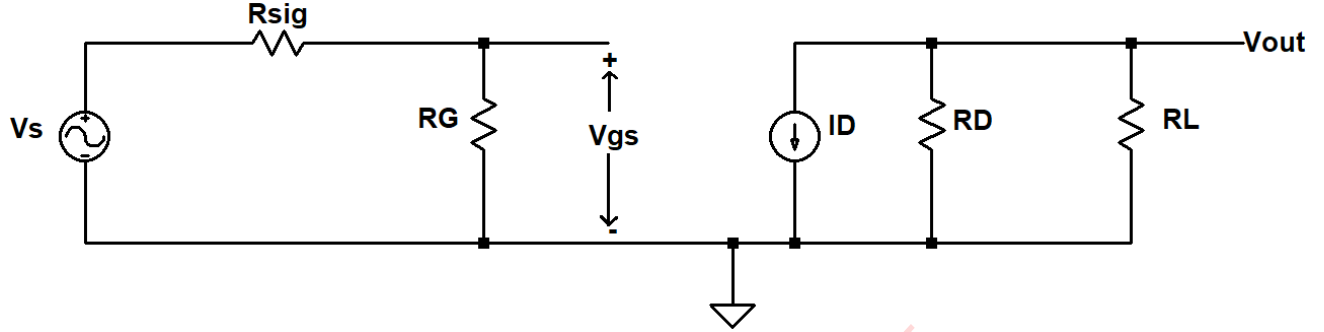


Figure 12: Small signal equivalent circuit

Voltage gain,  $A_V = \frac{V_{out}}{V_{in}}$

$$V_{out} = -g_m V_{gs} (R_D \parallel R_L) \quad \dots V_{in} = V_{gs}$$

$$\therefore A_V = \frac{-g_m V_{gs} (R_D \parallel R_L)}{V_{gs}} = -g_m (R_D \parallel R_L)$$

$$\therefore A_V = -(-1.1736 \times 10^{-3})(3k\Omega \parallel 3.9k\Omega)$$

$$\therefore \mathbf{A_V = -1.9901}$$

$$\therefore \mathbf{A_V = 5.9775dB}$$

...(2)

d.  $Z_i = R_G = 1M\Omega$

$$\therefore \mathbf{Z_i = 1M\Omega}$$

e. Voltage gain (with  $R_{sig}$ ):

$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$V_{in} = V_{gs}$$

$$\therefore V_{in} = \frac{R_G}{R_{sig} + R_G} \times V_s$$

$$\therefore \frac{V_{in}}{V_s} = \frac{1M\Omega}{1k\Omega + 1M\Omega} = 0.999$$

...(3)

$$\therefore A_{Vs} = (-1.9901)(0.999) \quad \dots(\text{from (2) and (3)})$$

$$\therefore \mathbf{A_{Vs} = -1.9881}$$

$$\therefore \mathbf{A_{Vs} = 5.9688dB}$$

f. Small signal low frequency equivalent circuit for  $C_{C1}$  alone is shown in figure 13:

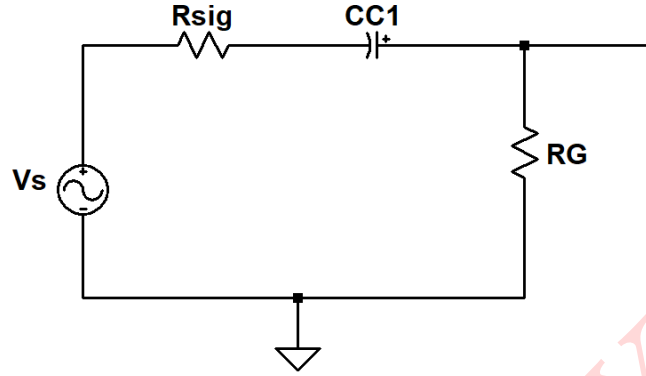


Figure 13: Small signal low frequency equivalent circuit for  $C_{C1}$  alone

$$f_{LCC1} = \frac{1}{2\pi R_{eq} C_{C1}}$$

$$R_{eq} = R_{sig} + R_G = 1k\Omega + 1M\Omega$$

$$\therefore R_{eq} = 1001k\Omega$$

$$\therefore f_{LCC1} = \frac{1}{2\pi(1001k\Omega)(0.1\mu F)}$$

$$\therefore f_{LCC1} = \mathbf{1.5899Hz}$$

Small signal low frequency equivalent circuit for  $C_{C2}$  alone is shown in figure 14:

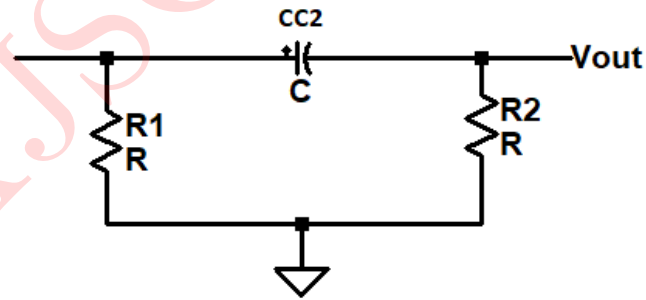


Figure 14: Small signal low frequency equivalent circuit for  $C_{C2}$  alone

$$f_{LCC2} = \frac{1}{2\pi R_{eq} C_{C2}}$$

$$R_{eq} = R_D + R_L = 3k\Omega + 3.9k\Omega$$

$$\therefore R_{eq} = 6.9k\Omega$$

$$\therefore f_{LCC2} = \frac{1}{2\pi(6.9k\Omega)(4.7\mu F)}$$

$$\therefore f_{LCC2} = \mathbf{4.9076Hz}$$

Small signal low frequency equivalent circuit for  $C_s$  alone is shown in figure 15:

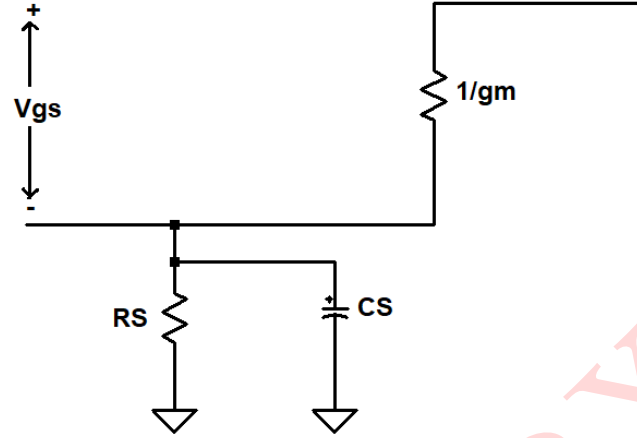


Figure 15: Small signal low frequency equivalent circuit for  $C_s$  alone

$$f_{LCS} = \frac{1}{2\pi R_{eq} C_s}$$

$$R_{eq} = R_s \parallel 1/g_m = 1.2k\Omega \parallel 852.08\Omega$$

$$\therefore R_{eq} = 498.3\Omega$$

$$f_{LCS} = \frac{1}{2\pi(498.3)(10\mu F)}$$

$$\therefore f_{LCS} = \mathbf{31.9413Hz}$$

g. Lower cut-off frequency is the highest among  $f_{LCC1}$ ,  $f_{LCC2}$  and  $f_{LCS}$  which is 31.9413Hz. This is the more dominant  $-3dB$  frequency.

$\therefore$  Lower cut-off frequency of the given CS JFET amplifier is **31.9413Hz**

### SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

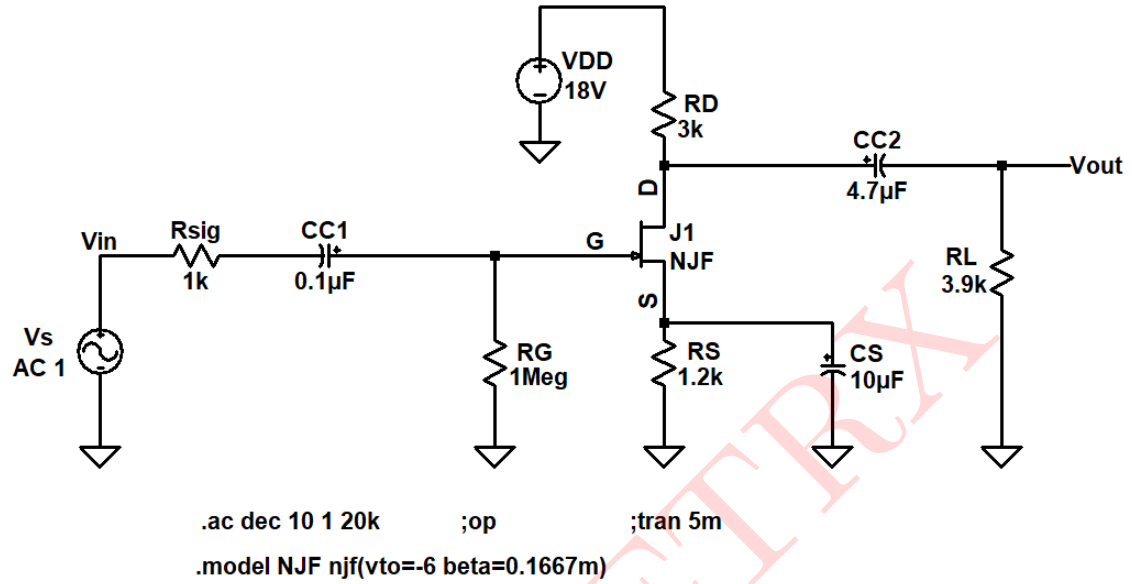


Figure 16: Circuit Schematic: Results

The frequency plots are shown in figures below:

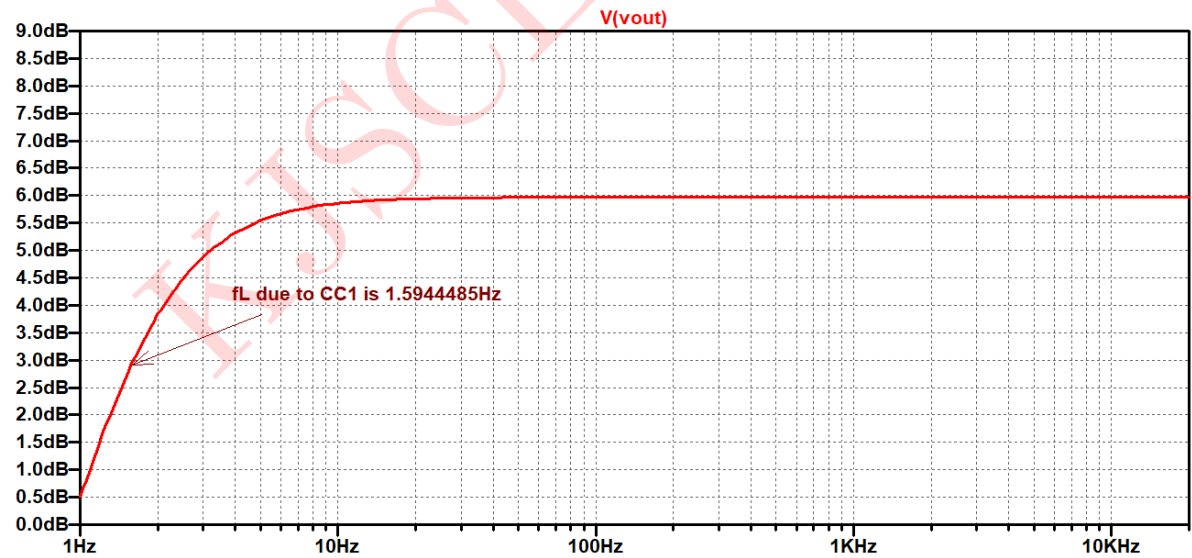


Figure 17: Low frequency response for  $C_{C1}$

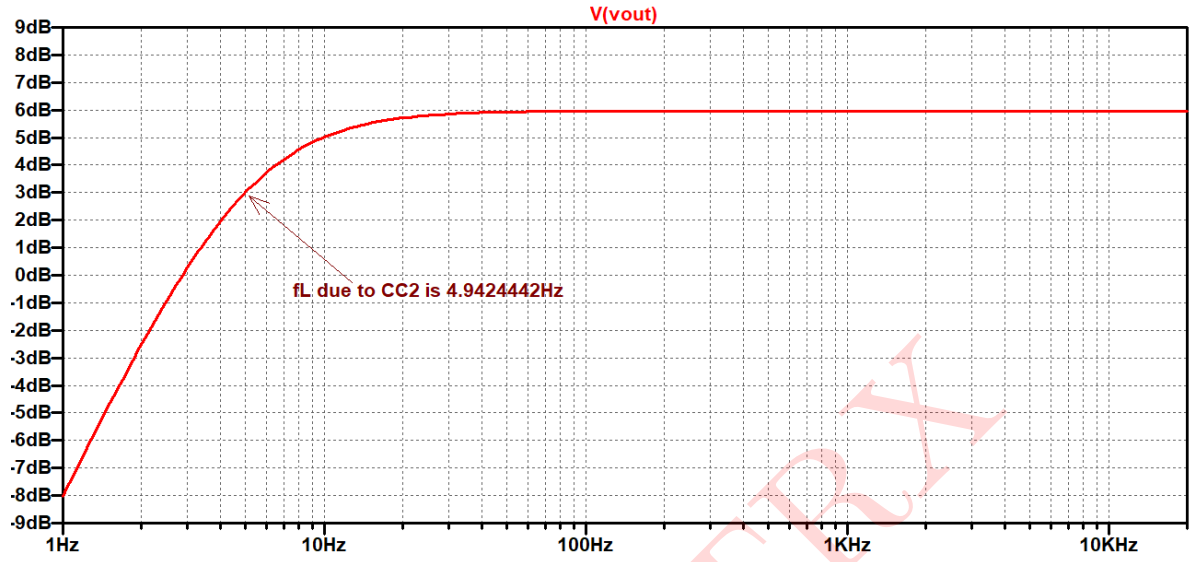


Figure 18: Low frequency response for  $C_{C2}$

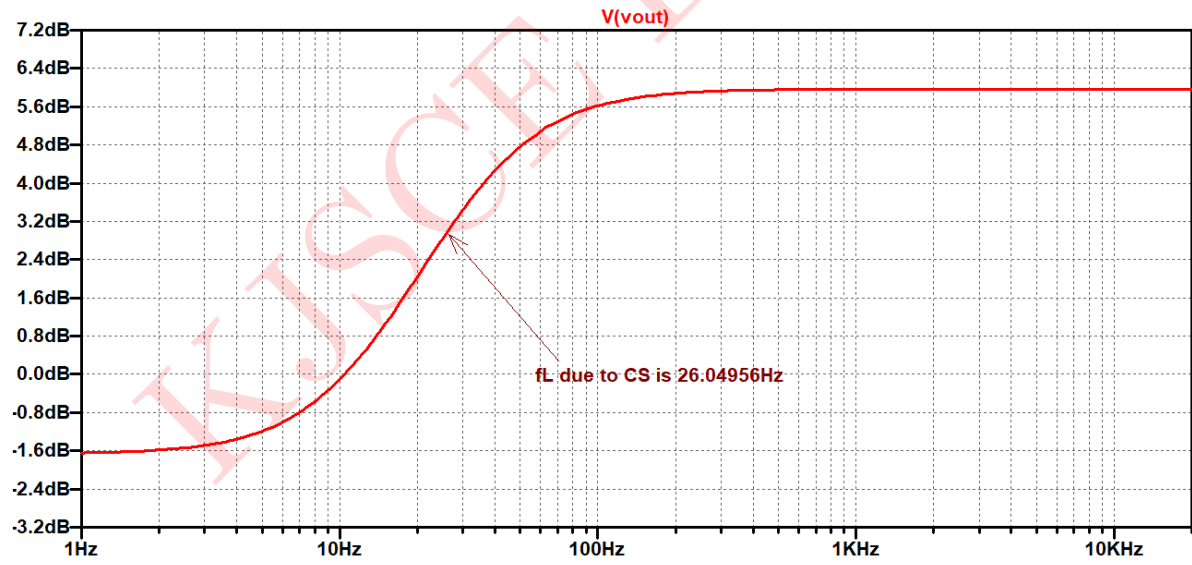


Figure 19: Low frequency response for  $C_s$

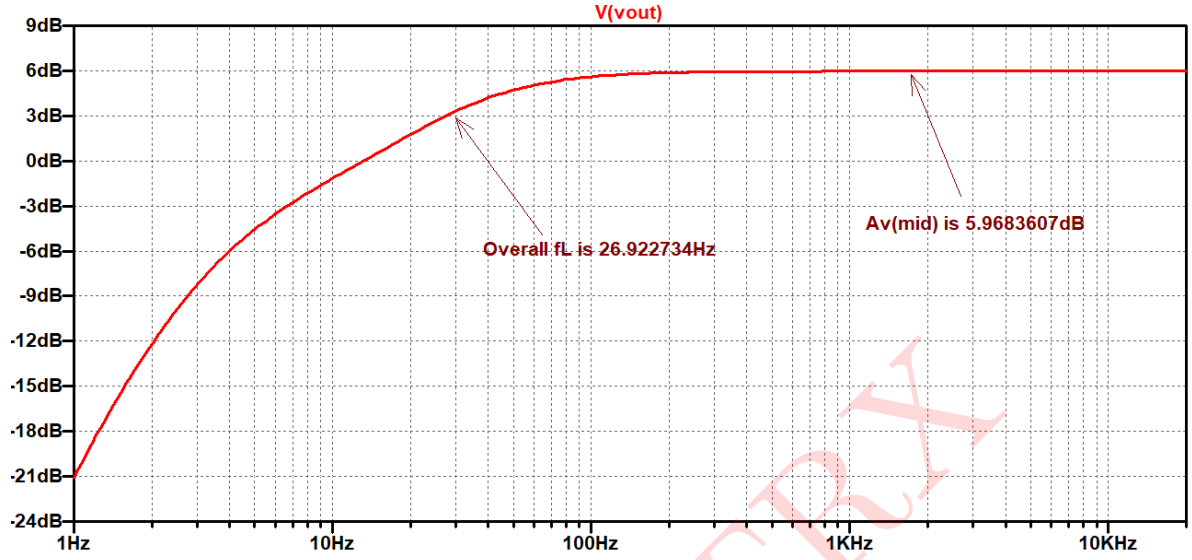


Figure 20: Low frequency response for overall circuit

Comparison between theoretical and simulated values:

Parameter	Theoretical value	Simulated value
$I_{DQ}$	2.0660mA	2.0662mA
$V_{GSQ}$	-2.4792V	-2.4794V
Lower cutoff frequency due to $C_{C1}$	1.5899Hz	1.5800Hz
Lower cutoff frequency due to $C_{C2}$	4.9076Hz	4.9521Hz
Lower cutoff frequency due to $C_s$	31.9413Hz	26.08896Hz
Overall cutoff frequency $f_L$	31.9413Hz	27.4881Hz
Midband voltage gain $A_{Vs(mid)}$	5.9688dB	5.9697dB

Table 2: Numerical 2

### Numerical 3:

For the network shown in figure 21:

- Determine  $V_{GSQ}$  and  $I_{DQ}$
- Find  $g_{mo}$  and  $g_m$
- Calculate midband gain  $A_V = V_o/V_s$
- Determine  $Z_i$
- Calculate  $A_{V_s} = V_o/V_s$
- Determine  $f_{LCC1}$ ,  $f_{LCC2}$  and  $f_{LCs}$
- Determine the lower cut-off frequency frequency.
- Higher cut-off frequency of the circuit.

Given:  $I_{DSS} = 6mA$ ,  $r_d = \infty$ ,  $V_P = -6V$ ,  $C_{wi} = 3pF$ ,  $C_{wo} = 5pF$ ,  $C_{gd} = 4pF$ ,  $C_{gs} = 6pF$ ,  $C_{ds} = 1pF$

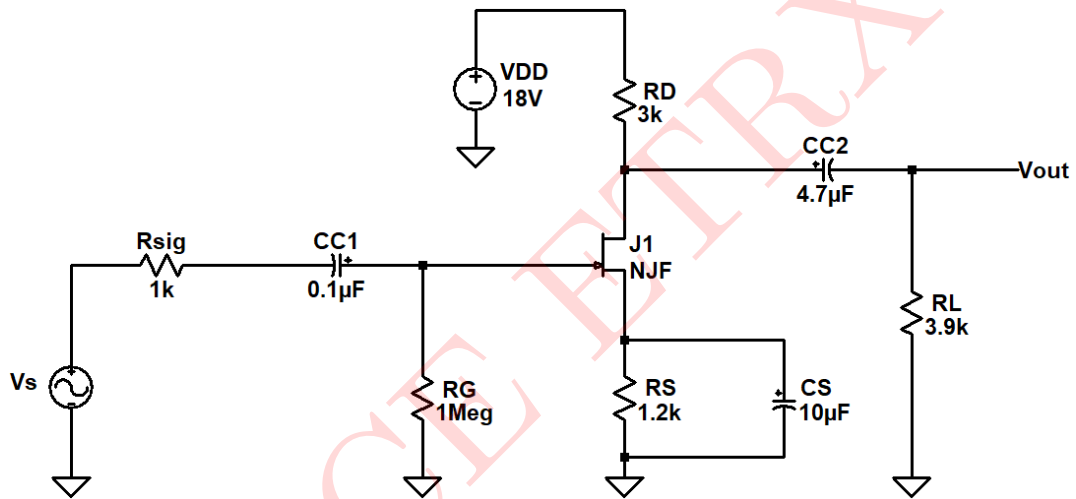


Figure 21: Circuit diagram

**Solution:** The circuit shown in figure 21 is a common-source JFET amplifier.

- DC analysis: All capacitors are open-circuited and DC equivalent circuit is shown in figure 22.

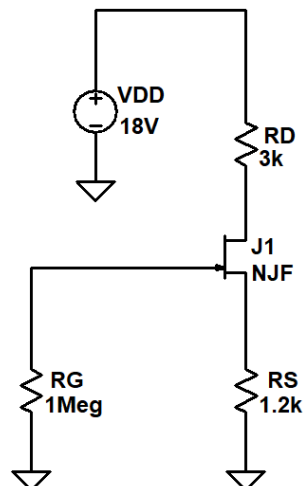


Figure 22: DC equivalent circuit

Applying KVL to G-S loop:

$$V_G - V_{GSQ} - I_S R_S = 0$$

$$\therefore -V_{GSQ} - I_D R_S = 0 \quad \dots (\because I_D = I_S \text{ and } V_G = 0V)$$

$$\therefore V_{GSQ} = -I_D R_S$$

$$\therefore I_{DQ} = \frac{-V_{GSQ}}{R_S} = \frac{-V_{GSQ}}{1.2k\Omega} \quad \dots(1)$$

$$\text{In saturation, } I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$\therefore \frac{-V_{GS}}{1.2k\Omega} = (6mA) \left[ 1 + \frac{V_{GS}}{6} \right]^2 \quad \dots(\text{from (1)})$$

$$-V_{GS} = 7.2 \left[ 1 + \frac{V_{GS}^2}{36} + \frac{V_{GS}}{3} \right]$$

$$-V_{GS} = 7.2 + 0.2V_{GS}^2 + 2.4V_{GS}$$

$$\therefore 0.2V_{GS}^2 + 3.4V_{GS} + 2.4V_{GS} = 0$$

$$\therefore V_{GS} = -2.4792V, -14.5208V$$

$$\text{Since } V_{GS} > V_P \quad \therefore \mathbf{V_{GSQ} = -2.4792V}$$

$$\therefore I_{DQ} = \frac{-(-2.4792V)}{1.2k\Omega} = \mathbf{2.0660mA}$$

$$\text{b. } g_{mo} = \frac{2I_{DSS}}{|V_P|} = \frac{2(6mA)}{6V}$$

$$\therefore \mathbf{g_{mo} = 2mA/V}$$

$$g_m = g_{mo} \left[ 1 - \frac{V_{GS}}{V_P} \right] = (2mA) \left[ 1 - \frac{2.4792}{6} \right]$$

$$\mathbf{g_m = 1.1736mA/V}$$



c. Small signal equivalent circuit is shown in figure 23:

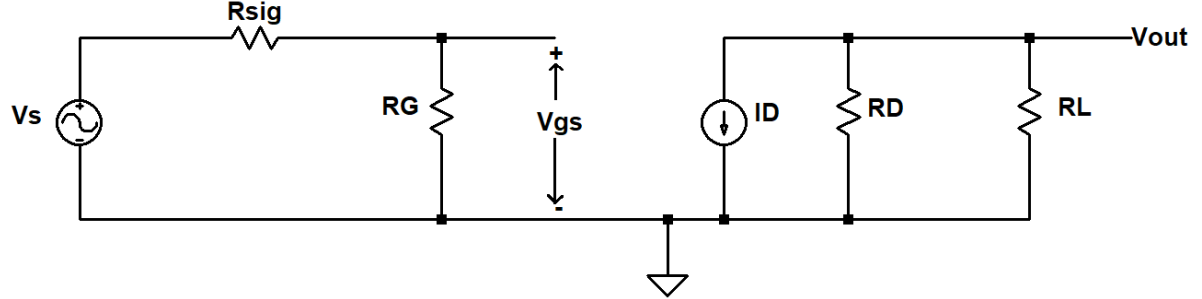


Figure 23: Small signal equivalent circuit

Voltage gain:  $A_V = \frac{V_{out}}{V_{in}}$

$$V_{out} = -g_m V_{gs} (R_D \parallel R_L)$$

$$V_{in} = V_{gs}$$

$$\therefore A_V = \frac{-g_m V_{gs} (R_D \parallel R_L)}{V_{gs}} = -g_m (R_D \parallel R_L)$$

$$\therefore A_V = -(1.1736 \times 10^{-3})(3k\Omega \parallel 3.9k\Omega)$$

$$\therefore \mathbf{A_V = -1.9901}$$

$$\therefore \mathbf{A_V = 5.9755dB}$$

...(2)

d.  $Z_i = R_G = 1M\Omega$

$$\therefore \mathbf{Z_i = 1M\Omega}$$

e. Voltage gain (with  $R_{sig}$ ):

$$A_{V_s} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$V_{in} = V_{gs}$$

$$\therefore V_{in} = \frac{R_G}{R_{sig} + R_G} \times V_s$$

$$\therefore \frac{V_{in}}{V_s} = \frac{1M\Omega}{1k\Omega + 1M\Omega} = 0.999$$

...(3)

$$\therefore A_{V_s} = (-1.9901)(0.999) \quad \dots(\text{from (2) and (3)})$$

$$\therefore \mathbf{A_{V_s} = -1.9881}$$

$$\therefore \mathbf{A_{V_s} = 5.9688dB}$$

f. Small signal low frequency equivalent circuit for  $C_{C1}$  alone is shown in figure 24:

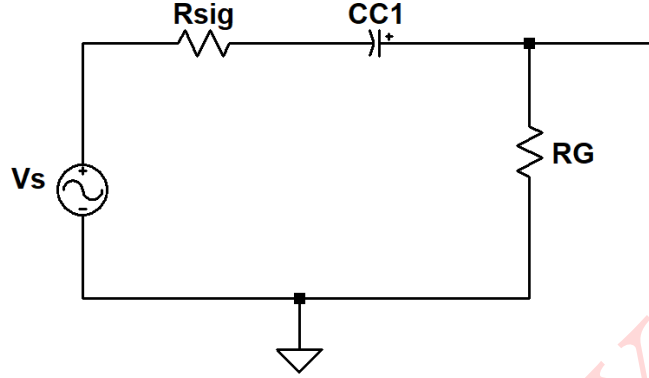


Figure 24: Small signal low frequency equivalent circuit for  $C_{C1}$  alone

$$f_{LCC1} = \frac{1}{2\pi R_{eq} C_{C1}}$$

$$R_{eq} = R_{sig} + R_G = 1k\Omega + 1M\Omega$$

$$\therefore R_{eq} = 1001k\Omega$$

$$\therefore f_{LCC1} = \frac{1}{2\pi(1001k\Omega)(0.1\mu F)}$$

$$\therefore f_{LCC1} = \mathbf{1.5899Hz}$$

Small signal low frequency equivalent circuit for  $C_{C2}$  alone is shown in figure 25:

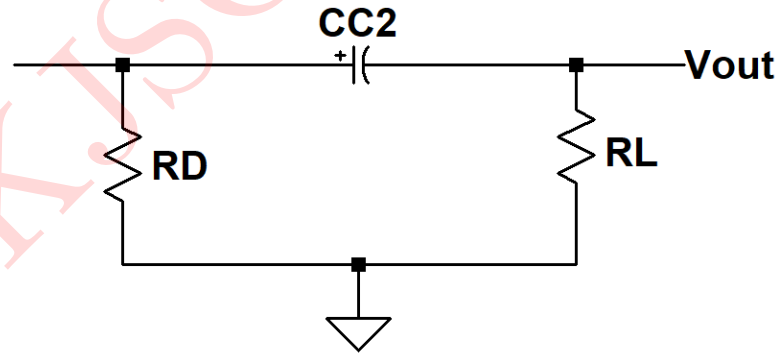


Figure 25: Small signal low frequency equivalent circuit for  $C_{C2}$  alone

$$f_{LCC2} = \frac{1}{2\pi R_{eq} C_{C2}}$$

$$R_{eq} = R_D + R_L = 3k\Omega + 3.9k\Omega$$

$$\therefore R_{eq} = 6.9k\Omega$$

$$\therefore f_{LCC2} = \frac{1}{2\pi(6.9k\Omega)(4.7\mu F)}$$

$$\therefore f_{LCC2} = \mathbf{4.9076Hz}$$

Small signal low frequency equivalent circuit for  $C_s$  alone is shown in figure 26:

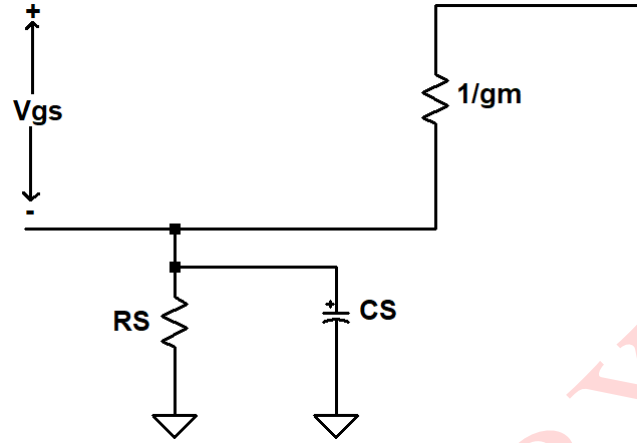


Figure 26: Small signal low frequency equivalent circuit for  $C_s$  alone

$$f_{LCS} = \frac{1}{2\pi R_{eq} C_s}$$

$$R_{eq} = R_s \parallel 1/g_m = 1.2k\Omega \parallel 852.08\Omega$$

$$\therefore R_{eq} = 498.3\Omega$$

$$f_{LCS} = \frac{1}{2\pi(498.3)(10\mu F)}$$

$$\therefore f_{LCS} = \mathbf{31.9413Hz}$$

g. Lower cut-off frequency is the highest among  $f_{LCC1}$ ,  $f_{LCC2}$  and  $f_{LCS}$  which is 31.9413Hz. This is the more dominant  $-3dB$  frequency.

$\therefore$  Lower cut-off frequency of the given CS JFET amplifier is **31.9413Hz**

h. Small signal high frequency equivalent circuit for effect of  $C_i$  alone is shown in figure 27:

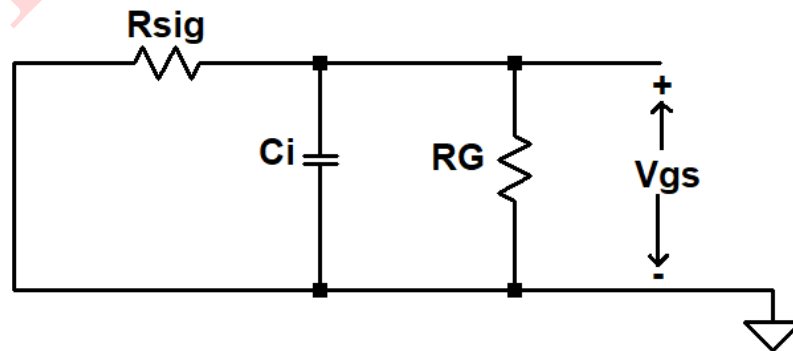


Figure 27: Small signal high frequency equivalent circuit for effect of  $C_i$  alone

$$f_{Hi} = \frac{1}{2\pi R_{eq} C_i}$$

$$R_{eq} = R_{sig} \parallel R_G = 1k\Omega \parallel 1M\Omega = 1k\Omega$$

$$C_i = C_{mi} + C_{gs} + C_{wi}$$

$$\text{where } C_{mi} = C_{gd}[1 - A_{V(mid)}] = (4pF)[1 + 1.9881]$$

$$\therefore C_{mi} = 11.9524pF$$

$$\therefore C_i = 11.9524pF + 6pF + 3pF$$

$$\therefore f_{Hi} = \frac{1}{2\pi(1k\Omega)(20.9523pF)} = 7.5960MHz$$

Small signal high frequency equivalent circuit for effect of  $C_o$  alone is shown in figure 28:

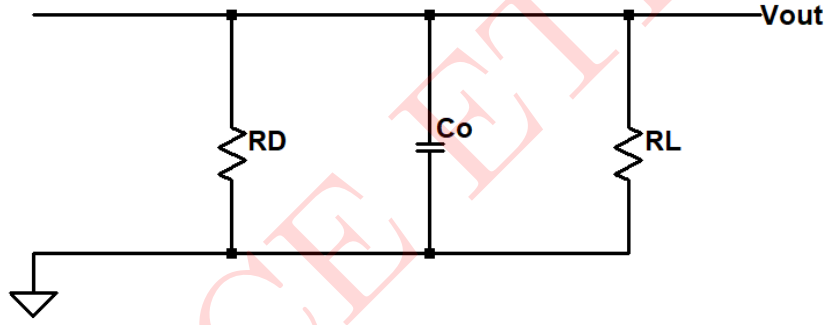


Figure 28: Small signal high frequency equivalent circuit for effect of  $C_o$  alone

$$f_{Ho} = \frac{1}{2\pi R_{eq} C_o}$$

$$R_{eq} = R_o \parallel R_L = 3k\Omega \parallel 3.9k\Omega = 1.6957k\Omega$$

$$C_o = C_{mo} + C_{ds} + C_{wo}$$

$$\text{where, } C_{mo} = C_{gd} \left[ 1 - \frac{1}{A_{V(mid)}} \right] = (4pF) \left[ 1 + \frac{1}{1.9881} \right]$$

$$C_{mo} = 6.0120pF$$

$$f_{Ho} = \frac{1}{2\pi R_{eq} C_o} = \frac{1}{2\pi(1.6957k\Omega)(12.012pF)}$$

$$f_{Ho} = 7.8137 \text{ MHz}$$

Higher cut-off frequency is the lowest value among  $f_{Hi}$  and  $f_{Ho}$

$\therefore$  Higher cut-off frequency is **7.5960MHz**

## SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

**JFET Parameters:**  $I_{DSS} = 6 \text{ mA}$

$$\beta = I_{DSS}/V_p \cdot V_p = 0.1667 \text{ m}$$

$C_{wi} = 3 \text{ pF}$ ,  $C_{wo} = 5 \text{ pF}$

$C_{gs} = 6 \text{ pF}$ ,  $C_{gd} = 4 \text{ pF}$

$C_{ds} = 1 \text{ pF}$

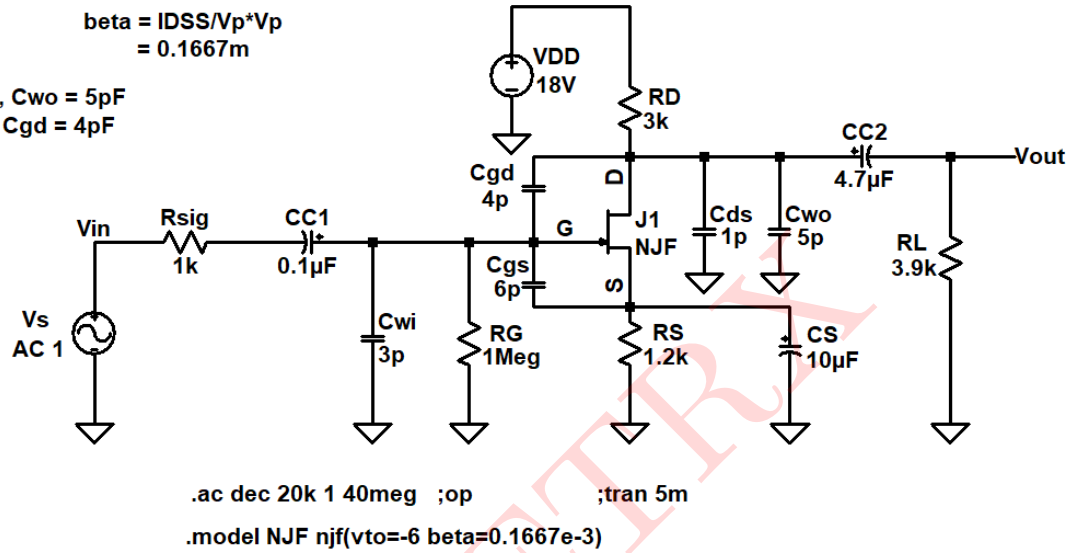


Figure 29: Circuit Schematic: Results

The frequency plots are shown in figures below:

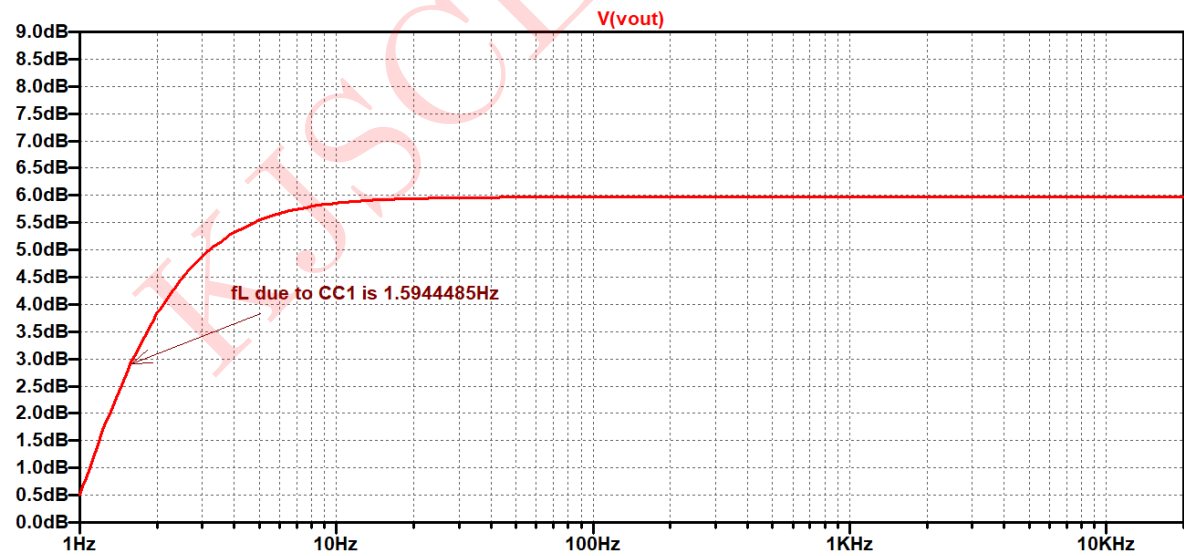


Figure 30: Low frequency response for  $C_{C1}$

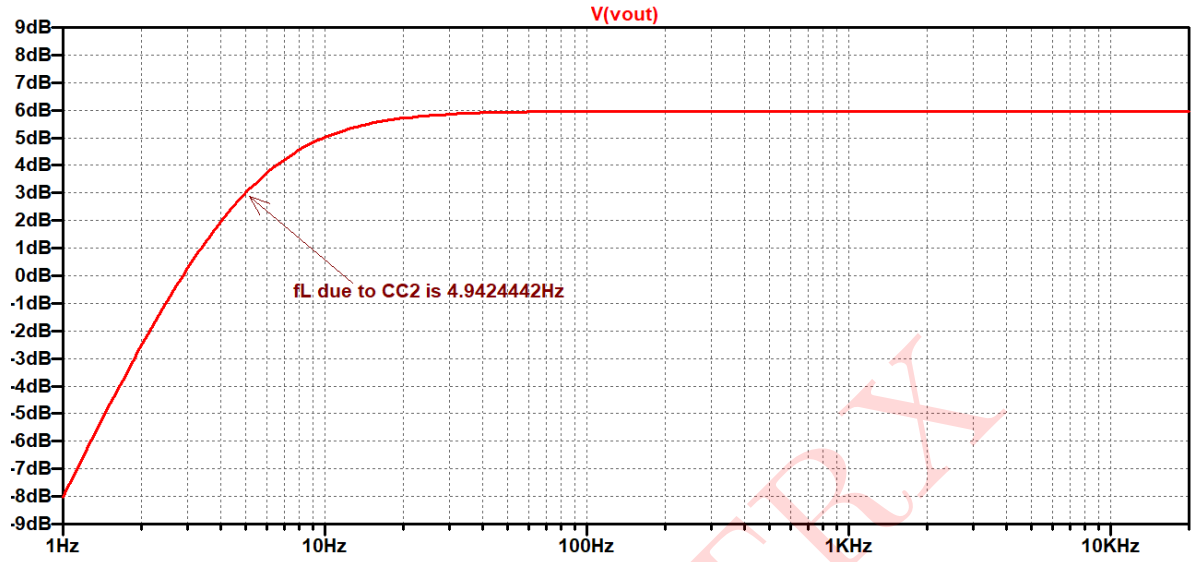


Figure 31: Low frequency response for  $C_{C2}$

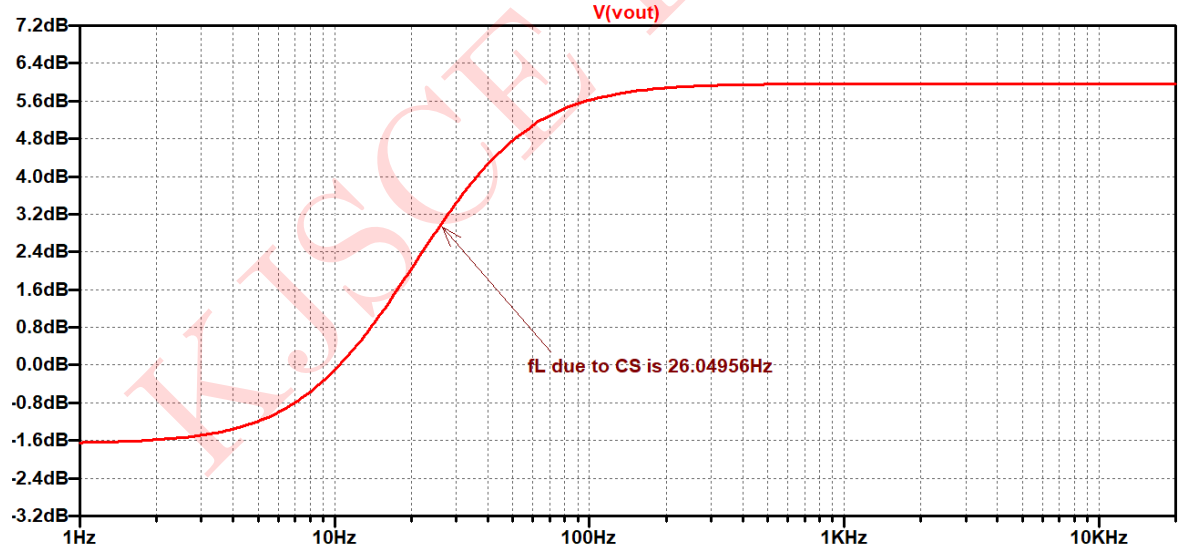


Figure 32: Low frequency response for  $C_s$

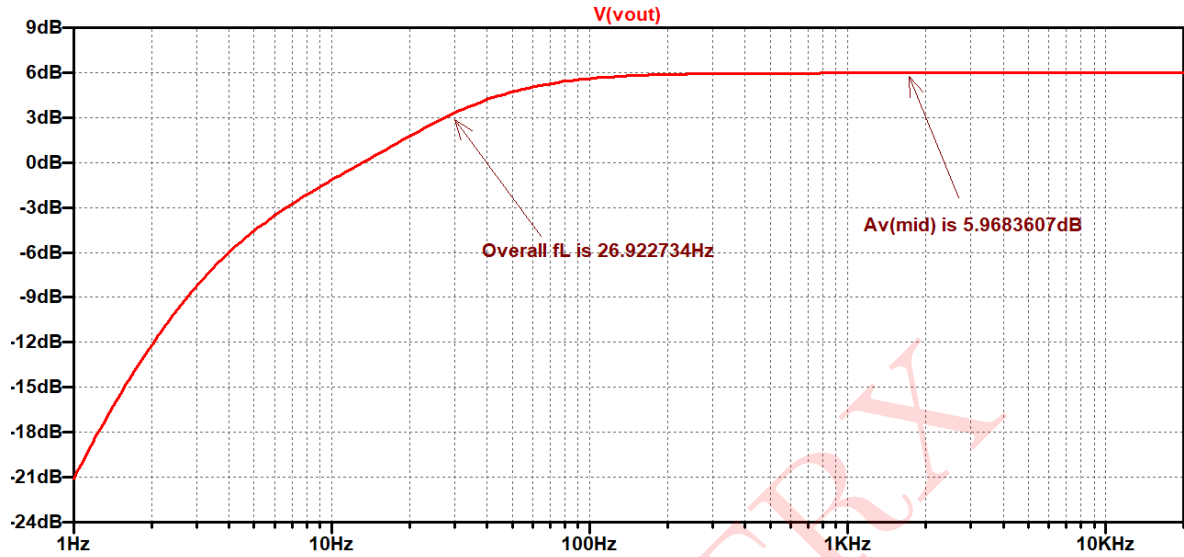


Figure 33: Overall low frequency response

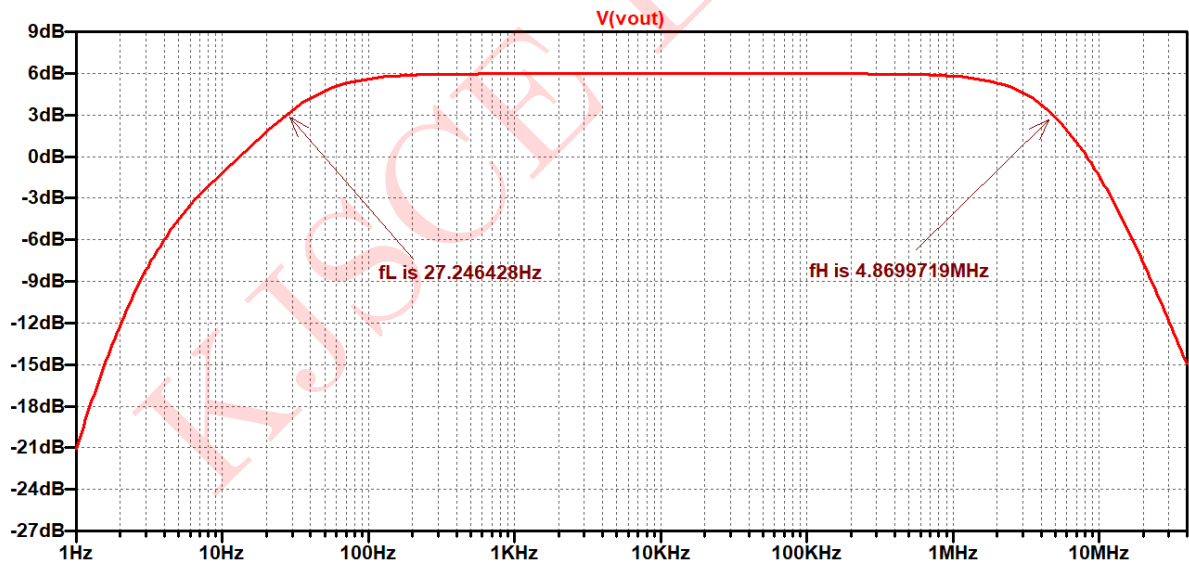


Figure 34: Total frequency response of circuit

**Comparison between theoretical and simulated values:**

Parameter	Theoretical value	Simulated value
$I_{DQ}$	2.0660mA	2.0662mA
$V_{GSQ}$	-2.4792V	-2.4794V
Lower cutoff frequency due to $C_{C1}$	1.5899Hz	1.5800Hz
Lower cutoff frequency due to $C_{C2}$	4.9076Hz	4.9521Hz
Lower cutoff frequency due to $C_s$	31.9413Hz	27.2464Hz
Overall cutoff frequency $f_L$	31.9413Hz	27.2464Hz
Overall cut-off frequency $f_H$	7.5960 MHz	4.8699MHz
Midband voltage gain $A_{Vs(mid)}$	5.9688dB	5.9697dB

Table 3: Numerical 3