

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Single Stage FET Amplifier

Numerical 1:

For the circuit shown below in figure 1, find A_V , R_1 and R_0

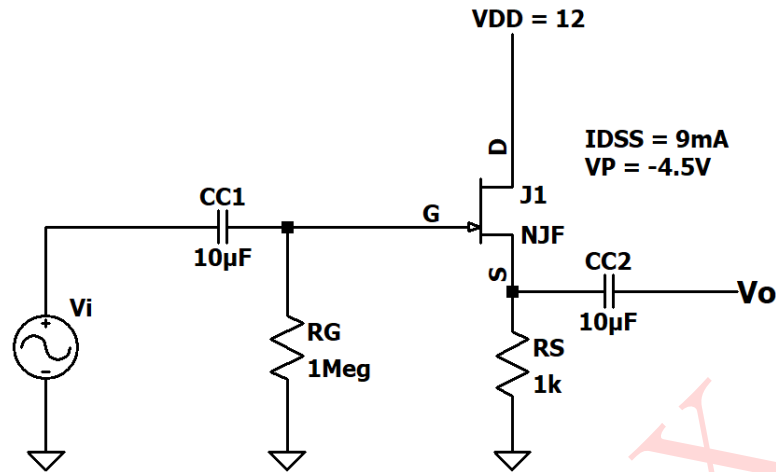


Figure 1: Circuit 1

Solution:

DC analysis:

∴ We are performing DC analysis all capacitors are open circuited

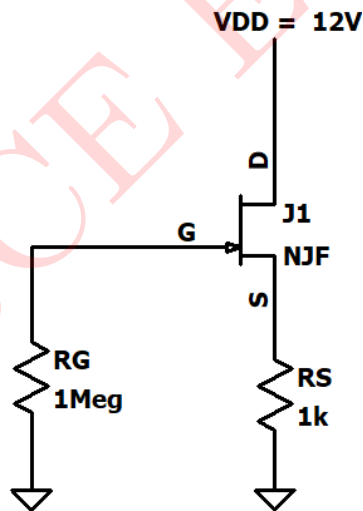


Figure 2: DC equivalent circuit

Applying KVL to gate-source loop,

$$I_g R_G - V_{GS} - I_D R_S = 0$$

$$0 - V_{GS} - I_D R_S = 0 \quad (\because I_g = 0, I_g R_G = 0)$$

$$\therefore V_{GS} = -I_D R_S$$

$$\therefore V_{GS} = -I_D (1k\Omega)$$

$$\therefore I_D = \frac{-V_{GS}}{1k\Omega} \quad \dots\dots(1)$$

Assuming JFET is working in saturation region,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 9mA \left(1 - \frac{V_{GS}}{-4.5} \right)^2$$

$$\frac{-V_{GS}}{1k\Omega} = 9mA \left(1 + \frac{V_{GS}}{4.5} \right)^2 \quad \dots [\text{from (1)}]$$

$$-V_{GS} = 1k\Omega \times 9mA \left(1 + \frac{V_{GS}}{4.5} \right)^2$$

$$-V_{GS} = 9 \left(1 + 2 \left(\frac{V_{GS}}{4.5} \right) + \frac{V_{GS}^2}{20.25} \right)$$

$$-V_{GS} = 9 + 18 \left(\frac{V_{GS}}{4.5} \right) + 9 \times \frac{V_{GS}^2}{20.25}$$

$$-V_{GS} = 9 + 4V_{GS} + 0.44V_{GS}^2$$

$$0 = 9 + 5V_{GS} + 0.44V_{GS}^2$$

$$V_{GS} = -2.242V \text{ or } V_{GS} = -9.121V$$

We reject the value $V_{GS} = -9.121V$ ($\because |V_P| > |V_{GS}|$)

$$\therefore V_{GS} = -\mathbf{2.242V}$$

$$\therefore I_D = \frac{-V_{GS}}{1k\Omega} = \frac{2.24V}{1k\Omega} = \mathbf{2.24mA}$$

Small signal parameters:

$$\begin{aligned} \text{i) } g_m &= 2 \times \frac{I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P} \right) \\ &= \frac{2 \times 9mA}{4.5V} \left[1 - \frac{(-2.24V)}{(-4.5V)} \right] \\ &= 4mA/V \left[1 - \frac{2.24V}{4.5V} \right] \\ &= 4mA/V [1 - 0.49] = \mathbf{2mA/V} \end{aligned}$$

$$\text{ii) } r_d = \infty$$

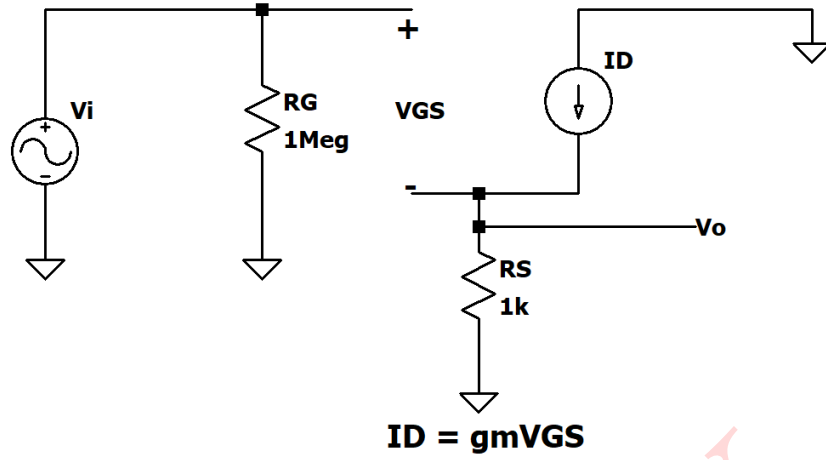


Figure 3: Small signal equivalent circuit

Input resistance,

$$Z_i = R_G = 1\text{M}\Omega$$

Output resistance,

$$\begin{aligned} Z_o &= \frac{1}{g_m} \parallel R_S \\ &= \frac{1}{2\text{mA/V}} \parallel 1\text{k}\Omega \\ &= 0.5\text{k}\Omega \parallel 1\text{k}\Omega \\ &= \frac{0.5\text{k}\Omega \times 1\text{k}\Omega}{0.5\text{k}\Omega + 1\text{k}\Omega} = \mathbf{0.333\text{k}\Omega} \end{aligned}$$

Voltage gain,

$$\begin{aligned} A_V &= \frac{V_o}{V_{in}} \\ &= \frac{(g_m V_{GS})(R_S)}{V_{GS} + V_{RS}} \\ &= \frac{(g_m V_{GS})(R_S)}{V_{GS} + g_m V_{GS} R_S} \\ &= \frac{(g_m V_{GS})(R_S)}{(V_{GS})[1 + g_m R_S]} \\ &= \frac{g_m R_S}{1 + g_m R_S} = \frac{2\text{mA/V} \times 1\text{k}\Omega}{1 + (2\text{mA/V} \times 1\text{k}\Omega)} = \frac{2}{1 + 2} = \mathbf{0.666} \end{aligned}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

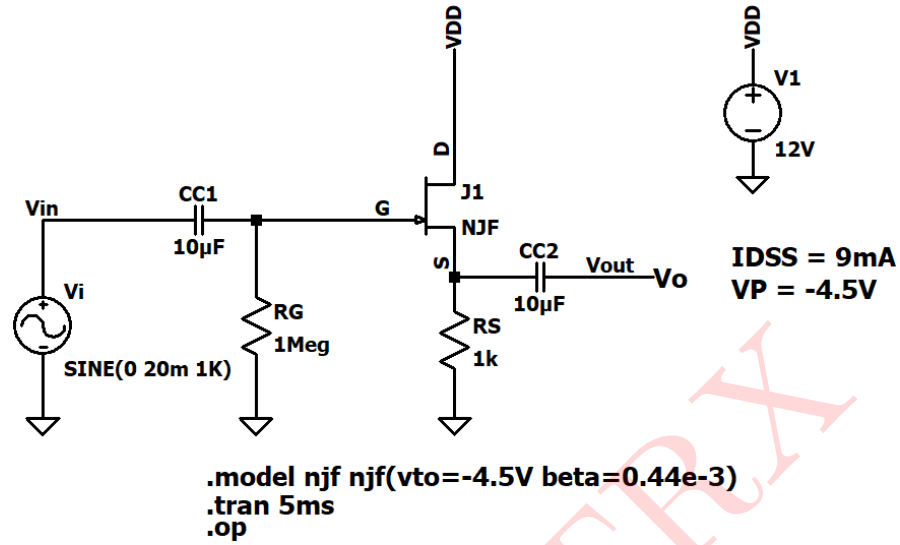


Figure 4: Circuit Schematic 1

The input and output waveforms are shown in figure 5.

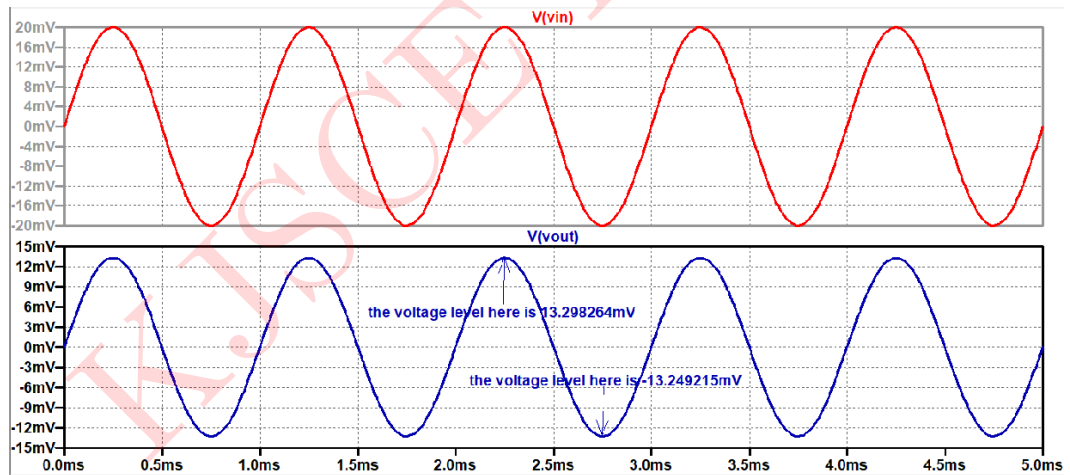


Figure 5: Input-Output waveforms

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	2.24mA	2.24247mA
V_{GS}	-2.242V	-2.242455V
A_V	0.666	0.6636

Table 1: Numerical 1

KJSCE ETRX

Numerical 2:

Determine V_o , Z_i , Z_o and A_V for the circuit given below in figure 6, if $V_i = 20mV$

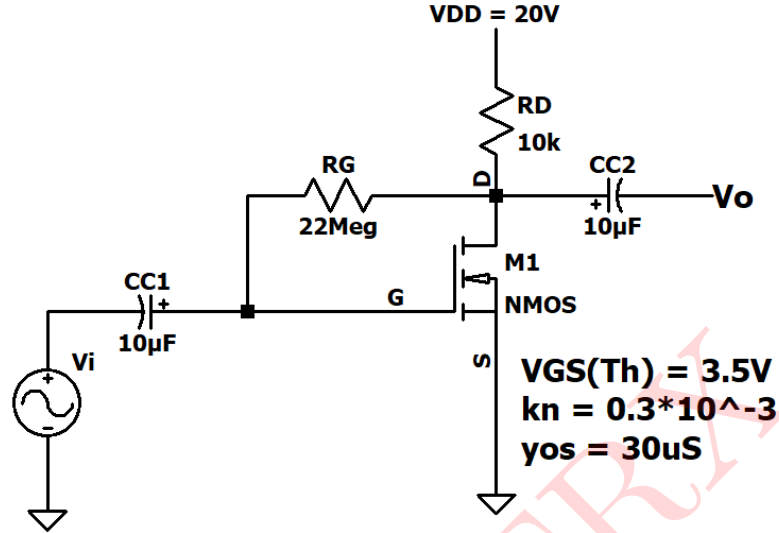


Figure 6: Circuit 2

Solution:

The above circuit is drain feedback bias consisting of N-channel E-MOSFET
DC analysis:

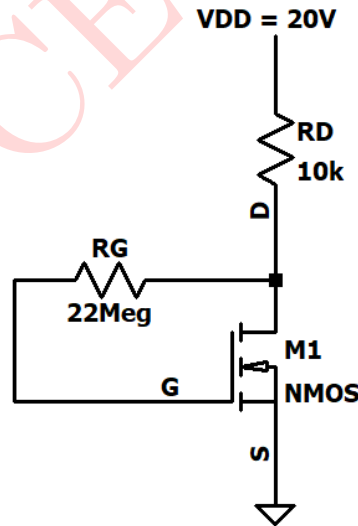


Figure 7: DC equivalent circuit

Since $I_g = 0$, $V_{GS} \approx V_{DS}$

Applying KVL to drain source loop,

$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$\therefore V_{DS} = V_{DD} - I_D R_D$$

$$V_{GS} = V_{DD} - I_D R_D \quad \dots(1)$$

In MOSFET,

$$I_{DQ} = k_n \left[V_{GSQ} - V_{GS(TH)} \right]^2$$

$$\therefore I_D = 0.3 \times 10^{-3} \text{mA/V}^2 [V_{GS} - 3.5V]^2$$

Substituting the value of I_D in equation (1),

$$\therefore V_{GS} = V_{DD} - I_D R_D$$

$$\therefore V_{GS} = 20V - (0.3 \times 10^{-3} [V_{GS} - 3.5V]^2)(10k\Omega)$$

$$\therefore V_{GS} = 20V - 3[V_{GS} - 3.5V]^2$$

$$\therefore V_{GS} = 20V - 3(V_{GS}^2 - 7V_{GS} + 12.25)$$

$$\therefore V_{GS} = 20V - (3V_{GS}^2 - 21V_{GS} + 36.75)$$

$$\therefore V_{GS} = 20V - 3V_{GS}^2 + 21V_{GS} - 36.75$$

$$\therefore V_{GS} = -3V_{GS}^2 + 21V_{GS} - 16.75$$

$$\therefore 0 = -3V_{GS}^2 + 20V_{GS} - 16.75$$

$$\therefore V_{GS} = 5.68V \text{ or } V_{GS} = 0.982V$$

We reject the value $V_{GS} = 0.982V$ ($\because |V_{GS}| > |V_{GS(TH)}|$)

$$\therefore V_{GS} = \mathbf{5.68V}$$

$$\therefore I_D = 0.3 \times 10^{-3} [V_{GS} - 3.5V]^2$$

$$= 0.3 \times 10^{-3} [5.68V - 3.5V]^2$$

$$= 0.3 \times 10^{-3} [2.18]^2 = \mathbf{1.425mA}$$

$$\therefore V_{GS} \approx V_{DS}$$

$$\therefore V_{DS} = \mathbf{5.68V}$$

Small signal parameters:

$$\text{i) } g_m = 2k_n (V_{GSQ} - V_{GS(TH)})$$

$$= 2 \times 0.3 \times 10^{-3} \text{mA/V}^2 (5.68 - 3.5)$$

$$= 0.6 \times 10^{-3} (2.18) = \mathbf{1.308mA/V}$$

$$\text{ii) } r_d = \frac{1}{y_{OS}} = \frac{1}{30\mu S} = \mathbf{33.33k\Omega}$$

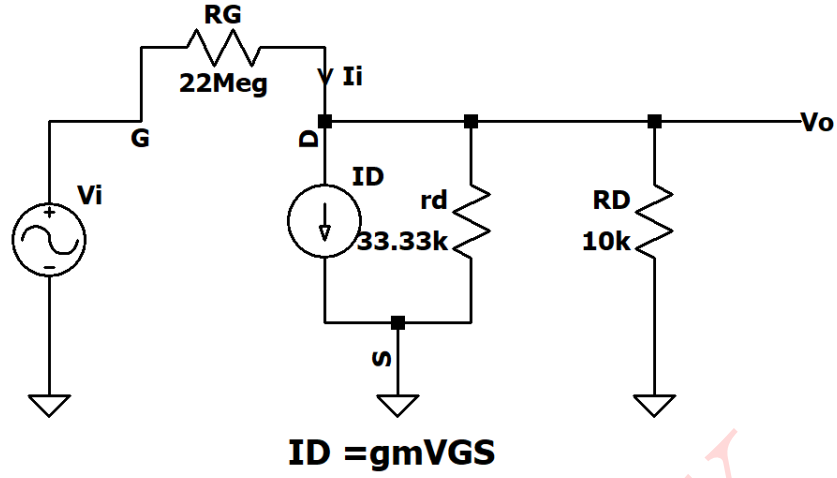


Figure 8: AC equivalent circuit

Applying KCL at D,

$$I_i = g_m V_{GS} + \frac{V_o}{r_d \parallel R_D}$$

$$\text{Also, } I_i = \frac{V_i - V_o}{R_G}$$

$$\therefore \frac{V_i - V_o}{R_G} = g_m V_i + \frac{V_o}{r_d \parallel R_D}$$

$$\therefore \frac{V_i}{R_G} - g_m V_i = \frac{V_o}{R_G} + \frac{V_o}{r_d \parallel R_D}$$

$$\therefore V_i \left[\frac{1}{R_G} - g_m \right] = V_o \left[\frac{1}{R_G} + \frac{1}{r_d \parallel R_D} \right]$$

$$\therefore \frac{1}{R_G} \approx \text{very small}$$

$$\therefore \frac{1}{R_G} - g_m \approx -g_m$$

$$\therefore V_i (-g_m) = V_o \left[\frac{1}{R_G} + \frac{1}{r_d \parallel R_D} \right]$$

$$\therefore \frac{V_o}{V_i} = -g_m (R_G \parallel r_d \parallel R_D)$$

$$\therefore A_V = -g_m (R_G \parallel r_d \parallel R_D)$$

$$\therefore A_V = -1.308 \text{ mA/V} (22 \text{ M}\Omega \parallel 33.33 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$= -1.308 \text{ mA/V} \left(22 \text{ M}\Omega \parallel \left(\frac{33.33 \text{ k}\Omega \times 10 \text{ k}\Omega}{33.33 \text{ k}\Omega + 10 \text{ k}\Omega} \right) \right)$$

$$= -1.308 \text{ mA/V} (22 \text{ M}\Omega \parallel 7.69 \text{ k}\Omega)$$

$$= -1.308 \text{ mA/V} \left(\frac{22 \text{ M}\Omega \times 7.69 \text{ k}\Omega}{22 \text{ M}\Omega + 7.69 \text{ k}\Omega} \right)$$

$$= -1.308 \text{ mA/V} (7.687 \text{ k}\Omega) = -10.05$$

Input impedance,

$$\begin{aligned}
 Z_i &= \frac{R_G + (r_d \parallel R_D)}{1 + g_m(r_d \parallel R_D)} \\
 &= \frac{22M\Omega + (33.33k\Omega \parallel 10k\Omega)}{1 + 1.308mA/V(33.33k\Omega \parallel 10k\Omega)} \\
 &= \frac{22M\Omega + \left(\frac{33.33k\Omega \times 10k\Omega}{33.33k\Omega + 10k\Omega} \right)}{1 + 1.308mA/V \left(\frac{33.33k\Omega \times 10k\Omega}{33.33k\Omega + 10k\Omega} \right)} \\
 &= \frac{22M\Omega + 7.69k\Omega}{1 + 1.308mA/V(7.69k\Omega)} = \mathbf{216.642k\Omega}
 \end{aligned}$$

Output impedance,

$$\begin{aligned}
 Z_o &= R_G \parallel r_d \parallel R_D \\
 &= 22M\Omega \parallel 33.33k\Omega \parallel 10k\Omega \\
 &= 22M\Omega \parallel \left(\frac{33.33k\Omega \times 10k\Omega}{33.33k\Omega + 10k\Omega} \right) \\
 &= 22M\Omega \parallel 7.69k\Omega \\
 &= \frac{22M\Omega \times 7.69k\Omega}{22M\Omega + 7.69k\Omega} = \mathbf{7.687k\Omega}
 \end{aligned}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

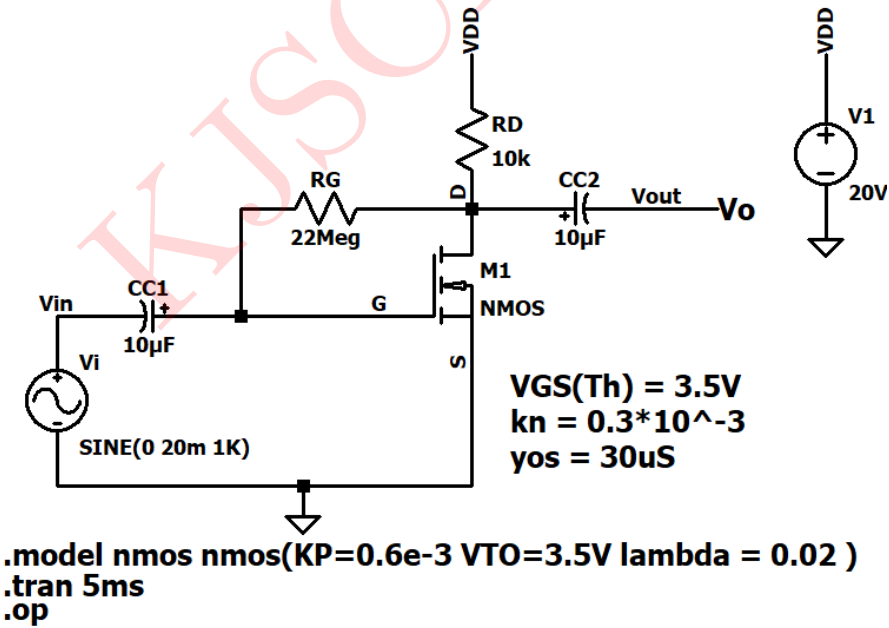


Figure 9: Circuit Schematic

The input and output waveforms are shown in figure 10.

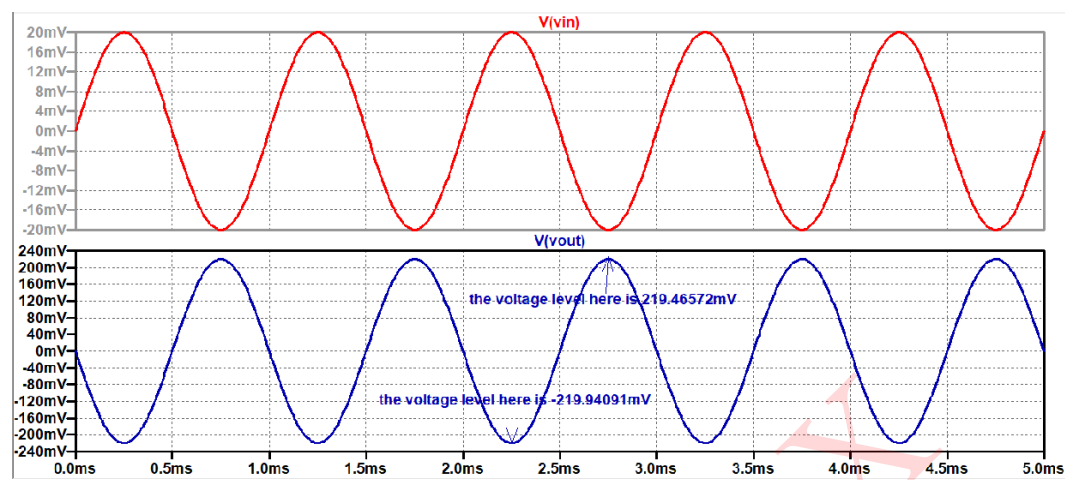


Figure 10: Input-Output waveforms

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	1.425mA	1.43155mA
V_{GS}	5.68V	5.68446V
A_V	-10.05	-10.985

Table 2: Numerical 2
