

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DC CIRCUITS

Numerical 1:

Introduce the ground terminal, write nodal equations, and solve for the node voltages for the current shown in the figure calculate the current through the resistance R_x and show its derivation in the figure.

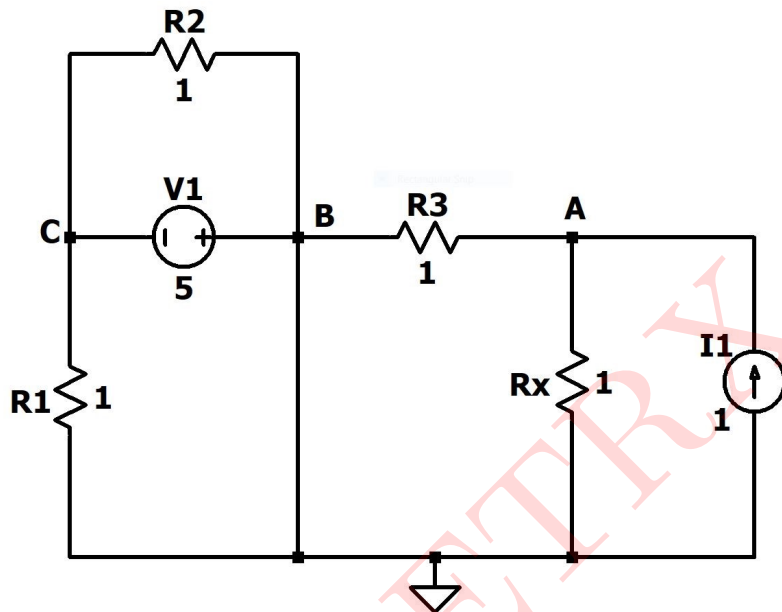


Figure 1: Circuit 1

Solution:

Using nodal analysis:

Node B is directly connected to ground, hence it get short and potential here is zero.

$$\therefore V_B = 0$$

As $V_B = 0$, node C is directly connected to a voltage source of 5V.

$$\therefore V_C = -5V$$

Applying KCL at node A

$$\frac{V_A - V_B}{1} + \frac{V_A}{1} = 1$$

$$\therefore 2V_A = 1V \quad \dots [\because V_B = 0]$$

$$\therefore V_A = 0.5V$$

$$\text{Current through resistance } R_X = \frac{V_A}{1}$$

$$\therefore I_{R_X} = 0.5\text{A}$$

Simulated Circuit:

The given circuit is simulated in LTspice and the results obtained are as follows:

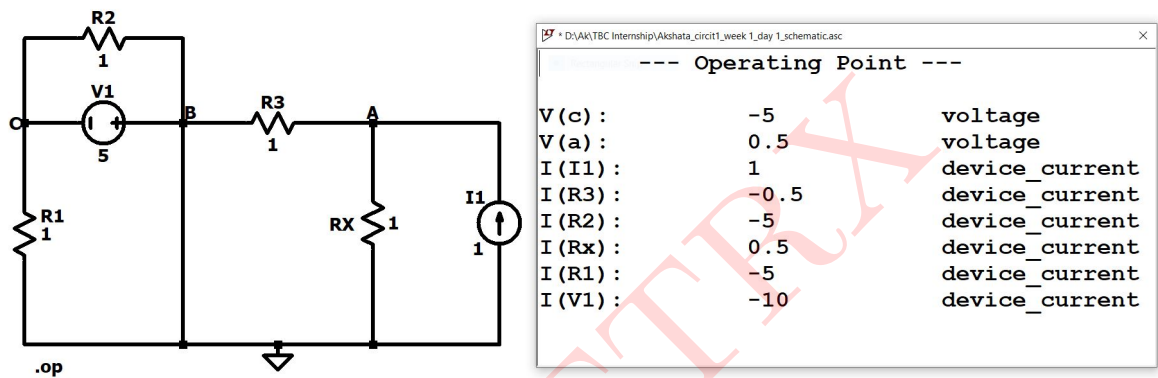


Figure 2: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_{R_X}	0.5A	0.5A
V_A	0.5V	0.5V
V_B	0V	0V
V_C	-5V	-5V

Numerical 2:

Use source transformation to find the current flowing through the $2\ \Omega$ resistor in the following circuit 2.

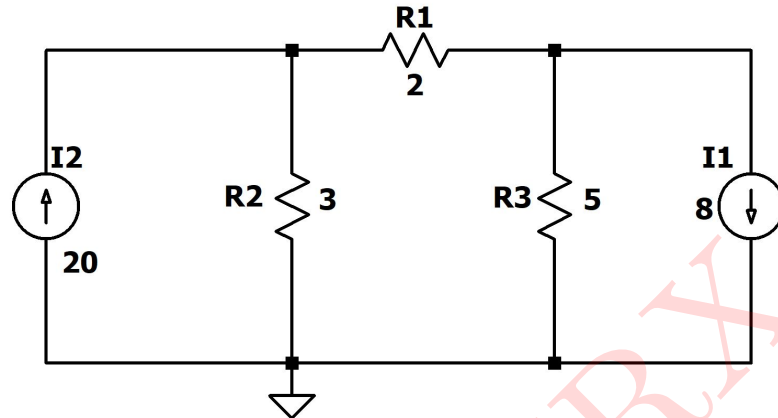


Figure 3: Circuit 2

Solution:

By applying source transformation, the circuit is reduced as,

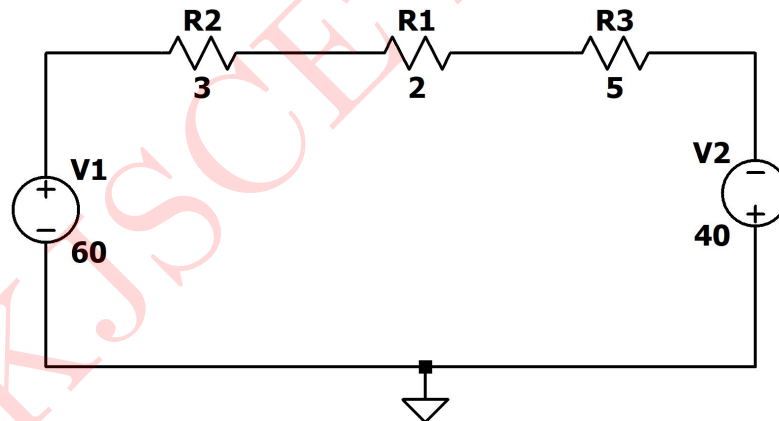


Figure 4: Modified circuit 1a after source transformation

After applying source transformation, 20A current source and parallel resistors gets converted to voltage source of 60V and a series resistance of $3\ \Omega$

$$V = I \times R$$

$$V = 20 \times 3$$

$$V = 60\text{V}$$

After applying source transformation, 8A current source and parallel resistors gets converted to voltage source of 40V and a series resistance of 5 Ω

$$V = I \times R$$

$$V = 8 \times 5$$

$$V = 40V$$

Now, Applying KVL to the entire loop

Assume current I flows in anticlockwise direction, We get

$$- 60 - 3i - 2i - 5i - 40 = 0$$

$$- 100 - 10i = 0$$

$$i = - \frac{100}{10}$$

$$i = - 10A$$

$$R_{2\Omega} = -10A$$

Hence the current flowing through 2 Ω resistor is $-10A$.

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

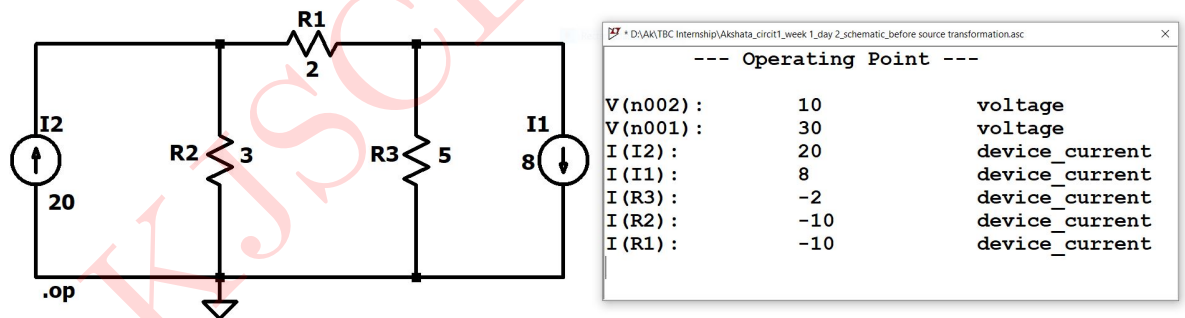


Figure 5: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{2\Omega}$	$-10A$	$-10A$

Numerical 3:

With the help of nodal analysis, calculate the values of nodal voltages V1 and V2 in the circuit 3.

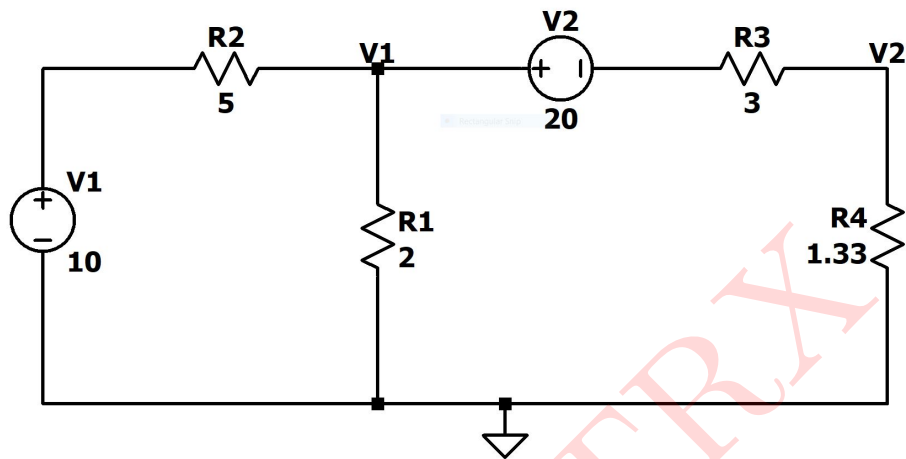


Figure 6: Circuit 3

Solution:

Assuming the current are moving away from the nodes

Applying KCL at V1,

$$\frac{V_1 - 10}{5} + \frac{V_1}{2} + \frac{V_1 - 20 - V_2}{3} = 0$$

$$31V_1 - 10V_2 = 260$$

.....(i)

Applying KCL at V2,

$$\frac{V_2 + 20 - V_1}{3} + \frac{V_2}{4/3} = 0$$

$$-4V_1 + 13V_2 = -80$$

.....(ii)

Solving equations (1) and (2) we get,

$$\mathbf{V_1 = 7.107V}$$

$$\mathbf{V_2 = 3.966V}$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

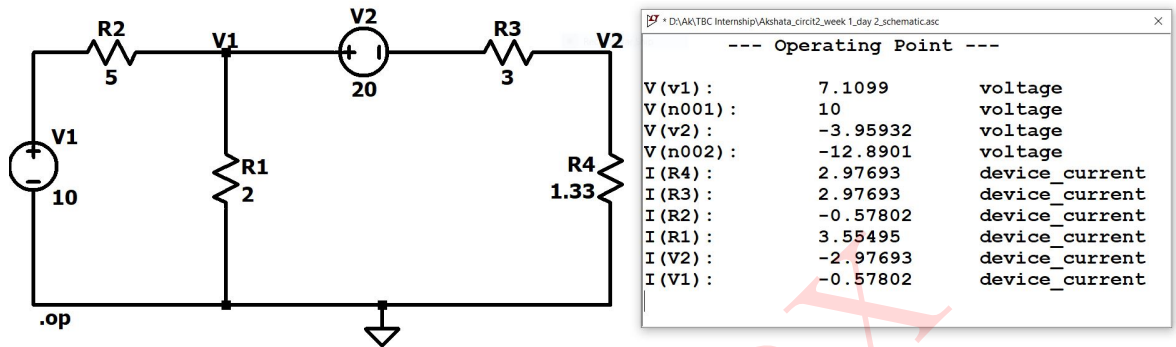


Figure 7: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_1	7.107V	7.1099V
V_2	-3.966V	-3.95932V

Numerical 4:

For the circuit shown below, find the equivalent resistance. All resistors are 22Ω .

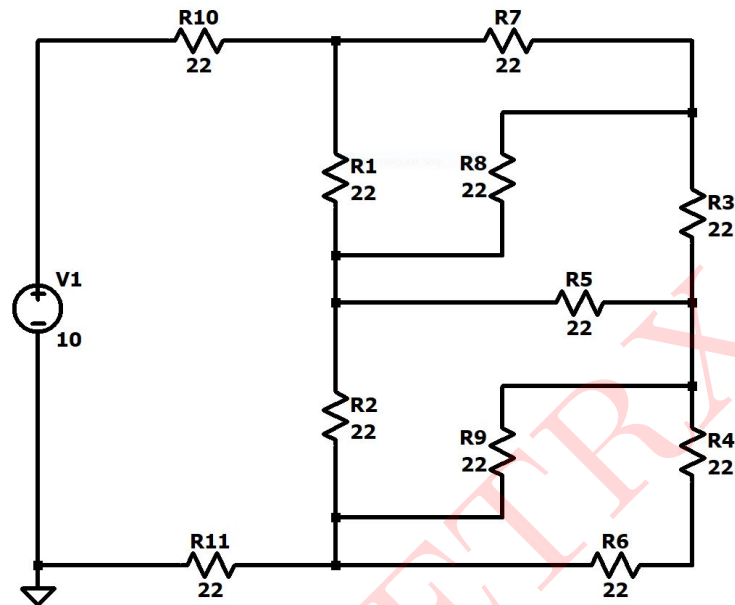


Figure 8: Circuit 4

Solution:

Converting Delta configuration of resistor to Star for Resistors R_1 , R_7 and R_8 .

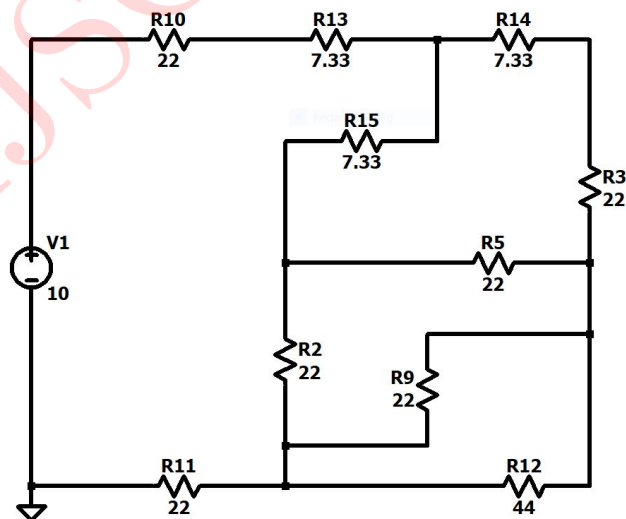


Figure 9: Modified circuit for figure 8

Adding resistances R_{10} and R_{13} , R_{14} and R_3 in series.

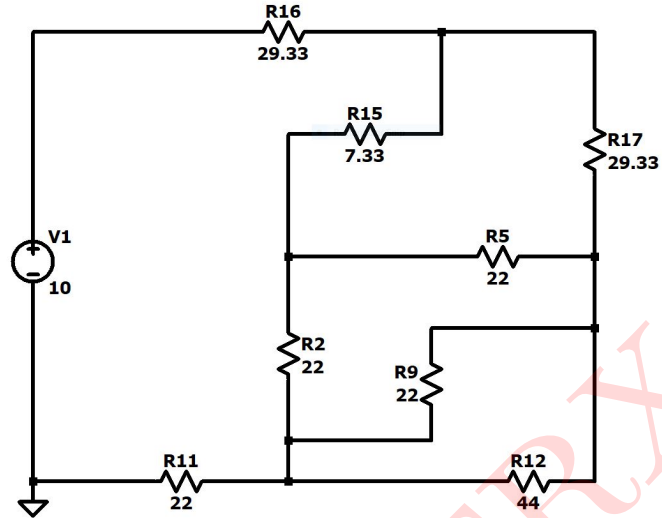


Figure 10: Circuit after adding the series resistances

Applying Delta to Star Conversion on R_5 , R_{15} and R_{17} .

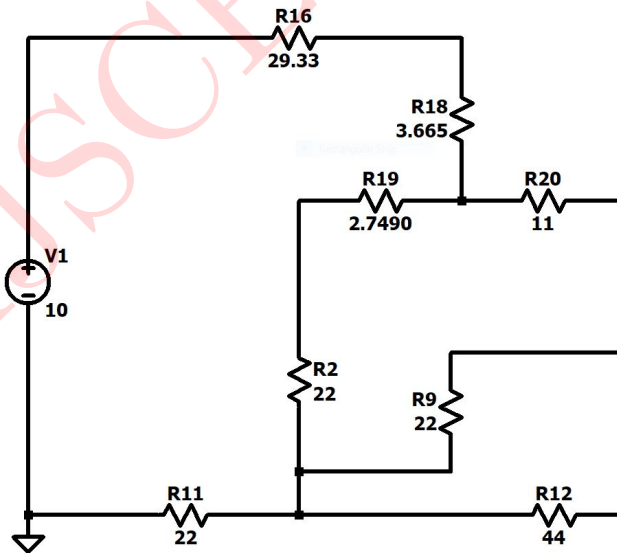


Figure 11: Modified circuit after delta to star conversion

Adding resistances R_{16} and R_{18} , R_2 and R_{19} in series, R_9 and R_{12} in parallel.

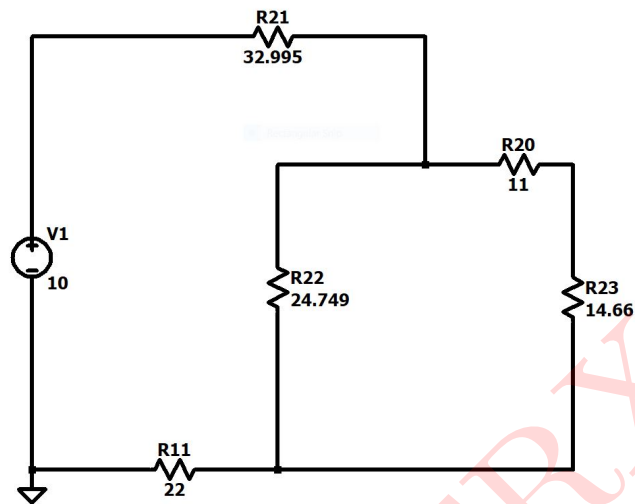


Figure 12: Modified circuit after series and parallel combination

Adding resistance R_{20} and R_{23} from Figure 2.12, we get:

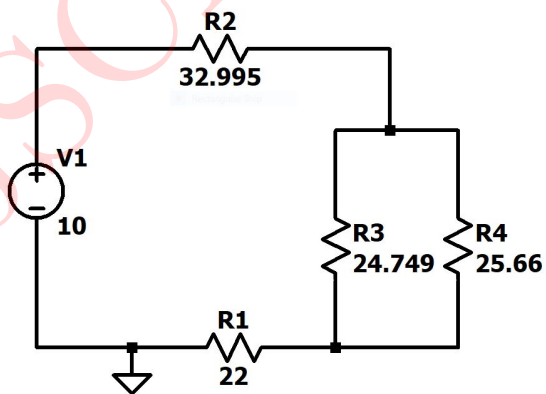


Figure 13: Modified circuit for previous figure

Finally, after solving the last series and parallel resistances from Figure 2.13, we get:

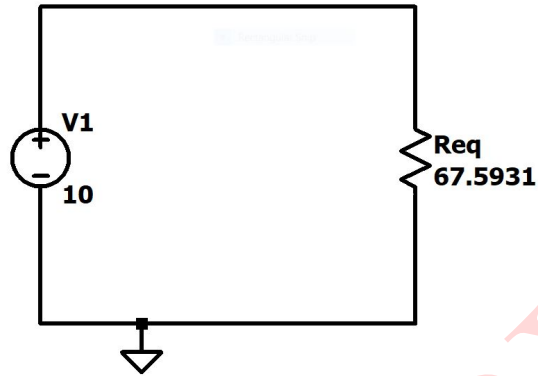


Figure 14: Modified circuit for calculating Equivalent Resistance

Hence, Equivalent Resistance $R_{eq} = 184.36364\Omega$

SIMULATED RESULTS:

The following circuit has been simulated in LTspice and the readings obtained are as follows:

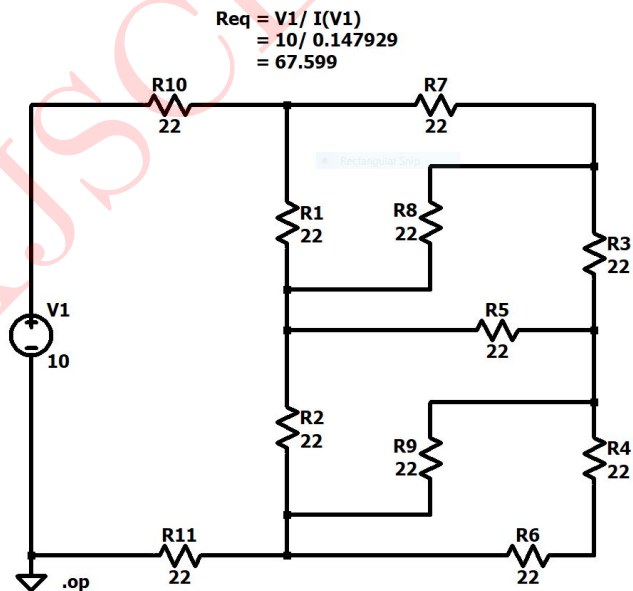


Figure 15: Circuit Schematic and Simulated Results

Comparison of theoretical and simulated values:

Quantity	Calculated Value	Simulated Value
R_{eq}	67.5931 Ω	67.599 Ω

KJSCE ETRX

Numerical 5:

Find Norton's equivalent circuit for the network shown in the figure 16. Verify it through its Thevenin's equivalent circuit.

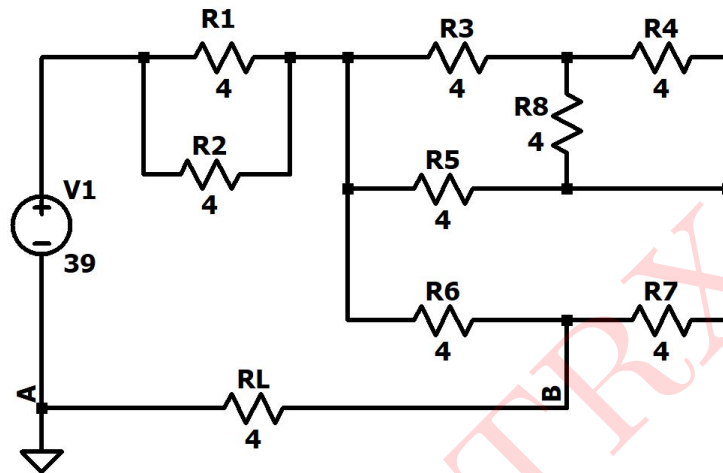


Figure 16: Circuit 5

Solution:

Replacing R_L by wire to calculate I_N and applying star delta transformation,

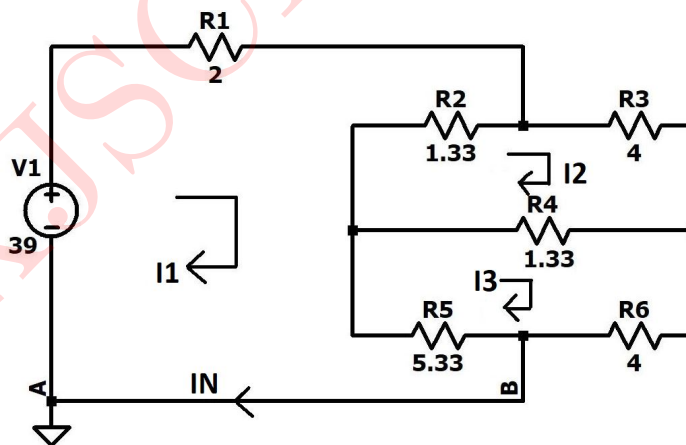


Figure 17: Modified circuit from previous figure

Applying KVL to loop (1),

$$39 - 2I_1 - \frac{4}{3}I_1 + \frac{4}{3}I_2 - \frac{16}{3}I_3 + \frac{16}{3}I_3 = 0$$

$$-\frac{26}{3}I_1 + \frac{4}{3}I_2 + \frac{16}{3}I_3 = 0 \quad \text{.....(i)}$$

Applying KVL to loop (2),

$$\frac{4}{3}I_2 - \frac{20}{3}I_2 + \frac{4}{3}I_3 = 0 \quad \text{.....(ii)}$$

Applying KVL to loop (3),

$$\frac{16}{3}I_1 + \frac{4}{3}I_2 - \frac{22}{3}I_3 = 0 \quad \text{.....(iii)}$$

By solving equation (i), (ii) and (iii),

$$I_1 = 7.24828A$$

$$I_2 = 2.22857A$$

$$I_3 = 3.90A$$

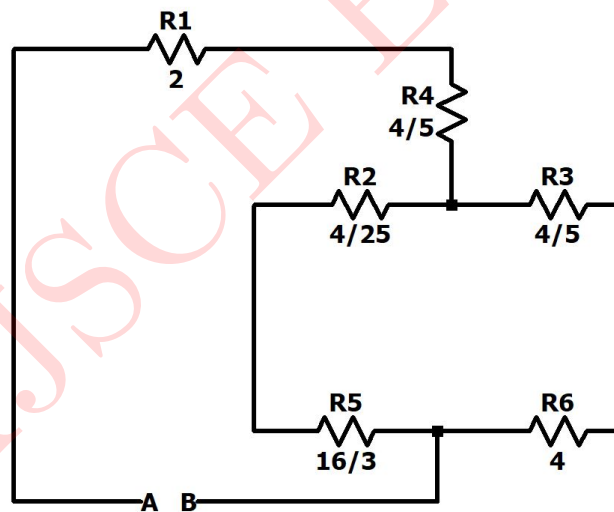


Figure 18: Circuit for calculating R_N

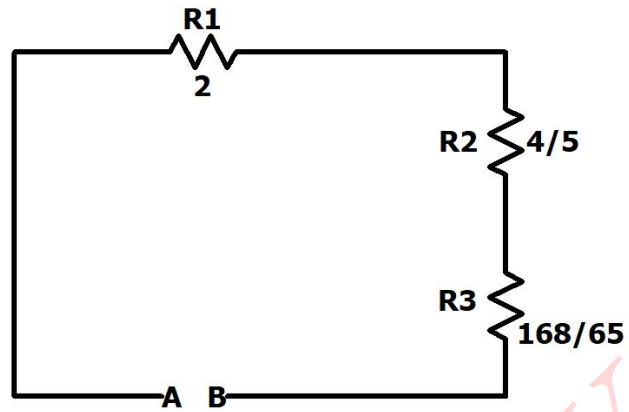


Figure 19: Modified circuit from previous figure

$$R_N = 2 + \frac{4}{5} + \frac{168}{65} = \frac{70}{13}$$

$$R_N = 5.3846\Omega$$

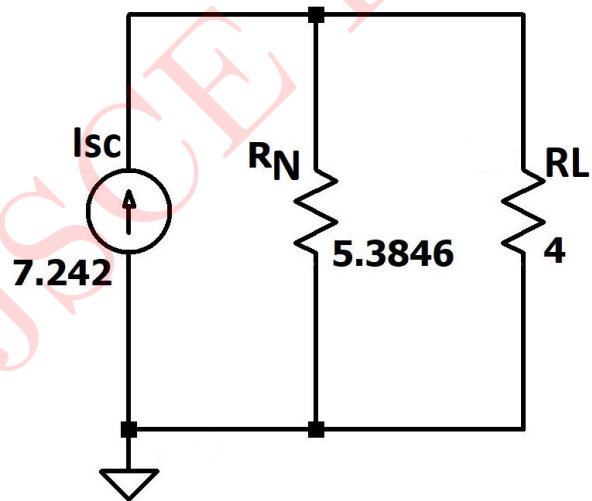


Figure 20: Norton's equivalent circuit

$$I_L = 7.242 \times \frac{\frac{70}{13}}{\frac{70}{13} + 4}$$

$$I_L = 4.153 \Omega$$

Verification using Thevenin's therorm,

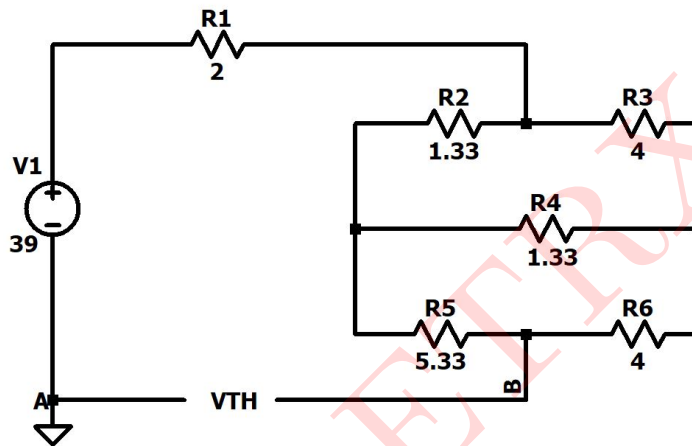


Figure 21: For calculating V_{TH}

$$V_{TH} = V_1$$

$$V_{TH} = 39V$$

$$R_{TH} = 5.3846\Omega$$

$$\therefore [V_1 = 39V]$$

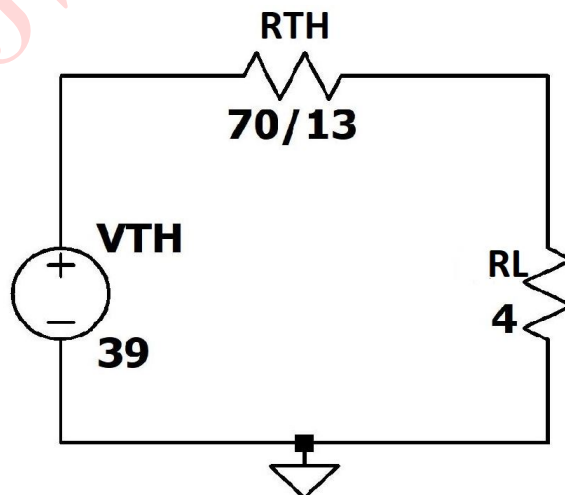


Figure 22: Thevenin's equivalent circuit

$$I_L = \frac{39}{\frac{70}{13} + 4}$$

$$I_L = 4.155A$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

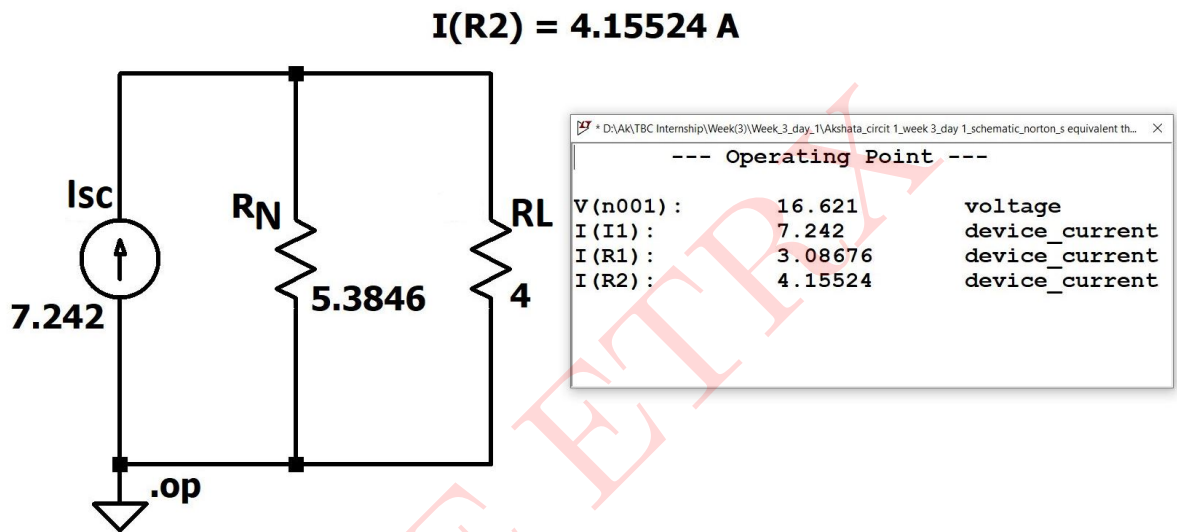


Figure 23: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_L	4.153A	4.1552A

Numerical 6:

Find the current and voltage in circuit 6 shown below.

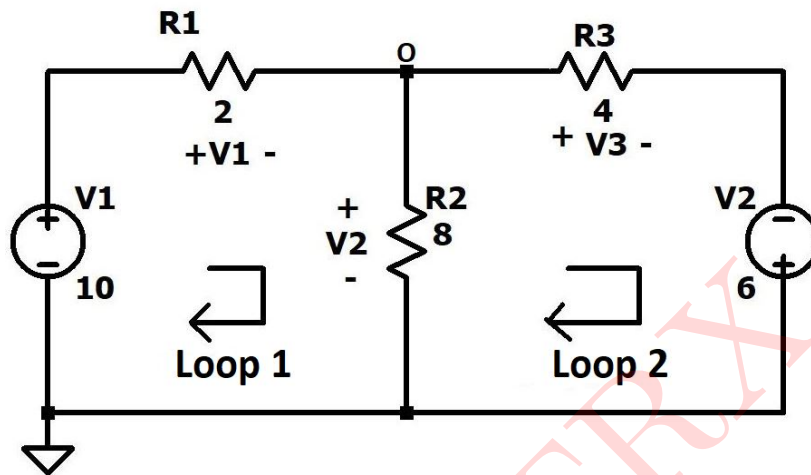


Figure 24: Circuit 6

Solution:

By Ohm's law,

$$V_1 = 2i_1$$

$$V_2 = 8i_2$$

$$V_3 = 4i_3$$

At node O, applying KCL

$$i_1 = i_2 + i_3$$

$$i_1 - i_2 - i_3 = 0$$

.....(1)

Applying KVL to loop I,

$$10 + V_1 - V_2 = 0$$

$$2i_1 + 8i_2 = 10$$

.....(2)

Applying KVL to loop II,

$$-V_3 + 6 + V_2 = 0$$

$$-8i_2 + 4i_3 = 6$$

.....(3)

Solving equations (1), (2) and (3), we get

$$i_1 = 3A$$

$$i_2 = 0.5A$$

$$i_3 = 2.5A$$

$$\therefore V_1 = 2i_1 = 2 \times 3$$

$$V_1 = 6V$$

$$\therefore V_2 = 8i_2 = 8 \times 0.5$$

$$V_2 = 4V$$

$$\therefore V_3 = 4i_3 = 4 \times 2.5$$

$$V_3 = 10V$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

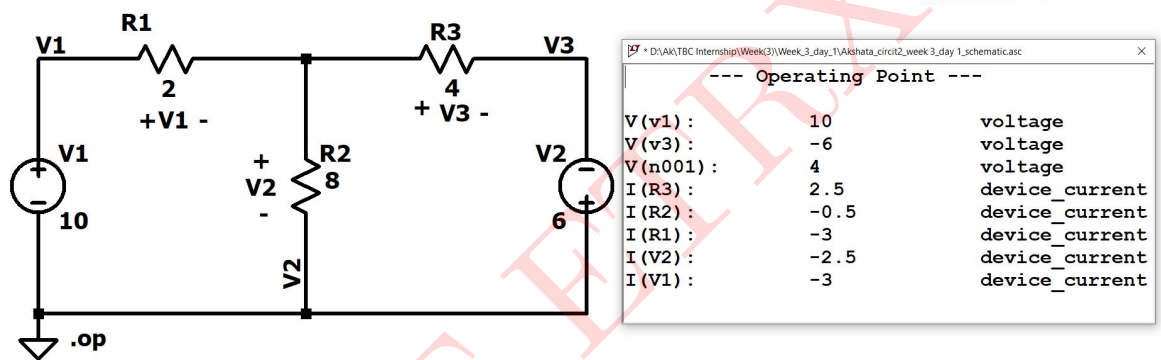


Figure 25: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V ₁	6V	6V
V ₂	4V	4V
V ₃	10V	10V
I ₁	3A	3A
I ₂	0.5A	0.5A
I ₃	2.5A	2.5A

Numerical 7:

Find V_x in the circuit 7 given below.

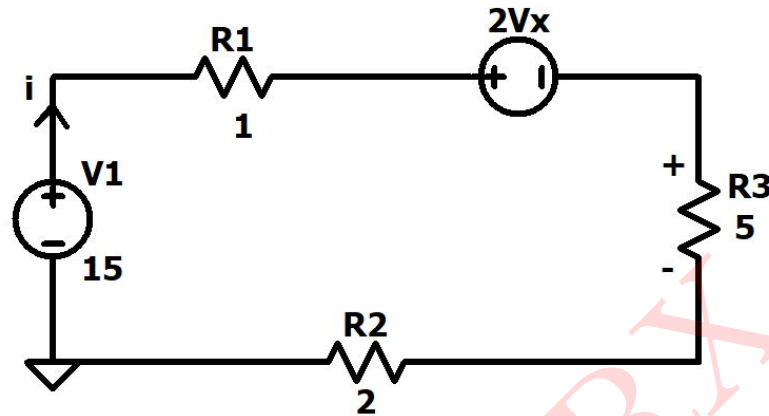


Figure 26: Circuit 7

Let i be the current flows through the circuit, applying KVL

$$-1(i) - 2V_x - 5(i) - 2(i) + 15 = 0$$

$$-8(i) + 15 - 2V_x = 0$$

Also,

$$V_x = 5i$$

$$-8i + 15 - 2V_x = 0$$

$$-8i + 15 - 2 \times 5i = 0$$

$$-18i + 15 = 0$$

$$i = \frac{15}{18} = \frac{5}{6} \text{ A}$$

$$V_x = 5 \times i = 5 \times \frac{5}{6}$$

$$\mathbf{V_x = 4.167A}$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

$$2 V_x = 2 * R_3 * I_3 = 2 * 5 * 0.833 = 8.33 \text{ V}$$

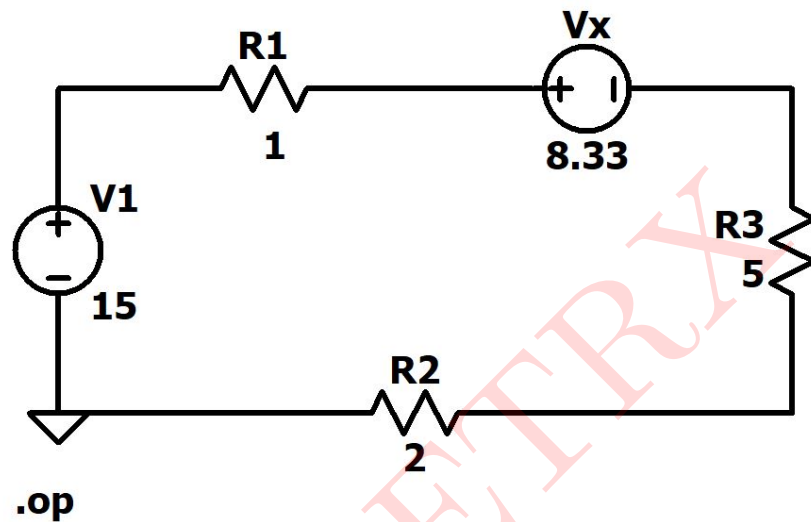


Figure 27: Circuit schematic and Simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_x	4.167V	4.16V
i	8.33Ω	8.33Ω

Numerical 8:

Find:

a) Thevenin voltage

b) Thevenin resistance

for two terminal network shown in the following figure 28

when, $R_1 = R_2 = R_3 = 1k\Omega$, $V_{s1} = V_{s2} = 10V$

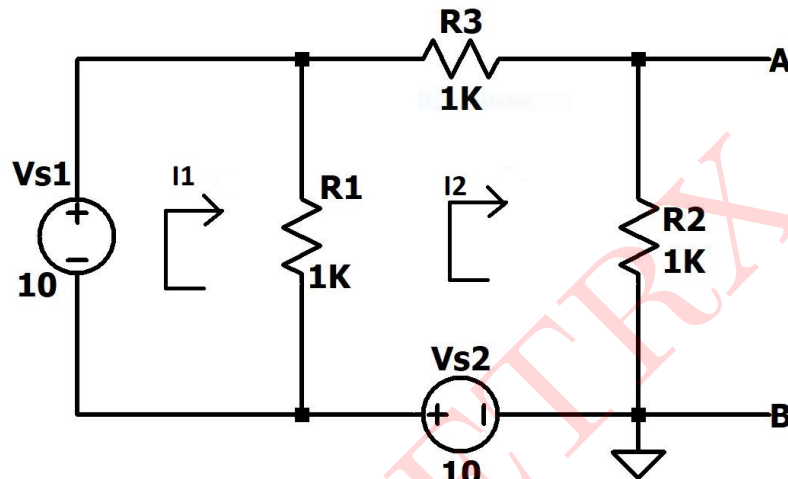


Figure 28: Circuit 8

Solution:

Applying KVL to loop (1),

$$-I_1 + I_2 + 10 = 0$$

$$-I_1 + I_2 = -10$$

.....(i)

Applying KVL to loop (2),

$$-3I_2 + I_1 + 10 = 0$$

$$I_1 - 3I_2 = -10$$

.....(ii)

By solving equation (i) and (ii),

$$I_1 = 20A$$

$$I_2 = 10A$$

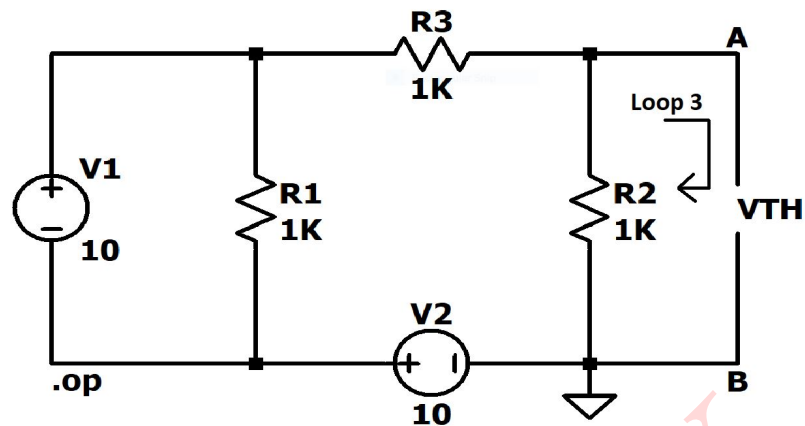


Figure 29: Circuit for calculating Thevenin's voltage

Applying KVL to loop (3),

$$-V_{TH} + I_2 = 0$$

$$\therefore V_{TH} = I_2$$

$$\therefore V_{TH} = 10V$$

For finding Thevenin's equivalent resistance, voltage source becomes short circuit and current source becomes open circuit.

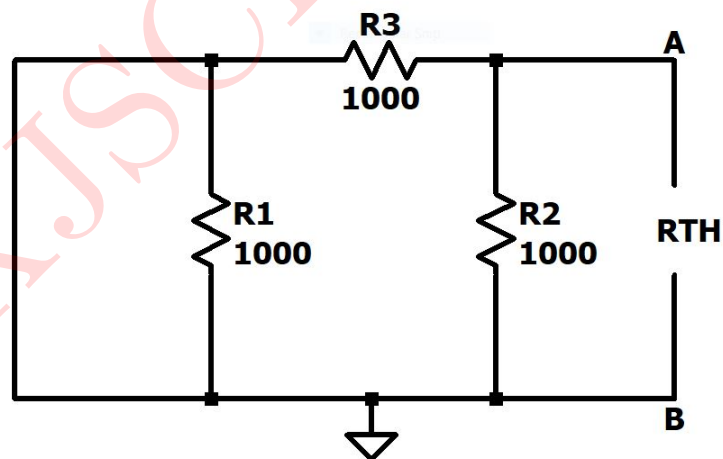


Figure 30: Circuit for calculating Thevenin's equivalent resistance

R_1 resistance gets shorted as it is connected in parallel with wire

$$\therefore R_{eq} = \frac{1}{\frac{1}{1} + \frac{1}{1}} = \frac{1}{2}$$

$$\therefore R_{TH} = 0.5 \text{ k } \Omega$$

$$\therefore R_{TH} = 500 \text{ } \Omega$$

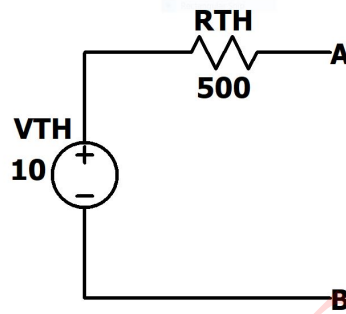


Figure 31: Thevenin's equivalent circuit for circuit 8

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

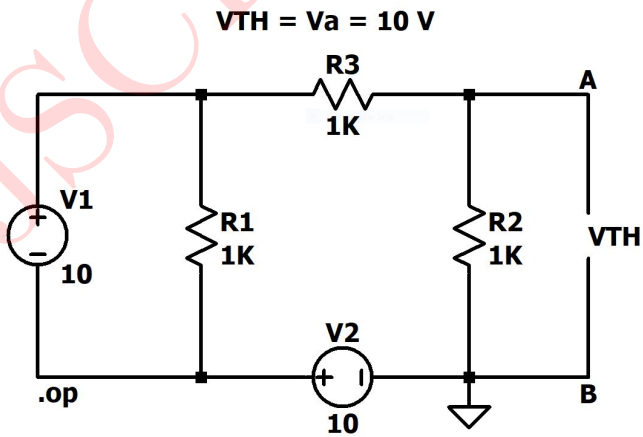


Figure 32: Circuit schematic and Simulated results for V_{TH}

$$R_{th} = V_{TH}/I(V_{th}) = 10/0.02 = 500 \text{ Ohms}$$

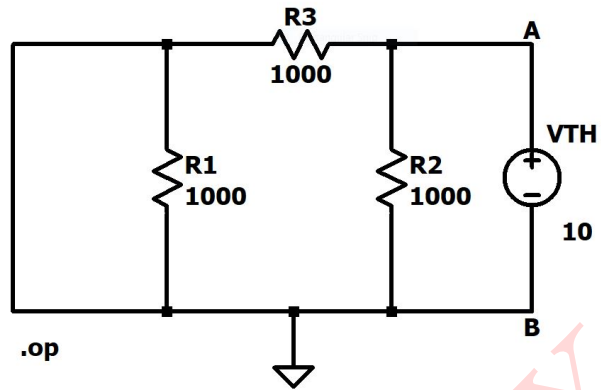


Figure 33: Circuit schematic and Simulated results for R_{TH}

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_{Th}	10V	10V
R_{Th}	500 Ω	500 Ω

Numerical 9:

Given the circuit 9 obtain the Norton equivalent as viewed from terminal C - D.

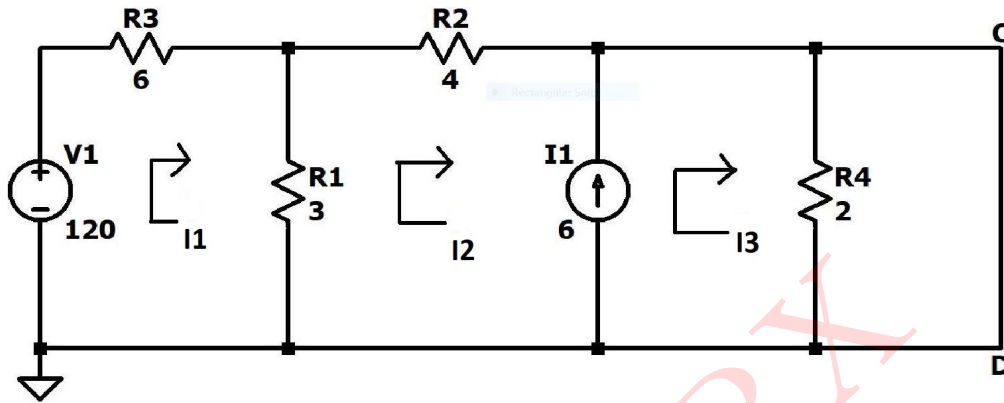


Figure 34: Circuit 9

Solution:

For finding Norton's current I_N applying mesh analysis,

From loop (1),

$$-9I_1 + 3I_2 = -120 \quad \text{.....(i)}$$

From loop (2),

Solving Supermesh,

$$I_2 - I_3 = -6 \quad \text{.....(ii)}$$

$$-3I_1 - 7I_2 - 2I_3 + 2I_N = 0 \quad \text{.....(iii)}$$

From loop (3),

$$2I_3 - 2I_N = 0 \quad \text{.....(iv)}$$

Solving above equations, we get

$$I_1 = \frac{140}{9}$$

$$I_2 = \frac{20}{3}$$

$$I_3 = \frac{38}{3}$$

$$I_N = \frac{38}{3}$$

$$\text{Norton current } I_N = \frac{38}{3} = 12.66\text{A}$$

For finding Norton equivalent resistance, voltage source becomes short circuit and current source becomes open circuit.

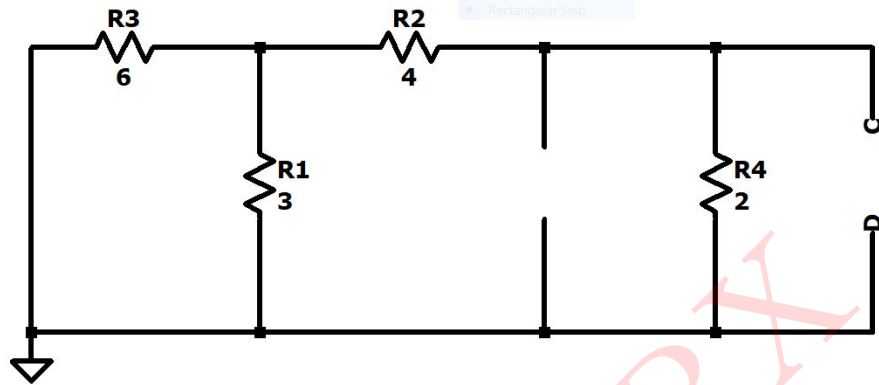


Figure 35: For calculating Norton's equivalent resistance

$$R_N = [(6 \parallel 3) + 4] \parallel 2 = \frac{3}{2}$$

$$\therefore R_N = 1.5 \, \Omega$$

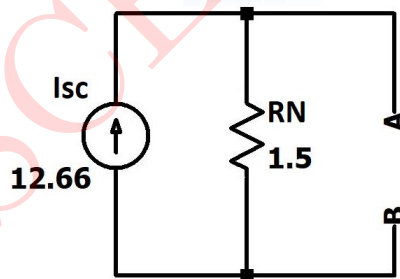


Figure 36: Norton's equivalent circuit

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

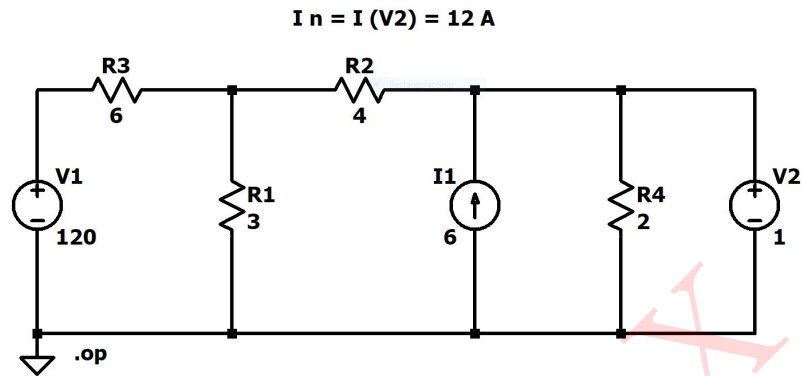


Figure 37: Circuit schematic and Simulated results for I_N

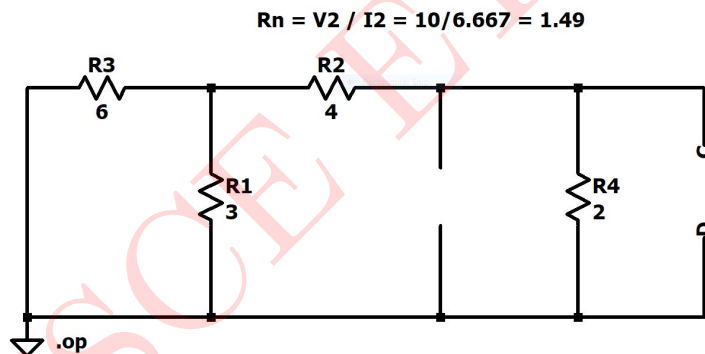


Figure 38: Circuit schematic and Simulated results for R_N

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_N	12.6V	12V
R_N	1.5Ω	1.49Ω

Numerical 10:

Find the value of R_L between A and B terminal for maximum power transfer theorem.

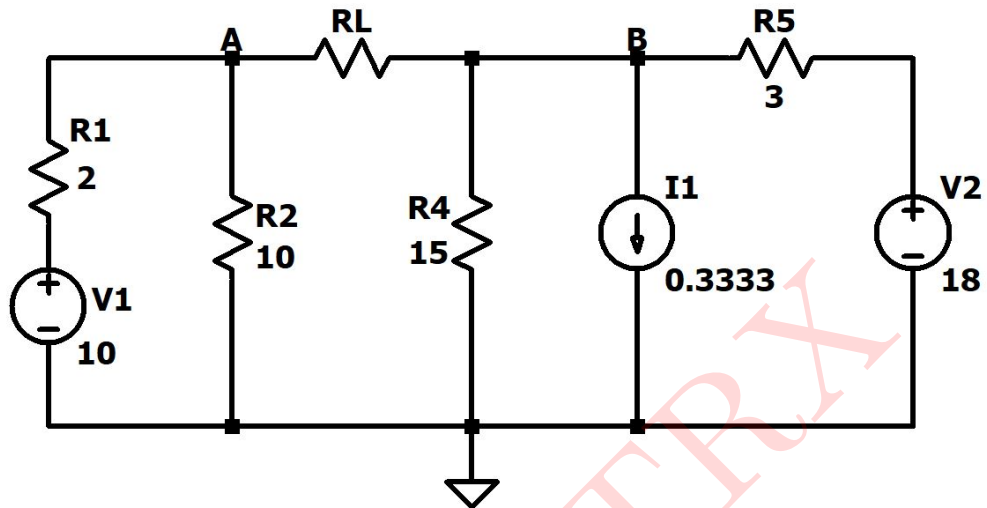


Figure 39: Circuit 10

Solution:

For finding V_{TH} , applying mesh analysis

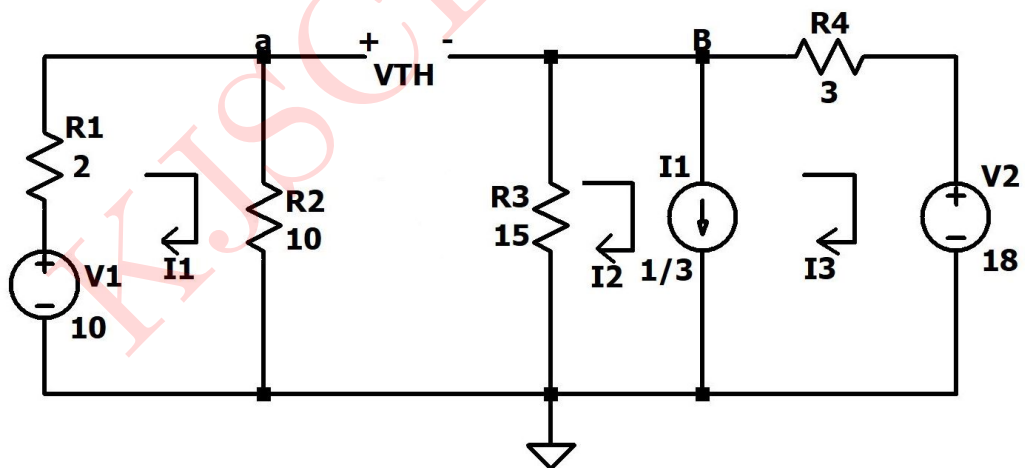


Figure 40: For calculating V_{TH}

From loop (1),

$$12I_1 + 10 = 0$$

$$\therefore I_1 = 0.8333A$$

.....(i)

Solving supermesh of loop (2) and (3),

$$I_2 - I_3 = \frac{1}{3} \quad \text{.....(ii)}$$

$$-15I_2 - 3I_3 + 18 = 0 \quad \text{.....(iii)}$$

On solving (ii) and (iii), we get

$$\therefore I_2 = -0.944\text{A}$$

$$\therefore I_3 = -1.277\text{A}$$

Now,

$$-V_{TH} + 15I_1 + 10I_1 = 0$$

$$\therefore V_{TH} = 5.8266\text{V}$$

For finding R_{TH} , voltage source becomes short circuit and current source becomes open circuit.

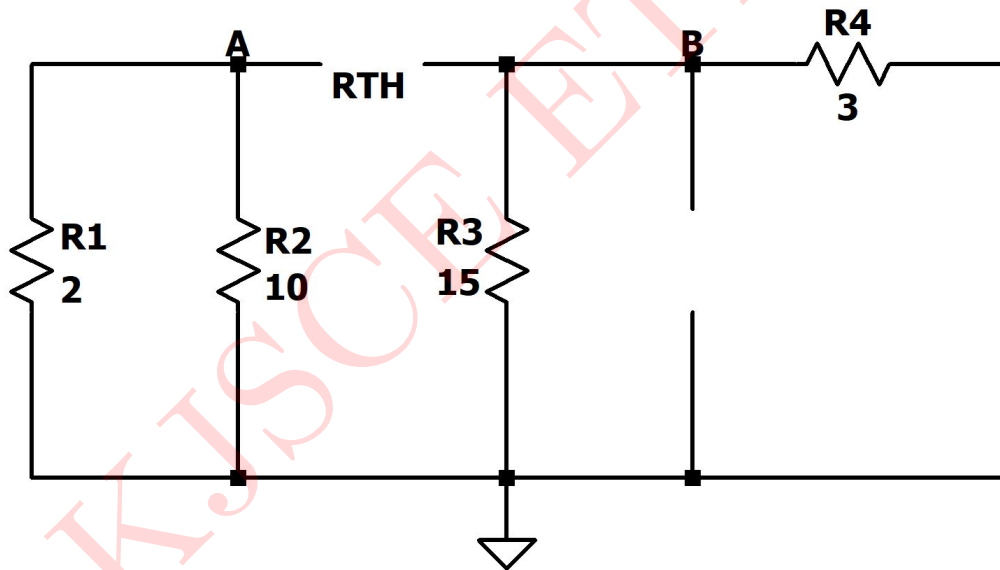


Figure 41: For calculating R_{TH}

$$(2 \parallel 10) + (3 \parallel 15) = \frac{5}{3} + \frac{5}{2} = \frac{25}{6}$$

$$\therefore R_{TH} = 4.1666 \Omega$$

∴ Maximum power:

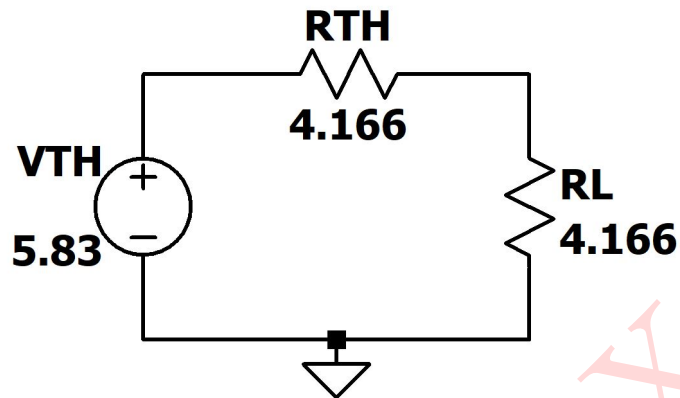


Figure 42: For calculating maximum power

$$P_{\text{MAX}} = \frac{V_{\text{TH}}^2}{4 \times R_{\text{TH}}}$$

$$P_{\text{MAX}} = \frac{(5.82)^2}{4 \times 4.1666}$$

$$\therefore P_{\text{MAX}} = 2.032 \text{ Watt}$$

Simulated Circuit:

The given circuit is simulated in LTspice and the results obtained are as follows:

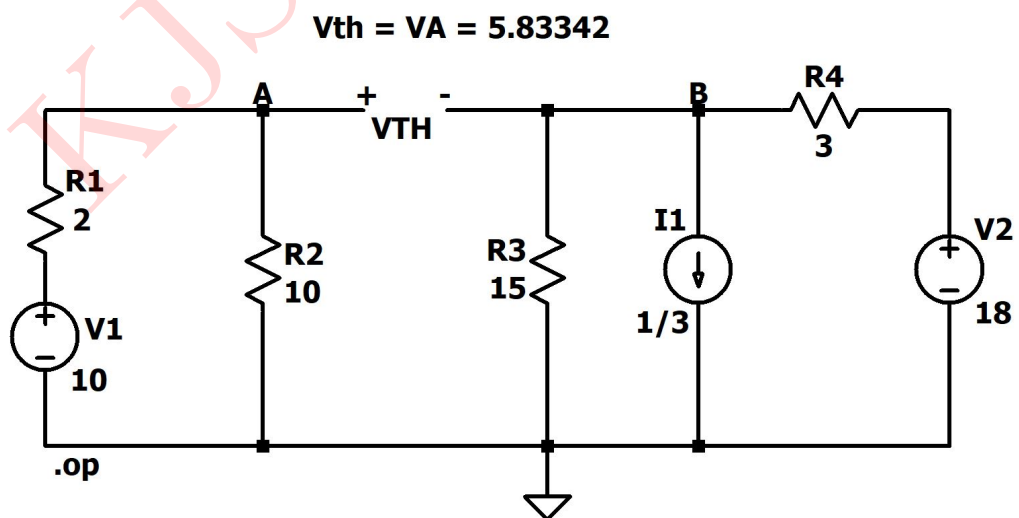


Figure 43: Circuit schematic and Simulated results for V_{TH}

$$\begin{aligned}
 \text{Max. Power} &= I \cdot I \cdot R_L \\
 &= 0.6997 \cdot 0.6997 \cdot 4.166 \\
 &= 2.039 \text{ W}
 \end{aligned}$$

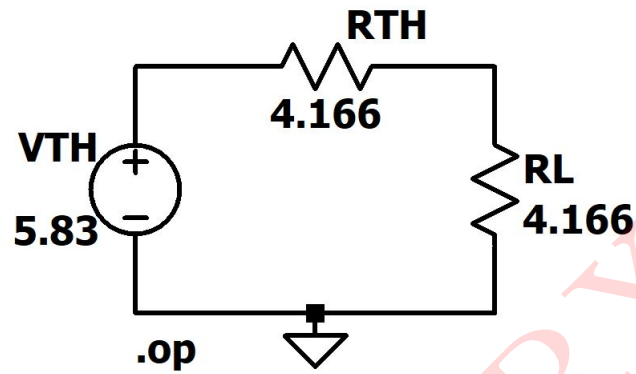


Figure 44: Circuit schematic and Simulated results for P_{MAX}

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_{TH}	5.82V	5.833V
R_{TH}	4.166Ω	4.166Ω
P_{MAX}	2.032W	2.039W

Numerical 11:

Find the value of resistor R_L for maximum power transfer theorem and maximum power.

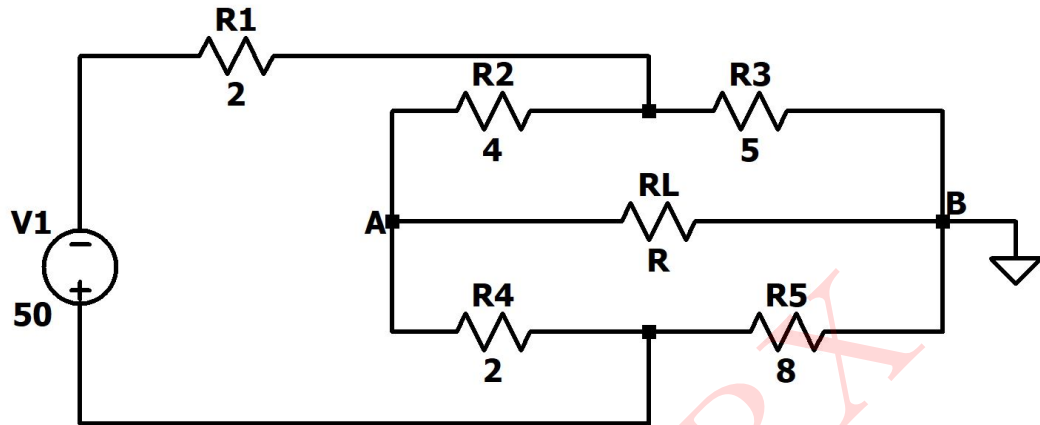


Figure 45: Circuit 11

Solution:

For finding V_{TH} , applying mesh analysis

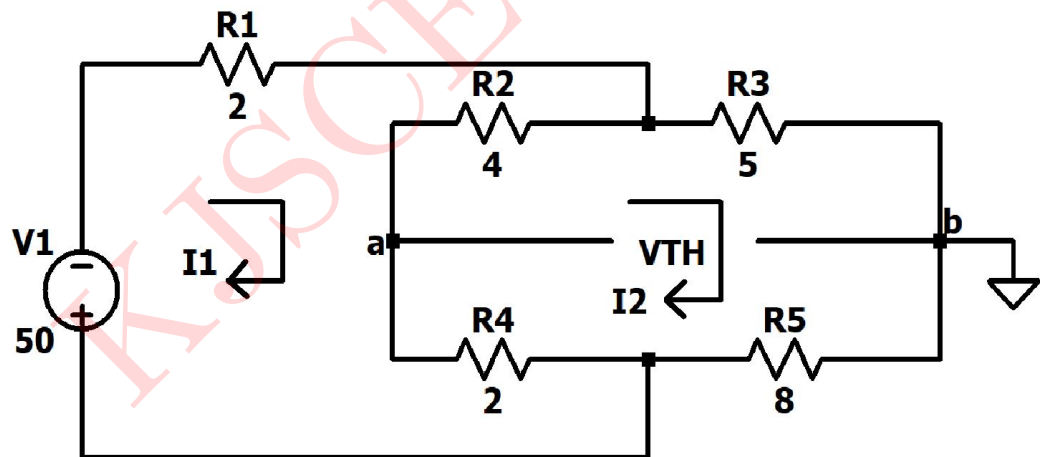


Figure 46: For calculating V_{TH}

From loop (1),

$$8I_1 - 6I_2 = 50 \quad \text{.....(i)}$$

$$6I_1 - 19I_2 = 0 \quad \text{.....(ii)}$$

On solving (i) and (ii), we get

$$\therefore I_1 = 8.189\text{A}$$

$$\therefore I_2 = 2.586\text{A}$$

Now,

$$-V_{\text{TH}} + 2I_1 - 10I_2 = 0$$

$$V_{\text{TH}} = 2I_1 - 10I_2 = 0$$

$$\therefore V_{\text{TH}} = -9.482\text{V}$$

For finding R_{TH} , voltage source becomes short circuit.

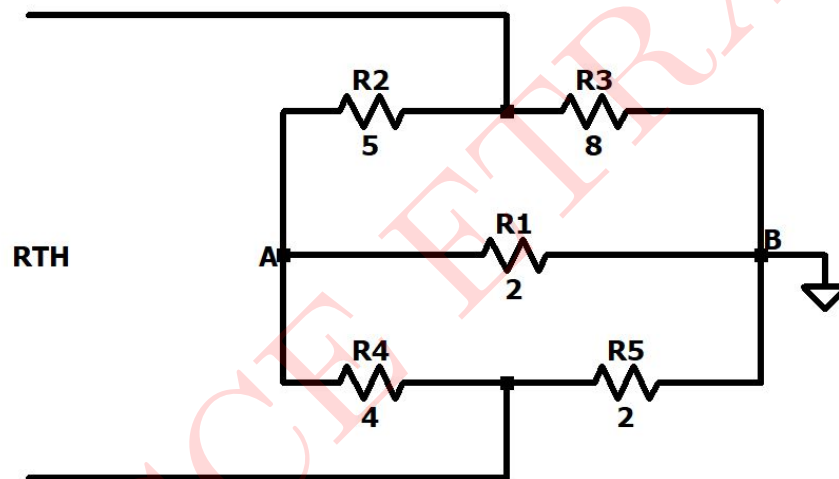


Figure 47: For calculating R_{TH}

After applying star delta transformation to 5Ω , 8Ω and 2Ω , we get

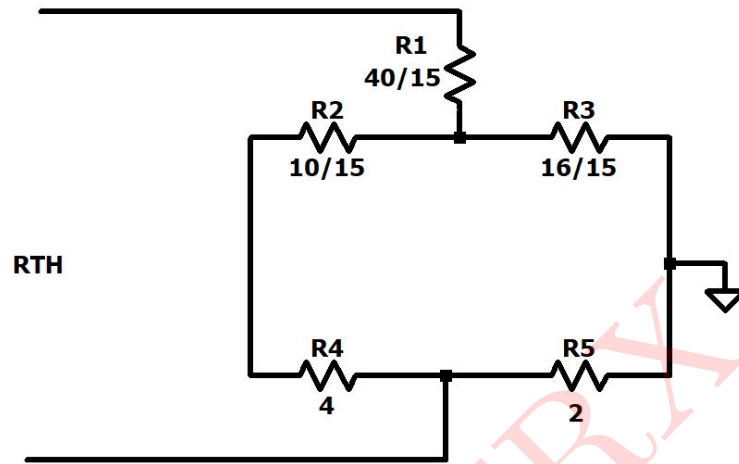


Figure 48: Modified circuit form previous figure

Applying series parallel transformation to R_2 , R_3 , R_4 and R_5 , we get

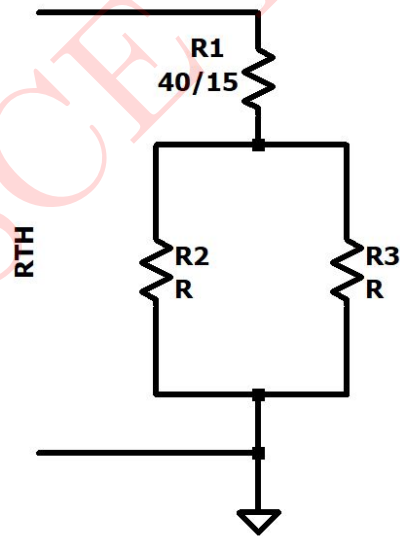


Figure 49: Modified circuit for calculating R_{TH}

$$R_{TH} = \frac{40}{15} + \left(\frac{14}{3} \parallel \frac{46}{15} \right)$$

$$\therefore R_{TH} = 4.51 \, \Omega$$

\therefore Maximum power :

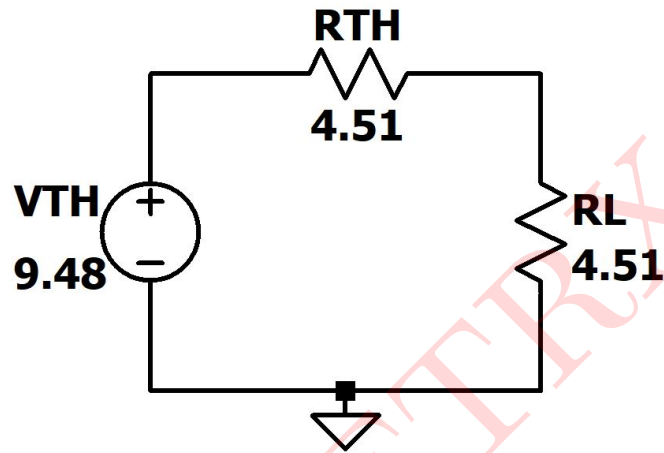


Figure 50: For calculating maximum power

$$P_{MAX} = \frac{V_{TH}^2}{4 \times R_{TH}}$$

$$P_{MAX} = \frac{(9.482)^2}{4 \times 4.51}$$

$$\therefore P_{MAX} = 4.98 \text{ Watt}$$

Simulated Circuit:

The given circuit is simulated in LTspice and the results obtained are as follows:

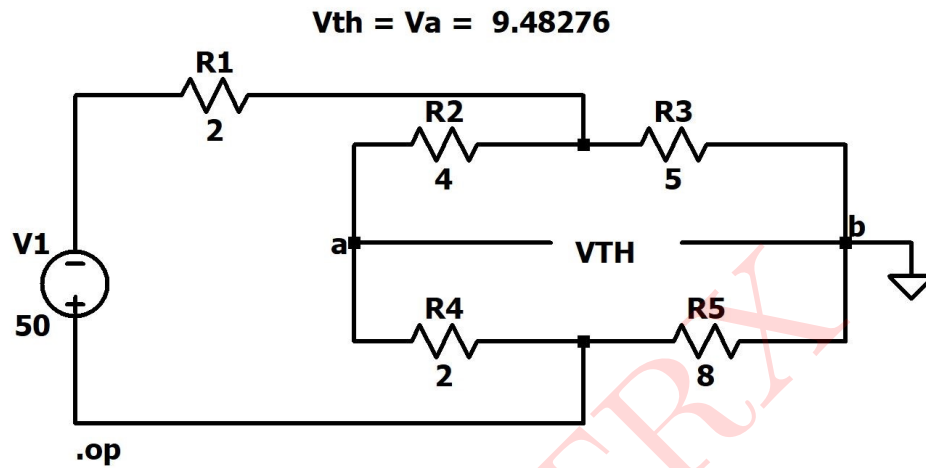


Figure 51: Circuit schematic and Simulated results for V_{TH}

$$\begin{aligned}\text{Max. Power} &= I \cdot I \cdot R_L \\ &= 1.051 \cdot 1.051 \cdot 4.51 \\ &= 4.98 \text{ W}\end{aligned}$$

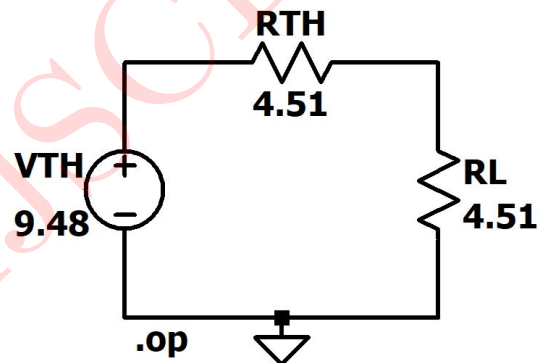


Figure 52: Circuit schematic and Simulated results for P_{MAX}

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_{TH}	9.48V	9.48V
R_{TH}	4.51 Ω	4.51 Ω
P_{MAX}	4.98W	4.98W

KJSCE ETRX