

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**

15<sup>th</sup> July, 2020

Numericals

**Numerical:** Determine the following for the circuit shown in figure 1. Assume

$$\beta_1 = \beta_2 = 100$$

- Name of the circuit
- Current flowing through resistors  $R_{S1}$ ,  $R_{S2}$ ,  $R_{C1}$  and  $R_{C2}$
- $V_{C1}$ ,  $V_{C2}$ ,  $V_{CE1}$ ,  $V_{CE2}$
- differential voltage gain
- Common mode gain
- CMRR (in dB)

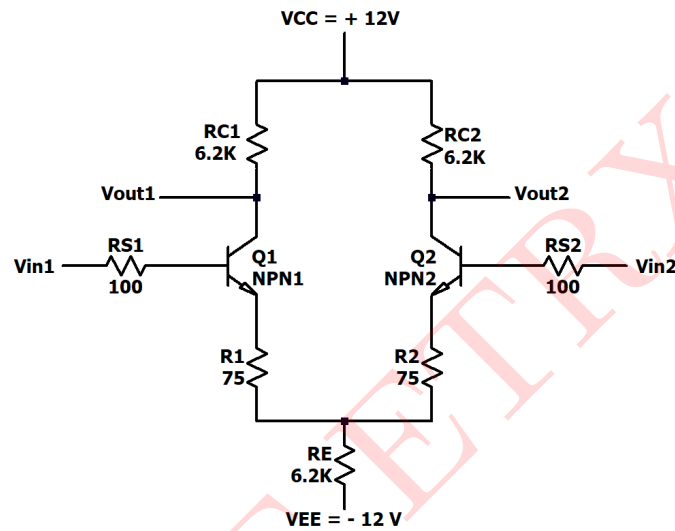


Figure 1: Circuit 1

**Solution:**

The given circuit is a Dual input Balanced output (DIBO) differential amplifier.

**DC ANALYSIS:**

Applying KVL to Base - Emitter loop;

$$-I_{B1}R_{S1} - V_{BE1} - I_{E1}R_{E1} - 2R_E I_{E1} - V_{EE} = 0$$

$$\text{But } V_{BE1} = V_{BE2} = 0.7V$$

$$\text{And } I_{E1} = (\beta + 1)I_{B1}$$

$$\therefore -I_{B1}R_{S1} - V_{BE1} - (\beta + 1)I_{B1}R_1 - (2R_E)(\beta + 1)I_{B1} - V_{EE} = 0$$

$$\therefore -V_{EE} - V_{BE1} = I_{B1}(R_{S1} + (\beta + 1)(R_1 + 2R_E))$$

$$\therefore I_{B1} = \frac{-V_{EE} - V_{BE1}}{R_{S1} + (1 + \beta)(R_1 + 2R_E)} = \frac{12 - 0.7}{100 + (101)(75 + (2 \times 6.2k))} = 8.96 \mu A$$

$$I_{C1} = \beta \times I_{B1} = 10 \times 8.96 \times 10^{-6} = 0.896 \text{ mA} \quad (\text{current flowing across } R_{C1})$$

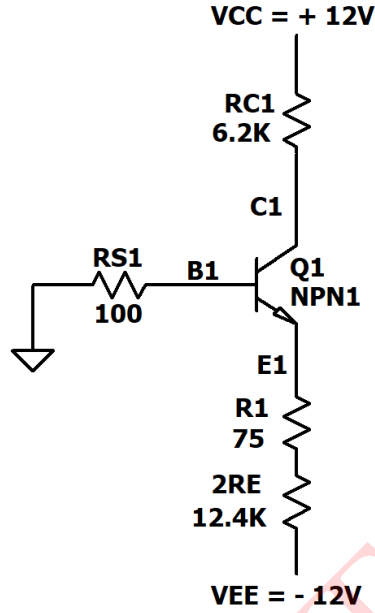


Figure 2: DC ANALYSIS

The DC values are the same for both the transistors

$$\therefore I_{B1} = I_{B2} = \mathbf{8.96\mu A}$$

$$I_{C1} = I_{C2} = 0.896mA$$

$$\therefore I_{B2} = \mathbf{8.96\mu A} \quad (\text{current flowing across } R_{S2})$$

$$I_{C2} = \mathbf{0.896mA} \quad (\text{current flowing across } R_{C2})$$

Applying KVL to the Common - Emitter loop;

$$V_{CE1Q} = V_{CC} + V_{EE} - I_{C1Q}(R_{C1} + 2R_E + R_1) \quad (\text{where } V_{EE} = 12V)$$

$$V_{CE1Q} = 12 + 12 - (0.896 \times 10^{-3})(3.2k + 75 + (2 \times 6.2k)) = \mathbf{7.2672V}$$

$$V_{CE1Q} = V_{CE2Q} = \mathbf{7.2672V}$$

$$\text{Also } V_{C1} = V_{CC} - I_{C1Q}R_{C1} = 12 - (0.896 \times 10^{-3})(6.2 \times 10^3) = \mathbf{6.44V}$$

$$V_{C1} = V_{C2} = \mathbf{6.44V}$$

#### AC ANALYSIS:

$$|A_d| = \frac{\beta R_C}{2(R_S + r_\pi + \beta R_1)}$$

$$\beta = \beta_1 = \beta_2 = 100$$

$$\text{And } r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$I_{CQ} = I_{C1Q} = I_{C2Q} = 0.896\text{mA}$$

$$r_{\pi} = \frac{100 \times 26 \times 10^{-3}}{0.896 \times 10^{-3}} = 2.901\text{k}\Omega$$

$$|A_d| = \frac{100 \times 3.2 \times 10^3}{2(100 + 2901 + (100)(75))} = 59.04$$

$$A_{cm} = \frac{R_C}{2R_E} = \frac{6.2k}{2 \times 6.2k} = 0.5$$

$$\text{CMRR} = \frac{A_d}{A_{cm}} = \frac{59.04}{0.5} = 118.18$$

$$\text{CMRR (in dB)} = 41.44\text{dB}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

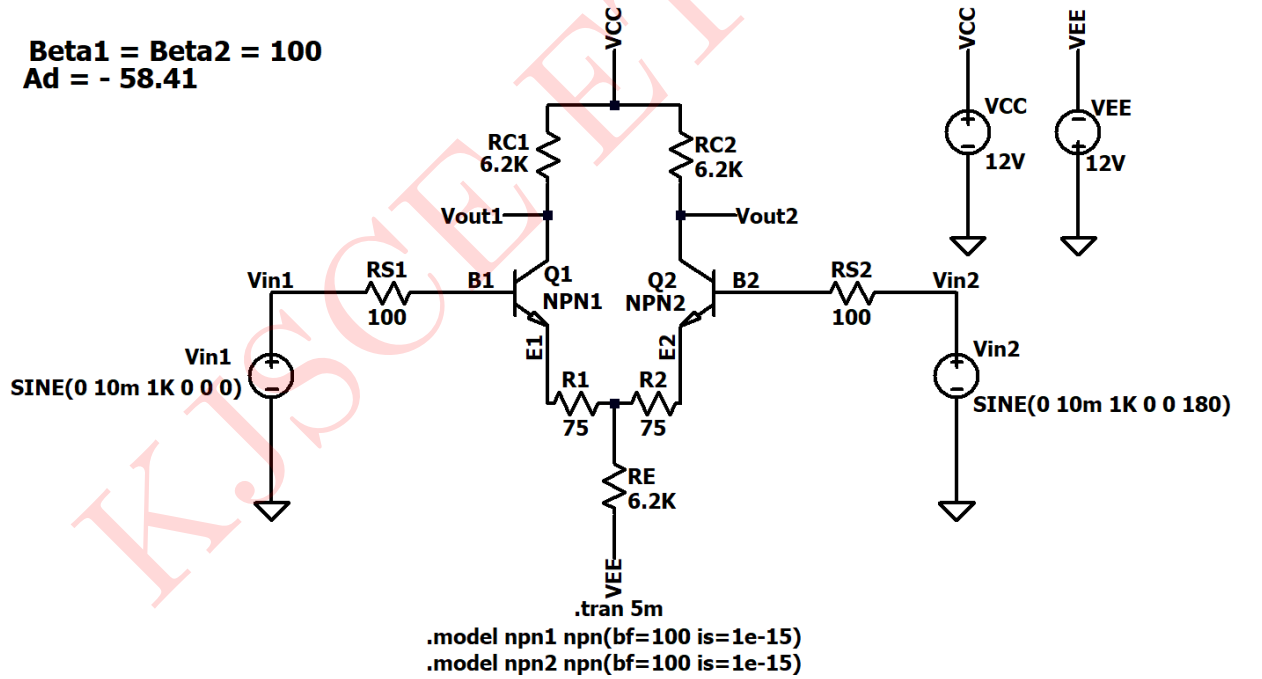


Figure 3: Circuit Schematic

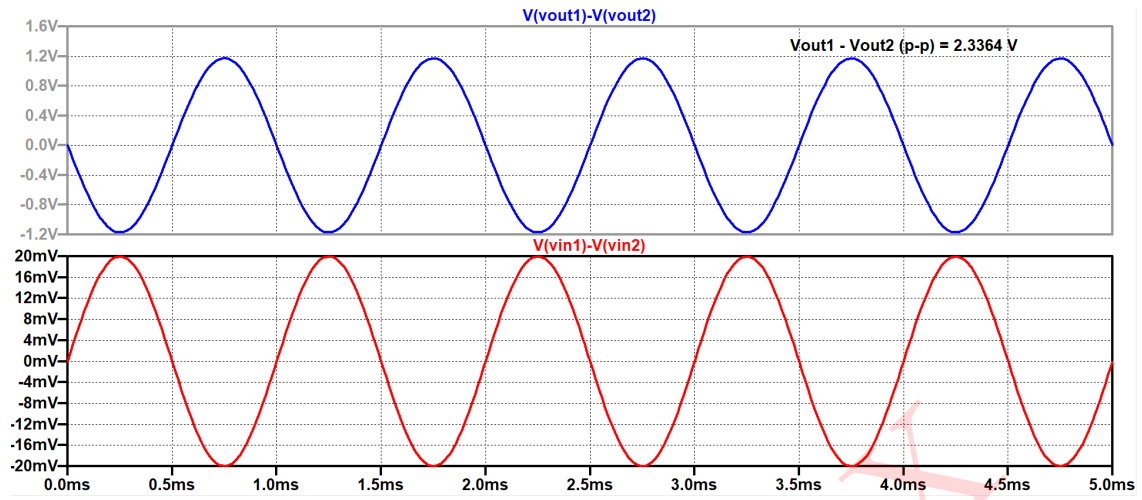


Figure 4: Input output Voltage waveform

Comparison between Theoretical and Simulated values :-

Parameters	Theoretical	Simulated
$I_{C1}$	0.896mA	0.8957mA
$I_{C2}$	0.896mA	0.8957mA
$V_{C1}$	6.44V	6.44V
$V_{C2}$	6.44V	6.44V
$V_{CE1}$	7.2672V	7.167V
$V_{CE2}$	7.2672V	7.167V
Differential voltage gain ( $ A_d $ )	59.04	58.41
Common mode voltage gain ( $A_{cm}$ )	0.5	—
CMRR (in dB)	45.44dB	—

Table 1: Numerical 1

**Numerical 2:** Consider the given circuit the transistor parameters are

$$k_{n1} = k_{n2} = 50\mu A/V^2, \lambda_1 = \lambda_2 = 0.02V^{-1} \text{ and } V_{TN1} = V_{TN2} = 1V$$

Determine  $I_S$ ,  $I_{D1}$ ,  $I_{D2}$ ,  $V_{D1}$ ,  $V_{D2}$ ,  $V_{DS1}$ ,  $V_{DS2}$

Calculate differential mode voltage gain  $A_d$ , common mode gain  $A_{cm}$  and CMRR (in dB)

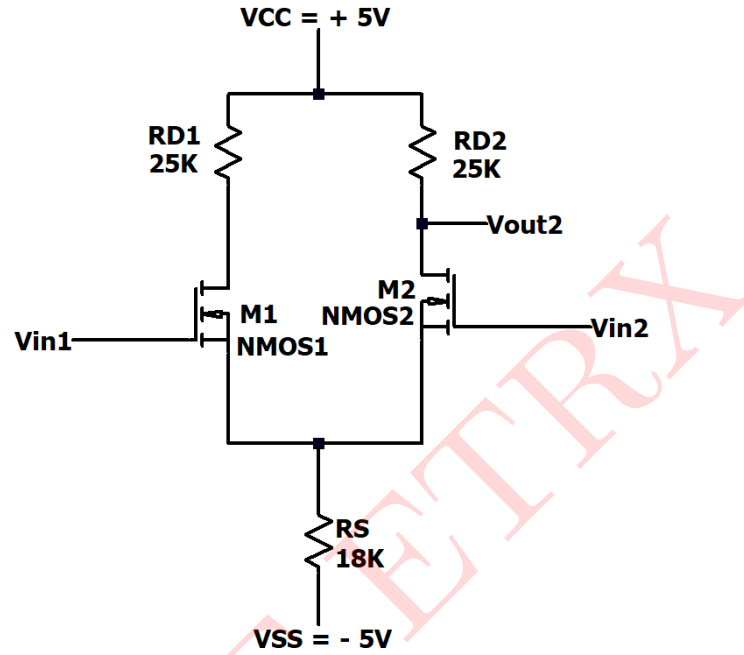


Figure 5: Circuit 2

**Solution:**

The given circuit is a Dual input Unbalanced output (DIUO) differential amplifier.

**DC ANALYSIS:**

Since both the transistors are identical we consider only one transistor

Applying KVL to Gate - Source loop;

$$-V_{GS1} - I_{S1}(2R_S) - V_{SS} = 0$$

But  $I_{D1} = I_{S1}$

$$\therefore V_{GS1} = 5 - I_{D1}(2 \times 18 \times 10^3) = 5 - I_{D1}(36 \times 10^3) \quad \text{.....1}$$

Applying KVL to the Drain - Source loop;

$$V_{DD} - I_{D1}R_{D1} - V_{DS1} - I_{S1}2R_S - V_{SS} = 0$$

$$I_{D1} = I_{S1}$$

$$\therefore V_{DS1} = V_{DD} - V_{SS} - I_{D1}(R_{D1} + 2R_S) = 5 - (-5) - I_{D1}(25k + 36k) = 10 - I_{D1}(61 \times 10^3) \quad \text{.....2}$$

Also we know that,

$$\begin{aligned}
I_{D1} &= k_{n1}(V_{GS1} - V_{TN1})^2(1 + \lambda_1 V_{DS1}) \\
&= 50 \times 10^{-6}(5 - I_{D1}(36 \times 10^3) - 1)^2 \times (1 + 0.02(10 - (61 \times 10^3)I_{D1})) \\
&= 50 \times 10^{-6}(4 - I_{D1}(36 \times 10^3))^2 \times (1 + 0.2 - I_{D1}(10^3)(1.22)) \\
&= 50 \times 10^{-6}(4 - I_{D1}(36 \times 10^3))^2 \times (1.2 - (1.22 \times 10^3 \times I_{D1})) \\
&= 50 \times 10^{-6}(16 - 288 \times 10^3 I_{D1} + (1296 \times 10^6 \times I_{D1}^2)) \times (1.2 - 1.22 \times 10^3 I_{D1}) \\
&= 50 \times 10^{-6}(19.2 - (345.6 \times 10^3 I_{D1}) + (1555.2)(10^6)(I_{D1}^2) - (19.52 \times 10^3 I_{D1}) \\
&\quad + (351.36 \times 10^6 I_{D1}^2) - (1581.12 \times 10^9 I_{D1}^3)) \\
&= 960 \times 10^{-6} - 17.28 I_{D1} + 77.76 \times 10^3 I_{D1}^2 - 0.976 I_{D1} + (17.568 \times 10^3 I_{D1}^2) - (79.256 \times 10^6)(I_{D1}^3) \\
&= 960 \times 10^{-6} - 18.256 I_{D1} + (95.328 \times I_{D1}^2 \times 10^3) - 79.056 \times 10^6 I_{D1}^3
\end{aligned}$$

$$\text{So, } 79.056 \times 10^6(I_{D1}^3) - (95.328 I_{D1}^2)(10^3) + (18.256 I_{D1}) - (960 \times 10^{-6}) = 0$$

On solving we get,

$$I_{D1} = 9.669 \times 10^{-4} A \text{ or}$$

$$I_{D1} = 7.808 \times 10^{-5} A \text{ or}$$

$$I_{D1} = 16.083 \times 10^{-4} A$$

$$\text{When } I_{D1} = 9.669 \times 10^{-4} A$$

$$V_{GS1} = 5 - (9.669 \times 10^{-4})(36 \times 10^3) = \mathbf{-29.8V}$$

$$\text{When } I_{D1} = 78.08 \mu A$$

$$V_{GS1} = 5 - (78.08 \times 10^{-6})(36 \times 10^3) = \mathbf{2.189V}$$

$$\text{When } I_{D1} = 16.083 \times 10^{-4} A$$

$$V_{GS1} = 5 - (16.083 \times 10^{-4})(36 \times 10^3) = \mathbf{-52.898V}$$

$$V_{GS1} \text{ can not be negative and } V_{GS} > V_{TN}$$

$$V_{GS1} = \mathbf{2.189V}$$

$$\text{And } I_{D1} = \mathbf{78.08 \mu A}$$

$$I_{D1} = I_{D2} = \mathbf{78.08 \mu A}$$

$$I_S = I_{D1} = \mathbf{78.08 \mu A}$$

$$V_{GS1} = V_{GS2} = \mathbf{2.189V}$$

$$V_{DS1} = V_{DS2} = 10 - (78.08 \times 61 \times 10^{-3}) = \mathbf{5.237V}$$

### AC ANALYSIS:

$$g_{m1} = 2k_{n1}(V_{GS1} - V_{TN1})(1 + \lambda V_{DS1}) = 2 \times 50 \times 10^{-6}(2.189 - 1)(1 + (0.02)(5.237)) \\ = \mathbf{0.131mA/V}$$

$$r_{d1} = \frac{1}{\lambda I_{D1}} = \frac{1}{0.02 \times 78.08 \times 10^{-6}} = \mathbf{640.368k\Omega}$$

As both transistors are identical,

$$g_{m1} = g_{m2} = \mathbf{0.131mA/V}$$

$$r_{d1} = r_{d2} = \mathbf{640.368k\Omega}$$

### Differential mode gain:

$$|A_d| = \frac{g_m(r_d \parallel R_D)}{2} = \frac{0.131 \times 10^{-3}(640.368k \parallel 25k)}{2} = \mathbf{1.57}$$

### Common mode voltage gain:

$$A_{cm} = \frac{g_m(r_d \parallel R_D)}{1 + 2g_m R_S} = \frac{0.131 \times 10^{-3}(640.386k \parallel 25k)}{1 + 2(0.121 \times 10^{-3} \times 18 \times 10^3)} = \mathbf{0.549}$$

$$CMRR = \frac{A_d}{A_{cm}} = \mathbf{2.859}$$

$$CMRR \text{ (in dB)} = \mathbf{9.1265dB}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

$$VTN1 = VTN2 = 1 \text{ V}$$

$$kn1 = kn2 = 50e-6 \text{ A / V}^2$$

$$\lambda_1 = \lambda_2 = 0.02 \text{ V}^{-1}$$

$$KP1 = KP2 = 2 * kn$$

$$KP1 = KP2 = 100e-6$$

$$A_d = 1.58$$

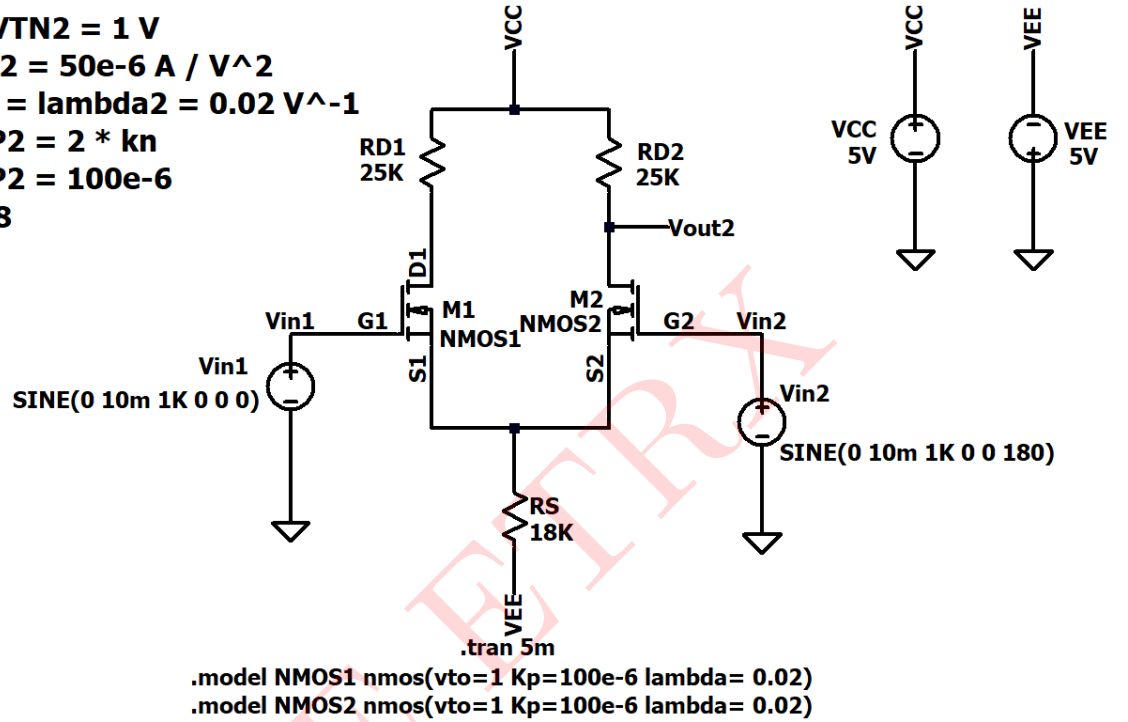


Figure 6: Circuit Schematic

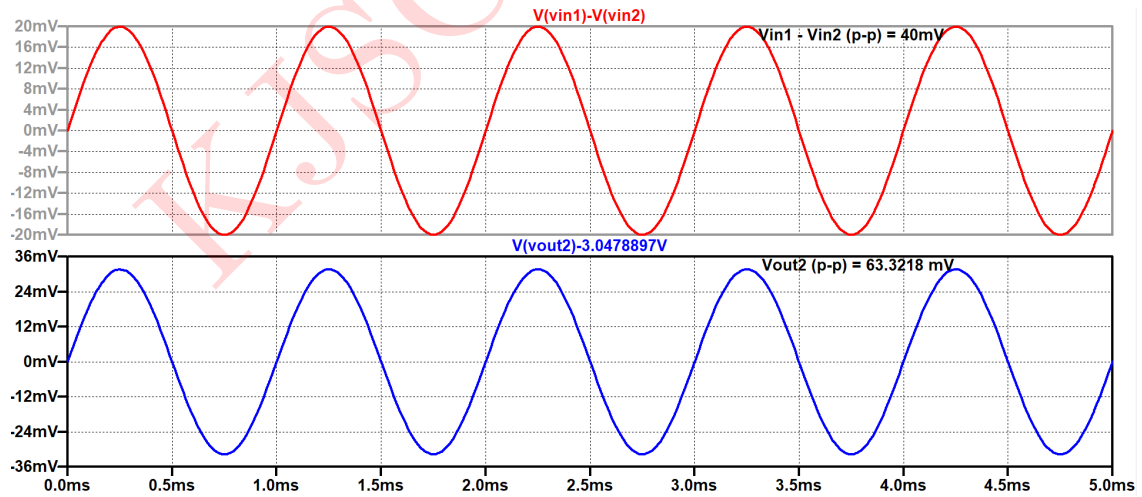


Figure 7: Input output Voltage waveform



**Comparison between Theoretical and Simulated values :-**

Parameters	Simulated	Theoretical
$I_{D1}$	$78.08\mu A$	$78.08\mu A$
$I_{D2}$	$78.08\mu A$	$78.08\mu A$
$I_S$	$78.08\mu A$	$78.08\mu A$
$V_{GS1}$	2.188V	2.189V
$V_{GS2}$	2.188V	2.189V
$V_{DS1}$	5.2368V	5.237V
$V_{DS2}$	5.2368V	5.237V
Differential voltage gain ( $ A_d $ )	1.58	1.57
Common mode voltage gain ( $A_{cm}$ )	—	0.549
CMRR (in dB)	—	9.1265dB

Table 2: Numerical 2

**Numerical 3:** For the amplifier shown in figure 1, find

- $I_{D1}$ ,  $I_{D2}$
- DC values of  $V_{o1}$ ,  $V_{o2}$
- Single ended output gain  $\left( \frac{V_{o1}}{V_1 - V_2} \right)$

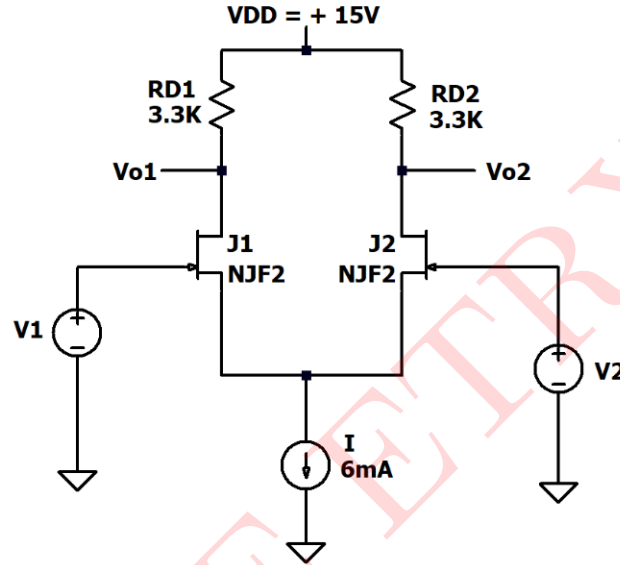


Figure 8: Circuit 3

**Solution:**

The given circuit is a differential amplifier using JFET.

$$i. I_{D1} = I_{D2} = \frac{I}{2} = \frac{6mA}{2} = \mathbf{3mA}$$

$$ii. \text{DC values of } V_{o1} = V_{o2} = V_{DD} - I_D R_D$$

where  $I_D = I_{D1} = I_{D2}$

$$V_{o1} = V_{o2} = 15 - (3 \times 10^{-3})(3.3 \times 10^3) = \mathbf{5.1V}$$

$\left( \frac{V_{o1}}{V_1 - V_2} \right)$  means that the output is taken from Drain  $D_1$  of transistor  $M_1$

We assume that  $V_{o2} > V_{o1}$

The circuit will be a Dual input Unbalanced output configuration.

$$A_d = \frac{V_{o1}}{V_1 - V_2} = \frac{-g_m R_D}{2}$$

We know that for JFET,  $I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

$$\text{so, } \frac{I_D}{I_{DSS}} = \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\therefore 1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_D}{I_{DSS}}}$$

$$\text{So, } g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_D}{I_{DSS}}} = \frac{2 \times 12 \times 10^{-3}}{25} \sqrt{\frac{3 \times 10^{-3}}{12 \times 10^{-3}}} = 4.8 \text{ mA/V}$$

$$A_d = \frac{V_{o1}}{V_1 - V_2} = \frac{-g_m R_D}{2} = \frac{(-4.8 \times 10^{-3})(3.3 \times 10^3)}{2} = -7.92$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

**IDSS = 12 mA**

**VP = - 2.5V**

**beta1 = beta2 = IDSS / (VP\*VP)**

**beta1 = beta2 = 1.92e-3**

**Ad = -7.91**

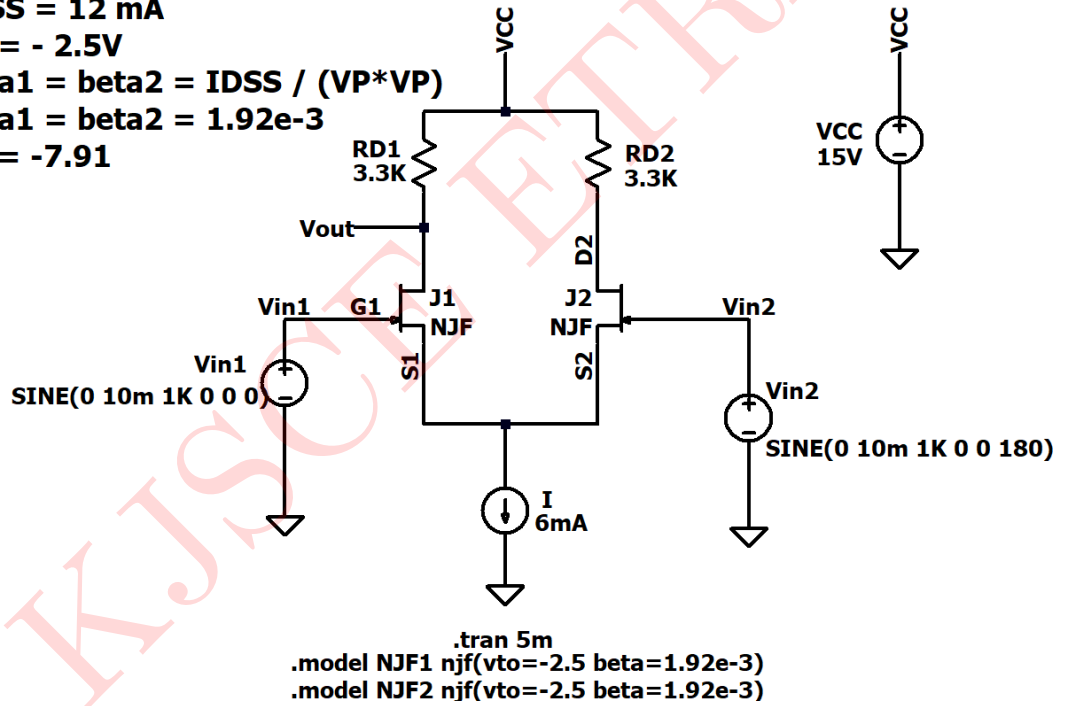


Figure 9: Circuit Schematic

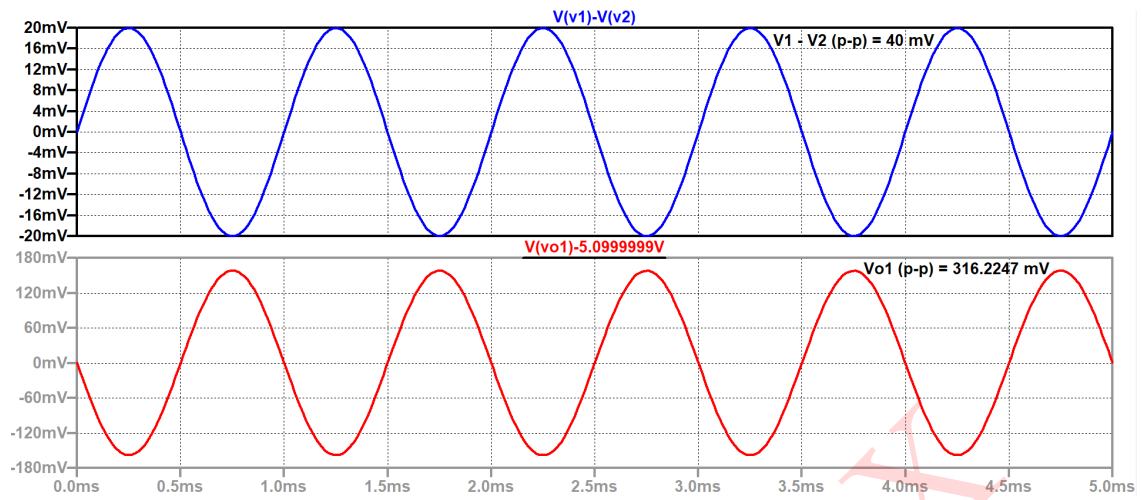


Figure 10: Input output Voltage waveform

#### Comparison between Theoretical and Simulated values :-

Parameters	Simulated	Theoretical
$I_{D1}, I_{D2}$	3mA	3mA
$V_{D1}, V_{D2}$	5.1V	5.1V
Differential voltage gain ( $A_d$ )	-7.91	-7.92

Table 3: Numerical 3

\*\*\*\*\*