

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DIODE APPLICATIONS**

**Numerical 1:**

Simulate a half wave rectifier circuit with input Amplitude = 150V peak,  $f = 50$  Hz and  $R_1 = 110\Omega$  using LTSpice. Select diode as 1N4148. Use 10:1 step down transformer.

Plot the following using LTSpice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

Also, calculate the efficiency of the Half wave rectifier circuit.

**SOLUTION:**

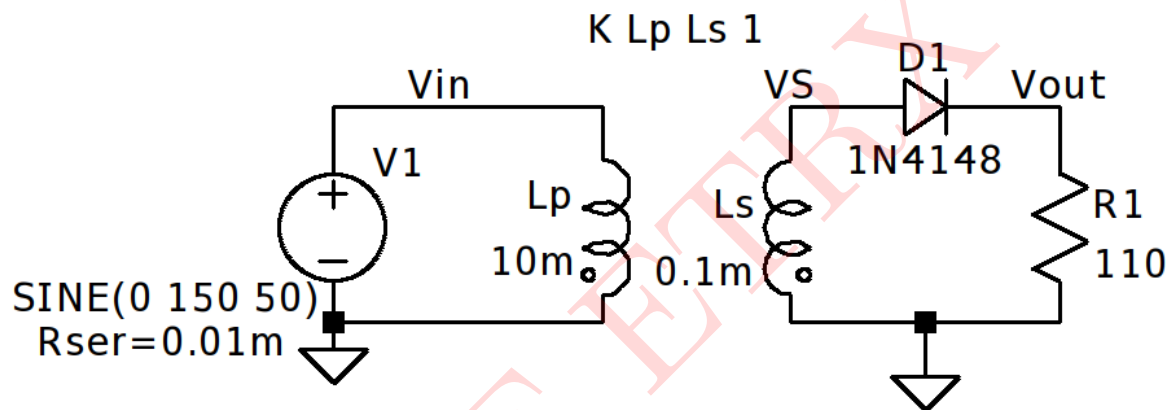


Figure 1: Circuit Diagram

$$V_m = \frac{V_1}{10}$$

$$V_m = 15V$$

$$I_m = \frac{V_m}{R_1}$$

$$I_m = \frac{15}{110}$$

$$I_m = 136.36mA$$

$$P_{DC} = \frac{V_m^2}{\pi^2 \times R_1}$$

$$P_{DC} = 0.2072W$$

$$P_{AC} = \frac{V_m^2}{4R_1}$$

$$P_{AC} = 0.51136W$$

$$\text{Efficiency} = \frac{P_{DC}}{P_{AC}} \times 100$$

$$\text{Efficiency} = 40.52\%$$

$$\text{PIV rating} = -V_m = -15V$$

### SIMULATED RESULTS:

The given circuit is simulated in LTSpice and the results obtained are as follows:

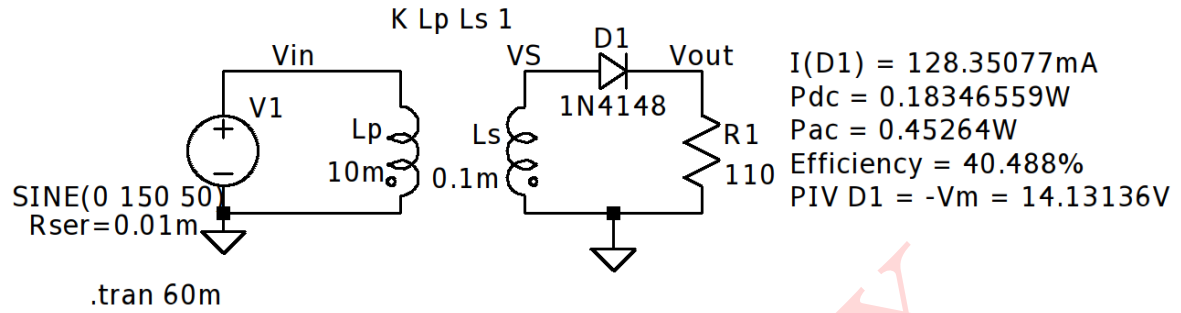


Figure 2: Circuit Schematic and Simulated Results

### Waveforms:

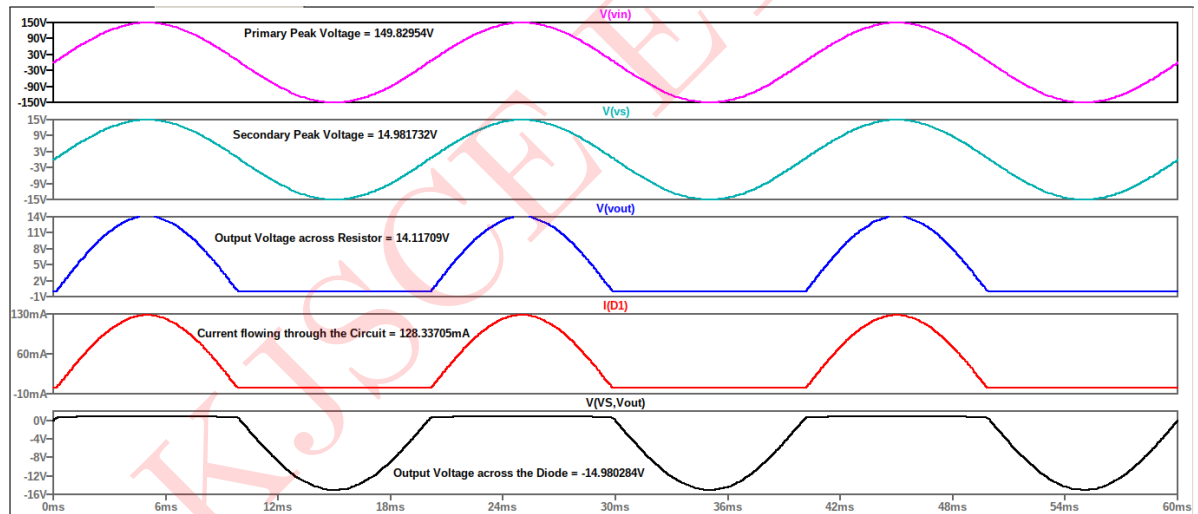


Figure 3: Simulated Waveforms

**Comparison of theoretical and simulated values:**

<b>Parameters</b>	<b>Theoretical Values</b>	<b>Simulated Values</b>
Output Peak Voltage	15V	14.113136V
Output Peak Current	113.36mA	128.3311mA
AC Power	0.51136W	0.51136W
DC Power	0.2072W	0.18346559W
Efficiency	40.52%	40.488%
PIV Rating	-15V	-14.113136V

Table 1: Numerical 1

**Numerical 2:**

Simulate a Full wave rectifier circuit with input Amplitude = 140V peak,  $f = 50$  Hz and  $R_1 = 110\Omega$  using LTSpice. Select diode as 1N4148. Use 10:1 step down center tap transformer. Plot the following using LTSpice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

Also, calculate the efficiency of the Full wave Center tapped rectifier circuit.

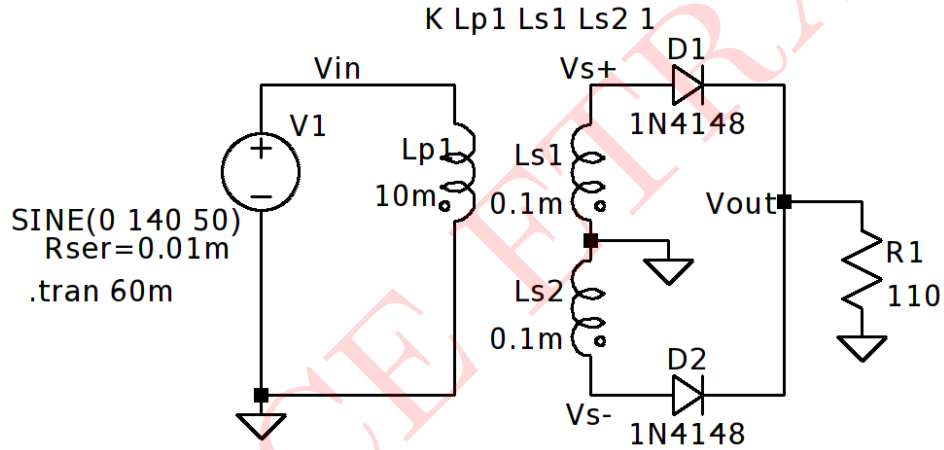
**SOLUTION:**

Figure 4: Circuit Diagram

$$V_m = \frac{V_1}{10}$$

$$V_m = 14V$$

$$I_m = \frac{V_m}{R_1}$$

$$I_m = \frac{14}{110}$$

$$I_m = 127.27mA$$

$$P_{DC} = \frac{4I_m^2 \times R_1}{\pi^2}$$

$$P_{DC} = 0.72211276W$$

$$P_{AC} = \frac{I_m^2 \times R_1}{2}$$

$$P_{AC} = 0.890871W$$

$$\text{Efficiency} = \frac{P_{DC}}{P_{AC}} \times 100$$

$$\text{Efficiency} = 81.0569\%$$

$$\text{PIV rating} = -2V_m = -28V$$

### SIMULATED RESULTS:

The given circuit is simulated in LTSpice and the results obtained are as follows:

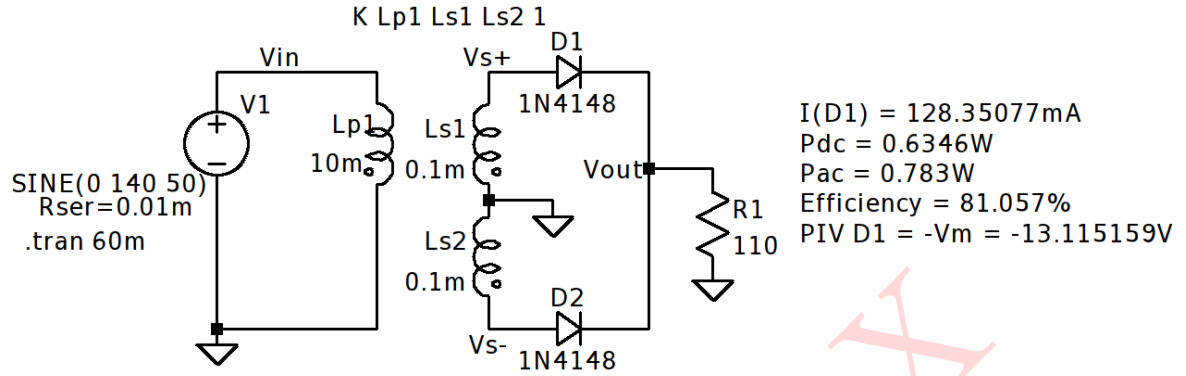


Figure 5: Circuit Schematic and Simulated Results

### Waveforms:

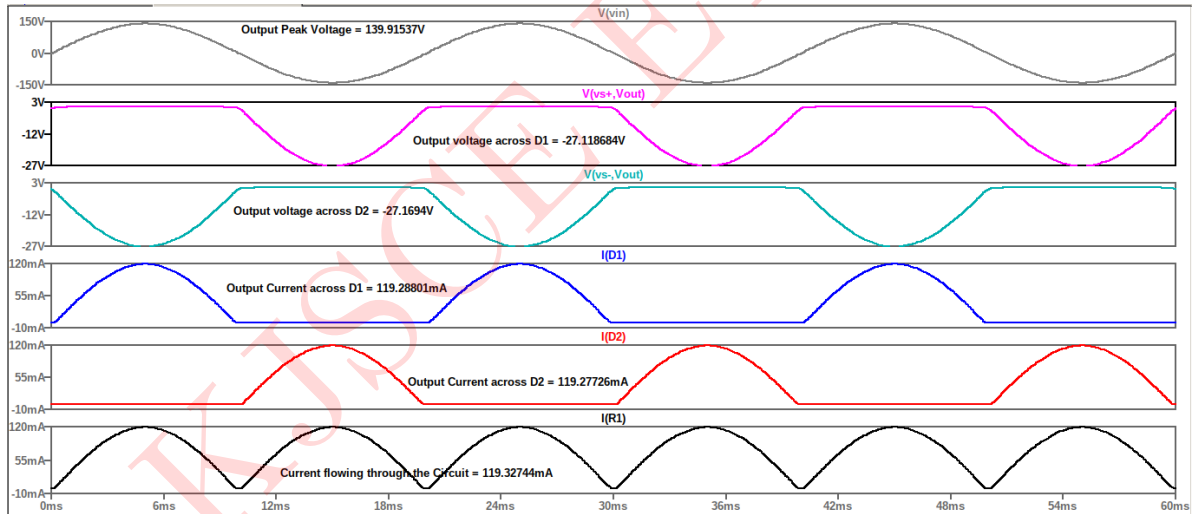


Figure 6: Simulated Waveforms

**Comparison of theoretical and simulated values:**

<b>Parameters</b>	<b>Theoretical Values</b>	<b>Simulated Values</b>
Output Peak Voltage	14V	13.115159V
Output Peak Current	127.27mA	119.30864mA
AC Power	0.890871W	0.783W
DC Power	0.72211276W	0.634W
Efficiency	81.0569%	81.057%
PIV Rating	-28V	-27.093769V

Table 2: Numerical 2