

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Single Stage BJT Amplifier

11th July, 2020

Numerical

1. For the network shown in figure 1

Find: a) Determine Z_i and Z_o

b) Find A_v

c) Repeat a) with $r_o = 20\text{k}\Omega$

d) Repeat b) with $r_o = 20\text{k}\Omega$

Given: $\beta = 60$, $R_B = 220\text{k}\Omega$, $R_C = 2.2\text{k}\Omega$, $r_o = 40\text{k}\Omega$, $C_{C1} = C_{C2} = 10\text{ }\mu\text{F}$

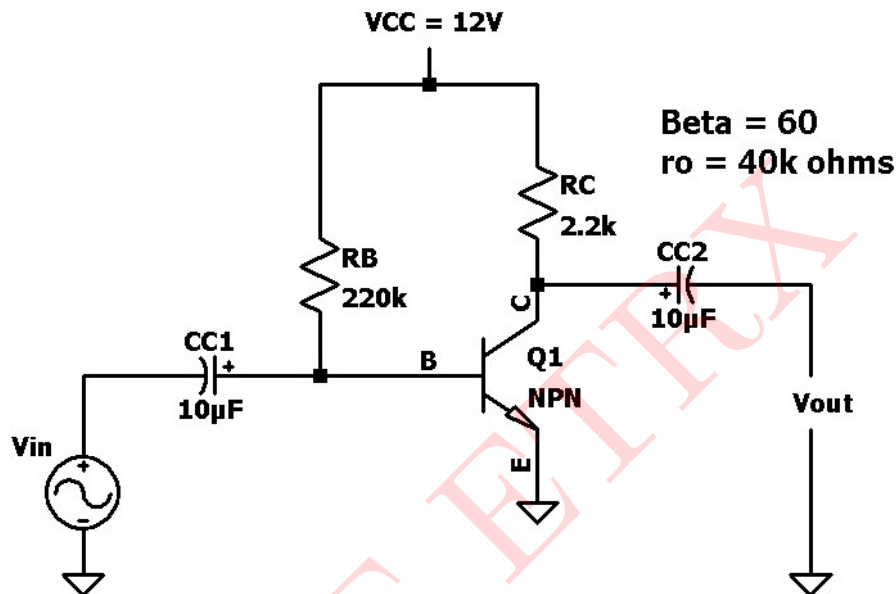


Figure 1: Circuit 1

Solution:

Above circuit is common emitter fixed biased BJT Amplifier

DC Analysis:

Applying KVL to input loop : $V_{BE} - V_{CC} - I_B R_B = 0$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B = \frac{12 - 0.7}{220 \times 10^3}$$

$$I_B = 51.3636\text{ }\mu\text{A}$$

$$I_C = \beta I_B$$

$$I_C = 3.0818\text{mA}$$

$$V_{CE} = V_C - V_E \quad (\text{put } V_E = 0)$$

$$V_{CE} = V_C$$

$$V_C = V_{CC} - I_C R_C = 12 - 3.0818 \times 10^{-3} \times 2.2 \times 10^3$$

$$V_C = 5.2\text{V}$$

Small signal parameters:

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26 \times 10^{-3}}{51.3636 \times 10^{-6}} = \mathbf{506.1950 \Omega}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{3.0818 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{118.53 \text{ mA/V}}$$

Small signal equivalent circuit:

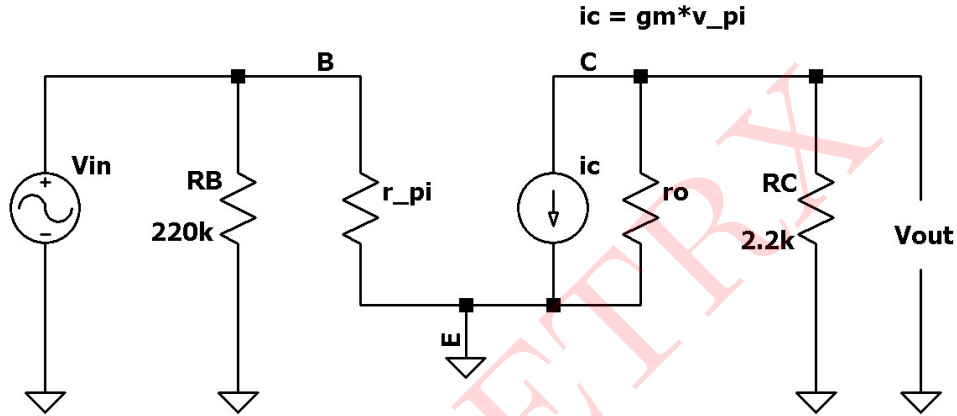


Figure 2: Small signal equivalent circuit

Input impedance $Z_i = R_B \parallel r_{\pi}$

$$Z_i = 505.032 \Omega$$

With $r_o = 20 \text{ k}\Omega$

$$Z_i = 505.032 \Omega$$

$$Z_o = r_o \parallel R_C = \mathbf{1981.981 \Omega}$$

$$A_v = -g_m(r_o \parallel R_C)$$

$$A_v = \mathbf{-234.924} \quad (\text{Negative sign indicates 180 out of phase between input and output})$$

With $r_o = 40 \text{ k}\Omega$

$$Z_o = r_o \parallel R_C$$

$$Z_o = 40 \times 10^3 \parallel 2.2 \times 10^3$$

$$Z_o = \mathbf{2085.308 \Omega}$$

$$A_v = \frac{V_o}{V_{in}} = -g_m(r_o \parallel R_C)$$

$$A_v = \mathbf{-247.171} \quad (\text{Negative sign indicates 180 out of phase between input and output})$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

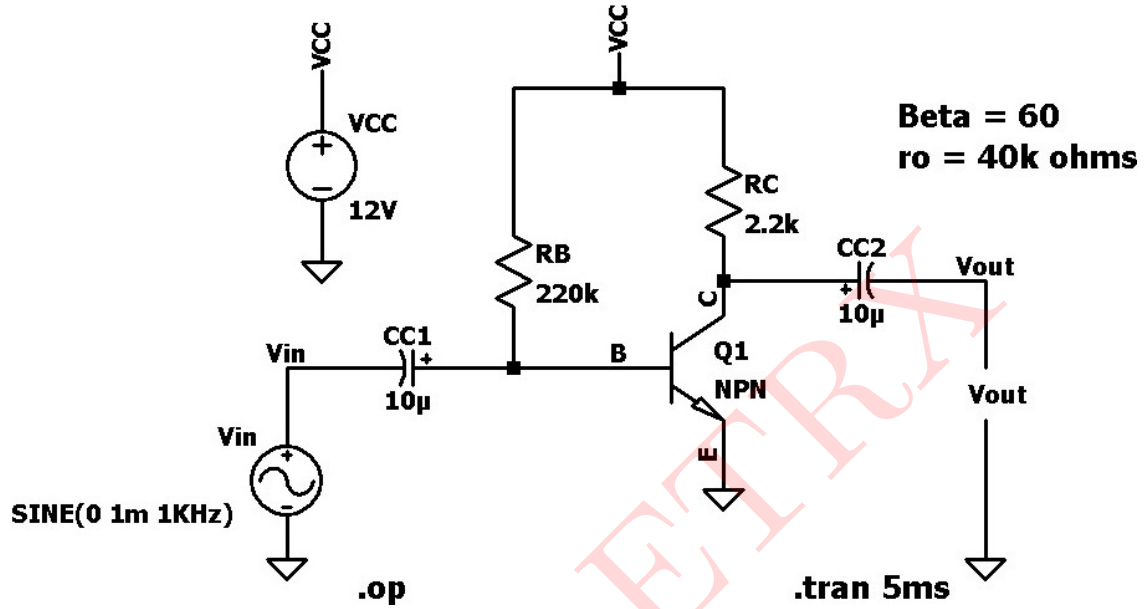


Figure 3: Circuit Schematic

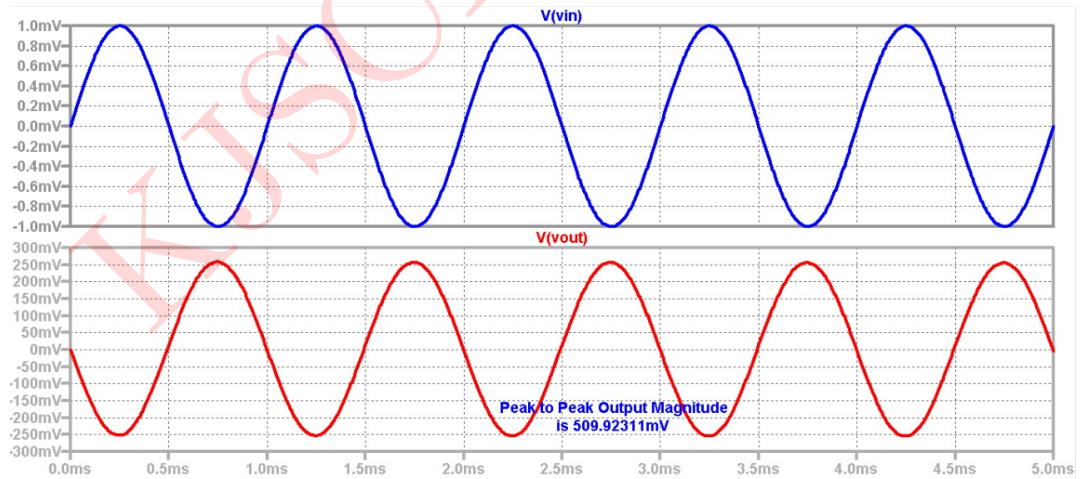


Figure 4: Input Output Waveform

Comparsion between simulated and theoretical values :

Parameters	Simulated	Observed
I_{BQ}	$51.3636\mu\text{A}$	$51.1651\mu\text{A}$
I_{CQ}	3.0818mA	3.1762mA
A_v	-247.171	-229.006
V_{CE}	5.2V	5.012V

Table 1: Numerical 1

KJSCE ETRX

2. For the network of figure 5

Find: a) Determine Z_i and Z_o ($r_o = \infty\Omega$)

b) A_v ($r_o = \infty\Omega$)

c) Repeat a) with $r_o = 50k\Omega$

d) Repeat b) with $r_o = 50k\Omega$

Given: $\beta = 100$, $R_B = 470k\Omega$, $R_C = 3k\Omega$, $V_{CC} = 12V$, $C_{C1} = C_{C2} = 10\mu F$

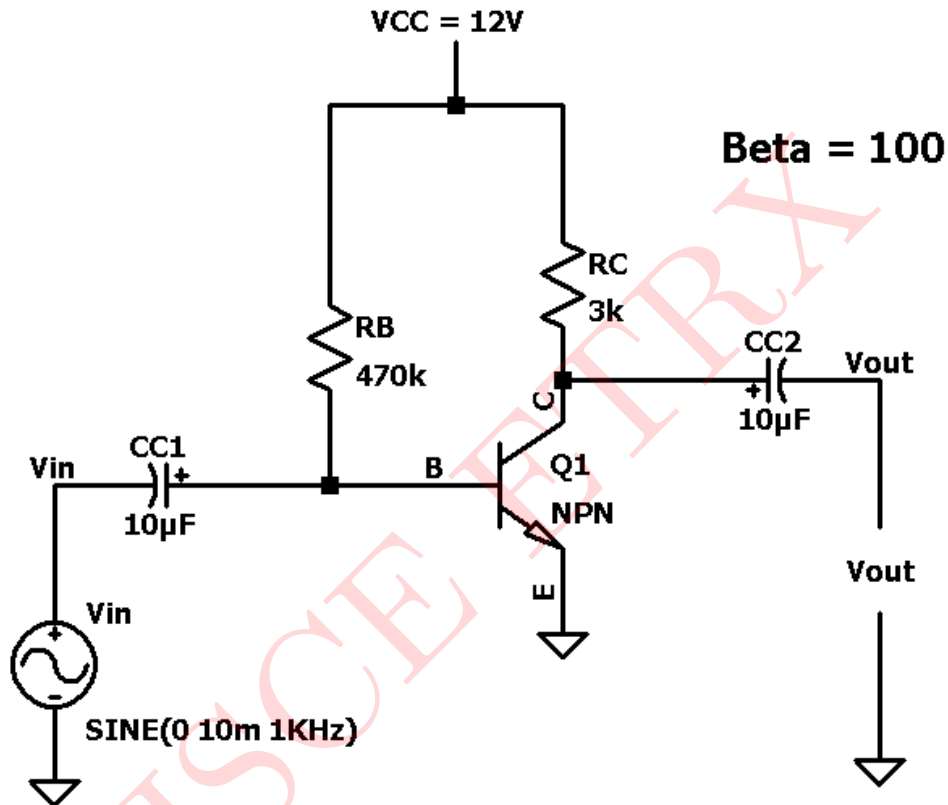


Figure 5: Circuit 2

Solution:

Above circuit is common emitter fixed biased BJT Amplifier

DC Analysis:

Applying KVL to input loop of circuit 2:

$$V_{BE} - V_{CC} - I_B R_B = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B = \frac{12 - 0.7}{470 \times 10^3}$$

$$I_B = 24.0425\mu A$$

$$I_C = \beta I_B$$

$$I_C = 2.4042mA$$

$$V_{CE} = V_C - V_E \quad (\text{bur } V_E = 0)$$

$$V_{CE} = V_C$$

$$V_C = V_{CC} - I_C R_C = 12 - 2.4042 \times 10^{-3} \times 3 \times 10^3$$

$$V_C = \mathbf{4.7874V}$$

Small signal parameters:

$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{26 \times 10^{-3}}{24.0425 \times 10^{-6}} = \mathbf{1081.418 \Omega}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.4042 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{92.4692 \text{ mA/V}}$$

Small signal equivalent circuit:

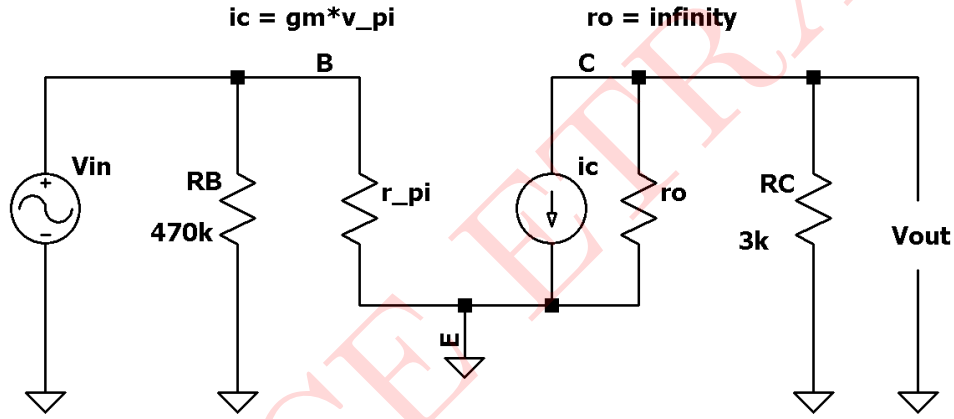


Figure 6: Small signal equivalent circuit

Input impedance

$$Z_i = R_B \parallel r_\pi$$

$$Z_i = 2470 \times 10^3 \parallel 1081.418$$

$$Z_i = \mathbf{1078.935\Omega}$$

$$Z_o = R_c \quad (r_o = \infty)$$

$$Z_o = \mathbf{3k\Omega}$$

$$A_v = \frac{V_o}{V_{in}} = -g_m(R_C)$$

$$A_v = \mathbf{-277.4076} \quad (\text{Negative sign indicates 180 out of phase between input and output})$$

With $r_o = 50 \text{ k}\Omega$

$$Z_o = r_o \parallel R_C = \mathbf{2830.1886\Omega}$$

$$A_v = -g_m(r_o \parallel R_C)$$

$$A_v = \mathbf{-261.7052} \quad (\text{Negative sign indicates 180 out of phase between input and output})$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

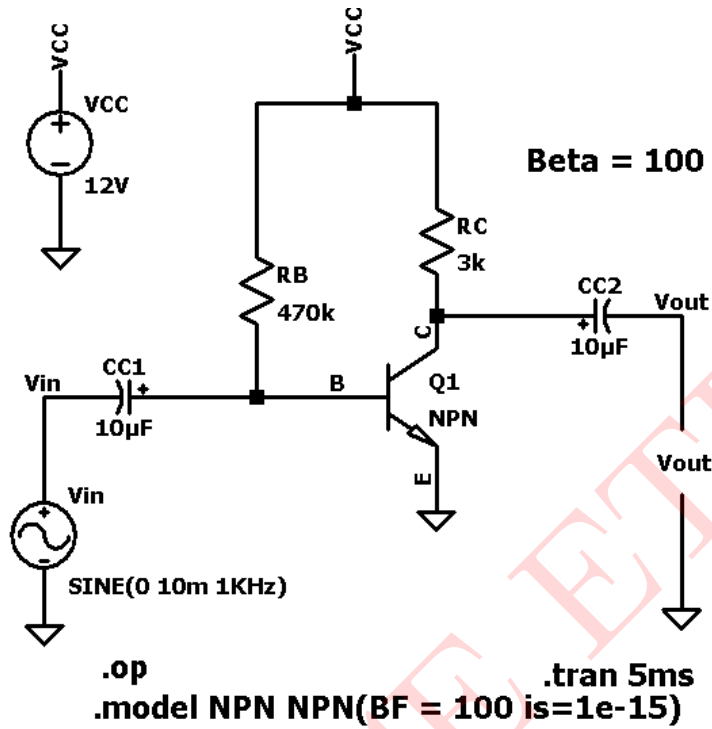


Figure 7: Circuit Schematic

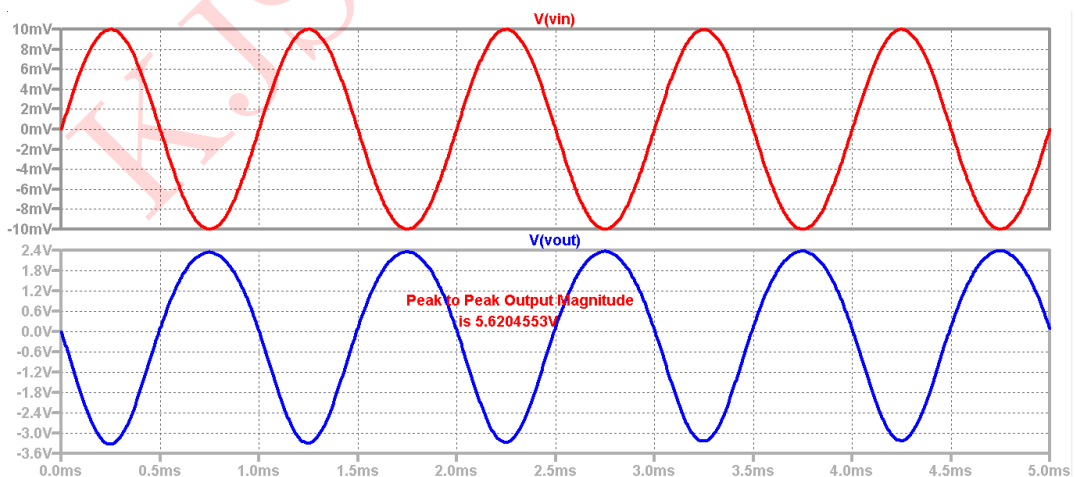


Figure 8: Input Output Waveforms

Comparsion between simulated and theoretical values :

Parameters	Simulated	Theoretical
I_{BQ}	$23.9635\mu\text{A}$	$24.0425\mu\text{A}$
I_{CQ}	2.3963mA	2.4042mA
$A_v(r_o = \infty)$	-281.45	-277.407
$A_v(r_o = 50k\Omega)$	-272.35V	-261.705V

Table 2: Numerical 2

KJSCE ETRX

3. For the network shown in figure 9
 Find: a) Find the Q point
 b) Find A_v
 c) Determine range in A_v if R_1 and R_2 vary by ± 5 percent

Given: $\beta = 100$, $R_1 = 33\text{k}\Omega$, $R_2 = 50\text{k}\Omega$, $V_{EE} = 3.3\text{V}$, $R_C = 2\text{k}\Omega$, $R_E = 1\text{k}\Omega$, $V_A = \infty$

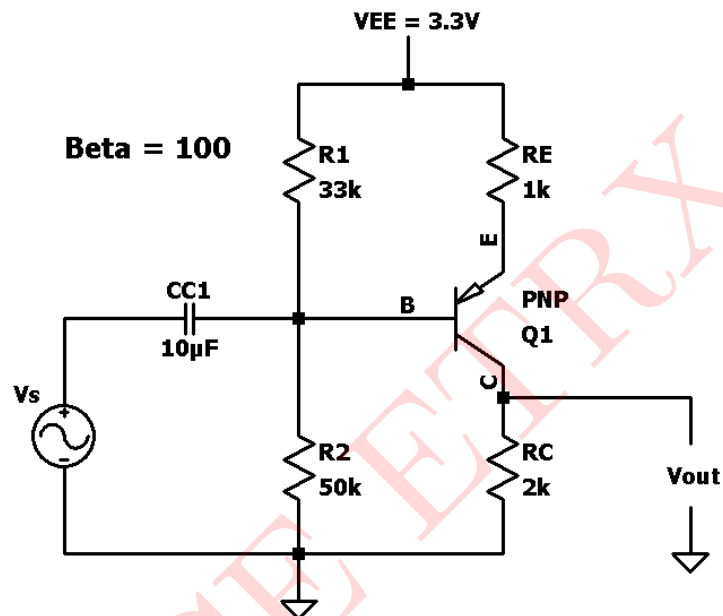


Figure 9: Circuit 3

Solution:

Above circuit is common emitter voltage divider BJT Amplifier

DC Analysis:

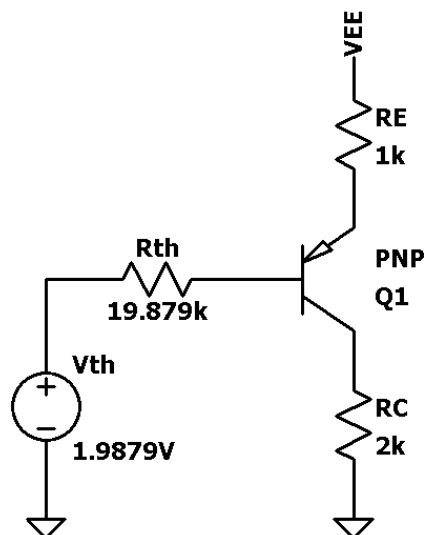


Figure 10: Thevenins equivalent circuit

$$R_{TH} = R_1 \parallel R_2$$

$$R_{TH} = 33 \times 10^3 \parallel 50 \times 10^3$$

$$R_{TH} = \mathbf{19879.51\Omega}$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) \times V_{CC}$$

$$V_{TH} = \frac{50 \times 10^3}{50 \times 10^3 + 33 \times 10^3}$$

$$V_{TH} = \mathbf{1.9879V}$$

Applying KVL to the input loop

$$V_{TH} - V_{EE} + V_{EB} - I_B R_{TH} + I_E R_E = 0$$

$$I_B = \frac{V_{EE} - V_{BE} - V_{TH}}{R_{TH} + (1 + \beta)R_E}$$

$$I_B = \frac{12 - 0.7 - 1.9879}{19879.51 + 101 \times 10^3}$$

$$I_B = \mathbf{5.0637\mu A}$$

$$I_C = \beta I_B$$

$$I_C = \mathbf{0.5063mA}$$

$$I_E = I_B + I_C$$

$$I_E = \mathbf{0.5113mA}$$

Applying KVL to output loop

$$V_{ECQ} = V_{EE} - I_E R_{EQ} - I_C R_{CQ}$$

$$V_{ECQ} = 3.3 - 0.5113 - 0.5063 \times 2$$

$$V_{ECQ} = \mathbf{1.7759V}$$

$$Q \text{ point} = (V_{CEQ}, I_{CQ})$$

$$Q \text{ point} = (\mathbf{1.77V}, \mathbf{0.506mA})$$

Small signal parameters:

$$r_o = 0 \quad r_\pi = \frac{V_T}{I_{BQ}} = \frac{26 \times 10^{-3}}{5.0637 \times 10^{-6}} = \mathbf{5134.58 \Omega}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5063 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{19.473 \text{ mA/V}}$$

Small signal equivalent circuit:

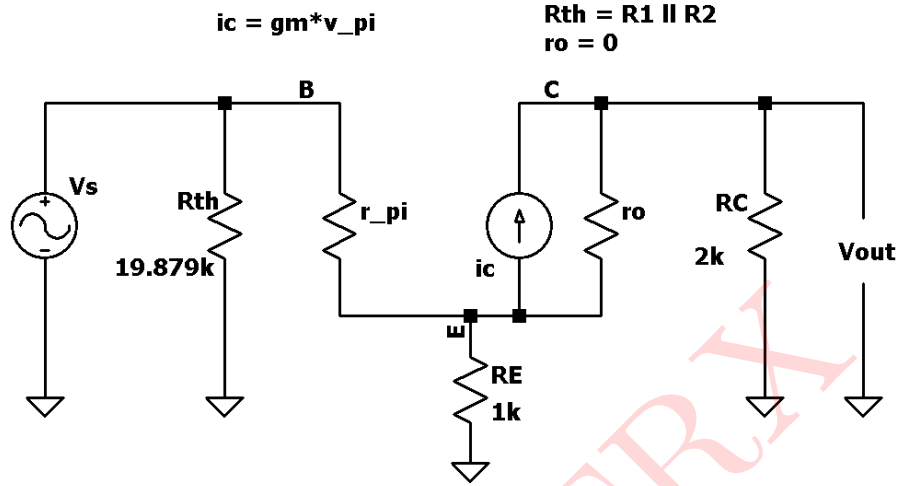


Figure 11: Small signal equivalent circuit

$$A_v = \frac{V_o}{V_{in}} = -g_m V_\pi (R_C)$$

$$V_{in} = V_S = V_\pi + \text{voltage drop at } R_E$$

$$V_{in} = V_\pi \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) \times R_E$$

$$V_{in} = V_\pi \left(1 + \left(\frac{1}{r_\pi} + g_m \right) R_E \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m V_\pi R_c}{V_\pi \left(1 + \left(\frac{1}{r_\pi} + g_m \right) R_E \right)}$$

$$A_v = \frac{-R_C}{\frac{1}{g_m} + R_E}$$

$$A_v = -1.9023 \quad (\text{Negative sign indicates } \angle 180 \text{ out of phase between input and output})$$

Approximate:

$$R_C = 2k\Omega \pm 5\% = 2.1k\Omega \text{ or } 1.9k\Omega$$

$$R_E = 1k\Omega \pm 5\% = 1.051k\Omega \text{ or } 0.95k\Omega$$

To find range of A_v :

$$\text{For } R_{C(max)} = 2.1k\Omega + R_{E(min)} = 0.95k\Omega$$

$$A_v = \frac{-R_{C(max)}}{\frac{1}{g_m} + R_{E(min)}} = \frac{-2.1 \times 10^3}{\frac{1}{19.473} + 0.95 \times 10^3}$$

$$A_v = -2.0971$$

$$\text{For } R_{C(min)} = 1.9k\Omega + R_{E(max)} = 1.05k\Omega$$

$$A_v = \frac{-R_{C(min)}}{\frac{1}{g_m} + R_{E(max)}} = \frac{-1.9 \times 10^3}{\frac{1}{19.473} + 1.05 \times 10^3}$$

$$A_v = -1.7251$$

Range is of A_v $1.725 \leq A_v \leq 2.097$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

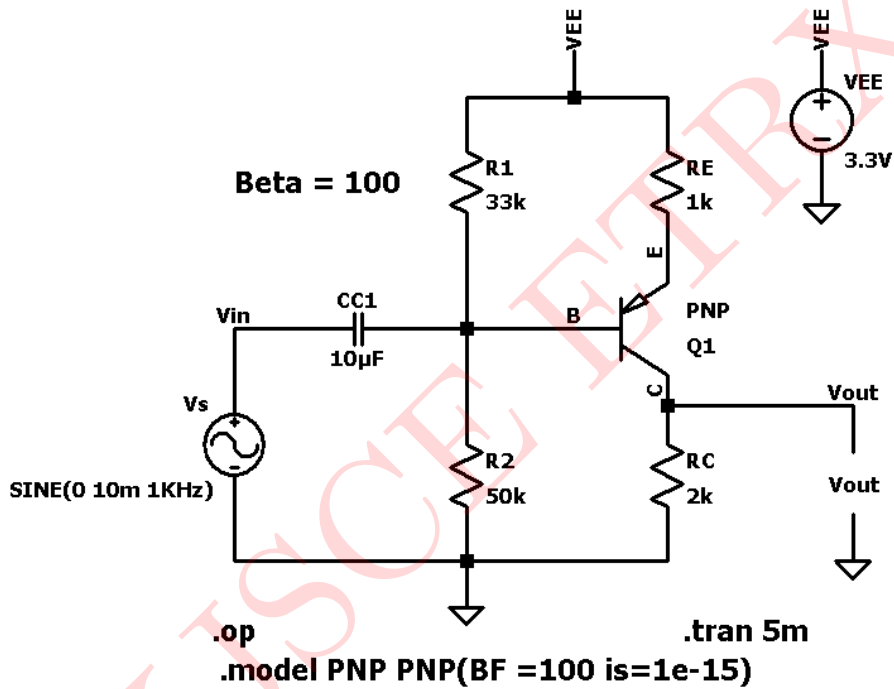


Figure 12: Circuit Schematic

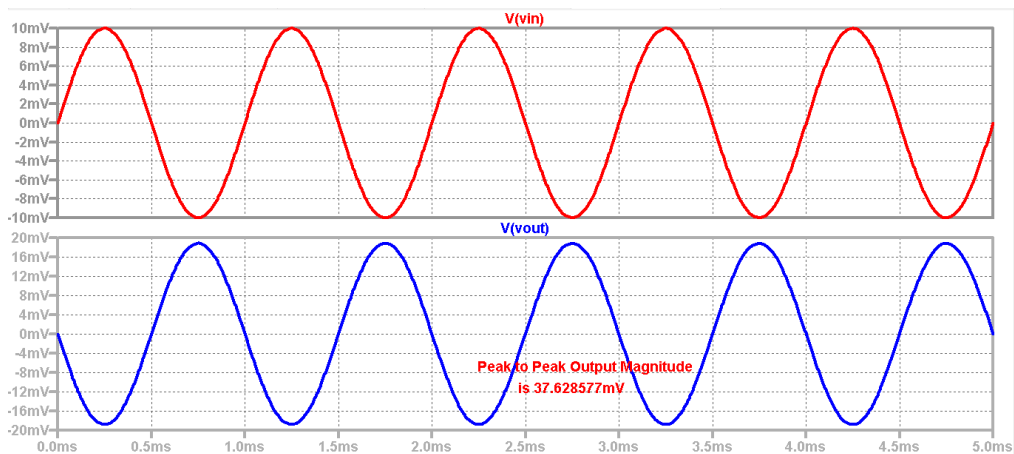


Figure 13: Circuit Schematic: Input Output Waveform

Comparsion between simulated and theoretical values :

Parameters	Simulated	Theoretical
I_{BQ}	$5.0865\mu\text{A}$	$5.0637\mu\text{A}$
I_{CQ}	0.5086mA	0.5063mA
I_{EQ}	0.5137mA	0.5113mA
A_v	-1.8814	-1.9023
V_{ECQ}	1.7689V	1.7759mA

Table 3: Numerical 3
