

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Oscillator Circuits

16th July, 2020

Numericals

Numerical 1: In a colpitt's Oscillator, amplifier components are $R_1 = 100k$, $R_2 = 18k$, $R_C = 12k$, $R_E = 1k$, $C_{C1} = 1\mu F$, $C_E = 150\mu F$, $C_{C2} = 1\mu F$, $V_{CC} = 10V$. Select the LC tank circuit such that frequency of oscillations is close to 90kHz.

BJT transistor: 2N2222

Also comment on the phase shift offered by LC Tank circuit.

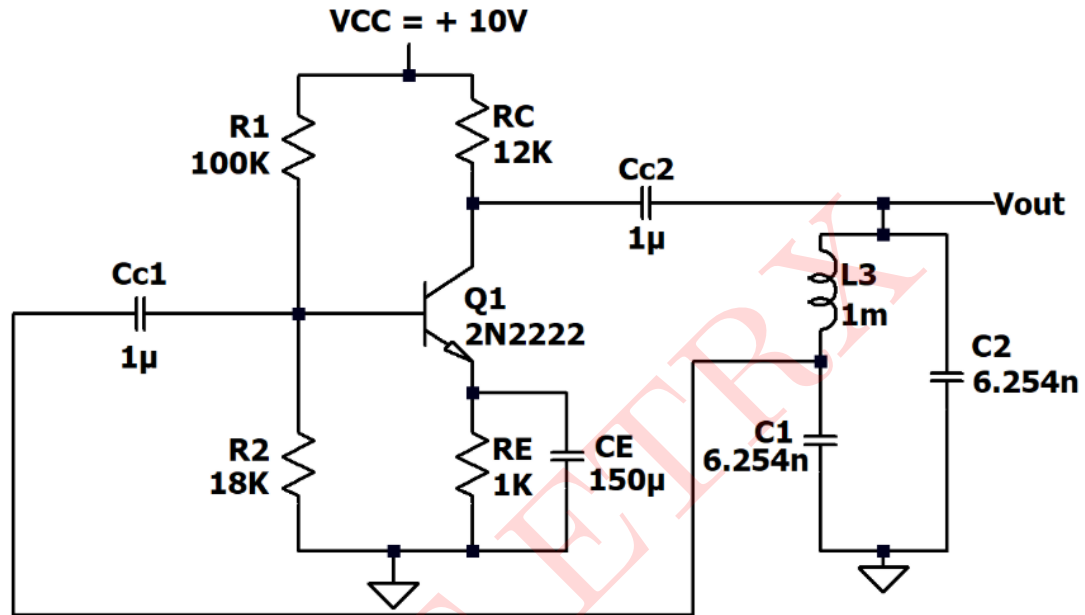


Figure 1: Circuit 1

Solution:

Frequency of oscillations for a Colpitt's Oscillator is given as:

$$f_o = \frac{1}{2\pi\sqrt{C_{eq}L_3}}$$

$$\text{Where, } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\text{Let } L_3 = 1mH$$

Since we want the frequency of oscillations to be close to 90kHz

$$f_o \approx 90kHz$$

$$\therefore 90 \times 10^3 = \frac{1}{2\pi\sqrt{10^{-3} \times C_{eq}}}$$

$$\therefore 10^{-3} \times C_{eq} = \frac{1}{(90 \times 10^3 \times 2\pi)^2}$$

$$\therefore C_{eq} = \frac{10^3}{(90 \times 10^3 \times 2\pi)} = 3.127\text{nF}$$

Let $C_1 = C_2$

$$\therefore C_1 = C_2 = 2 \times 3.127\text{nF} = 6.254\text{nF}$$

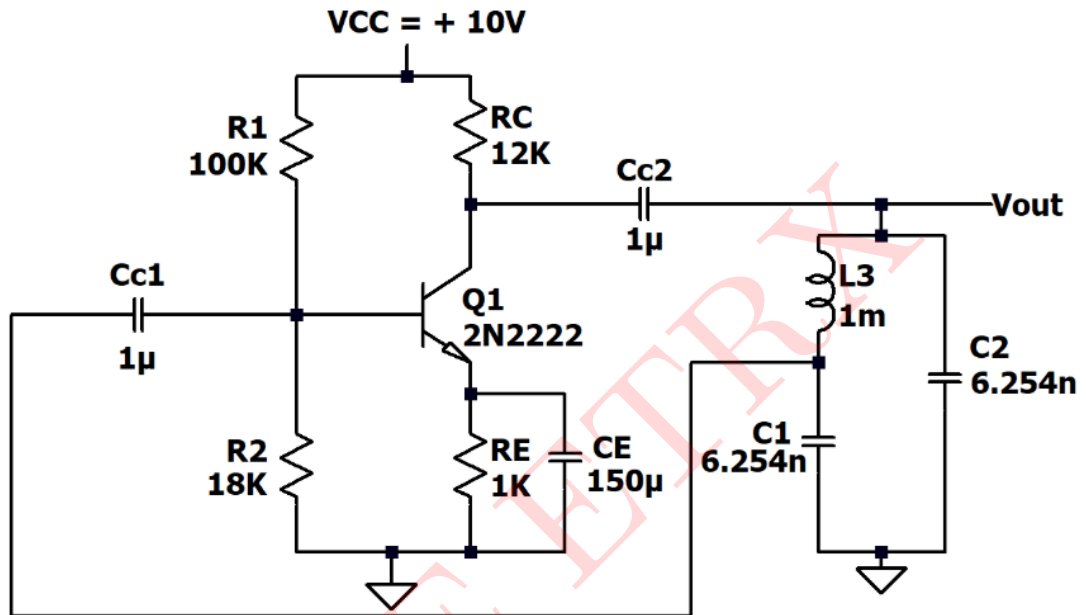


Figure 2: Colpitt's Oscillator

Frequency of oscillations = **90kHz**

$$\therefore \text{Time period of oscillations} = \frac{1}{f_o} = \frac{1}{90 \times 10^3} = 11.11\mu\text{sec}$$

$$\text{Feedback fraction (K)} = \frac{V_f}{V_o} = \frac{IX_{C2}}{IX_{C1}} = \frac{C_1}{C_2} = \frac{6.254 \times 10^{-9}}{6.254 \times 10^{-9}} = 1$$

Feedback fraction = 1

Phase shift provided by common emitter amplifier is 180°

Phase shift provided by the LC tank circuit is 180°

So the total phase shift of the entire circuit is 360° (or 0°)

Thus, the total phase shift = 360° (or 0°)

SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

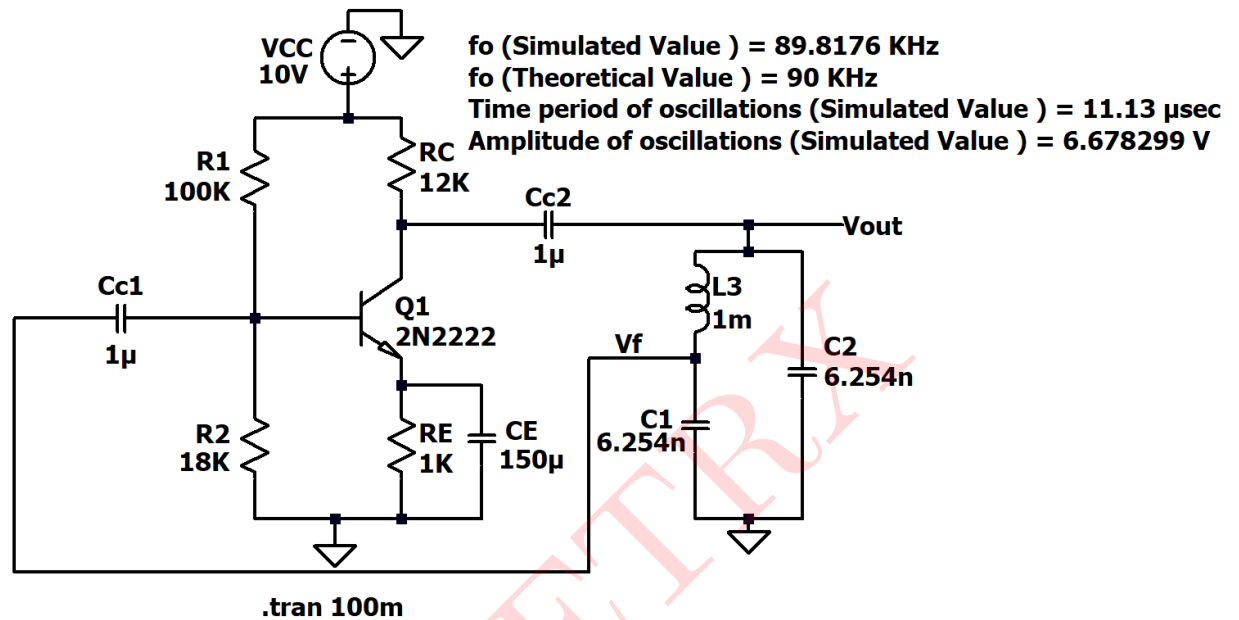


Figure 3: Circuit Schematic

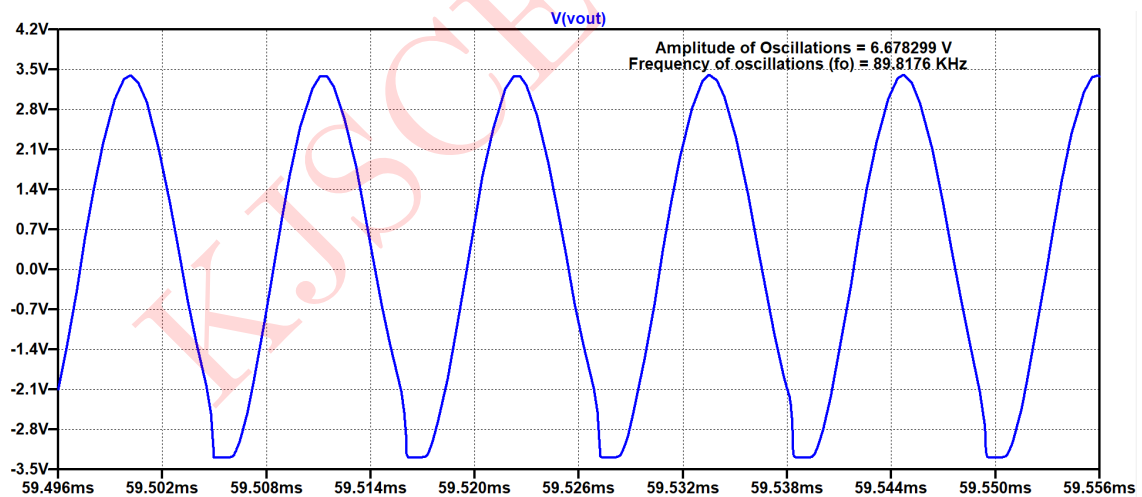


Figure 4: Output voltage waveform

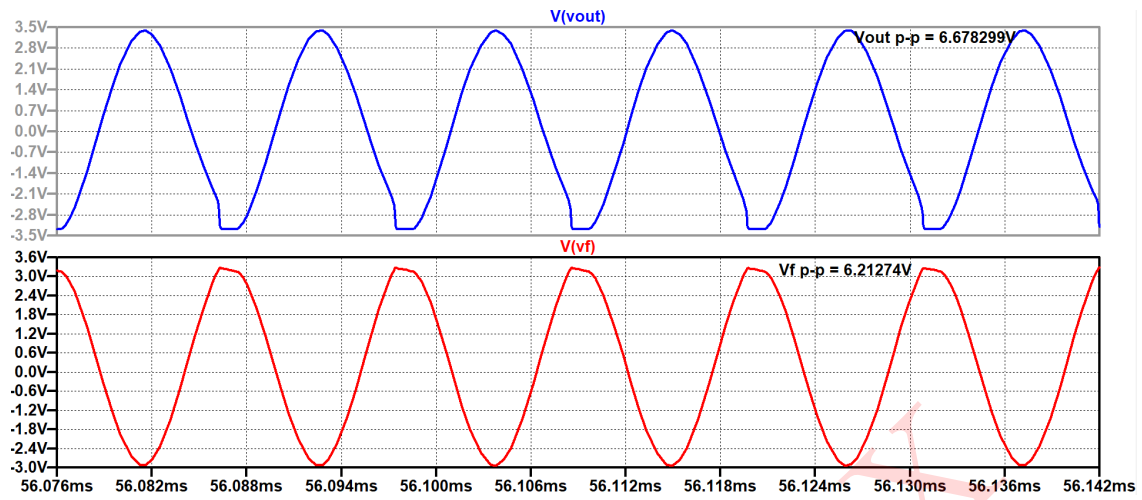


Figure 5: Phase shift between output voltage and feedback voltage

Comparison between Theoretical and Simulated values :-

Parameters	Theoretical	Simulated
Frequency of oscillations (f_o)	90kHz	89.8176kHz
Time period of oscillations	$11.11\mu sec$	$11.13\mu sec$
Amplitude of oscillations	—	6.6783V
Feedback signal V_f amplitude	—	6.21274V
Feedback fraction	1	0.93
Phase shift offered by tank circuit	180°	180°

Table 1: Numerical 1

Numerical 2: In a colpitt's Oscillator, amplifier components are $R_1 = 100k$, $R_2 = 18k$, $R_C = 12k$, $R_E = 1k$, $C_{C1} = 1\mu F$, $C_E = 150\mu F$, $C_{C2} = 1\mu F$, $V_{CC} = 10V$. Select the LC tank circuit such that frequency of oscillations is close to 550kHz.

BJT transistor: 2N2222

Also comment on the phase shift offered by LC Tank circuit.

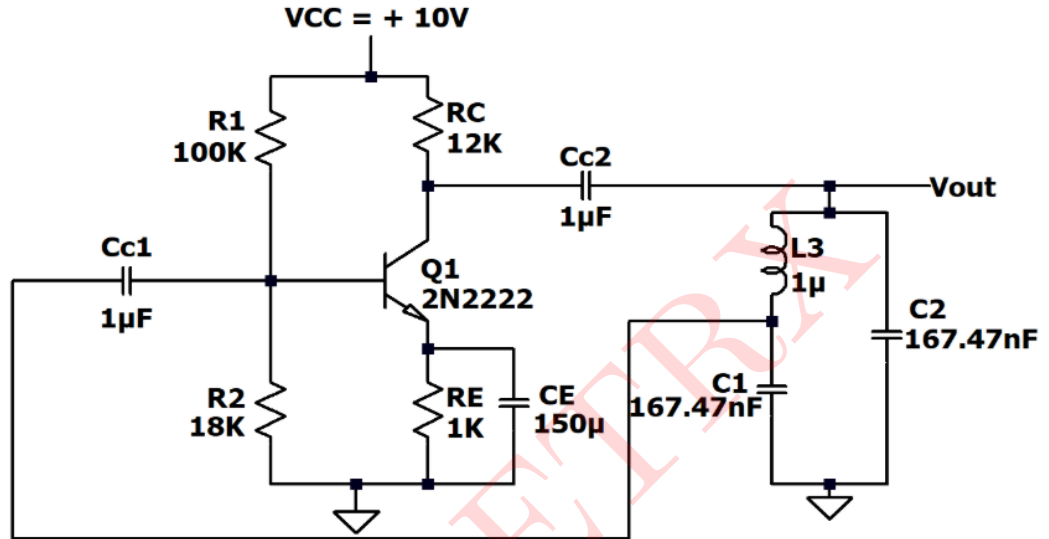


Figure 6: Circuit 2

Solution:

Frequency of oscillations for a Colpitt's Oscillator is given as:

$$f_o = \frac{1}{2\pi\sqrt{C_{eq}L_3}}$$

$$\text{Where, } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\text{Let } L_3 = 1\mu H$$

Since we want the frequency of oscillations to be close to 90kHz

$$f_o \approx 550kHz$$

$$\therefore 550 \times 10^3 = \frac{1}{2\pi\sqrt{10^{-6} \times C_{eq}}}$$

$$\therefore 10^{-6} \times C_{eq} = \frac{1}{(550 \times 10^3 \times 2\pi)^2}$$

$$\therefore C_{eq} = \frac{10^6}{(90 \times 10^3 \times 2\pi)} = \mathbf{83.73nF}$$

$$\text{Let } C_1 = C_2$$

$$\therefore C_1 = C_2 = 2 \times 83.73nF = \mathbf{167.47nF}$$

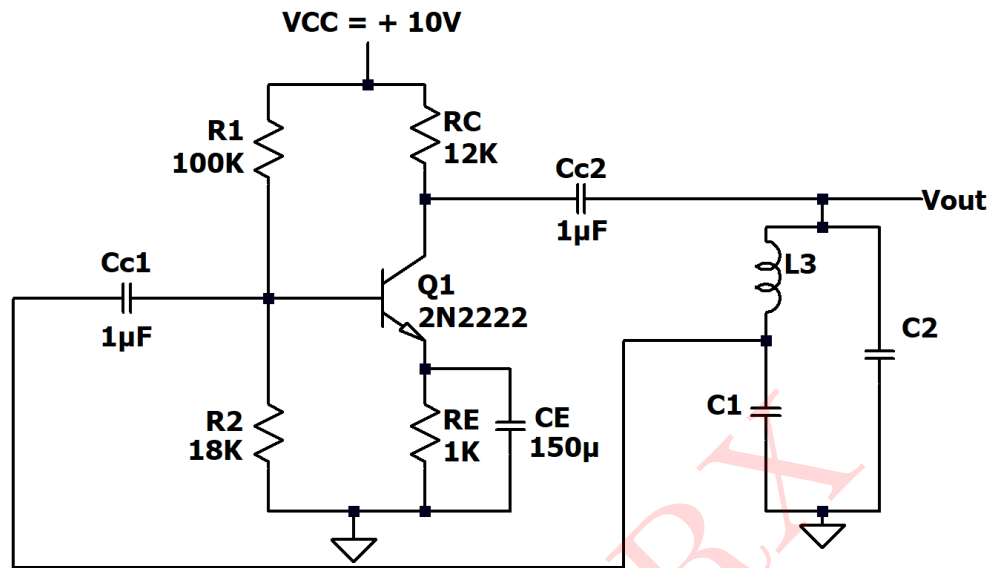


Figure 7: Colpitt's Oscillator

Frequency of oscillations = **550kHz**

$$\therefore \text{Time period of oscillations} = \frac{1}{f_o} = \frac{1}{550 \times 10^3} = \mathbf{1.818 \mu\text{sec}}$$

$$\text{Feedback fraction (K)} = \frac{V_f}{V_o} = \frac{IX_{C2}}{IX_{C1}} = \frac{C_1}{C_2} = \frac{167.47 \times 10^{-9}}{167.47 \times 10^{-9}} = \mathbf{1}$$

Feedback fraction = 1

Phase shift provided by common emitter amplifier is 180°

Phase shift provided by the LC tank circuit is 180°

So the total phase shift of the entire circuit is 360° (or 0°)

Thus, the total phase shift = 360° (or 0°)

SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

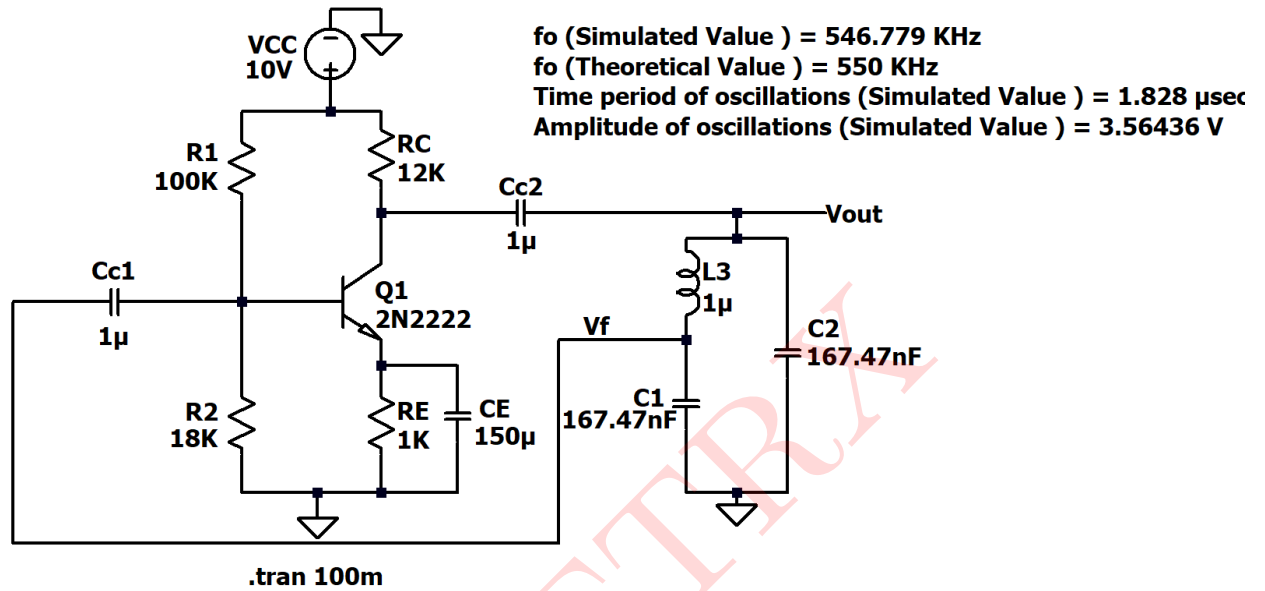


Figure 8: Circuit Schematic

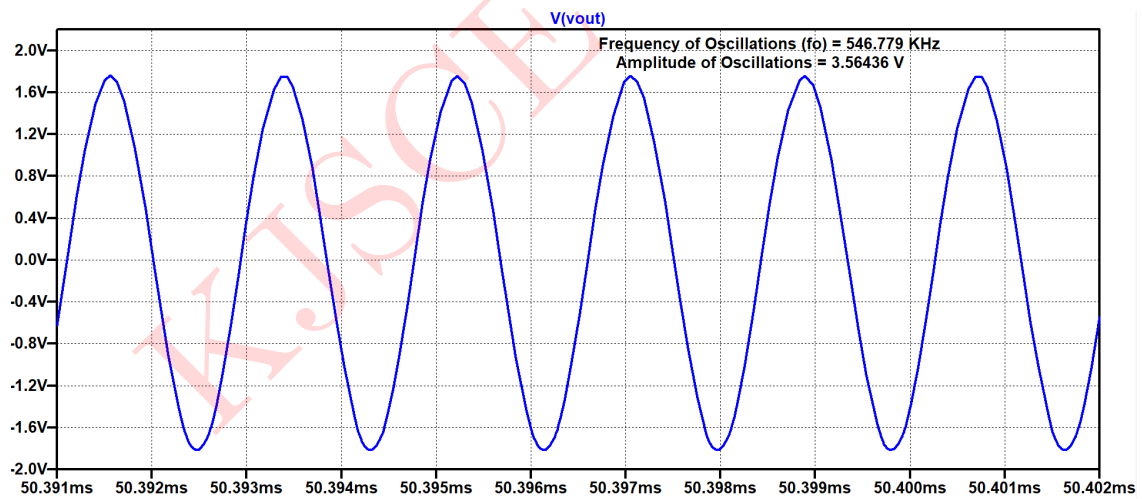


Figure 9: Output voltage waveform

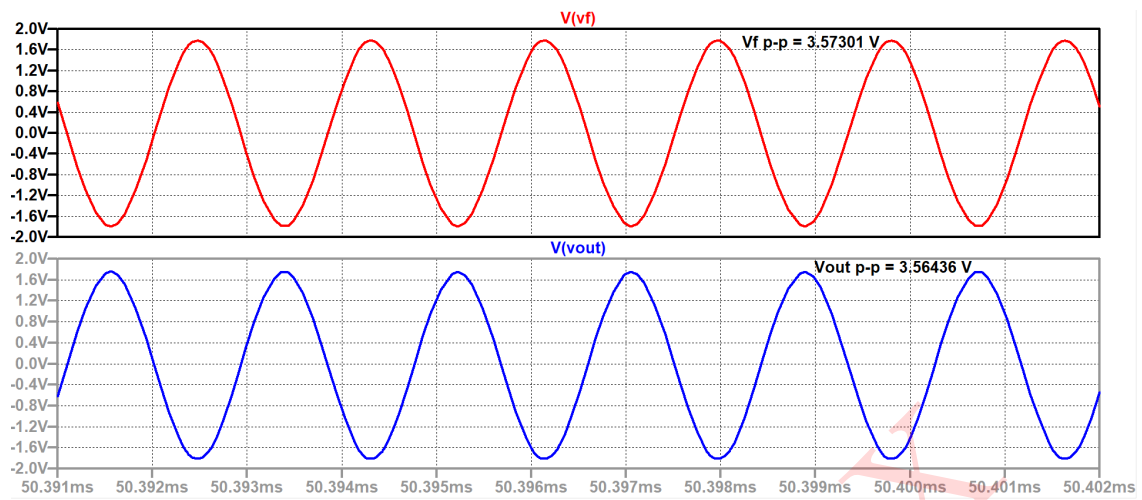


Figure 10: Phase shift between output voltage and feedback voltage

Comparison between Theoretical and Simulated values :-

Parameters	Theoretical	Simulated
Frequency of oscillations (f_o)	550kHz	546.779kHz
Time period of oscillations	$1.818\mu\text{sec}$	$1.828\mu\text{sec}$
Amplitude of oscillations	—	3.5644V
Feedback signal V_f amplitude	—	3.5730V
Feedback fraction	1	1
Phase shift offered by tank circuit	180°	180°

Table 2: Numerical 2
