

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1:

Simulate a half wave rectifier circuit with input Amplitude = 200V peak, $f = 50$ Hz, $R_1 = 120\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

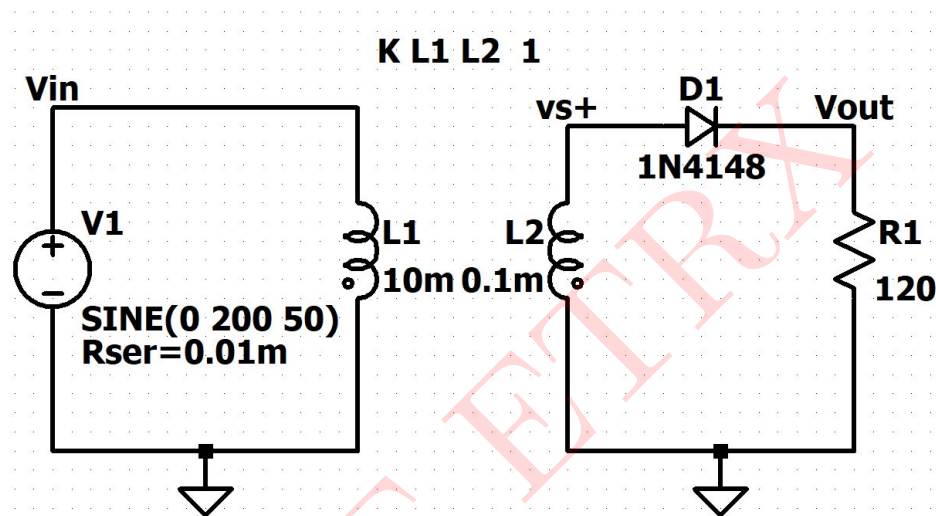


Figure 1: Circuit 1

Solution:

$$\frac{V_m}{V_1} = \frac{N_2}{N_1}$$

$$V_m = \frac{1}{10} \times 200$$

$$\therefore V_m = 20V$$

$$P_{dc} = \frac{(V_m)^2}{(\pi)^2 \times R_1} = \frac{(20)^2}{(3.14)^2 \times 120}$$

$$\therefore P_{dc} = 0.3377W$$

$$P_{ac} = \frac{(V_m)^2}{4 \times (R_s + R_1)} = \frac{(20)^2}{4 \times (0.01 \times 10^{-3} + 120)}$$

$$\therefore P_{ac} = 0.833W$$

$$\text{Efficiency} = \frac{P_{dc}}{P_{ac}} \times 100 = 40.54$$

$$\therefore \eta = 40.54\%$$

$$I_m = \frac{V_m}{(R_s + R_1)} = \frac{20}{(0.01 \times 10^{-3} + 120)}$$

$$\therefore I_m = 0.116A$$

$$PIV = -V_m = -20V$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

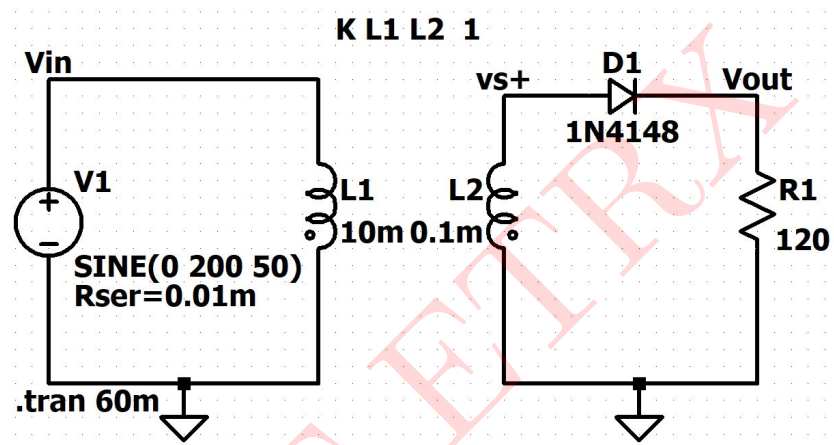


Figure 2: Circuit schematic for circuit 1

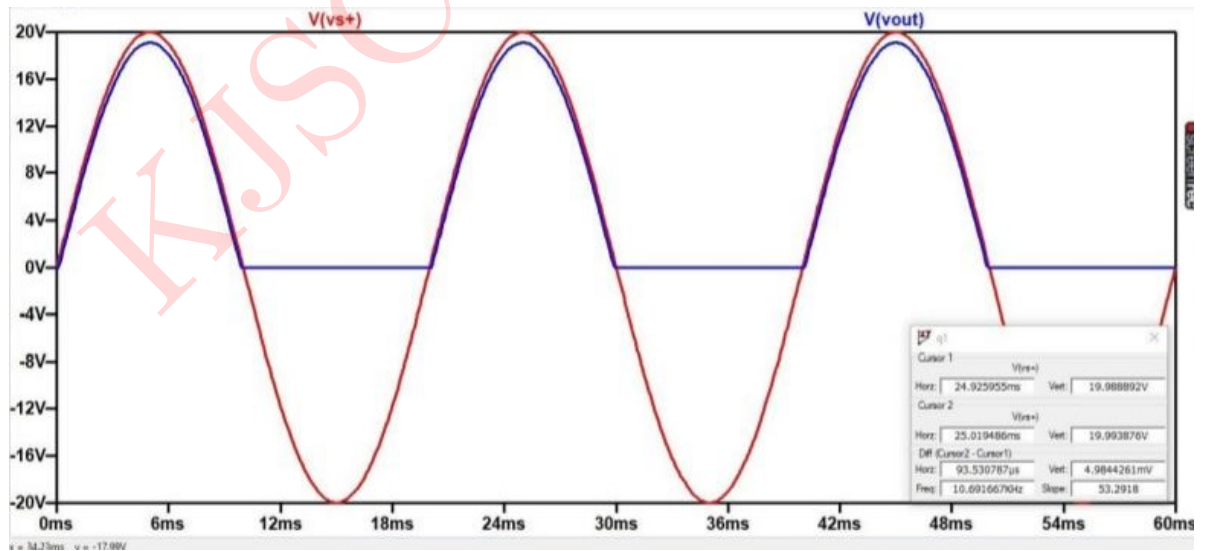


Figure 3: Peak value of V_m

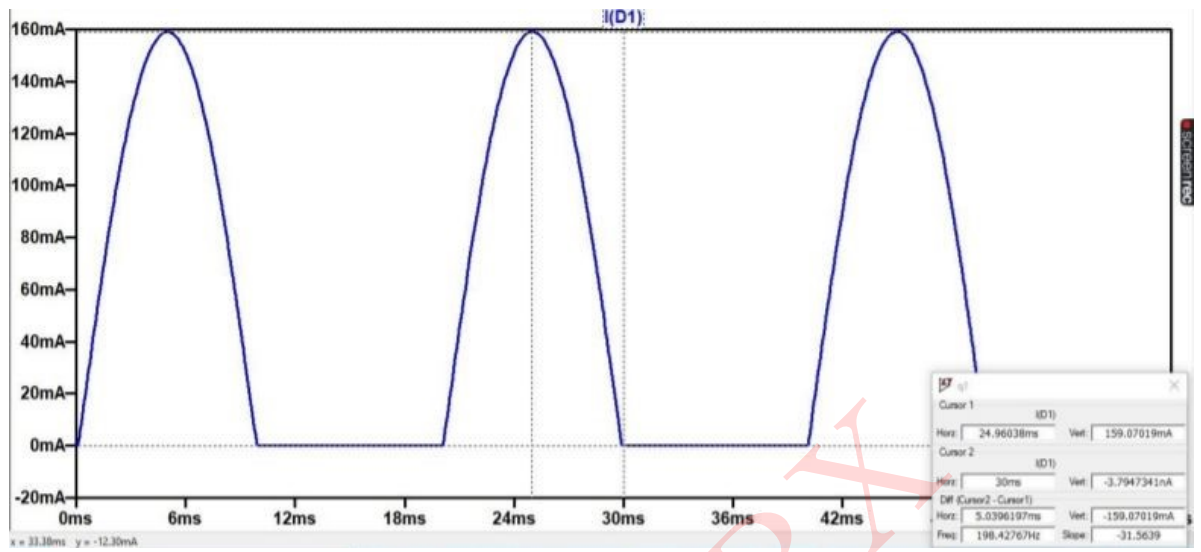


Figure 4: Peak value of I_m

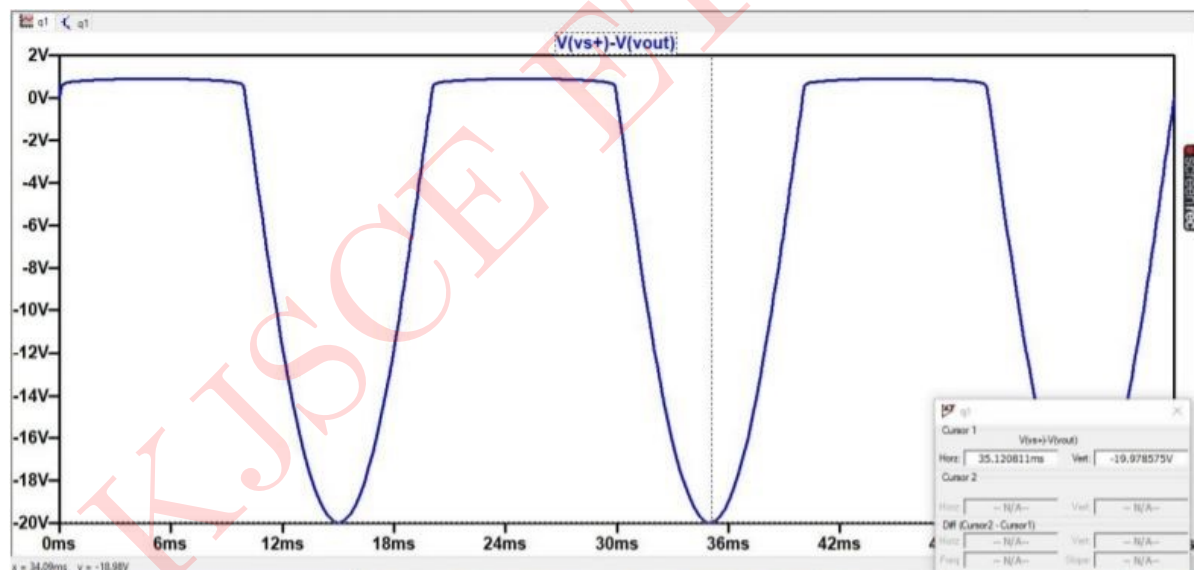


Figure 5: P_{IV} rating

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak V_m	20V	19.983V
Output peak I_m	0.166A	0.159A
AC power	0.833W	0.758W
DC power	0.337W	0.3047W
Efficiency	40.54%	40.19%
PIV	-20V	-19.983V

KJSCE ETRX

Numerical 2:

Simulate a Full wave rectifier circuit with input Amplitude = 200V peak, $f = 50$ Hz, and $R_1 = 120\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down center tap transformer.

Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the diode
- Current flowing through the circuit

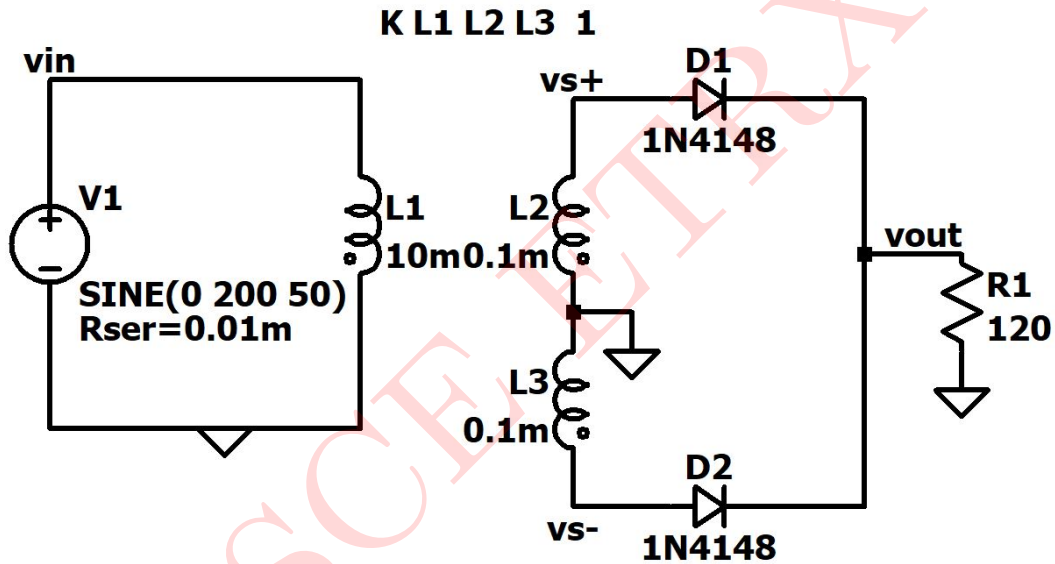


Figure 6: Circuit 2

Solution:

$$\frac{V_m}{V_1} = \frac{N_2}{N_1}$$

$$\therefore V_m = 20V$$

$$I_m = \frac{V_m}{(R_s + R_1)} = \frac{20}{(0.01 \times 10^{-3} + 120)}$$

$$\therefore I_m = 0.116A$$

$$P_{dc} = \frac{4 \times (I_m)^2}{(\pi)^2} \times R_1 = \frac{4 \times (0.166)^2}{(3.14)^2} \times 120$$

$$\therefore P_{dc} = 1.34016W$$

$$P_{ac} = \frac{(I_m)^2}{2} \times (R_s + R_1) = \frac{(0.166)^2}{2} \times (0.01 \times 10^{-3} + 120)$$

$$\therefore P_{ac} = 1.656W$$

$$PIV = -2 \times V_m = -40V$$

$$\text{Efficiency} = \frac{P_{dc}}{P_{ac}} \times 100 = 80.977\%$$

$$\therefore \eta = 80.977\%$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

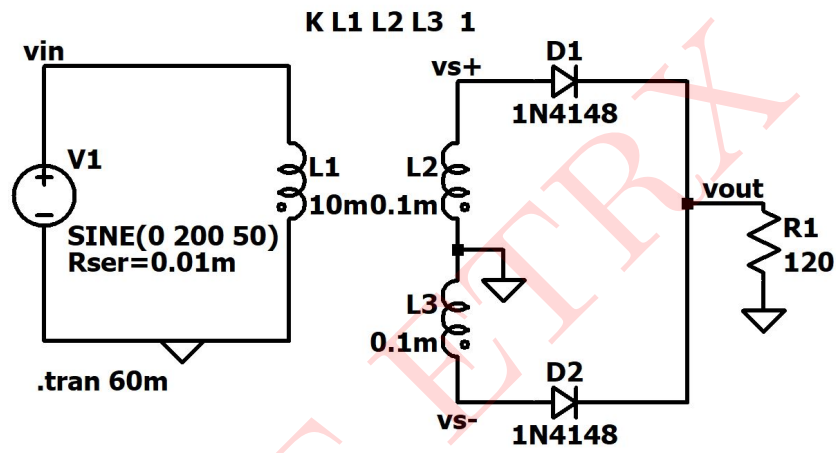


Figure 7: Circuit schematic for circuit 2

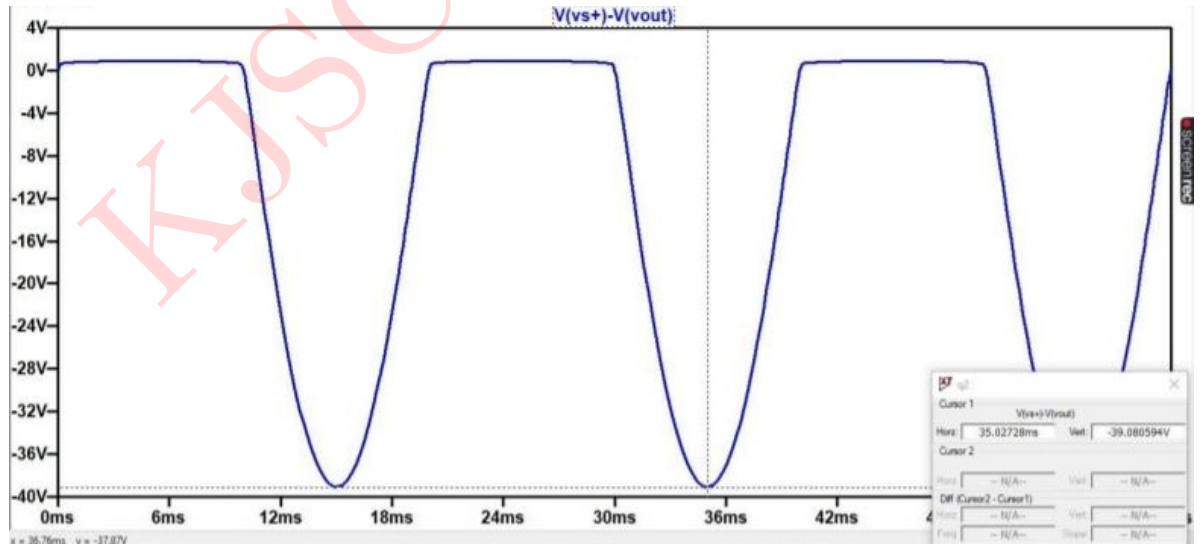


Figure 8: P_{IV} rating

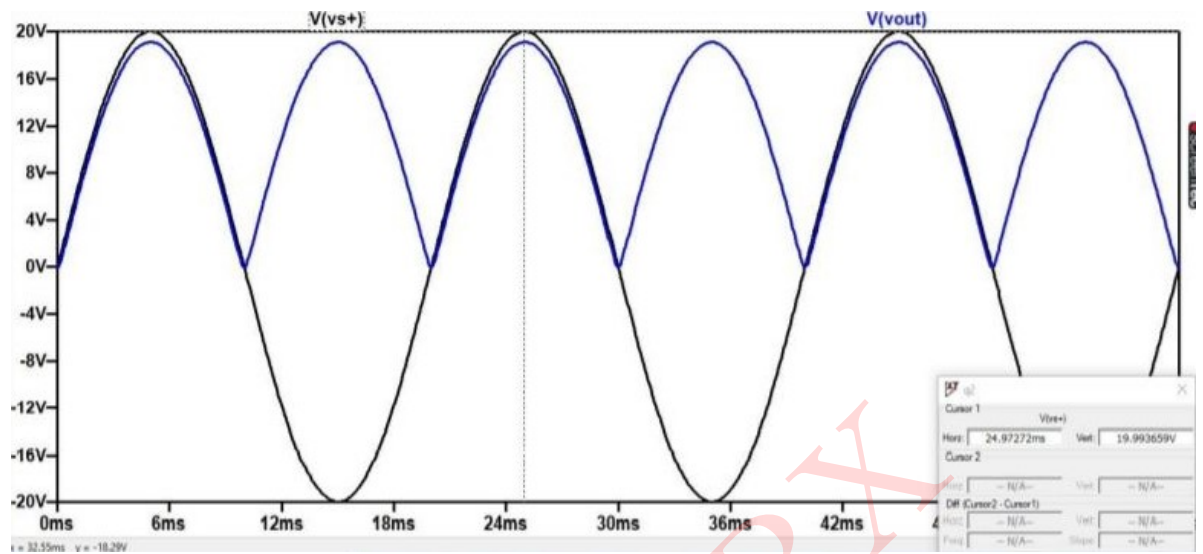


Figure 9: Peak value of V_m

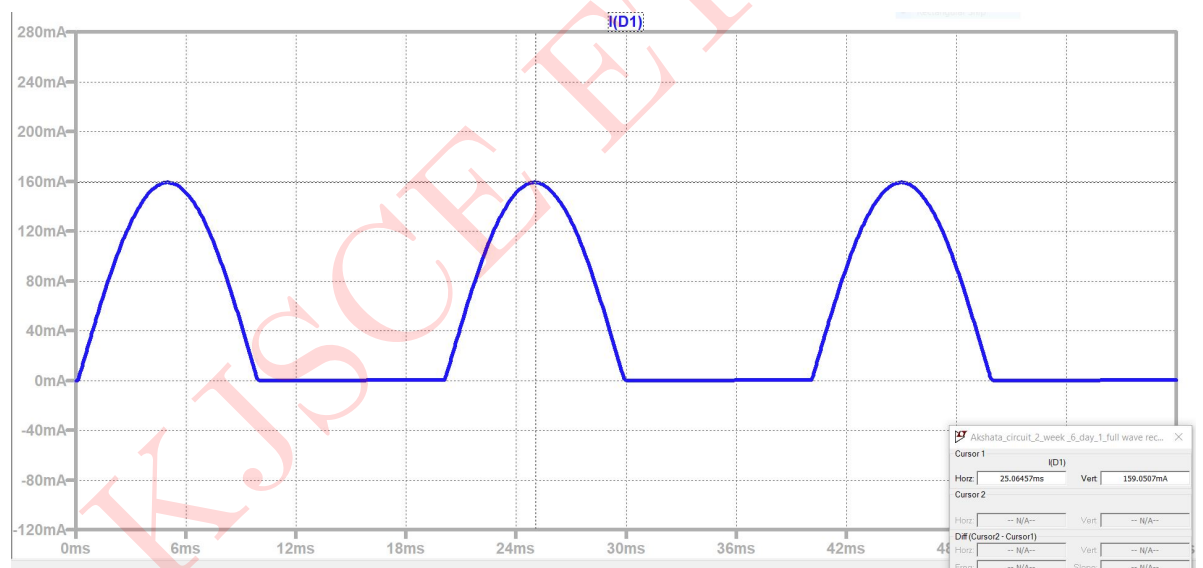


Figure 10: Peak value of I_m

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak V_m	20V	19.983V
Output peak I_m	0.166A	0.159A
AC power	1.65W	1.516W
DC power	1.34W	1.229W
Efficiency	80.977%	81.06%
PIV rating	-40V	-39.083V

KJSCE ETRX