

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Darlington Amplifier**

Q1. Calculate DC voltages at each mode and DC currents in the give circuit.

Given:  $R_1 = 82k\Omega$ ,  $R_2 = 39k\Omega$ ,  $R_E = 820\Omega$ ,  $C_{C1} = 10\mu F$ ,  $C_{C2} = 10\mu F$ ,  $V_{CC} = 10V$ ,  $\beta = 100$ .

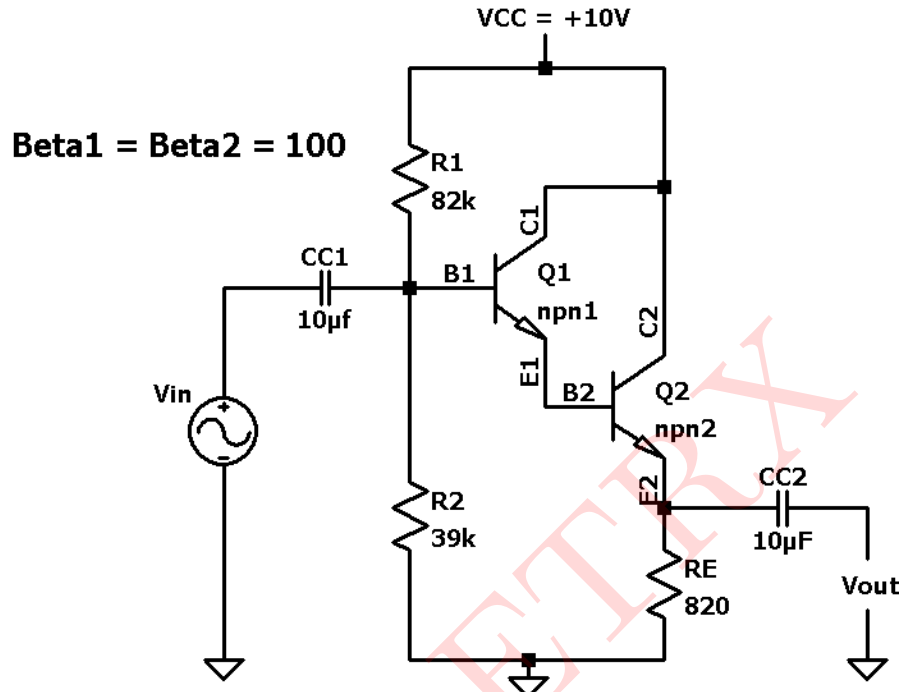


Figure 1: Circuit 1

**Solution:**

DC Analysis:

$$V_{BE} = V_{BE1} + V_{BE2} = 0.7 + 0.7 = 1.4V$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) \times V_{CC} = \left( \frac{39k}{82k + 39k} \right) 10 = 3.223V$$

$$R_{TH} = R_1 \parallel R_2 = 82k \parallel 39k = 26.429k\Omega$$

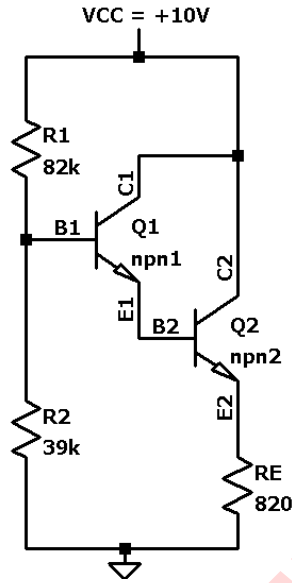


Figure 2: DC equivalent circuit

By thevenins equivalent circuit

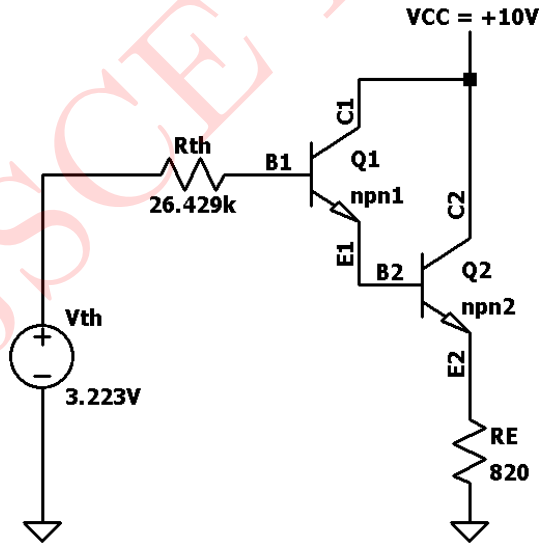


Figure 3: Thevenin equivalent circuit

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)^2 R_E} = \frac{3.223 - 1.4}{26.429k + (101)^2 \times 820} = 0.18149\mu A$$

$$I_{C1} = \beta I_{B1} = 0.018149mA$$

$$I_{E1} = I_{B1} + I_{C1} = 0.01833mA$$

$$\text{Now, } I_{E1} = I_{B2} = 0.01833mA$$

$$I_{C2} = \beta I_{B2} = 1.83304mA$$

$$I_{E2} = I_{C2} + I_{B2} = 1.83304 + 0.01833 = 1.85137mA$$

$$V_{E2} = I_{E2} R_E = 1.85137mA \times 820\Omega = 1.5181V$$

$$V_{C2} = 10\text{V}$$

$$V_{CE2} = V_{C2} - V_{E2} = 10 - 1.5181 = 8.4819\text{V}$$

$$Q \text{ point} = (I_C, V_{CE}) = (1.83304\text{mA}, 8.4819\text{V})$$

Small signal parameters:

$$r_{\pi1} = \frac{\beta V_T}{I_{C1}} = \frac{100 \times 26\text{mV}}{0.018149\text{mA}} = 143.258\text{k}\Omega$$

$$r_{\pi2} = \frac{\beta V_T}{I_{C2}} = \frac{100 \times 26\text{mV}}{1.83305\text{mA}} = 1.418\text{k}\Omega$$

Mid frequency equivalent circuit:

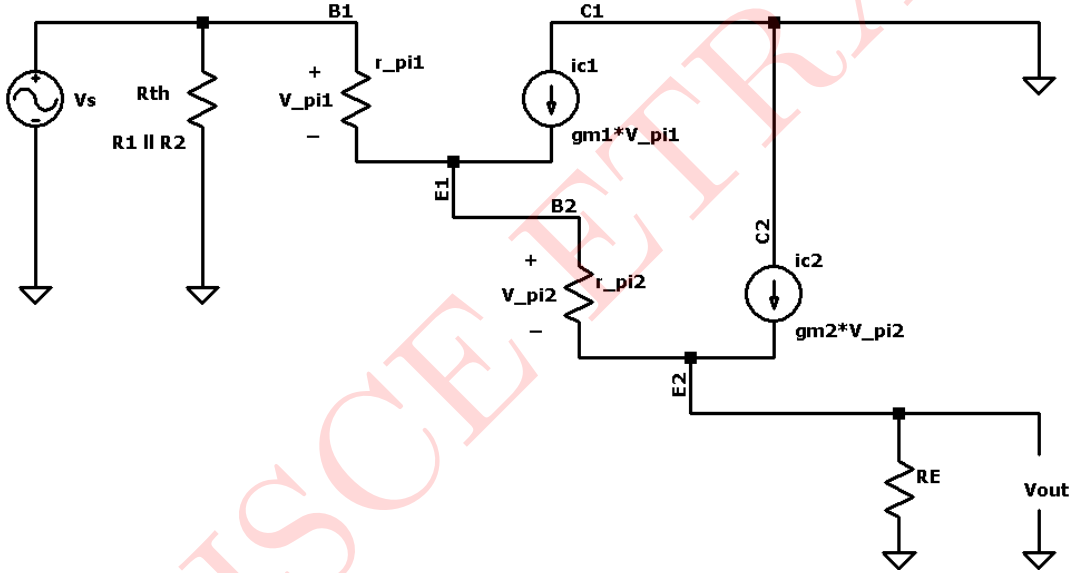


Figure 4: Mid frequency equivalent circuit

$$Z_{i2} = r_{\pi} + (1 + \beta)R_E = 1.418\text{k} + (101) \times 820 = 82.238\text{k}\Omega$$

$$Z_{i1} = r_{\pi} + (1 + \beta)Z_{i2} = 143.258\text{k} + (101) \times 82.238\text{k} = 8.449\text{M}\Omega \text{ (very high)}$$

$$Z_i = R_1 \parallel R_2 \parallel Z_{i1} = 82\text{k} \parallel 39\text{k} \parallel 8.449\text{M} = 26.3465\text{k}\Omega \text{ (} R_1 \text{ and } R_2 \text{ decreases input impedance)}$$

$$Z_{o2} = \frac{Z_{o1} + r_{\pi2}}{1 + \beta}$$

$$Z_{o1} = \frac{(R_1 \parallel R_2) + r_{\pi1}}{1 + \beta} = \frac{26.429\text{k} + 143.258\text{k}}{101} = 1.680\text{k}\Omega$$

$$Z_{o2} = \frac{1.680\text{k} + 1.418\text{k}}{101} = 30.6732\text{ }\Omega \text{ (Very low)}$$

$$Z_o = Z_{o2} \parallel R_E = 30.6732 \parallel 820 = 29.5671\text{ }\Omega \text{ (very low)}$$

$A_i$  Current gain:

$$A_{i_1} = \frac{I_{E1}}{I_{B1}} = (1 + \beta) = \mathbf{101}$$

$$A_{i_2} = \frac{I_{E2}}{I_{B2}} = (1 + \beta) = \mathbf{101}$$

$$A_{i_t} = A_{i_2} \times A_{i_1} = 101 \times 101 = \mathbf{10201} \text{ ( very high)}$$

$$A_{i_s} = \frac{I_o}{I_i} = \frac{I_o}{I_{B2}} \times \frac{I_{B2}}{I_{B1}} \times \frac{I_{B1}}{I_i}$$

$$\frac{I_{B1}}{I_i} = \frac{R_{TH}}{R_{TH} + Z_i} = \frac{26.429k}{26.429k + 8.449M} = \mathbf{3.1183mA}$$

$$A_{i_s} = 101.118mA = \mathbf{31.8097} \text{ (Presence of } R_{TH} \text{ reduces current gain)}$$

$A_v$  Voltage Gain:

$$A_{V_2} = \frac{V_o}{V_1} = \frac{R_E}{Z_{i2}} \times A_{i_2} = 101 \times \frac{820}{82.238k} = \mathbf{1.007}$$

$$A_{V_1} = \frac{V_1}{V_i} = \frac{Z_{i1}}{Z_{i2}} \times A_{i_1} = 101 \times \frac{82.238k}{8.449M} = \mathbf{0.98307}$$

$$A_{V_T} = A_{V_2} \times A_{V_1} = 1.0070 \times 0.98307 = \mathbf{0.98995}$$

$$A_{V_{Ts}} = A_{V_T} \times \frac{Z_i}{Z_i + R_{sig}} = \mathbf{0.98997} \text{ (}\because R_{sig} = 0\text{)}$$

$$A_{V_{Ts}} \text{indB} = 20 \log_{10}(0.98995) = \mathbf{-0.08775dB}$$

## SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

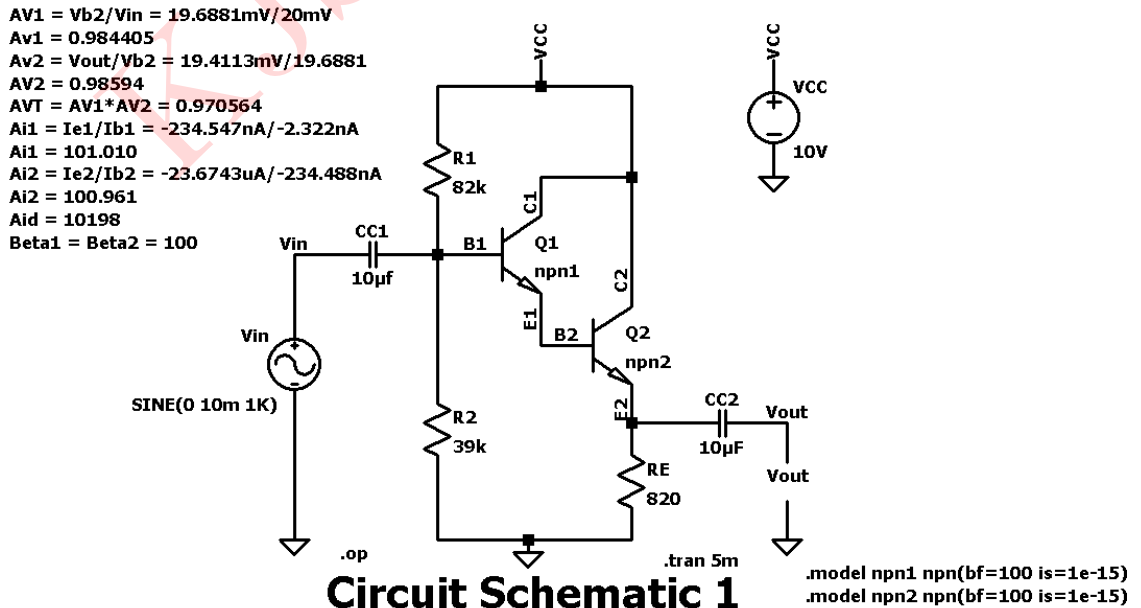


Figure 5: Circuit Schematic

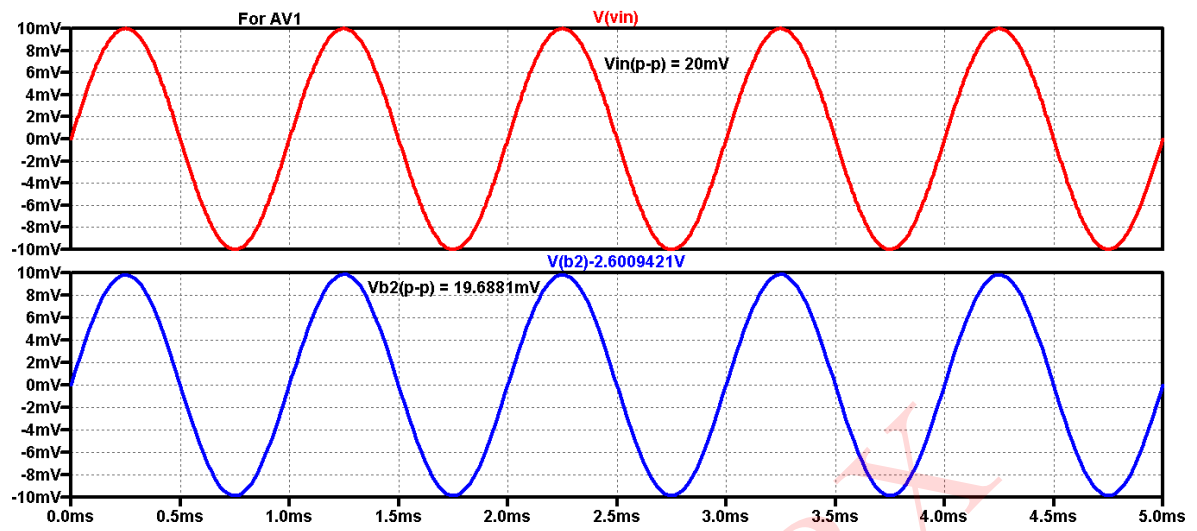


Figure 6: Input output waveform for  $A_{V_1}$

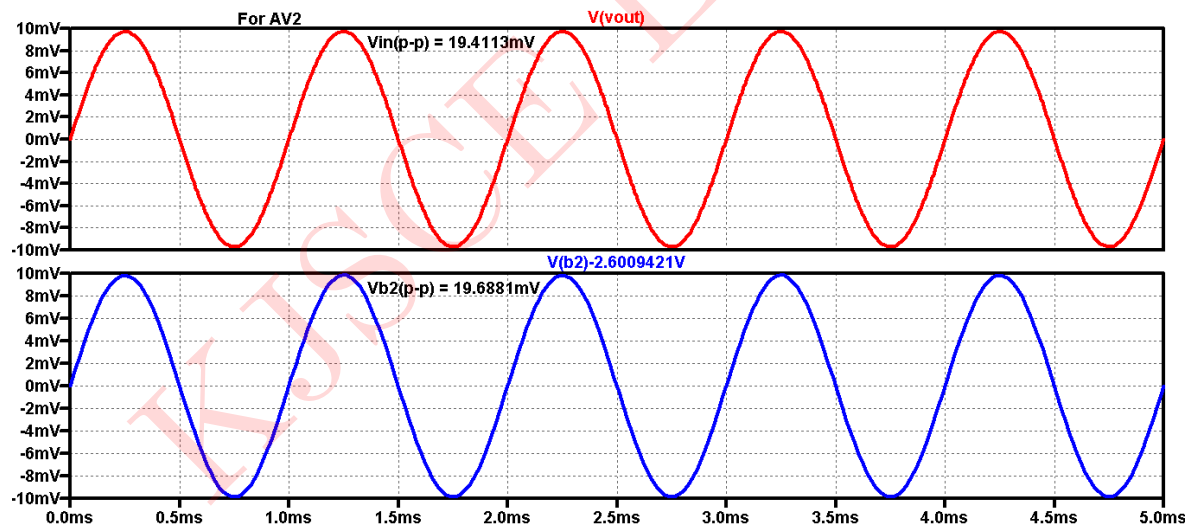


Figure 7: Input output waveform for  $A_{V_2}$

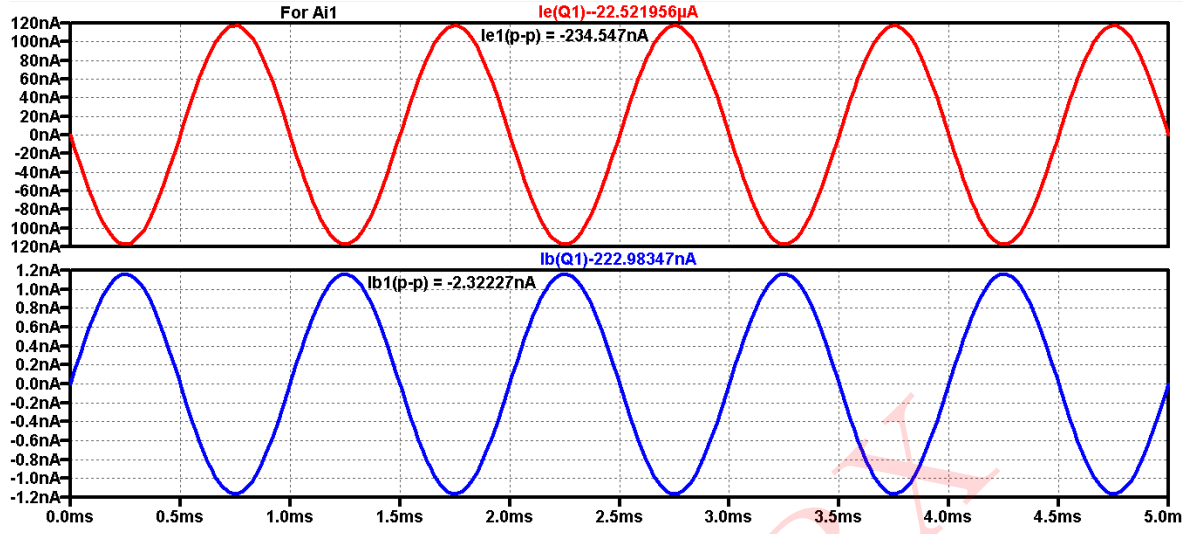


Figure 8: Input output waveform for  $A_{i1}$

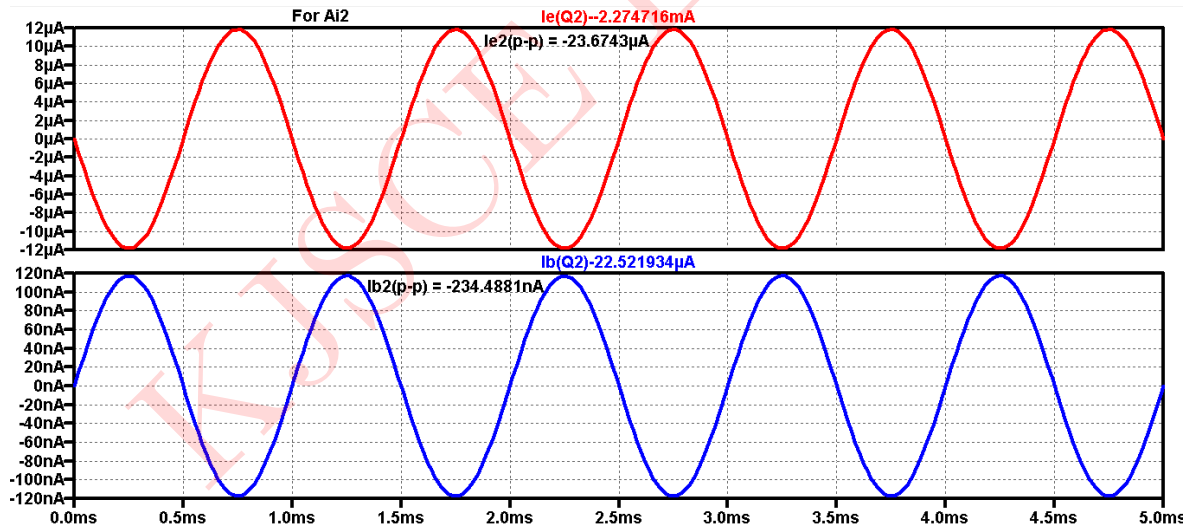


Figure 9: Input output waveform for  $A_{i2}$

### Comparison of Theoretical and Simulated Values:

Parameters	Simulated	Theoretical
<b>Stage 1:</b>		
$I_{B1}, I_{C1}$	0.2229 $\mu$ A, 0.0222mA	0.18149 $\mu$ A, 0.018149mA
$I_{E1}$	0.02252mA	0.01833mA
<b>Stage 2:</b>		
$I_{B2}, I_{C2}$	0.02252mA, 2.225mA	0.01833mA, 1.83304mA
$I_{E2}, V_{E2}$	2.274mA, 1.865V	1.85137mA, 1.5181V
$V_{C2}, V_{CE2}$	10V, 8.135V	10V, 8.4819V
$A_{V1}$	0.984404	0.98307
$A_{V2}$	0.98594	1.0070
$A_{VT}$	0.97056	0.98995
$A_{i1}$	101.010	101
$A_{i2}$	100.961	101
$A_{iT}$	10198	10201
$Z_i$	—	26.3456k $\Omega$
$Z_o$	—	29.5671 $\Omega$

Table 1: Numerical 1

\*\*\*\*\*