

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1:

Simulate a Half Wave Rectifier circuit with input amplitude $V = 150\text{V}$ peak, $f = 50\text{ Hz}$ and $R_1 = 110\Omega$ using LT spice. Select diode as IN4148. Use 10:1 step down transformer.

Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

Also, calculate the efficiency of the Half wave rectifier circuit.

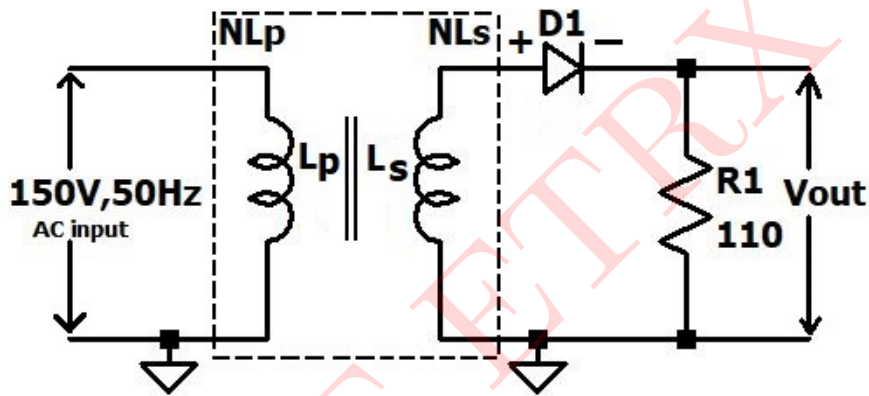


Figure 1: Half Wave Rectifier

Solution:

$$\frac{N_{L_s}}{N_{L_p}} = \frac{1}{10} \quad R_1 = 110\Omega, V = 150\text{V}, f = 50\text{Hz} \quad \dots(\text{given})$$

$$\frac{V_m}{V} = \frac{N_{L_s}}{N_{L_p}}$$

where V_m is secondary voltage and V is input voltage.

$$\therefore V_m = \frac{1}{10} \times 150 = 15\text{V}$$

$$P_{dc} = \frac{V_m^2}{\pi^2 \times R_1} = \frac{(15)^2}{(3.14)^2 \times 110}$$

$$\therefore P_{dc} = 0.207\text{W}$$

$$P_{ac} = \frac{V_m^2}{4 \times (R_s + R_1)} = \frac{(15)^2}{4 \times (0.01 \times 10^{-3} + 110)}$$

$$\therefore P_{ac} = 0.51136\text{W}$$

$$\text{Efficiency}(\eta\%) = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.207}{0.51136} \times 100$$

$$\therefore \text{Efficiency}(\eta\%) = 40.48\%$$

$$I_m = \frac{V_m}{(R_s + R_1)} = \frac{15}{(0.01 \times 10^{-3} + 110)}$$

$$\therefore I_m = 136.3\text{mA}$$

$$\text{PIV} = -V_m = -15\text{V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

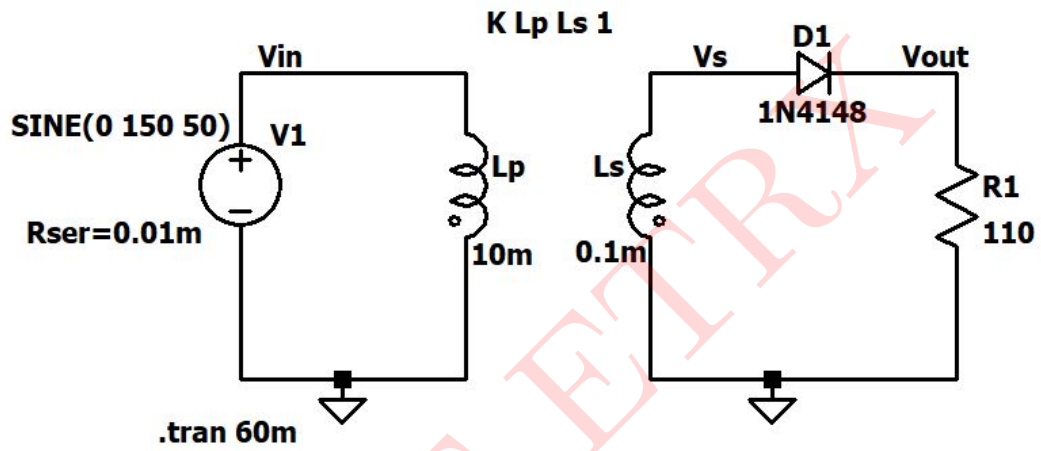


Figure 2: Circuit Schematic for Half Wave Rectifier

Graphs are shown in Figure 3.

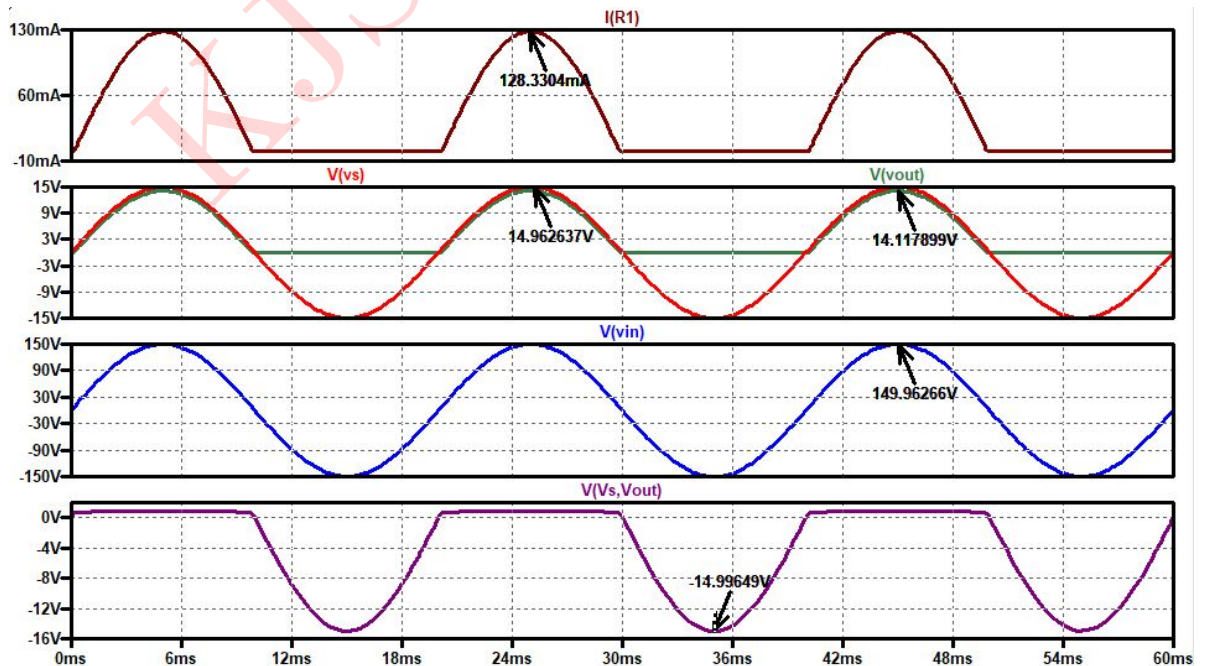


Figure 3: Graphs for Figure 2

For Figure 2,

$$V_m = \mathbf{14.96V}, I_m = \mathbf{128.33mA} \quad \text{..(from Figure 3)}$$

$$P_{dc} = \frac{V_m^2}{\pi^2 \times R_1} = \frac{(14.96)^2}{(3.14)^2 \times 110}$$

$$\therefore P_{dc} = \mathbf{0.2061W}$$

$$P_{ac} = \frac{V_m^2}{4 \times (R_s + R_1)} = \frac{(14.96)^2}{4 \times (0.01 \times 10^{-3} + 110)}$$

$$\therefore P_{ac} = \mathbf{0.5086W}$$

$$\text{Efficiency}(\eta\%) = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.2061}{0.5086} \times 100$$

$$\therefore \text{Efficiency}(\eta\%) = \mathbf{40.52\%}$$

$$\text{PIV} = -V_m = \mathbf{-14.96V}$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_m	15V	14.96V
I_m	136.3mA	128.33mA
P_{ac}	0.51136W	0.5086W
P_{dc}	0.207W	0.2061W
Efficiency($\eta\%$)	40.48%	40.52%
PIV rating	-15V	-14.96V

Table 1: Numerical 1

Numerical 2:

Simulate a Full Wave Rectifier circuit with input Amplitude $V = 140\text{V}$ peak, $f = 50\text{ Hz}$ and $R_1 = 110\ \Omega$ using LT spice. Select diode as IN4148. Use 10:1 step down center tap transformer.

Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

Also, calculate the efficiency of the Full wave Center tapped rectifier circuit.

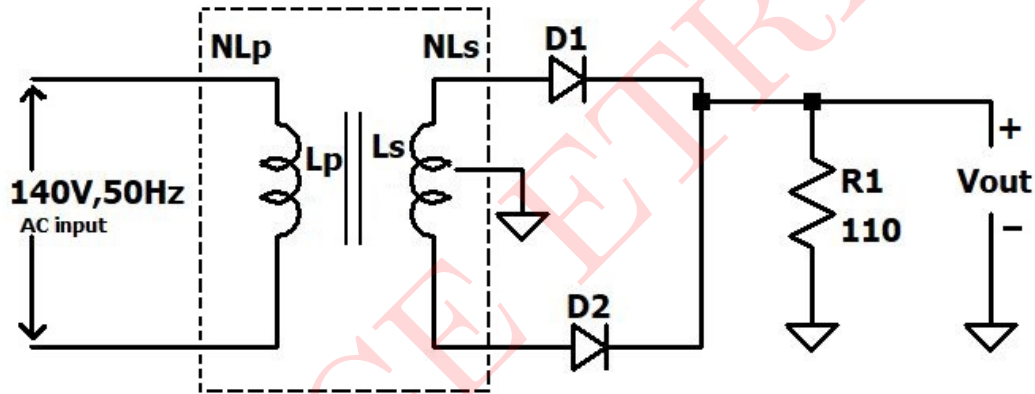


Figure 4: Full Wave Rectifier

Solution:

$$\frac{N_{Ls}}{N_{Lp}} = \frac{1}{10} \quad R_1 = 110\Omega, V = 140\text{V}, f = 50\text{Hz} \quad \dots(\text{given})$$

$$\frac{V_m}{V} = \frac{N_{Ls}}{N_{Lp}}$$

where V_m is secondary voltage and V is input voltage.

$$\therefore V_m = \frac{1}{10} \times 140 = 14\text{V}$$

$$I_m = \frac{V_m}{(R_s + R_1)} = \frac{14}{(0.01 \times 10^{-3} + 110)}$$

$$\therefore I_m = 127.2\text{mA}$$

$$P_{dc} = \frac{(2I_m)^2}{\pi^2} \times R_1 = \frac{(2 \times 127.2 \times 10^{-3})^2 \times 110}{(3.1415)^2}$$

$$\therefore P_{dc} = 0.7213\text{W}$$

$$P_{ac} = \frac{I_m^2}{2} \times (R_s + R_1) = \frac{(127.2 \times 10^{-3})^2 \times (0.01 \times 10^{-3} + 110)}{2}$$

$$\therefore P_{ac} = 0.8898\text{W}$$

$$\text{Efficiency}(\eta\%) = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.7213}{0.8898} \times 100$$

$$\therefore \text{Efficiency}(\eta\%) = 81.063\%$$

$$\text{PIV} = -V_m = -14\text{V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

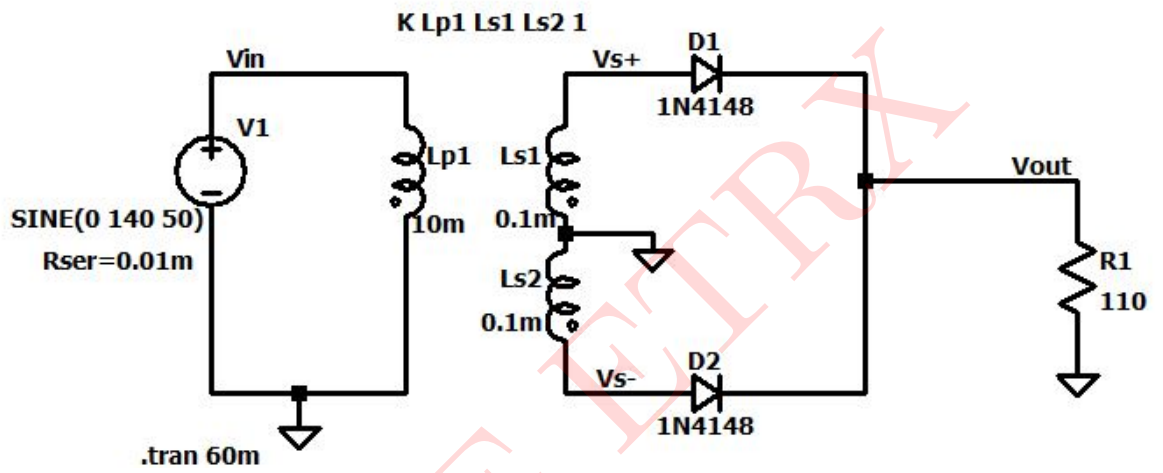


Figure 5: Circuit Schematic for Full Wave Rectifier

Graphs are shown in Figure 6.

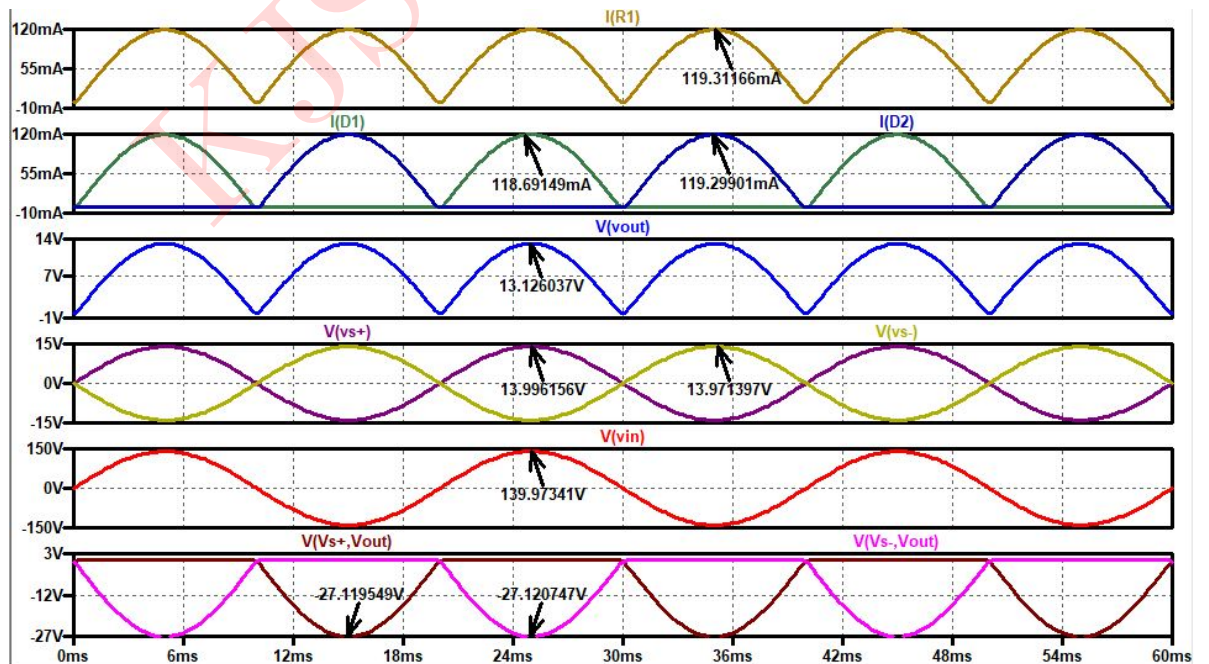


Figure 6: Graphs for Figure 5

For Figure 5,

$$V_m = \mathbf{13.126V}, I_m = \mathbf{119.31mA} \quad \text{..(from Figure 6)}$$

$$P_{dc} = \frac{(2I_m)^2}{\pi^2} \times R_1 = \frac{(2 \times 119.31 \times 10^{-3})^2 \times 110}{(3.1415)^2}$$

$$\therefore P_{dc} = \mathbf{0.6346W}$$

$$P_{ac} = \frac{I_m^2}{2} \times (R_s + R_1) = \frac{(127.2 \times 10^{-3})^2 \times (0.01 \times 10^{-3} + 110)}{2}$$

$$\therefore P_{ac} = \mathbf{0.7829W}$$

$$\text{Efficiency}(\eta\%) = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.7213}{0.8898} \times 100$$

$$\therefore \text{Efficiency}(\eta\%) = \mathbf{81.057\%}$$

$$\text{PIV} = -V_m = \mathbf{-13.126V}$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
V_m	14V	13.126V
I_m	127.2mA	119.31mA
P_{ac}	0.8898W	0.7829W
P_{dc}	0.7213W	0.6346W
Efficiency($\eta\%$)	81.063%	81.057%
PIV rating	-14V	-13.126V

Table 2: Numerical 2
