

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Low and High-frequency response of single-stage amplifier

Numerical 1:

For the circuit given below in figure 1,

- Determine r_π
- Find $A_{V_{mid}} = V_o/V_i$
- Calculate Z_i
- Find $A_{V_{S_{mid}}} = V_o/V_S$
- Determine $f_{L_{CC1}}$ and $f_{L_{CC2}}$
- Determine lower cut-off frequency

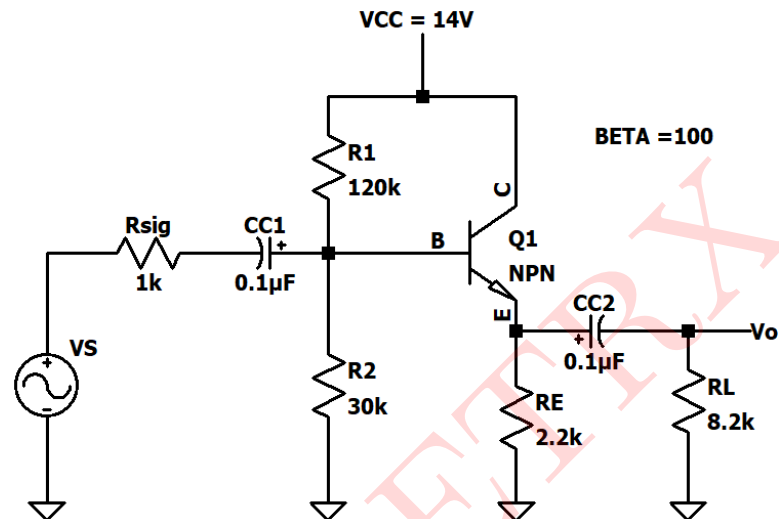


Figure 1: Circuit 1

Solution:

DC analysis:

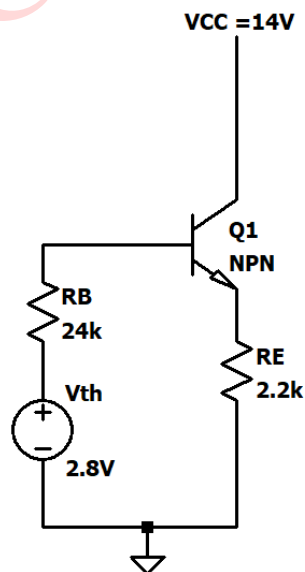


Figure 2: Thevenin's equivalent circuit

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{30k\Omega}{120k\Omega + 30k\Omega} \times 14V = \mathbf{2.8V}$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{120k\Omega \times 30k\Omega}{120k\Omega + 30k\Omega} = \mathbf{24k\Omega}$$

Applying KVL to base-emitter loop,

$$V_{TH} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$2.8V - I_B(24k\Omega) - 0.7V - (101)I_B(2.2k\Omega) = 0$$

$$2.1V - I_B[(24k\Omega + 101(2.2k\Omega))] = 0$$

$$I_B = \frac{2.1V}{24k\Omega + 101(2.2k\Omega)} = \mathbf{8.52\mu A}$$

$$\therefore I_C = \beta I_B = (100)(8.52\mu A) = \mathbf{0.852mA}$$

Small signal parameters:

$$\text{i) } g_m = \frac{I_C}{V_T} = \frac{0.852mA}{26mV} = \mathbf{32.76mA/V}$$

$$\text{ii) } r_o = \frac{V_A}{I_C} = \infty$$

$$\text{iii) } r_\pi = \beta \times \frac{V_T}{I_C} = 100 \times \frac{26mV}{0.852\mu A} = \mathbf{3.051k\Omega}$$

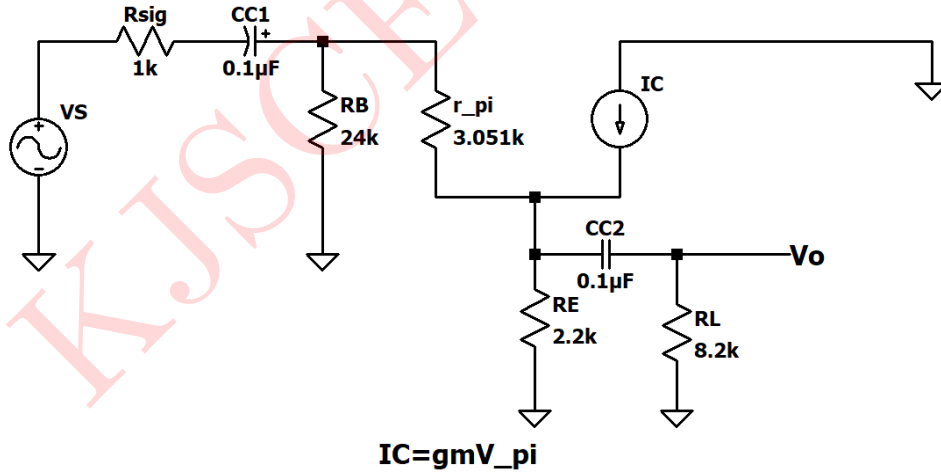


Figure 3: Low frequency AC equivalent circuit

For C_{C1} :

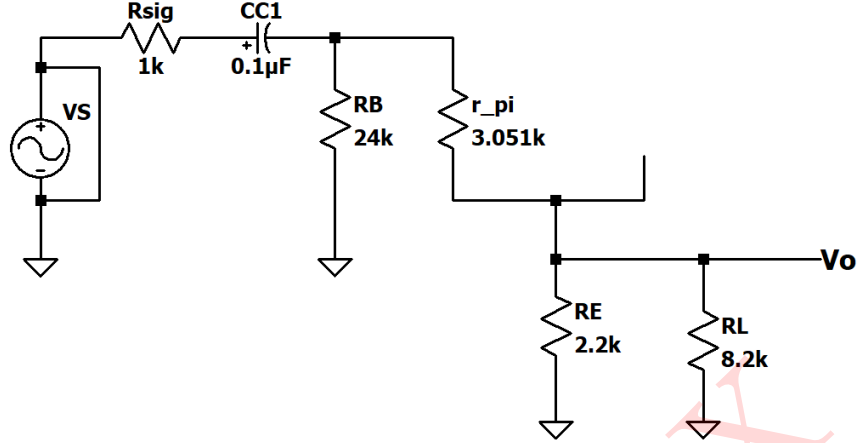


Figure 4: Small signal low frequency equivalent circuit for C_{C1} alone

$$\begin{aligned}
 R_i &= R_B \parallel [r_\pi + (1 + \beta)(R_E \parallel R_L)] \\
 &= 24k\Omega \parallel [3.051k\Omega + (101)(2.2k\Omega \parallel 8.2k\Omega)] \\
 &= 24k\Omega \parallel \left[3.051k\Omega + 101 \left(\frac{2.2k\Omega \times 8.2k\Omega}{2.2k\Omega + 8.2k\Omega} \right) \right] \\
 &= 24k\Omega \parallel [3.051k\Omega + 101(1.73k\Omega)] \\
 &= 24k\Omega \parallel [178.24k\Omega] \\
 &= \frac{24k\Omega \times 178.24k\Omega}{24k\Omega + 178.24k\Omega} = \mathbf{21.15k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 R_{eqCC1} &= R_i + R_{sig} \\
 &= 21.15k\Omega + 1k\Omega = \mathbf{22.15k\Omega}
 \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C1} alone is,

$$\begin{aligned}
 f_{LCC1} &= \frac{1}{2\pi R_{eqCC1} C_{C1}} \\
 &= \frac{1}{2\pi \times 22.15k\Omega \times 0.1\mu F} = \mathbf{71.88Hz}
 \end{aligned}$$

For C_{C2} :

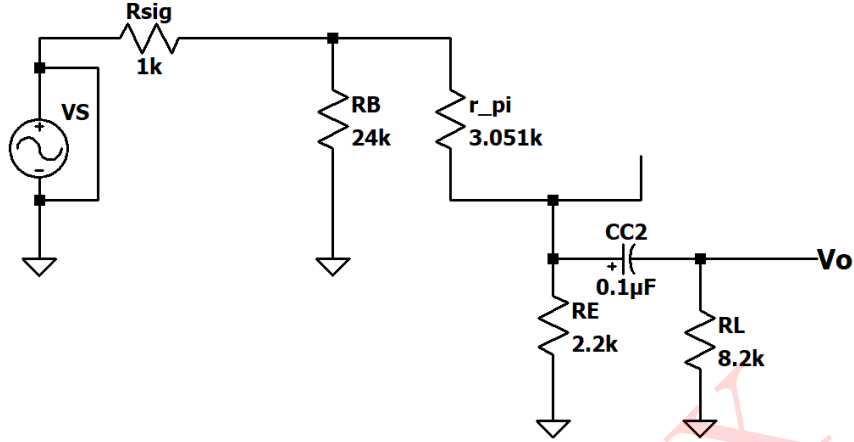


Figure 5: Small signal low frequency equivalent circuit for C_{C2} alone

$$\begin{aligned}
 R_o &= R_E \parallel \left[\frac{r_\pi + (R_S \parallel R_B)}{1 + \beta} \right] \\
 &= 2.2k\Omega \parallel \left[\frac{3.051k\Omega + (1k\Omega \parallel 24k\Omega)}{101} \right] \\
 &= 2.2k\Omega \parallel \left[\frac{3.051k\Omega + \left(\frac{1k\Omega \times 24k\Omega}{1k\Omega + 24k\Omega} \right)}{101} \right] \\
 &= 2.2k\Omega \parallel \left[\frac{3.051k\Omega + 0.96k\Omega}{101} \right] \\
 &= 2.2k\Omega \parallel 0.04k\Omega \\
 &= \frac{2.2k\Omega \times 0.04k\Omega}{2.2k\Omega + 0.04k\Omega} = \mathbf{0.03k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 R_{eqCC2} &= R_o + R_L \\
 &= 0.03k\Omega + 8.2k\Omega = \mathbf{8.239k\Omega}
 \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C2} alone is,

$$\begin{aligned}
 f_{LCC1} &= \frac{1}{2\pi R_{eqCC2} C_{C2}} \\
 &= \frac{1}{2\pi \times 8.239k\Omega \times 0.1\mu F} = \mathbf{193.27Hz}
 \end{aligned}$$

Since, f_{LCC2} is the largest among f_{LCC1} and f_{LCC2} , it is the lower cut-off frequency of the overall circuit.

$$\therefore f_L = \mathbf{193.27Hz}$$

Mid-frequency AC equivalent circuit:

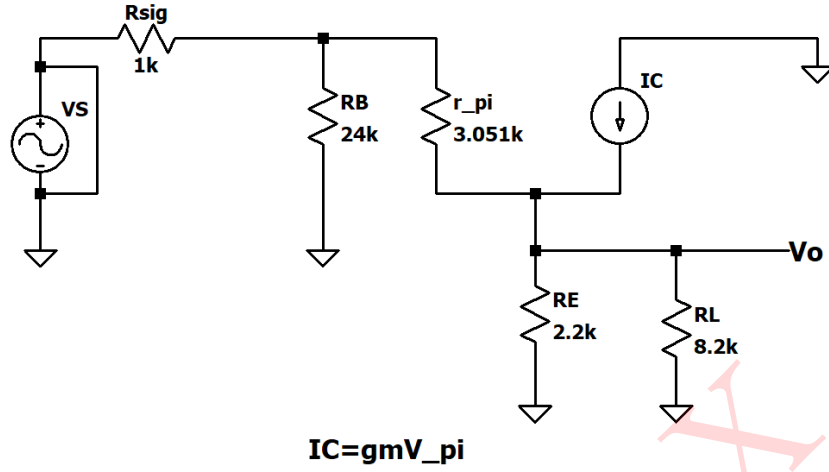


Figure 6: Mid-frequency AC equivalent circuit

Input impedance,

$$\begin{aligned}
 Z_i &= R_B \parallel [r_\pi + (1 + \beta)(R_E \parallel R_L)] \\
 &= 24k\Omega \parallel [3.051k\Omega + (101)(2.2k\Omega \parallel 8.2k\Omega)] \\
 &= 24k\Omega \parallel \left[3.051k\Omega + 101 \left(\frac{2.2k\Omega \times 8.2k\Omega}{2.2k\Omega + 8.2k\Omega} \right) \right] \\
 &= 24k\Omega \parallel [3.051k\Omega + 101(1.73k\Omega)] \\
 &= 24k\Omega \parallel [178.24k\Omega] \\
 &= \frac{24k\Omega \times 178.24k\Omega}{24k\Omega + 178.24k\Omega} = \mathbf{21.15k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 A_{V_{mid}} &= \frac{V_o}{V_{in}} \\
 &= \frac{(R_E \parallel R_L)}{\frac{1}{g_m} + (R_E \parallel R_L)} \\
 &= \frac{2.2k\Omega \parallel 8.2k\Omega}{\frac{1}{32.76mA/V} + (2.2k\Omega \parallel 8.2k\Omega)} \\
 &= \frac{\frac{2.2k\Omega \times 8.2k\Omega}{2.2k\Omega + 8.2k\Omega}}{0.03k\Omega + \left(\frac{2.2k\Omega \times 8.2k\Omega}{2.2k\Omega + 8.2k\Omega} \right)} \\
 &= \frac{1.73k\Omega}{0.03k\Omega + 1.73k\Omega} \\
 &= \frac{1.73k\Omega}{1.76k\Omega} = \mathbf{0.982}
 \end{aligned}$$

$$\begin{aligned}
A_{V_{S_{mid}}} &= \frac{V_o}{V_S} \\
&= \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_S} \\
&= A_V \times \frac{V_{in}}{V_S} \\
&= A_V \times \frac{Z_i}{Z_i + R_{sig}} \\
&= 0.982 \times \frac{21.15k\Omega}{21.15k\Omega + 1k\Omega} \\
&= 0.982 \times \frac{21.15k\Omega}{22.15k\Omega} = \mathbf{0.937}
\end{aligned}$$

$$\therefore A_{V_{S_{mid}}} \text{ in dB} = 20 \log_{10}(0.937) = \mathbf{-0.565 \text{ dB}}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

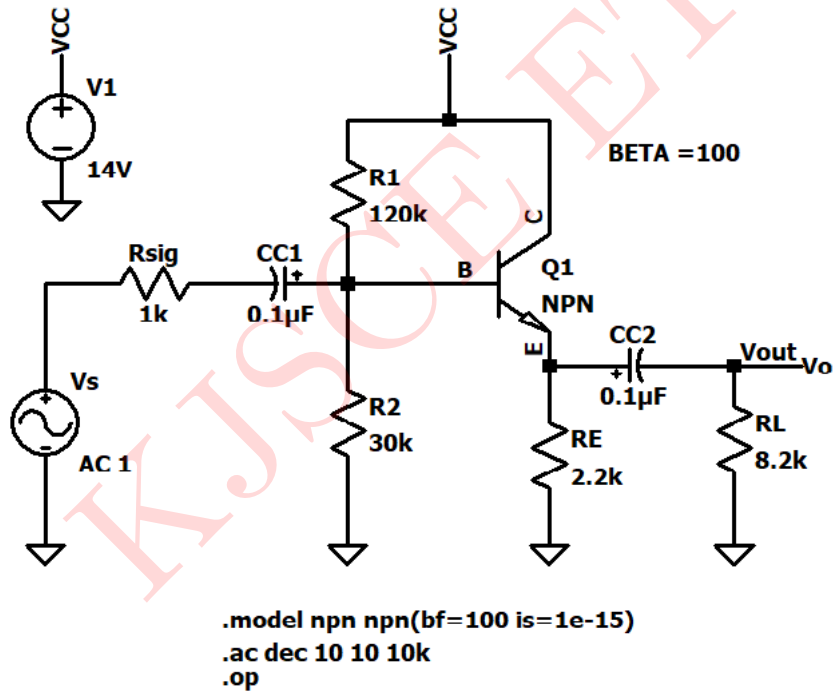


Figure 7: Circuit Schematic 1

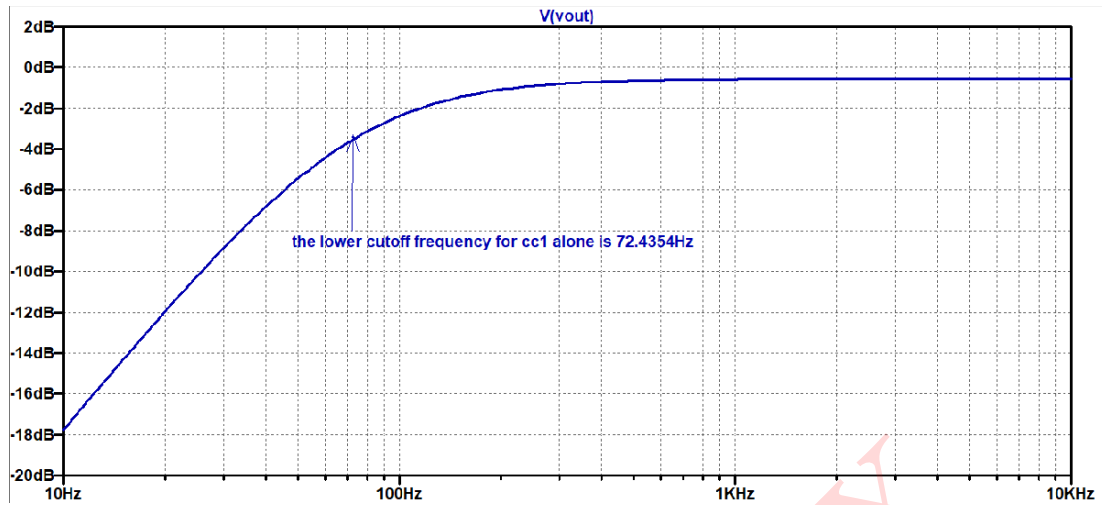


Figure 8: Lower frequency response for C_{C1}

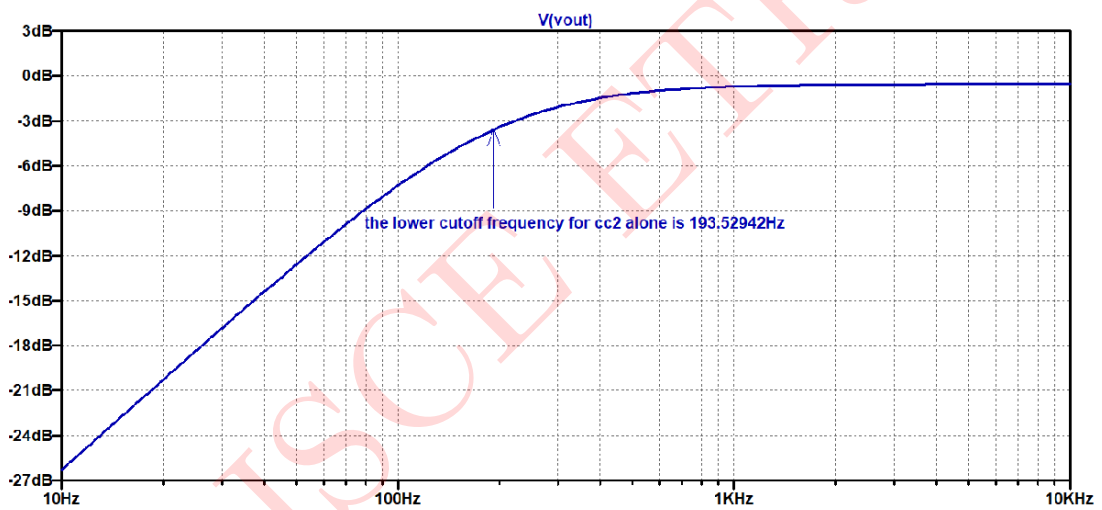


Figure 9: Lower frequency response for C_{C2}

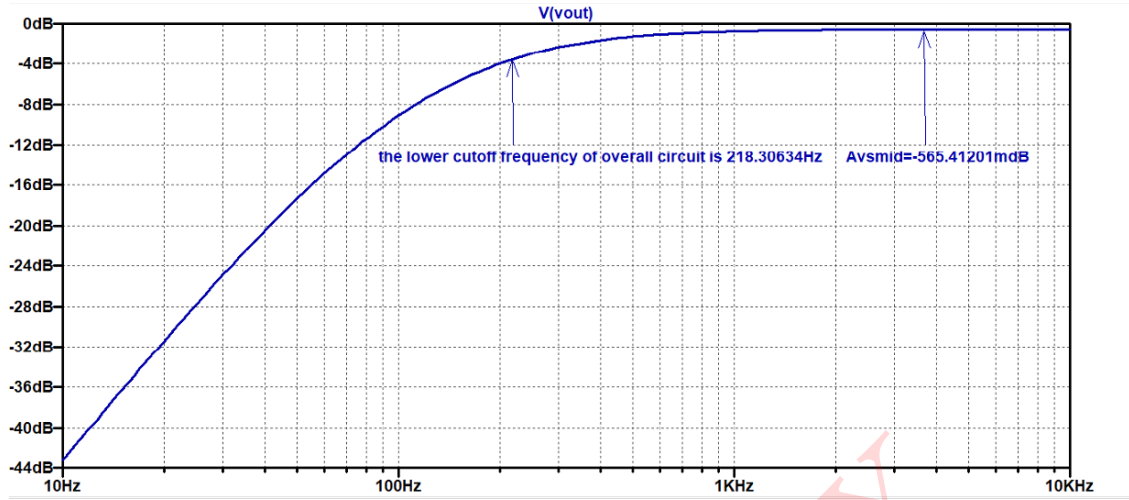


Figure 10: Lower frequency response for overall circuit

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_C	0.852mA	0.84874mA
Lower cut-off frequency due to C_{C1}	71.88Hz	72.435Hz
Lower cut-off frequency due to C_{C2}	193.27Hz	193.529Hz
Overall cut-off frequency f_L	193.27Hz	218.306Hz
Midband voltage gain $A_{V_{smid}}$	-0.565dB	-0.56541dB

Table 1: Numerical 1

Numerical 2:

For the circuit given below in figure 11,

- Determine V_{GSQ} and I_{DQ}
- Find g_{m_o} and g_m
- Calculate the midband gain of $A_V = V_o/V_i$
- Determine Z_i
- Calculate $A_V = V_o/V_s$
- Determine f_{LCC1} , f_{LCC2} and f_{LCS}
- Determine the low cut-off frequency

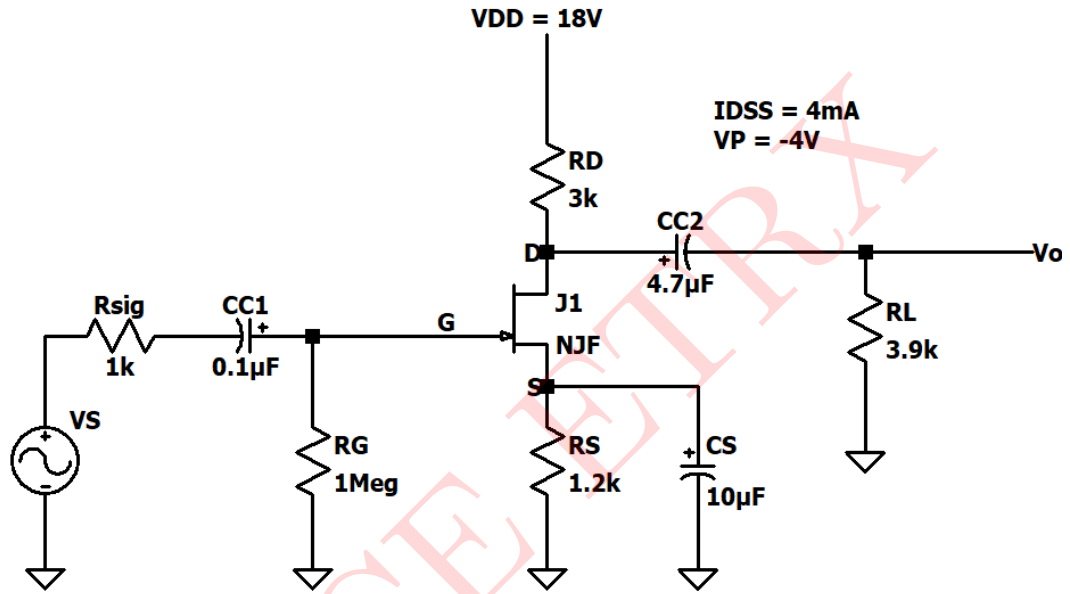


Figure 11: Circuit 2

Solution:

DC analysis:

Applying KVL in gate-source loop,

$$-I_g R_G - V_{GS} - I_D R_S = 0$$

$$0 - V_{GS} - I_D R_S = 0 \quad (\because I_g = 0, I_g R_G = 0)$$

$$\therefore V_{GS} = -I_D R_S \quad \dots(1)$$

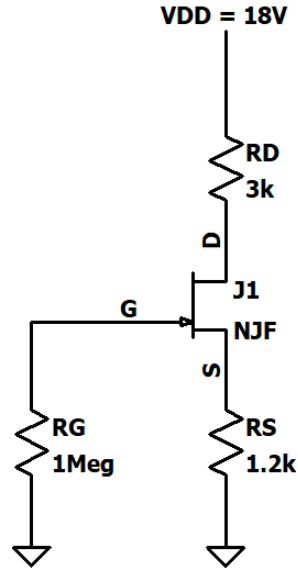


Figure 12: DC equivalent circuit

In JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Substituting this value of I_D in equation (1)

$$\therefore V_{GS} = I_D R_S$$

$$\therefore V_{GS} = -I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\therefore V_{GS} = -4mA(1.2k\Omega) \left(1 - \frac{V_{GS}}{-4} \right)^2$$

$$\therefore V_{GS} = -4.8 \left(1 + \frac{V_{GS}}{4} \right)^2$$

$$\therefore V_{GS} = -4.8 \left(1 + \frac{2V_{GS}}{4} + \frac{V_{GS}^2}{16} \right)$$

$$\therefore V_{GS} = -4.8 - 2.4V_{GS} - 0.3V_{GS}^2$$

$$\therefore 0 = -4.8 - 3.4V_{GS} - 0.3V_{GS}^2$$

$$\therefore V_{GS} = -1.65V \text{ or } V_{GS} = -9.68V$$

We reject the value $V_{GS} = -9.68V$ because $V_{GS} > V_P$

$$\therefore V_{GSQ} = -1.65V$$

$$\therefore I_D = I_{DSS} \left(1 - \frac{(-1.65)}{(-4)} \right)^2$$

$$= 4mA \left(1 - \frac{1.65}{4} \right)^2$$

$$= 4mA (0.5875)^2$$

$$\therefore I_{DQ} = 1.38mA$$

Small signal parameters:

$$\begin{aligned}
 \text{i) } g_m &= \left| \frac{2I_{DSS}}{V_P} \right| \left(1 - \frac{V_{GSQ}}{V_P} \right) \\
 &= \frac{1 \times 4mA}{4V} \left(1 - \frac{(-1.65V)}{(-4V)} \right) \\
 &= \frac{1 \times 4mA}{4V} \left(1 - \frac{1.65V}{4V} \right) \\
 &= \frac{1 \times 4mA}{4V} (0.5875) = 1.175mA/V
 \end{aligned}$$

$$r_d = 50k\Omega$$

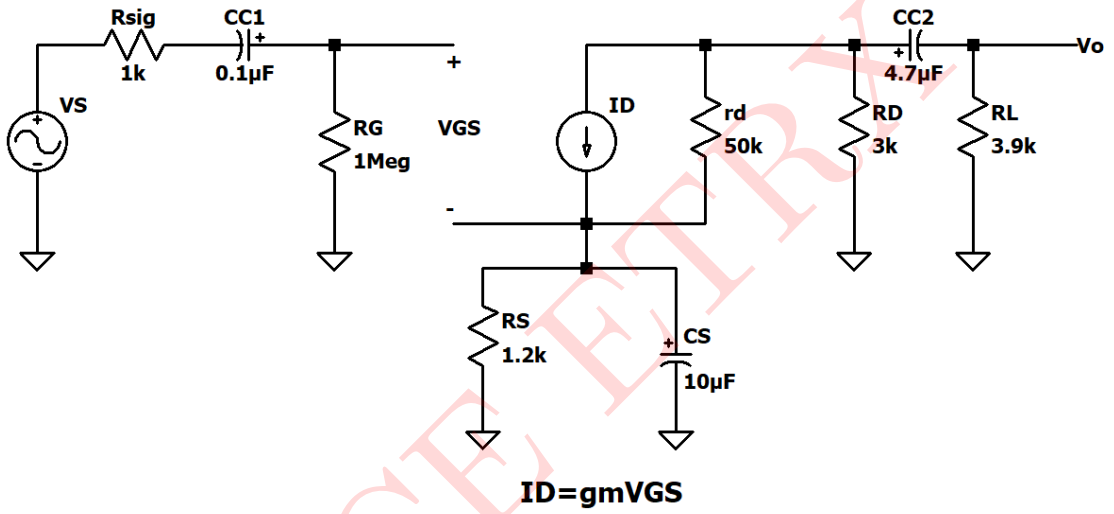


Figure 13: Low frequency AC equivalent circuit

For C_{C1} :

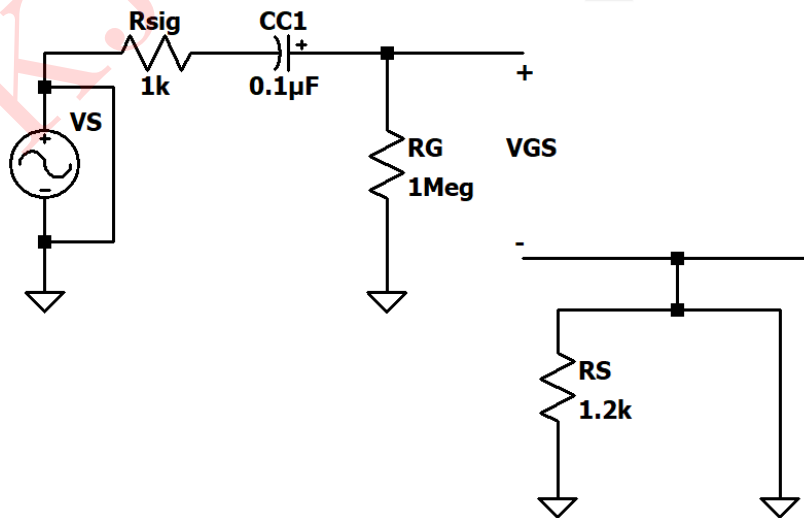


Figure 14: Small signal AC equivalent circuit for C_{C1} alone

$$R_i = R_G = 1\text{M}\Omega$$

$$\begin{aligned} R_{eq_{CC1}} &= R_i + R_{sig} \\ &= 1\text{M}\Omega + 1\text{k}\Omega = \mathbf{1001\text{k}\Omega} \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C1} alone is,

$$\begin{aligned} f_{L_{CC1}} &= \frac{1}{2\pi R_{eq_{CC1}} C_{C1}} \\ &= \frac{1}{2\pi \times 1001\text{k}\Omega \times 0.1\mu\text{F}} = \mathbf{1.59\text{Hz}} \end{aligned}$$

For C_{C2} :

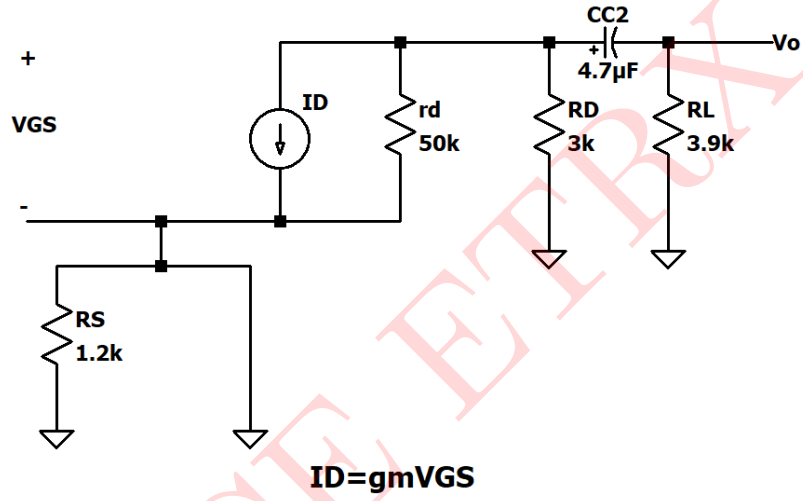


Figure 15: Small signal low frequency equivalent circuit for C_{C2} alone

$$\begin{aligned} R_o &= R_D \parallel r_d \\ &= 3\text{k}\Omega \parallel 50\text{k}\Omega \\ &= \frac{3\text{k}\Omega \times 50\text{k}\Omega}{3\text{k}\Omega + 50\text{k}\Omega} = \mathbf{2.83\text{k}\Omega} \end{aligned}$$

$$\begin{aligned} R_{eq_{CC2}} &= R_o + R_L \\ &= 2.83\text{k}\Omega + 3.9\text{k}\Omega = \mathbf{6.73\text{k}\Omega} \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C2} alone is,

$$\begin{aligned} f_{L_{CC2}} &= \frac{1}{2\pi R_{eq_{CC2}} C_{C2}} \\ &= \frac{1}{2\pi \times 6.73\text{k}\Omega \times 4.7\mu\text{F}} = \mathbf{5.03\text{Hz}} \end{aligned}$$

For C_S :

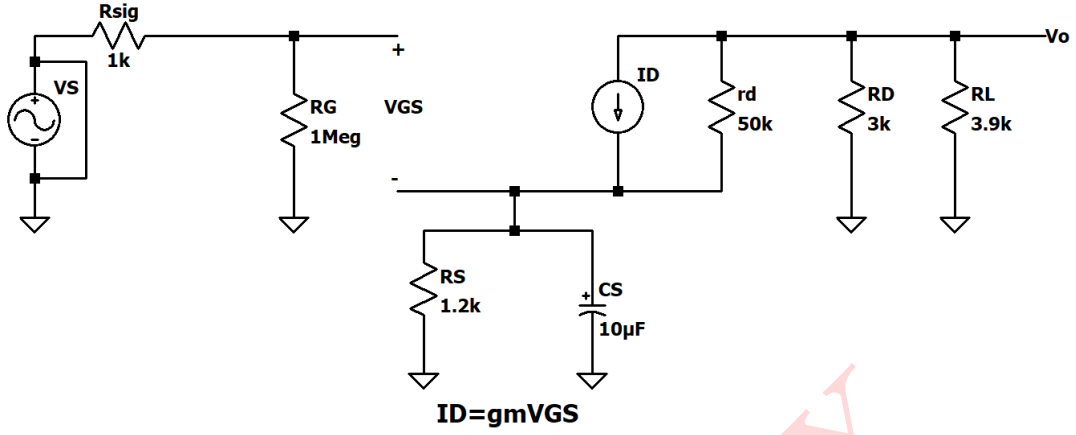


Figure 16: Small signal low frequency equivalent circuit for C_S alone

$$\begin{aligned}
 R_{eq_{CS}} &= \frac{R_S}{1 + \frac{R_S(1 + g_m r_d)}{(r_d + R_D \parallel R_L)}} \\
 &= \frac{1.2k\Omega}{1 + \frac{1.2(1 + (1.175mA/V \times 50k\Omega))}{(50k\Omega + (3k\Omega \parallel 3.9k\Omega))}} \\
 &= \frac{1.2k\Omega}{1 + \frac{1.2(59.75)}{\left(50k\Omega + \frac{3k\Omega \times 3.9k\Omega}{3k\Omega + 3.9k\Omega}\right)}} \\
 &= \frac{1.2k\Omega}{1 + \frac{71.7k\Omega}{51.69k\Omega}} \\
 &= \frac{1.2k\Omega}{1 + 1.38k\Omega} = \mathbf{0.504k\Omega}
 \end{aligned}$$

\therefore The lower cut-off frequency due to C_S alone is,

$$\begin{aligned}
 f_{LS} &= \frac{1}{2\pi R_{eq_{CS}} C_S} \\
 &= \frac{1}{2\pi \times 0.504k\Omega \times 10\mu F} = \mathbf{31.59Hz}
 \end{aligned}$$

Since $f_{L_{CS}}$ is the largest of $f_{L_{CC1}}$ and $f_{L_{CC2}}$, the lower cut-off frequency of the overall circuit(f_L) is 31.59Hz.

Mid-frequency AC equivalent circuit:

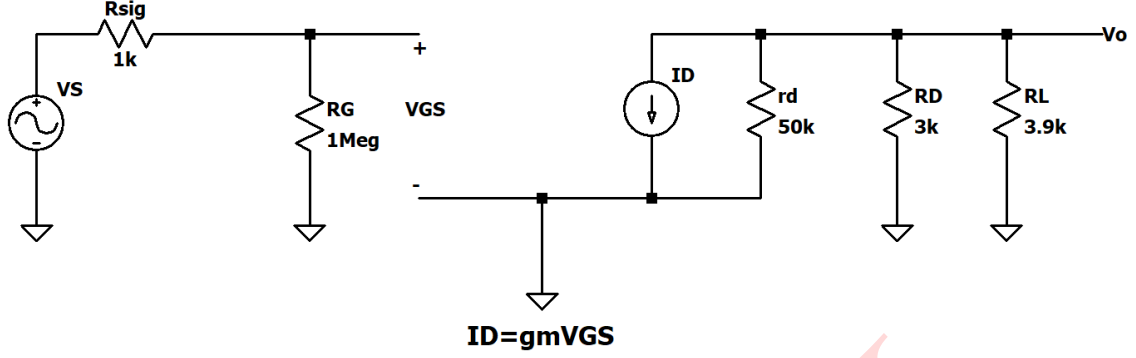


Figure 17: Mid-frequency AC equivalent circuit

$$\begin{aligned}
 A_{V_{mid}} &= \frac{V_o}{V_i} \\
 &= \frac{(-g_m V_{GS})(R_L \parallel R_D \parallel r_d)}{V_{GS}} \\
 &= -g_m(R_L \parallel R_D \parallel r_d) \\
 &= -1.175 \text{ mA/V} (3.9 \text{ k}\Omega \parallel 3 \text{ k}\Omega \parallel 50 \text{ k}\Omega) \\
 &= -1.175 \text{ mA/V} \left[3.9 \text{ k}\Omega \parallel \left(\frac{3 \text{ k}\Omega \times 50 \text{ k}\Omega}{3 \text{ k}\Omega + 50 \text{ k}\Omega} \right) \right] \\
 &= -1.175 \text{ mA/V} [3.9 \text{ k}\Omega \parallel 2.83 \text{ k}\Omega] \\
 &= -1.175 \text{ mA/V} \left(\frac{3 \text{ k}\Omega \times 50 \text{ k}\Omega}{3 \text{ k}\Omega + 50 \text{ k}\Omega} \right) \\
 &= -1.175 \text{ mA/V} \times 1.63 \text{ k}\Omega = -1.92
 \end{aligned}$$

Input impedance,

$$Z_i = R_G = 1 \text{ M}\Omega$$

$$\begin{aligned}
 A_{V_{S_{mid}}} &= \frac{V_o}{V_S} \\
 &= \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_S} \\
 &= A_V \times \frac{V_{in}}{V_S} \\
 &= A_V \times \frac{Z_i}{Z_i + R_{sig}} \\
 &= A_V \times \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 1 \text{ k}\Omega} \\
 &= -1.92 \times 0.99 = -1.91
 \end{aligned}$$

$$\therefore A_{V_{S_{mid}}} \text{ in dB} = 20 \log_{10}(1.91) = 5.62 \text{ dB}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

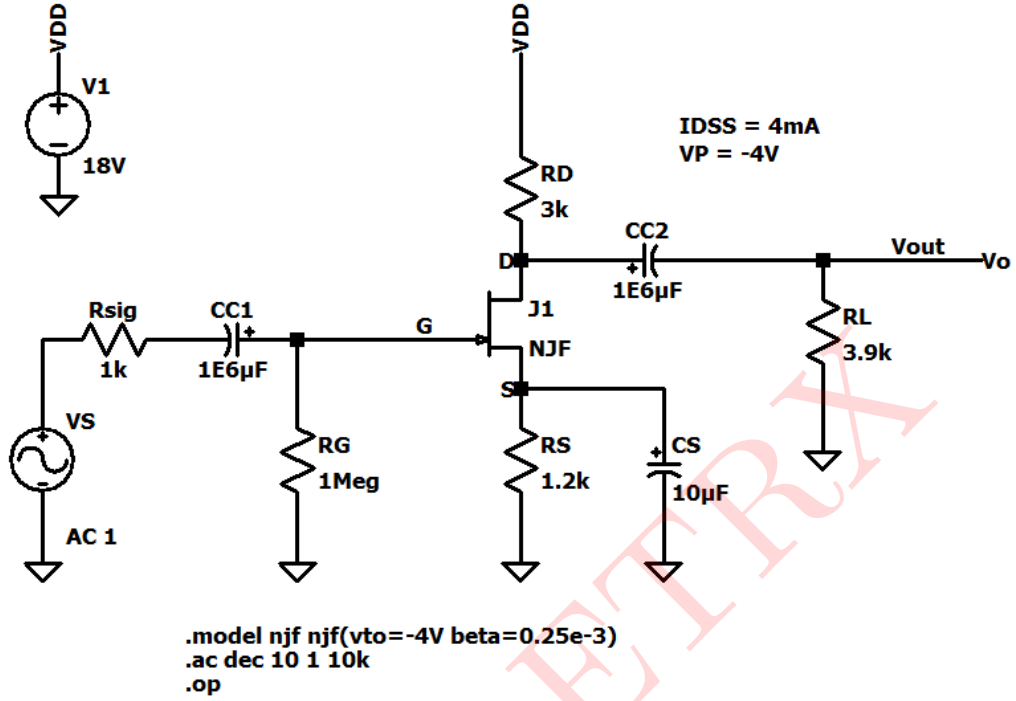


Figure 18: Circuit Schematic

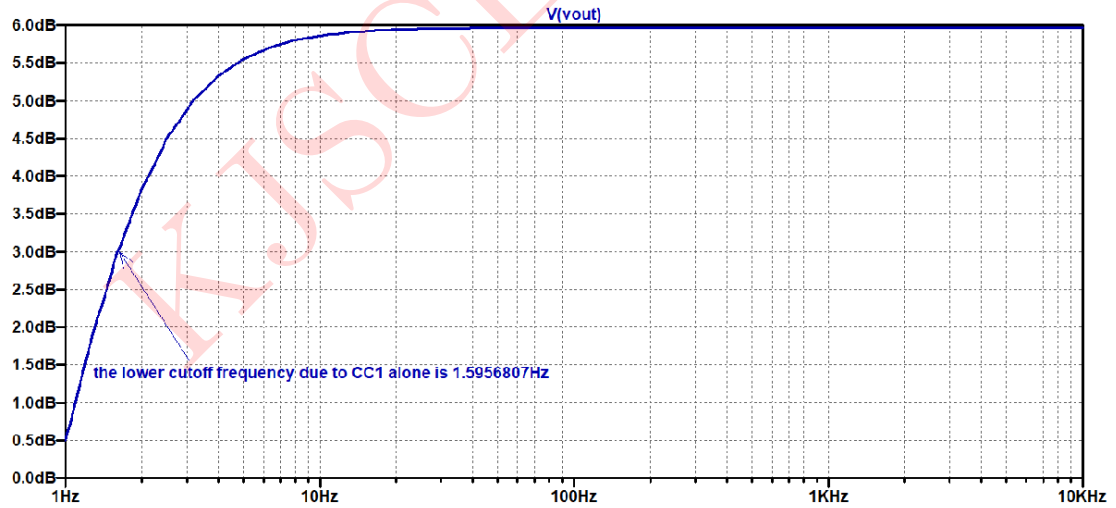


Figure 19: Lower frequency response for C_C

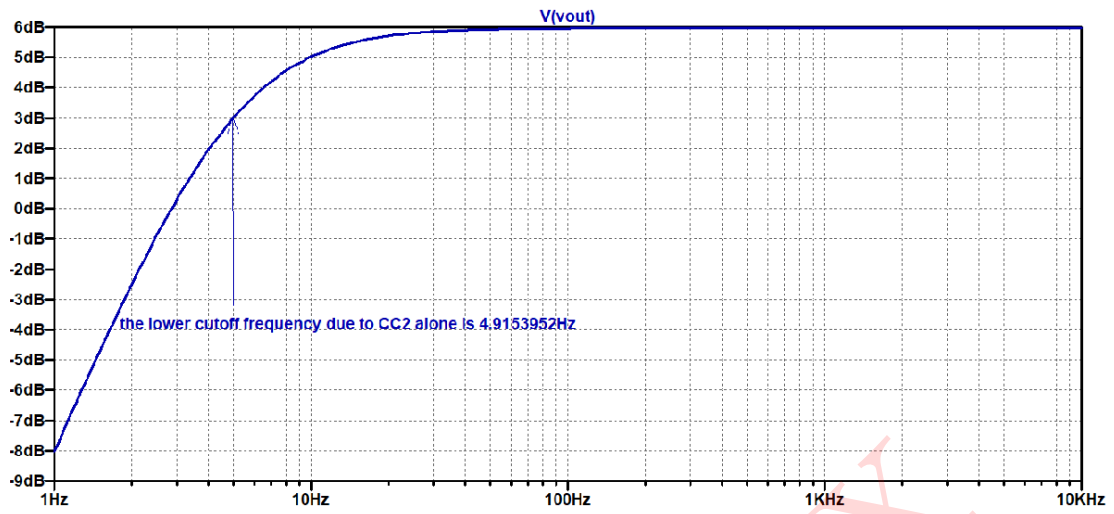


Figure 20: Lower frequency response for C_{C2}

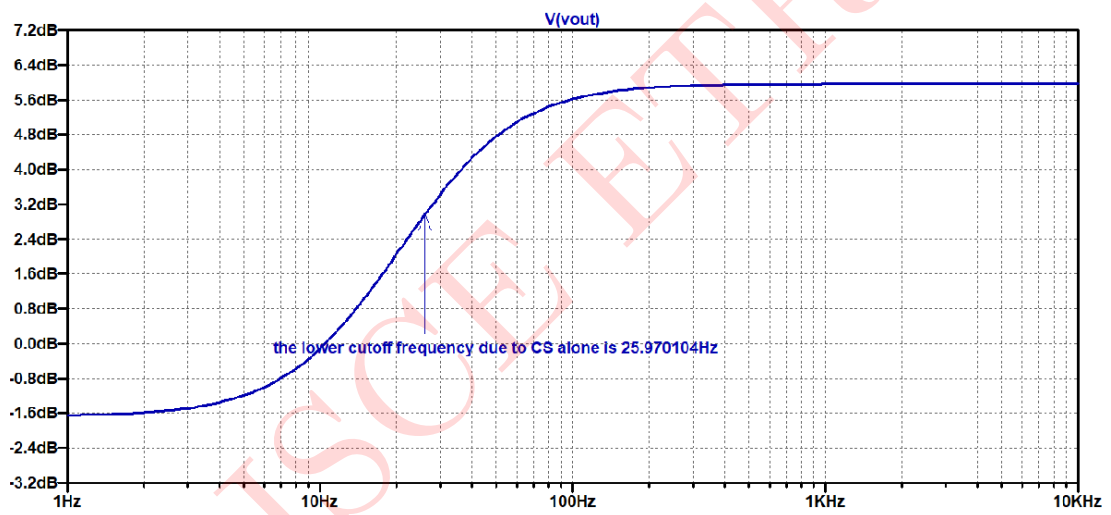


Figure 21: Lower frequency response for C_S

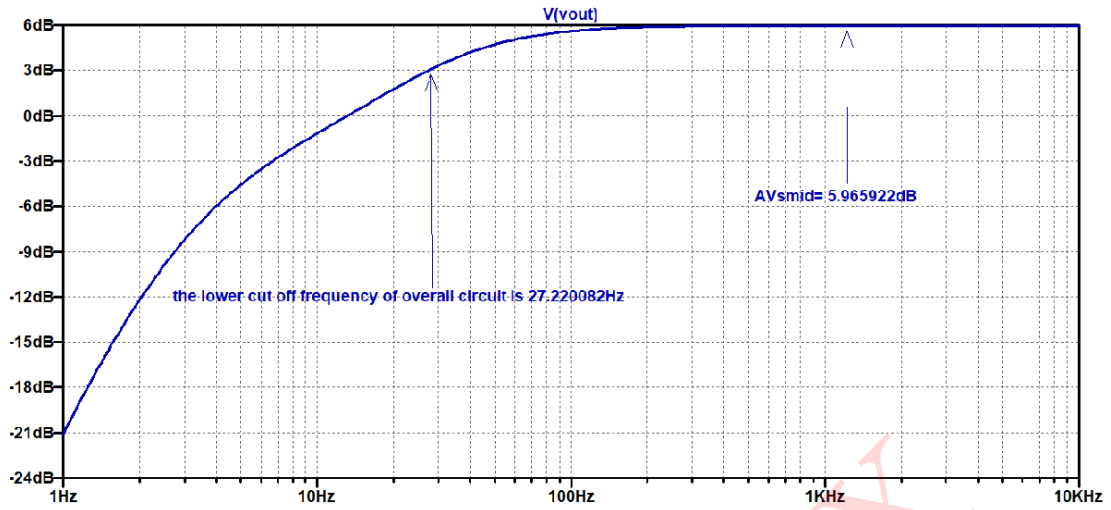


Figure 22: Lower frequency response for overall circuit

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_{DQ}	1.38mA	1.37mA
V_{GSQ}	-1.65V	-1.65281V
Lower cut-off frequency due to C_{C1}	1.59Hz	1.59568Hz
Lower cut-off frequency due to C_{C2}	5.03Hz	4.9153Hz
Overall cut-off frequency f_L	31.59Hz	27.2200Hz
Midband voltage gain $A_{V_{S_{mid}}}$ in dB	5.62dB	5.9659dB

Table 2: Numerical 2

Numerical 3:

For the network given below in figure 23,

- Determine V_{GSQ} and I_{DQ}
- Find g_{m_o} and g_m
- Calculate the midband gain of $A_V = V_o/V_i$
- Determine Z_i
- Calculate $A_V = V_o/V_s$
- Determine $f_{L_{CC1}}$, $f_{L_{CC2}}$ and $f_{L_{CS}}$
- Determine the low cut-off frequency
- Determine the higher cut-off frequency

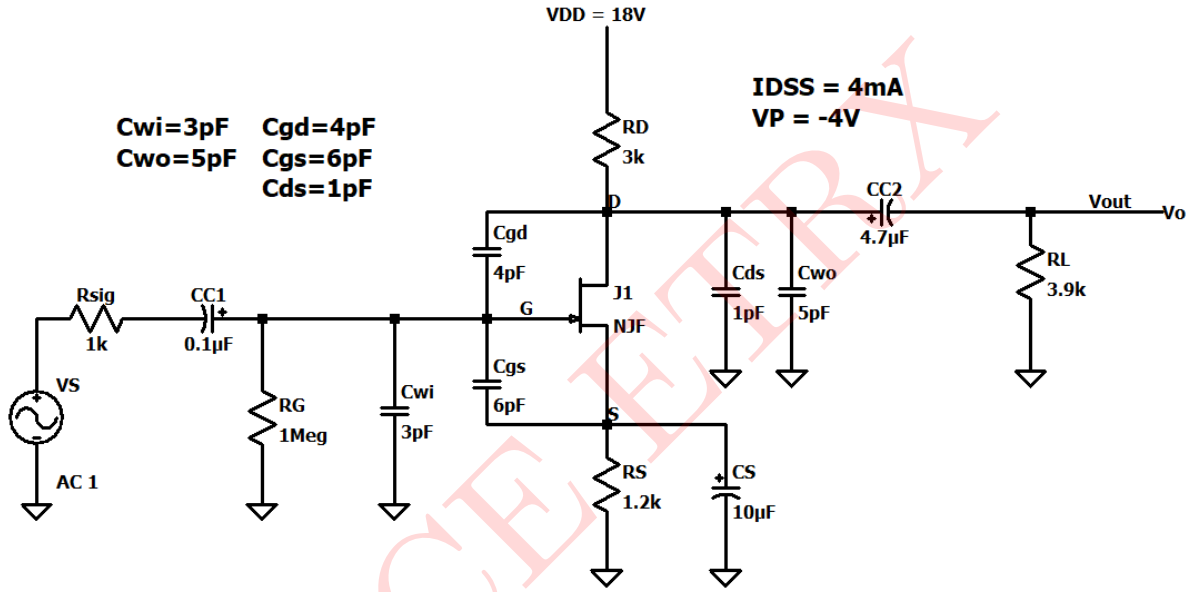


Figure 23: Circuit 3

Solution:

DC analysis:

Applying KVL in gate-source loop,

$$-I_g R_G - V_{GS} - I_D R_S = 0$$

$$0 - V_{GS} - I_D R_S = 0 \quad (\because I_g = 0, I_g R_G = 0)$$

$$\therefore V_{GS} = -I_D R_S \quad \dots(1)$$

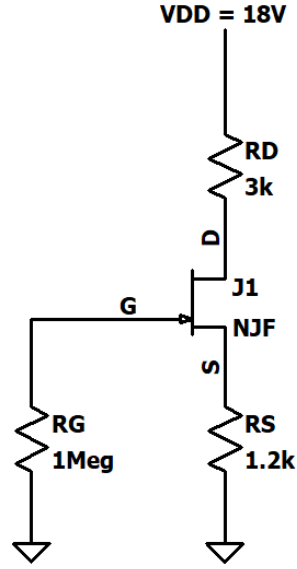


Figure 24: DC equivalent circuit

In JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Substituting this value of I_D in equation (1)

$$\therefore V_{GS} = I_D R_S$$

$$\therefore V_{GS} = -I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\therefore V_{GS} = -4mA(1.2k\Omega) \left(1 - \frac{V_{GS}}{-4} \right)^2$$

$$\therefore V_{GS} = -4.8 \left(1 + \frac{V_{GS}}{4} \right)^2$$

$$\therefore V_{GS} = -4.8 \left(1 + \frac{2V_{GS}}{4} + \frac{V_{GS}^2}{16} \right)$$

$$\therefore V_{GS} = -4.8 - 2.4V_{GS} - 0.3V_{GS}^2$$

$$\therefore 0 = -4.8 - 3.4V_{GS} - 0.3V_{GS}^2$$

$$\therefore V_{GS} = -1.65V \text{ or } V_{GS} = -9.68V$$

We reject the value $V_{GS} = -9.68V$ because $V_{GS} > V_P$

$$\therefore V_{GSQ} = -1.65V$$

$$\therefore I_D = I_{DSS} \left(1 - \frac{(-1.65)}{(-4)} \right)^2$$

$$= 4mA \left(1 - \frac{1.65}{4} \right)^2$$

$$= 4mA (0.5875)^2$$

$$\therefore I_{DQ} = 1.38mA$$

Small signal parameters:

$$\begin{aligned}
 \text{i) } g_m &= \left| \frac{2I_{DSS}}{V_P} \right| \left(1 - \frac{V_{GSQ}}{V_P} \right) \\
 &= \frac{1 \times 4mA}{4V} \left(1 - \frac{(-1.65V)}{(-4V)} \right) \\
 &= \frac{1 \times 4mA}{4V} \left(1 - \frac{1.65V}{4V} \right) \\
 &= \frac{1 \times 4mA}{4V} (0.5875) = 1.175mA/V
 \end{aligned}$$

$$r_d = 50k\Omega$$

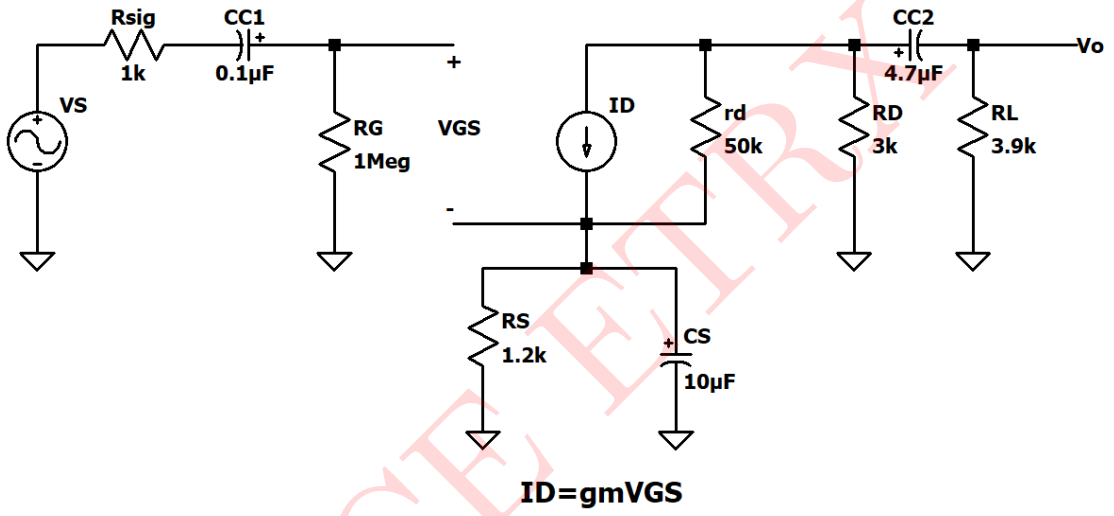


Figure 25: Low frequency AC equivalent circuit

For C_{C1} :

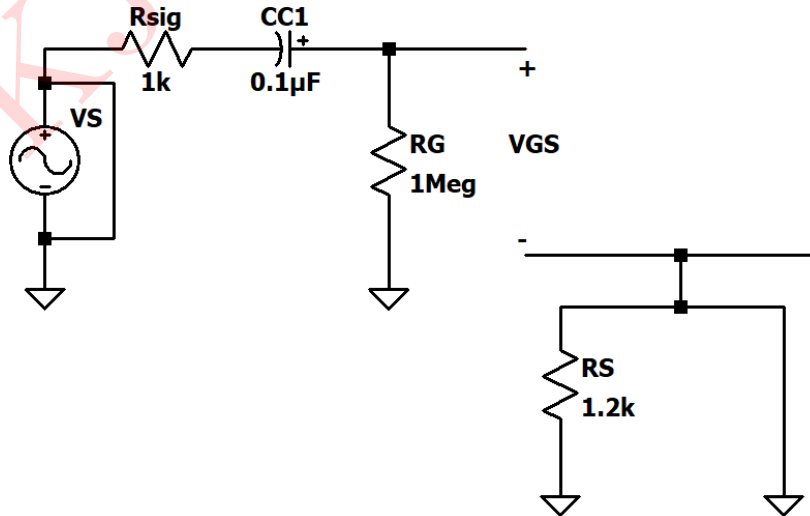


Figure 26: Small signal AC equivalent circuit for C_{C1} alone

$$R_i = R_G = 1\text{M}\Omega$$

$$\begin{aligned} R_{eq_{CC1}} &= R_i + R_{sig} \\ &= 1\text{M}\Omega + 1\text{k}\Omega = \mathbf{1001\text{k}\Omega} \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C1} alone is,

$$\begin{aligned} f_{L_{CC1}} &= \frac{1}{2\pi R_{eq_{CC1}} C_{C1}} \\ &= \frac{1}{2\pi \times 1001\text{k}\Omega \times 0.1\mu\text{F}} = \mathbf{1.59\text{Hz}} \end{aligned}$$

For C_{C2} :

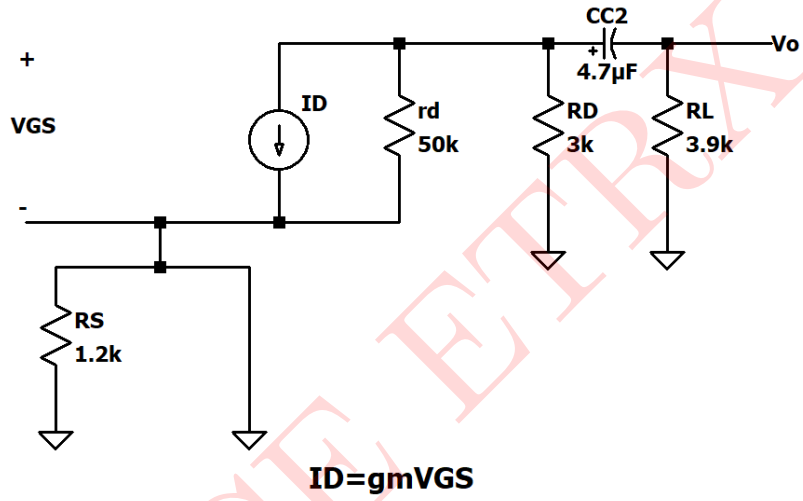


Figure 27: Small signal low frequency equivalent circuit for C_{C2} alone

$$\begin{aligned} R_o &= R_D \parallel r_d \\ &= 3\text{k}\Omega \parallel 50\text{k}\Omega \\ &= \frac{3\text{k}\Omega \times 50\text{k}\Omega}{3\text{k}\Omega + 50\text{k}\Omega} = \mathbf{2.83\text{k}\Omega} \end{aligned}$$

$$\begin{aligned} R_{eq_{CC2}} &= R_o + R_L \\ &= 2.83\text{k}\Omega + 3.9\text{k}\Omega = \mathbf{6.73\text{k}\Omega} \end{aligned}$$

\therefore The lower cut-off frequency due to C_{C2} alone is,

$$\begin{aligned} f_{L_{CC2}} &= \frac{1}{2\pi R_{eq_{CC2}} C_{C2}} \\ &= \frac{1}{2\pi \times 6.73\text{k}\Omega \times 4.7\mu\text{F}} = \mathbf{5.03\text{Hz}} \end{aligned}$$

For C_S :

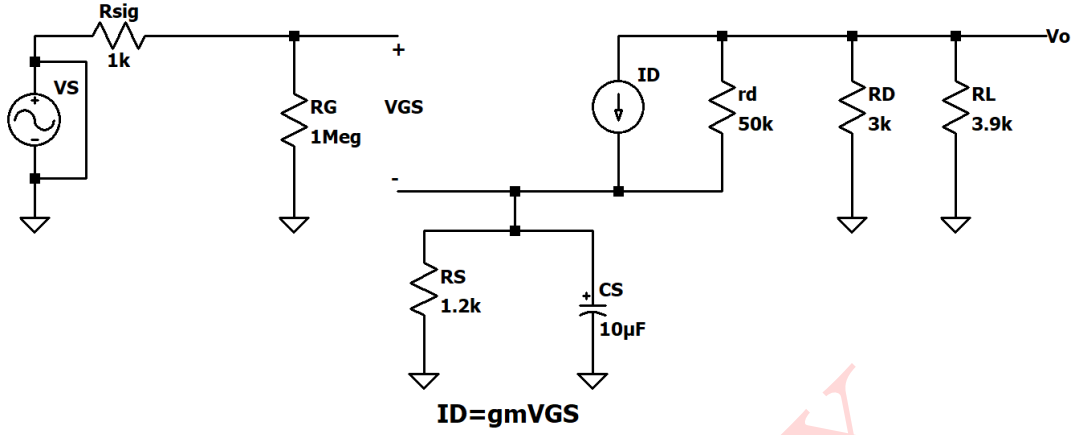


Figure 28: Small signal low frequency equivalent circuit for C_S alone

$$\begin{aligned}
 R_{eqCS} &= \frac{R_S}{1 + \frac{R_S(1 + g_m r_d)}{(r_d + R_D \parallel R_L)}} \\
 &= \frac{1.2k\Omega}{1 + \frac{1.2(1 + (1.175mA/V \times 50k\Omega))}{(50k\Omega + (3k\Omega \parallel 3.9k\Omega))}} \\
 &= \frac{1.2k\Omega}{1 + \frac{1.2(59.75)}{\left(50k\Omega + \frac{3k\Omega \times 3.9k\Omega}{3k\Omega + 3.9k\Omega}\right)}} \\
 &= \frac{1.2k\Omega}{1 + \frac{71.7k\Omega}{51.69k\Omega}} \\
 &= \frac{1.2k\Omega}{1 + 1.38k\Omega} = 0.504k\Omega
 \end{aligned}$$

\therefore The lower cut-off frequency due to C_S alone is,

$$\begin{aligned}
 f_{LCS} &= \frac{1}{2\pi R_{eqCS} C_S} \\
 &= \frac{1}{2\pi \times 0.504k\Omega \times 10\mu F} = 31.59Hz
 \end{aligned}$$

Since f_{LCS} is the largest of f_{LCC1} and f_{LCC2} , the lower cut-off frequency of the overall circuit(f_L) is 31.59Hz.

Mid-frequency AC equivalent circuit:

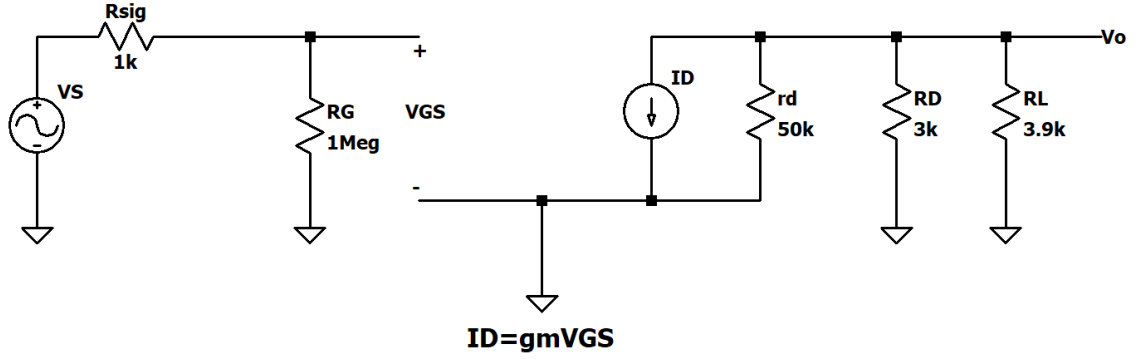


Figure 29: Mid-frequency AC equivalent circuit

$$\begin{aligned}
 A_{V_{mid}} &= \frac{V_o}{V_i} \\
 &= \frac{(-g_m V_{GS})(R_L \parallel R_D \parallel r_d)}{V_{GS}} \\
 &= -g_m(R_L \parallel R_D \parallel r_d) \\
 &= -1.175 \text{mA/V} (3.9 \text{k}\Omega \parallel 3 \text{k}\Omega \parallel 50 \text{k}\Omega) \\
 &= -1.175 \text{mA/V} \left[3.9 \text{k}\Omega \parallel \left(\frac{3 \text{k}\Omega \times 50 \text{k}\Omega}{3 \text{k}\Omega + 50 \text{k}\Omega} \right) \right] \\
 &= -1.175 \text{mA/V} [3.9 \text{k}\Omega \parallel 2.83 \text{k}\Omega] \\
 &= -1.175 \text{mA/V} \left(\frac{3 \text{k}\Omega \times 50 \text{k}\Omega}{3 \text{k}\Omega + 50 \text{k}\Omega} \right) \\
 &= -1.175 \text{mA/V} \times 1.63 \text{k}\Omega = -1.92
 \end{aligned}$$

Input impedance,

$$Z_i = R_G = 1 \text{M}\Omega$$

$$\begin{aligned}
 A_{V_{S_{mid}}} &= \frac{V_o}{V_S} \\
 &= \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_S} \\
 &= A_V \times \frac{V_{in}}{V_S} \\
 &= A_V \times \frac{Z_i}{Z_i + R_{sig}} \\
 &= A_V \times \frac{1 \text{M}\Omega}{1 \text{M}\Omega + 1 \text{k}\Omega} \\
 &= -1.92 \times 0.99 = -1.91
 \end{aligned}$$

$$\therefore A_{V_{S_{mid}}} \text{ in dB} = 20 \log_{10}(1.91) = 5.62 \text{dB}$$

High frequency equivalent circuit:

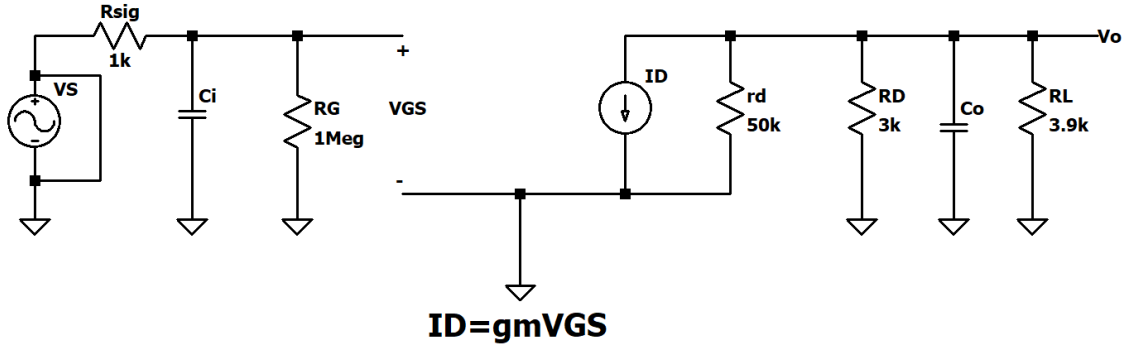


Figure 30: High frequency equivalent circuit

$$\begin{aligned}
 \text{i) } C_i &= C_{gs} + C_{mi} + C_{wi} \\
 \therefore C_{mi} &= C_{gd}(1 - A_{V_{S_{mid}}}) \\
 \therefore C_{mi} &= 4pF(1 - (-1.91)) \\
 \therefore C_{mi} &= 4pF(2.91) = \mathbf{11.64pF} \\
 \therefore C_i &= 6pF + 11.64pF + 3pF = \mathbf{20.64pF}
 \end{aligned}$$

$$\begin{aligned}
 \text{i) } C_o &= C_{wo} + C_{mo} + C_{ds} \\
 \therefore C_{mo} &= C_{gd} \left(1 - \frac{1}{A_{V_{S_{mid}}}} \right) \\
 \therefore C_{mo} &= 4pF \left(1 - \frac{1}{(-1.91)} \right) \\
 \therefore C_{mi} &= 4pF \left(1 + \frac{1}{1.91} \right) = \mathbf{6.09pf} \\
 \therefore C_o &= 5pF + 6.09pF + 1pF = \mathbf{12.09pF}
 \end{aligned}$$

For f_{H_i} ,

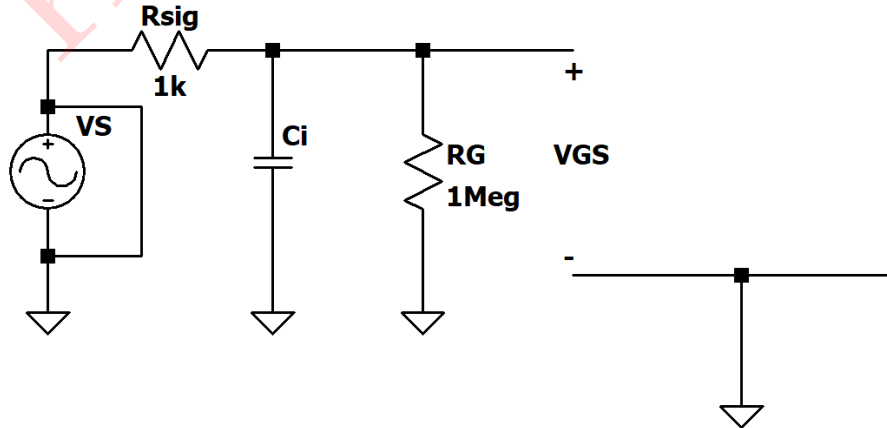


Figure 31: High frequency equivalent circuit for C_i

$$\begin{aligned}
R_{eq} &= R_{sig} \parallel R_G \\
&= 1k\Omega \parallel 1M\Omega \\
&= \frac{1k\Omega \times 1M\Omega}{1k\Omega + 1M\Omega} = \mathbf{0.99k\Omega}
\end{aligned}$$

$$\begin{aligned}
f_{H_i} &= \frac{1}{2\pi R_{eq} C_i} \\
&= \frac{1}{2\pi \times 0.99k\Omega \times 20.64pF} = \mathbf{7.79MHz}
\end{aligned}$$

For f_{H_o} ,

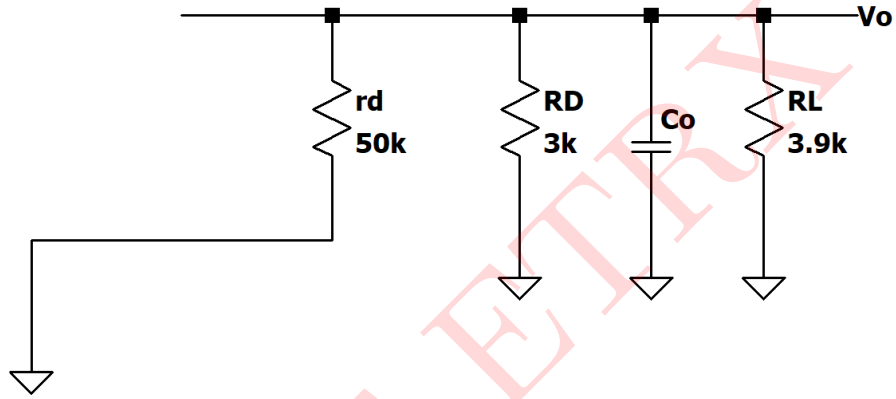


Figure 32: High frequency equivalent circuit for C_o

$$\begin{aligned}
R_{eq} &= R_d \parallel R_D \parallel R_L \\
&= 50k\Omega \parallel 3k\Omega \parallel 3.9k\Omega \\
&= 50k\Omega \parallel \left(\frac{3k\Omega \times 3.9k\Omega}{3k\Omega + 3.9k\Omega} \right) \\
&= 50k\Omega \parallel 1.69k\Omega \\
&= \frac{50k\Omega \times 1.69k\Omega}{50k\Omega + 1.69k\Omega} = \mathbf{1.63k\Omega}
\end{aligned}$$

$$\begin{aligned}
f_{H_o} &= \frac{1}{2\pi R_{eq} C_o} \\
&= \frac{1}{2\pi \times 1.63k\Omega \times 12.09pF} = \mathbf{8.08MHz}
\end{aligned}$$

$\therefore f_{H_i}$ is the lowest among f_{H_i} and f_{H_o} , the lower cut-off frequency of overall circuit(f_H) is 7.79Hz.

$$\therefore f_H = \mathbf{7.79MHz}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

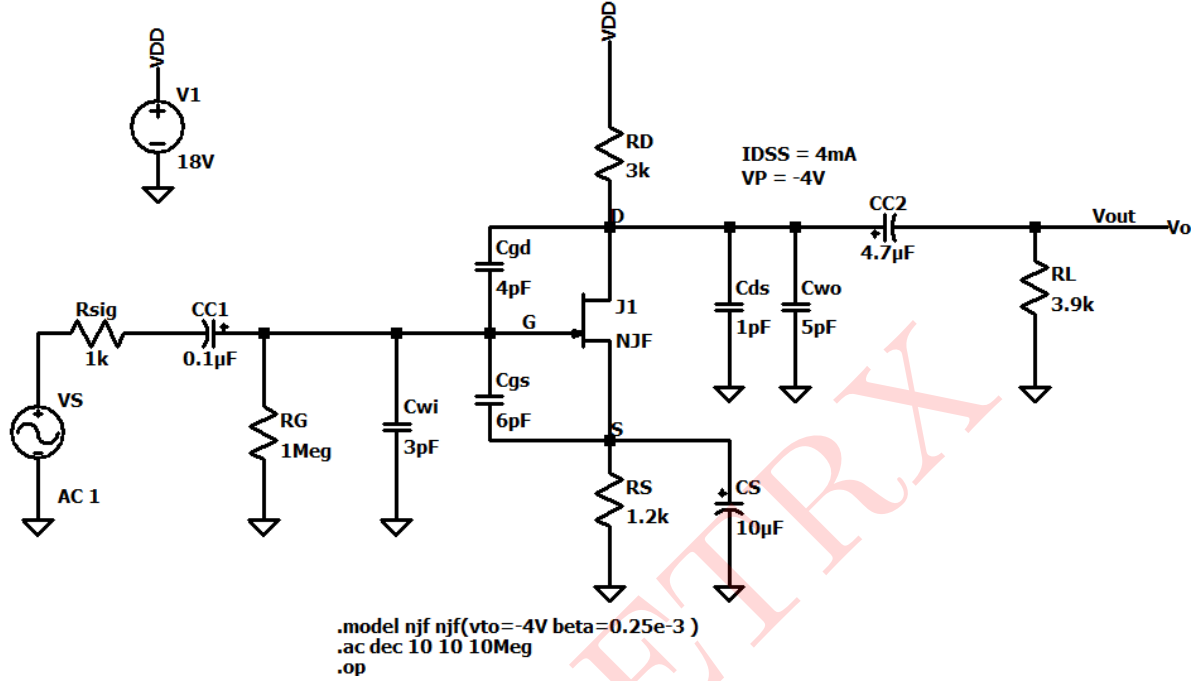


Figure 33: Circuit Schematic

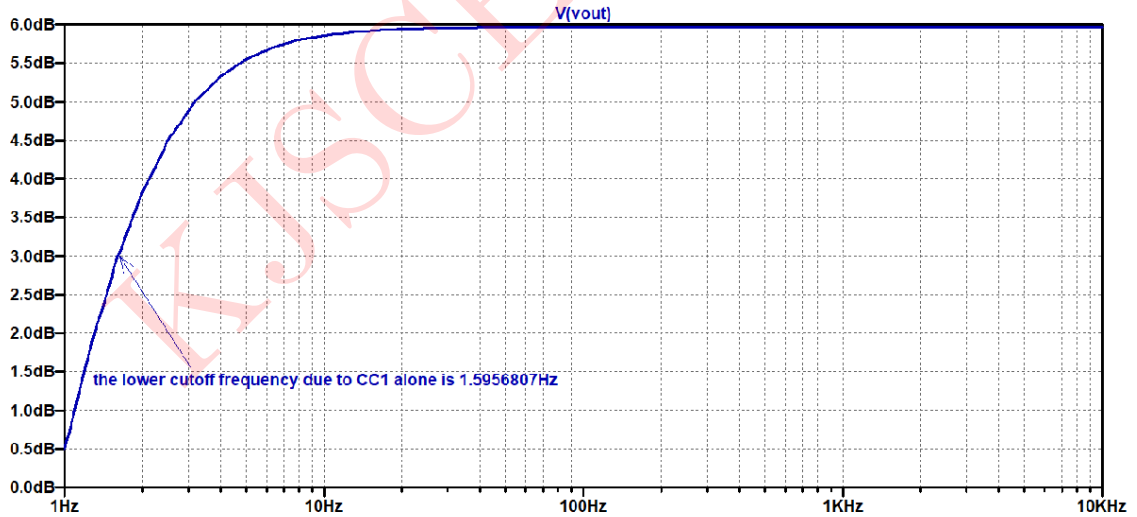


Figure 34: Lower frequency response for C_{C1}

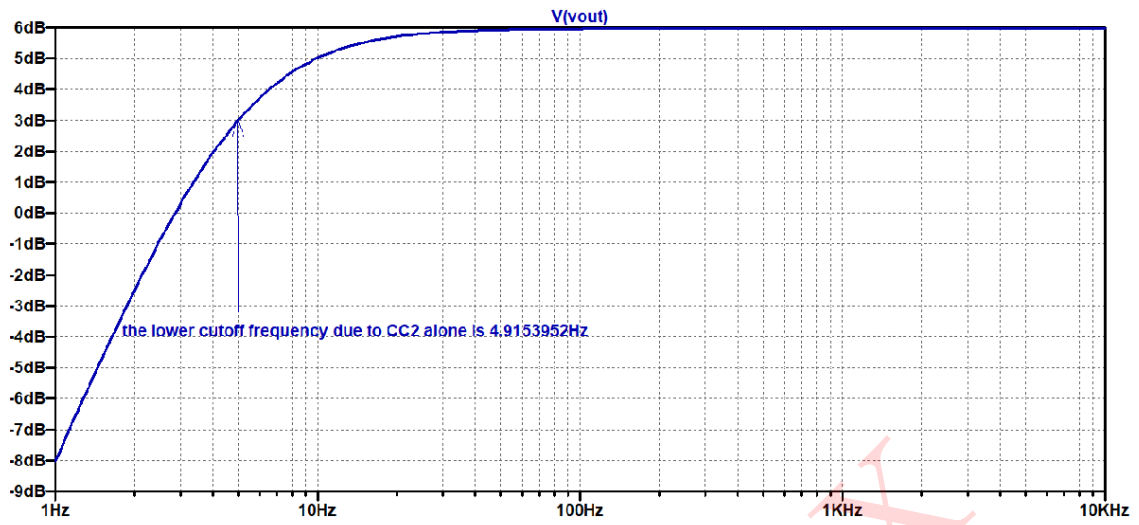


Figure 35: Lower frequency response for $CC2$

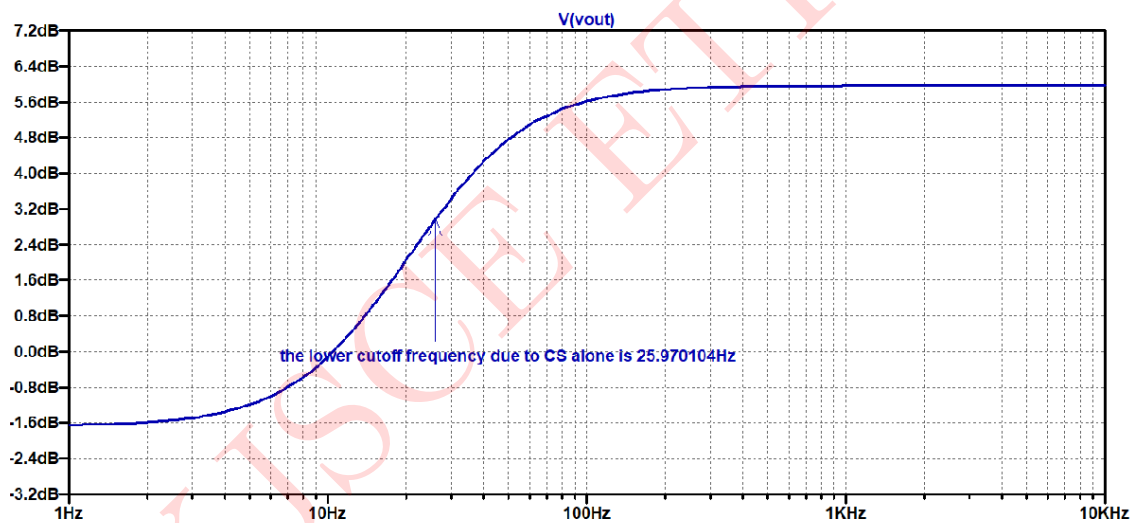


Figure 36: Lower frequency response for CS

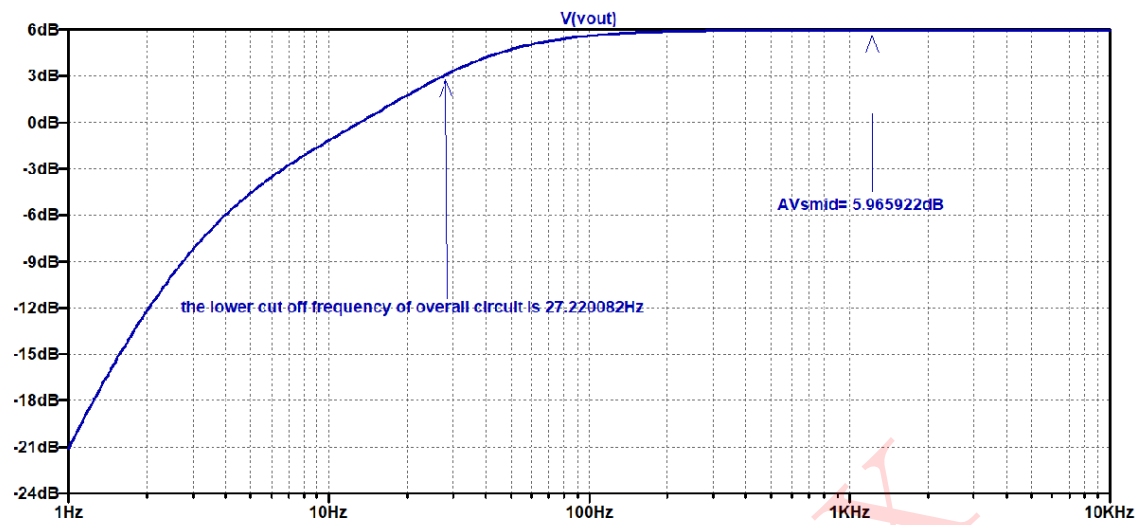


Figure 37: Lower frequency response for overall circuit

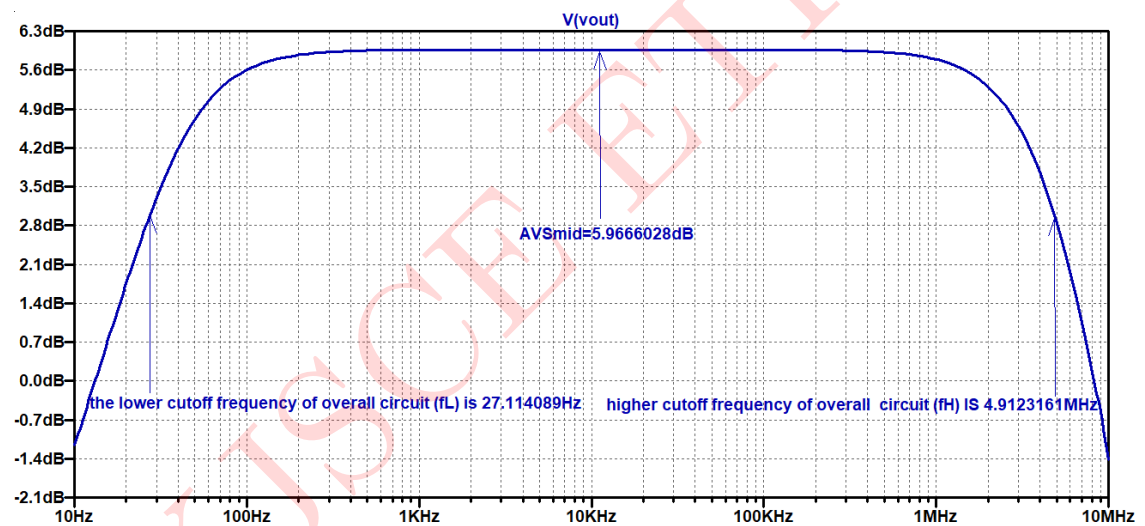


Figure 38: Higher frequency response for overall circuit

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_{DQ}	1.38mA	1.377mA
V_{GSQ}	-1.65V	-1.65281V
Lower cut-off frequency due to C_{C1}	1.59Hz	1.59568Hz
Lower cut-off frequency due to C_{C2}	5.03Hz	4.9153Hz
Overall cut-off frequency f_L	31.59Hz	27.2200Hz
Midband voltage gain $A_{V_{S_{mid}}}$ in dB	5.62dB	5.9659dB
Overall cut-off frequency f_H	7.79MHz	4.912MHz

Table 3: Numerical 3
