

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Cascode Amplifier**

12<sup>th</sup> July, 2020

Numericals

**Numerical 1:** A two stage circuit is shown in figure 1. Its BJT parameters are  $\beta_1 = \beta_2 = 200$  and  $V_{BE1} = V_{BE2} = 0.7$

- Calculate DC parameters i.e.  $V_{B1}$ ,  $V_{B2}$ ,  $V_{E1}$ ,  $V_{E2}$ ,  $V_{C1}$ ,  $V_{C2}$
- Calculate Input impedance of the circuit.
- Calculate output impedance of the circuit.
- Calculate voltage gain of the circuit.

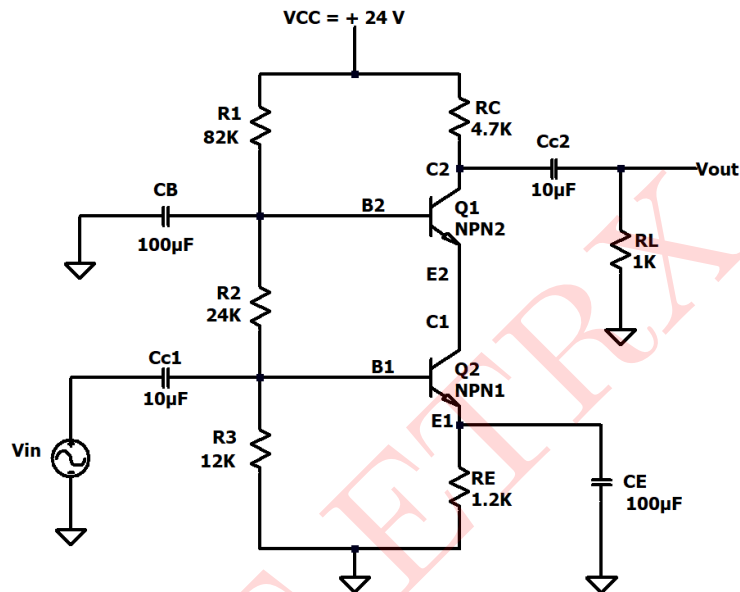


Figure 1: Circuit 1

**Solution:**

**DC ANALYSIS:**

$f = 0$ , thus  $X_C = \infty$ , So we replace each capacitor with short circuit,

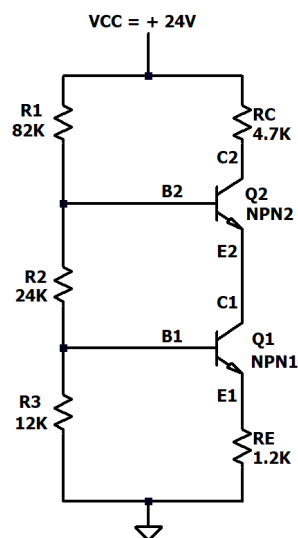


Figure 2: DC Equivalent Circuit

Assuming,  $I_{B1}$ ,  $I_{B2}$  are very small

$$\text{so, } I_{C1} = I_{C2} = I_{E1} = I_{E2}$$

$$\text{Now, } V_{B1} = \frac{R_3}{R_1 + R_2 + R_3} \times V_{CC} = \frac{12k}{82k + 24k + 12k} \times 24 = \mathbf{2.44V}$$

$$\text{And, } V_{B2} = \frac{R_2 + R_3}{R_2 + R_3 + R_1} \times V_{CC} = \frac{24k + 12k}{24k + 12k + 82k} \times 24 = \mathbf{7.322V}$$

$$V_{BE1} = V_{B1} - V_{E1}$$

$$V_{E1} = V_{B1} - V_{BE1} = 2.44 - 0.7 = \mathbf{1.74V}$$

$$V_{E1} = I_{E1} R_E$$

$$\therefore I_{E1} = \frac{1.74}{1.2 \times 10^3} = \mathbf{1.45mA}$$

$$I_{C1} = I_{C2} = I_{E1} = I_{E2} = \mathbf{1.45mA}$$

$$V_{C2} = V_{CC} - I_C R_C = 24 - (1.45 \times 10^{-3})(4.7 \times 10^3) = \mathbf{17.185V}$$

$$V_{E2} = V_{B2} - V_{BE2} = 7.322 - 0.7 = \mathbf{6.622V}$$

$$V_{E2} = V_{C1} = \mathbf{6.622V}$$

$$V_{CE1} = V_{C1} - V_{E1} = 6.622 - 1.74 = \mathbf{4.882V}$$

$$V_{CE2} = V_{C2} - V_{E2} = 17.185 - 6.622 = \mathbf{10.563V}$$

### Small Signal Parameters:

$$\text{Since } I_{CQ1} = I_{CQ2}$$

$$r_\pi = r_{\pi1} = r_{\pi2}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{200 \times 26 \times 10^{-3}}{1.45 \times 10^{-3}} = \mathbf{3.586k\Omega}$$

$$g_m = g_{m1} = g_{m2}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.45 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{55.76mA/V}$$

### Mid frequency AC equivalent circuit:

All the capacitors are replaced by short circuits and DC sources are replaced by open circuit.

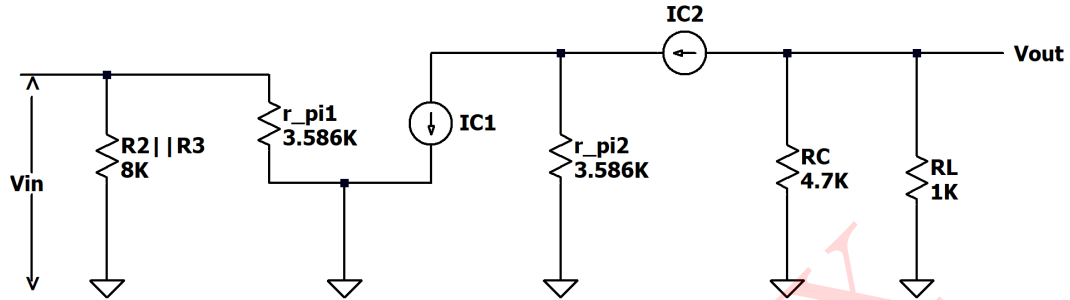


Figure 3: AC mid frequency Equivalent Circuit

### Input impedance:

$$Z_i = R_1 \parallel R_3 \parallel r_{\pi 1} = 24k \parallel 12k \parallel 3.589k = \mathbf{2.4760k\Omega}$$

### Output impedance:

$$Z_o = R_C \parallel R_L = 4.7k \parallel 1k = \mathbf{824.56\Omega}$$

### Finding out $A_{VT}$ :

$$A_{VT} = A_{V1} \times A_{V2}$$

Where,  $A_{V1}$  is the gain of CE stage and  $A_{V2}$  is the gain of CB stage

$$\text{Now, } A_{V1} = \frac{-g_m r_{\pi}}{1 + \beta} = \frac{-55.76 \times 10^{-3} \times 3.586 \times 10^3}{1 + 200} = \mathbf{-0.994}$$

$$\text{Also, } A_{V2} = g_m (R_C \parallel R_L) = 55.76 \times 10^{-3} (1k \parallel 4.7k) = \mathbf{45.977}$$

$$A_{VT} = A_{V1} \times A_{V2} = -0.994 \times 45.977 = \mathbf{-45.7}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

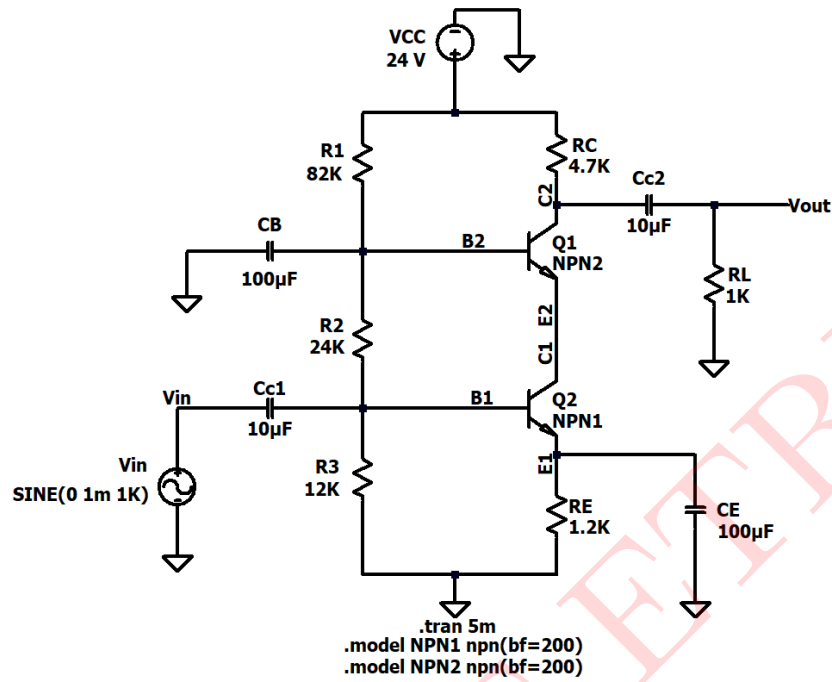


Figure 4: Circuit Schematic

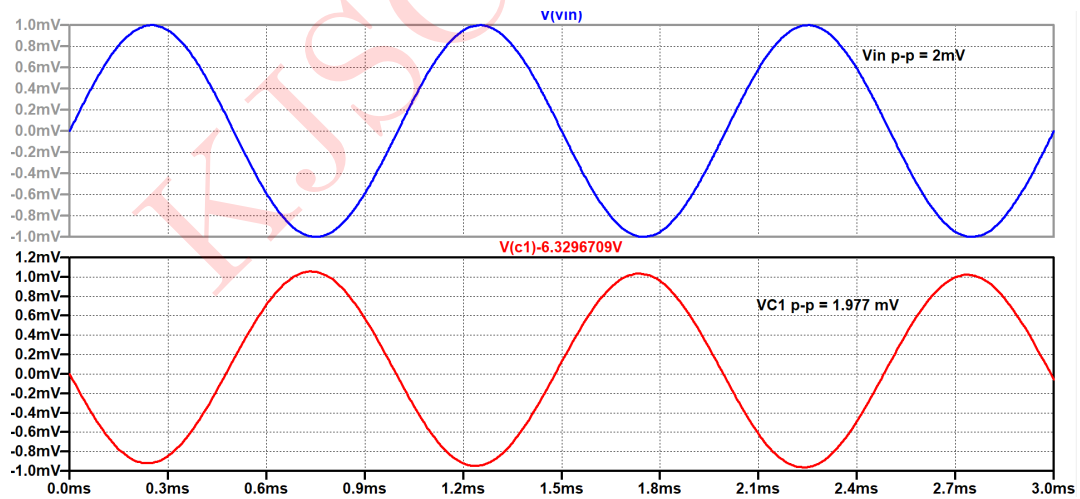


Figure 5: Input output waveform for stage 1

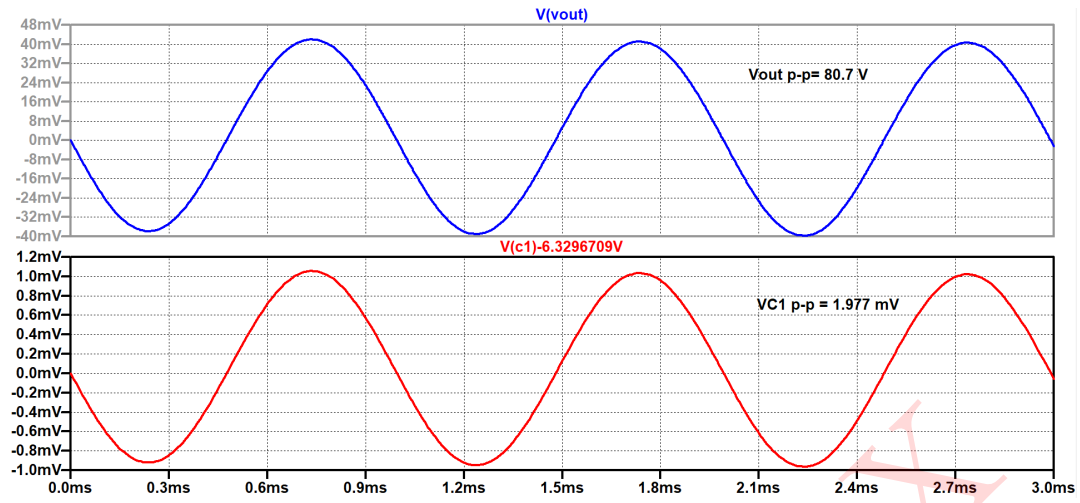


Figure 6: Input output waveform for stage 2

#### Comparison between Theoretical and Simulated values :-

Parameter	Theoretical	Simulated
$I_{C1}$	1.45mA	1.3mA
$I_{C2}$	1.45mA	1.3mA
$I_{E1}$	1.45mA	1.3mA
$I_{E2}$	1.45mA	1.3mA
$V_{C1}$	6.622V	6.33V
$V_{C2}$	17.185V	18.03V
$V_{E1}$	6.622V	6.33V
$V_{E2}$	3.736V	3.943V
$V_{B1}$	2.44V	2.319V
$V_{B2}$	7.322V	7.11V
$V_{CE1}$	4.882V	4.79V
$V_{CE2}$	10.563V	11.7V
voltage gain of first stage	-0.994	-0.9884
voltage gain of second stage	45.977	40.82
overall voltage gain	-45.7	-40.4
input impedance	2.476k $\Omega$	-
output impedance	824.56 $\Omega$	-

Table 1: Numerical 1

**Numerical 2 :** A two stage circuit is shown in figure 7. Its EMOS parameters are  $k_{n1} = k_{n2} = 1mA/V^2$  and  $V_{TN1} = V_{TN2} = 1V$

- Calculate DC parameters i.e.  $V_{G1}$ ,  $V_{G2}$ ,  $V_{GS1}$ ,  $V_{GS2}$ ,  $V_{D1}$ ,  $V_{D2}$ ,  $V_{S1}$ ,  $V_{DS1}$ ,  $V_{DS2}$ ,  $I_{D1}$ ,  $I_{D2}$
- Calculate input impedance of the circuit.
- Calculate output impedance of the circuit.
- Calculate voltage gain of the circuit.

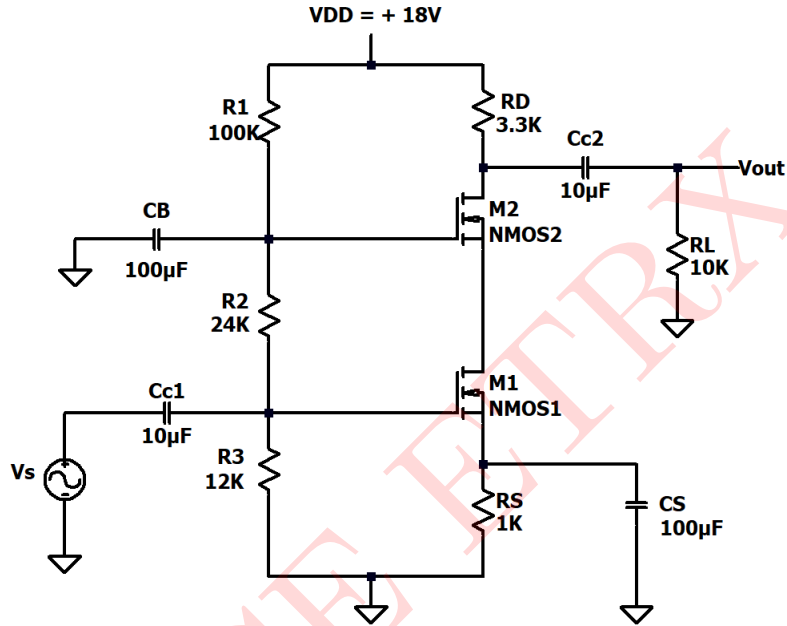


Figure 7: Circuit 2

**Solution:**

**DC ANALYSIS:**

$f = 0$ , thus  $X_C = \infty$ , So we replace each capacitor with short circuit,

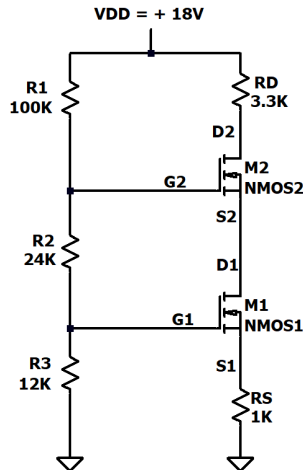


Figure 8: DC Equivalent Circuit

$$V_{G1} = \frac{R_3}{R_1 + R_2 + R_3} \times V_{DD} = \frac{12k}{100k + 24k + 12k} \times 18 = \mathbf{1.588V}$$

$$V_{G2} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \times V_{DD} = \frac{12k + 24k}{100k + 24k + 12k} \times 18 = \mathbf{4.764V}$$

$$V_{GS1} = V_{G1} - V_{S1} = 1.588 - I_{D1}R_S = 1.588 - 1000I_{D1} \quad \text{.....1}$$

$$I_{D1} = k_{n1}(V_{GS1} - V_{TN1})^2 = 1 \times 10^{-3}(V_{GS1} - 1)^2 \quad \text{.....2}$$

$$\therefore V_{GS1} = 1.588 - (V_{GS1} - 1)^2$$

$$V_{GS1} = 1.588 - (V_{GS1}^2 - 2V_{GS1} + 1)$$

$$\therefore V_{GS1}^2 - V_{GS1} - 0.588 = 0$$

$$\therefore V_{GS1} = -0.415V \text{ or } 1.415V$$

$$\text{But } V_{GS1} > V_D$$

$$\therefore V_{GS1} = 1.415V$$

$$I_{D1} = 1 \times 10^{-3}(1.415 - 1)^2 = (0.415)^2 \times 10^{-3} = \mathbf{0.172mA}$$

$$I_{D1} = I_{D2} = \mathbf{0.172mA}$$

$$V_{D2} = V_{DD} - I_{D2}R_D = 18 - (0.172 \times 10^{-3})(3.3 \times 10^3) = \mathbf{17.432V}$$

$$V_{S1} = I_{D1}R_S = \mathbf{0.172V}$$

$$V_{GS1} = V_{GS2} = \mathbf{1.415V}$$

$$\text{Now, } V_{GS2} = V_{G2} - V_{S2}$$

$$V_{S2} = V_{G2} - V_{GS2} = 4.764 - 1.415 = \mathbf{3.349V}$$

$$V_{DS2} = V_{D2} - V_{S2} = \mathbf{14.083V}$$

$$V_{D1} = V_{S2} = \mathbf{3.349V}$$

$$V_{DS1} = V_{D1} - V_{S1} = 3.349 - 0.172 = \mathbf{3.177V}$$

**Small Signal Parameters:**

$$g_{m1} = g_{m2} = 2k_n(V_{GS} - V_{TN}) = 2 \times 1 \times 10^{-3}(1.415 - 1) = \mathbf{0.83mA/V}$$

**Mid frequency AC equivalent circuit:**

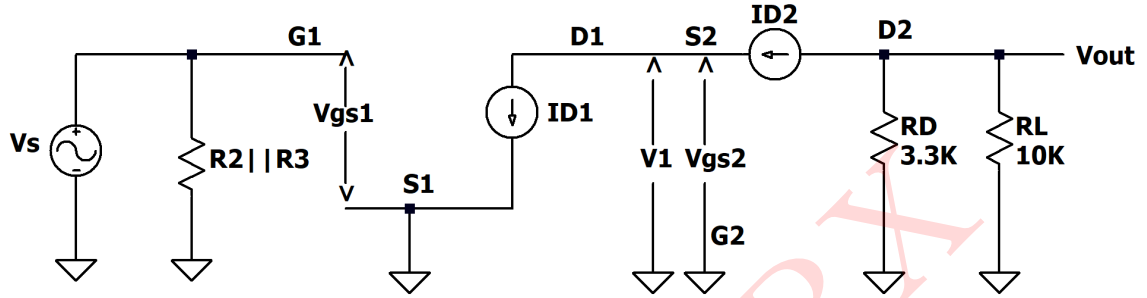


Figure 9: AC mid frequency Equivalent Circuit

Here,  $g_{m2}V_{gs2} = g_{m1}V_{gs1}$

$$R_G = R_2 \parallel R_3$$

**Input impedance:**

$$Z_i = R_G = R_2 \parallel R_3 = 24k \parallel 12k = \mathbf{8k\Omega}$$

**Output impedance:**

$$Z_o = R_D \parallel R_L = 3.3k \parallel 10k = \mathbf{2.481k\Omega}$$

**Finding out  $A_{VT}$ :**

$$A_{VT} = A_{V1} \times A_{V2}$$

$$\text{Now, } A_{V1} = \frac{V_1}{V_S} = \frac{-V_{gs2}}{V_{gs1}} = \mathbf{-1}$$

$$\text{Also, } A_{V2} = \frac{V_o}{V_1} = \frac{-g_m V_{gs2} R_D \parallel R_L}{-V_{gs2}} = g_m (R_D \parallel R_L) = 0.83 \times 10^{-3} (33k \parallel 10k) = \mathbf{2.059}$$

$$A_{VT} = A_{V1} \times A_{V2} = -1 \times 2.059 = \mathbf{-2.059}$$



### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

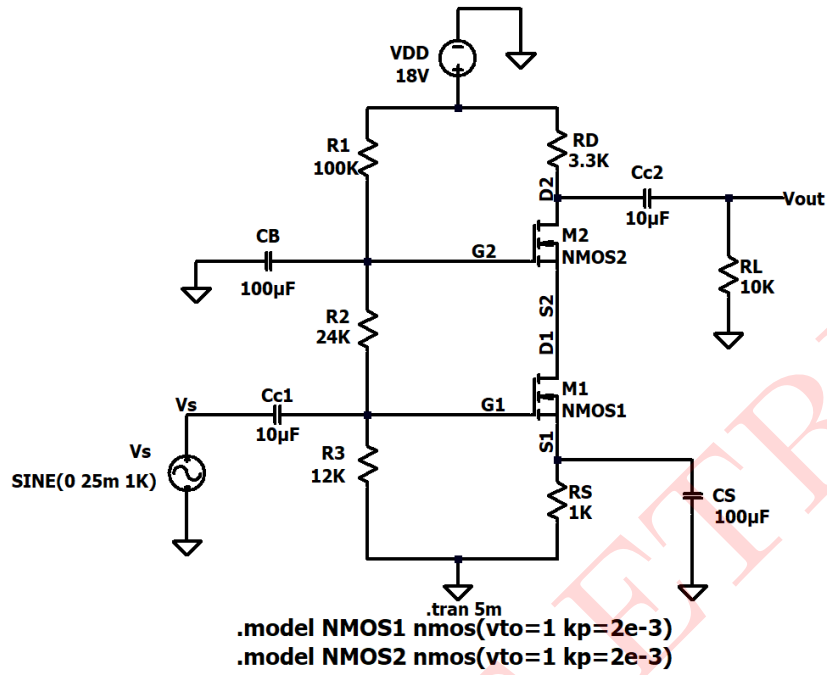


Figure 10: Circuit Schematic

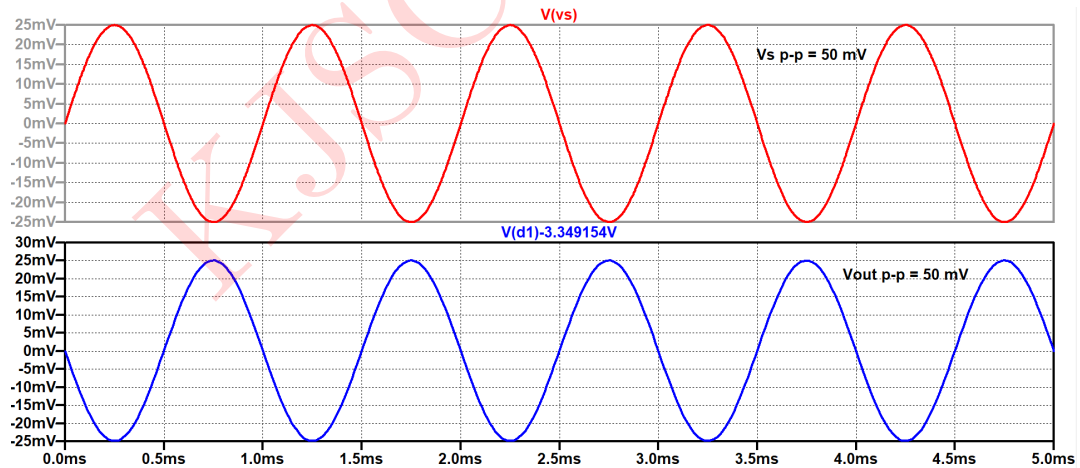


Figure 11: Input output waveform for stage 1

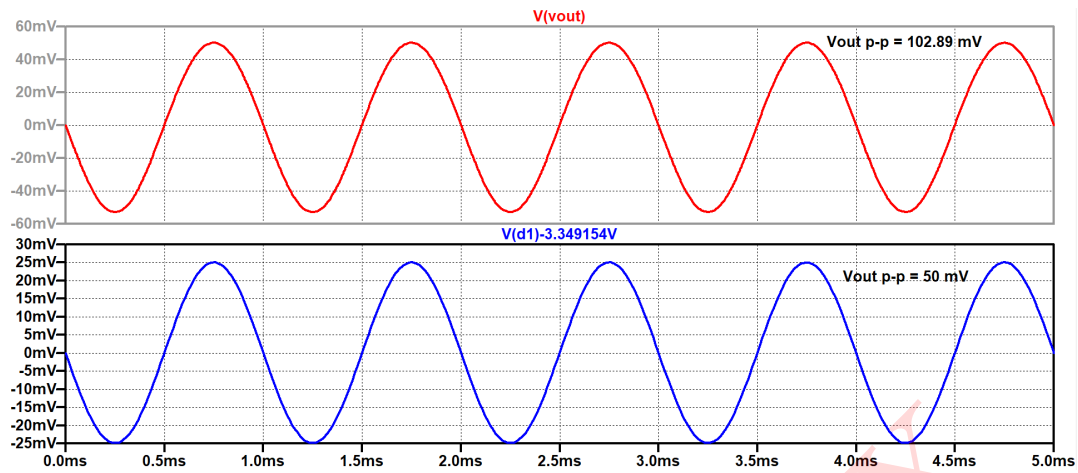


Figure 12: Input output waveform for stage 2

#### Comparison between Theoretical and Simulated values :-

Parameter	Theoretical	Simulated
$V_{G1}$	1.588V	1.588V
$V_{D1}$	3.349V	3.2V
$V_{S1}$	0.172V	0.0244V
$I_{D1}$	0.172mA	0.172mA
$V_{GS1}$	1.415V	1.415V
$V_{G2}$	4.764V	4.764V
$V_{D2}$	17.4324V	17.43V
$V_{S2}$	3.349V	3.2V
$I_{D2}$	0.172mA	0.172mA
$V_{GS2}$	1.415V	1.415V
voltage gain of first stage	-1	-1
voltage gain of second stage	2.059	2.058
overall voltage gain	-2.059	-2.058
input impedance	$8k\Omega$	—
output impedance	$2.481\Omega$	—

Table 2: Numerical 2

\*\*\*\*\*