

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascode Amplifier

Numerical 1: For the circuit shown in figure 1, Calculate 1st and 2nd stage DC parameters. Calculate voltage gain of 1st and 2nd stage and overall voltage gain in dB. Calculate input impedance, output impedance and output voltage.

Given: $\beta_1 = \beta_2 = 200$

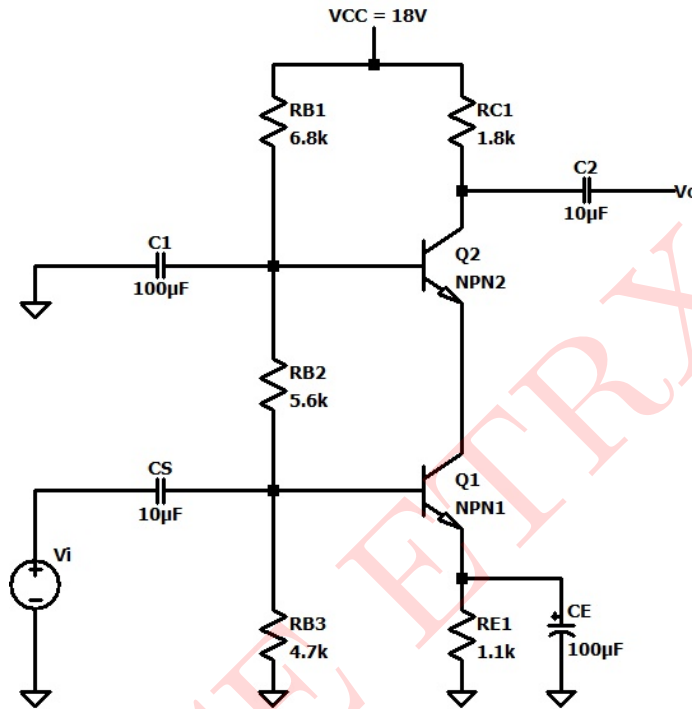


Figure 1: Circuit 1

Solution:

The given circuit 1 is a CE-CB cascade amplifier employing npn BJT.

For DC biasing, the capacitors acts as an open source.

DC Analysis:

$$V_{B1} = \frac{R_{B3}}{R_{B1} + R_{B2} + R_{B3}} V_{CC} \quad \dots(\text{Voltage divider})$$

$$V_{B1} = \frac{4.7 \times 10^3}{6.8 \times 10^3 + 5.6 \times 10^3 + 4.7 \times 10^3} \times 18 = \mathbf{4.947 \text{ V}}$$

$$V_{B2} = \frac{R_{B2} + R_{B3}}{R_{B1} + R_{B2} + R_{B3}} V_{CC} \quad \dots(\text{Voltage divider})$$

$$V_{B2} = \frac{5.6 \times 10^3 + 4.7 \times 10^3}{6.8 \times 10^3 + 5.6 \times 10^3 + 4.7 \times 10^3} \times 18 = \mathbf{10.842 \text{ V}}$$

 


Figure 2: DC Equivalent circuit

Voltage across terminal E_1 can be given as,

$$V_{E_1} = V_{B_1} - V_{BE_1}$$

$$V_{E_1} = 4.947 - 0.7 = \mathbf{4.247 \text{ V}}$$

$$V_{E_2} = V_{B_2} - V_{BE_2}$$

$$V_{E_2} = 10.842 - 0.7 = \mathbf{10.142 \text{ V}}$$

V_{E_2} and V_{C_1} are connected to each other, so voltages are equal

$$V_{C_1} = V_{E_2} = \mathbf{10.142 \text{ V}}$$

$$I_{E_1} = \frac{V_{E_1}}{R_{E_1}}$$

$$I_{E_1} = \frac{4.947}{1.1} = \mathbf{3.86 \text{ mA}}$$

$$I_{B_1} = \frac{I_{E_1}}{1 + \beta_1}$$

$$I_{B_1} = \frac{3.86 \times 10^{-3}}{1 + 200} = \mathbf{19.2 \mu A}$$

$$I_{C_1} = \beta_1 I_{B_1}$$

$$I_{C_1} = 200 \times 19.2 \times 10^{-6} = \mathbf{3.84 \text{ mA}}$$

Terminal C_1 and terminal E_2 are connected together, so the current flowing through then will be same.

$$I_{E_2} = I_{C_1} = \mathbf{3.84 \text{ mA}}$$

$$I_{B_2} = \frac{I_{E_1}}{1 + \beta_1}$$

$$I_{B_2} = \frac{3.84 \times 10^{-3}}{1 + 200} = \mathbf{19.1 \text{ } \mu\text{A}}$$

$$I_{C_2} = \beta I_{B_2}$$

$$I_{C_2} = 200 \times 19.1 \times 10^{-6} = \mathbf{3.82 \text{ mA}}$$

Voltage across terminal C_2 is given as,

$$V_{C_2} = V_{CC} - I_{C_2} R_{C_2}$$

$$V_{C_2} = 18 - 3.82 \times 10^{-3} \times 1.8 \times 10^3 = \mathbf{11.124 \text{ V}}$$

AC Analysis:

Small signal parameters:

$$r_{\pi_1} = \frac{\beta_1 V_T}{I_{E_1}}$$

$$r_{\pi_1} = \frac{200 \times 26 \times 10^{-3}}{3.86 \times 10^{-3}} = \mathbf{1.347 \text{ k}\Omega}$$

$$r_{\pi_2} = \frac{\beta_2 V_T}{I_{E_2}}$$

$$r_{\pi_2} = \frac{200 \times 26 \times 10^{-3}}{3.84 \times 10^{-3}} = \mathbf{1.354 \text{ k}\Omega}$$

$$g_{m_1} = \frac{I_{C_1}}{V_T}$$

$$g_{m_1} = \frac{3.84 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{147.69 \text{ mA/V}}$$

$$g_{m_2} = \frac{I_{C_2}}{V_T}$$

$$g_m = \frac{3.82 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{146.92 \text{ mA/V}}$$

Small Signal Equivalent Circuit is shown in figure 4:

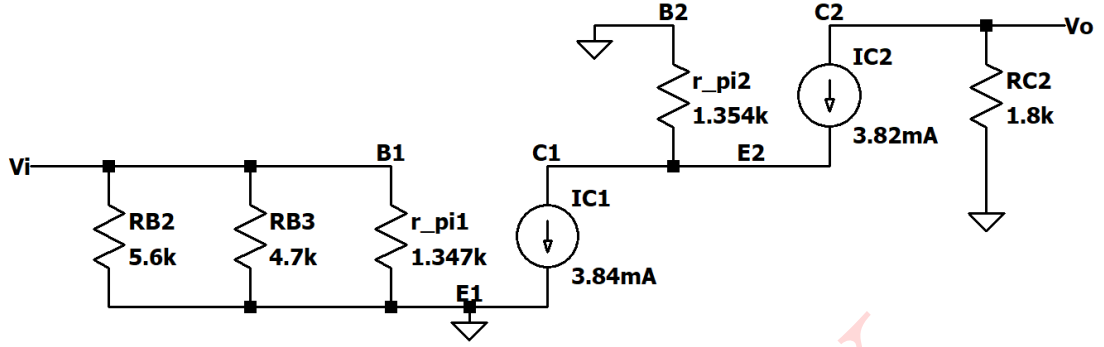


Figure 3: Small Signal Equivalent Circuit

Input impedance of stage 1:

$$Z_i = (R_B \parallel r_{\pi_1})$$

$$Z_i = (R_{B_2} \parallel R_{B_3} \parallel r_{\pi_1})$$

$$Z_i = (5.6 \times 10^3 \parallel 4.7 \times 10^3 \parallel 1.347 \times 10^3) = \mathbf{882.045 \Omega}$$

Output impedance of stage 2:

$$Z_o = R_{C_2} = \mathbf{1.8 \text{ k}\Omega}$$

Stage 2 Voltage gain:

$$A_{V_2} = \frac{-g_{m_2} V_{\pi_2} (R_{C_2})}{V_{\pi_2}}$$

$$A_{V_2} = -g_{m_2} R_{C_2}$$

$$A_{V_2} = -146.92 \times 10^{-3} \times 1.8 \times 10^3 = \mathbf{-264.456}$$

Stage 1 voltage gain:

$$A_{V_1} = \frac{-g_{m_1} V_{\pi_1} \left(\frac{r_{\pi_2}}{1 + \beta_2} \right)}{V_{\pi_1}}$$

$$A_{V_1} = -g_m \left(\frac{r_{\pi_2}}{1 + \beta_2} \right)$$

$$A_{V_1} = -147.69 \times 10^{-3} \left(\frac{1.35 \times 10^3}{1 + 200} \right) = \mathbf{-0.994}$$

Overall voltage gain:

$$A_{VT} = A_{V_1} \times A_{V_2}$$

$$A_{VT} = (-0.994) \times (-264.456) = \mathbf{262.869}$$

$$A_{VT} \text{ in dB} = 20 \log_{10}(|A_{VT}|)$$

$$A_{VT} \text{ in dB} = 20 \log_{10}(262.869) = \mathbf{48.3947 \text{ dB}}$$

Output Voltage:

$$V_o = A_{VT} V_i$$

$$V_o = 262.869 \times 5 \times 10^{-3} = 1.314 \text{ V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

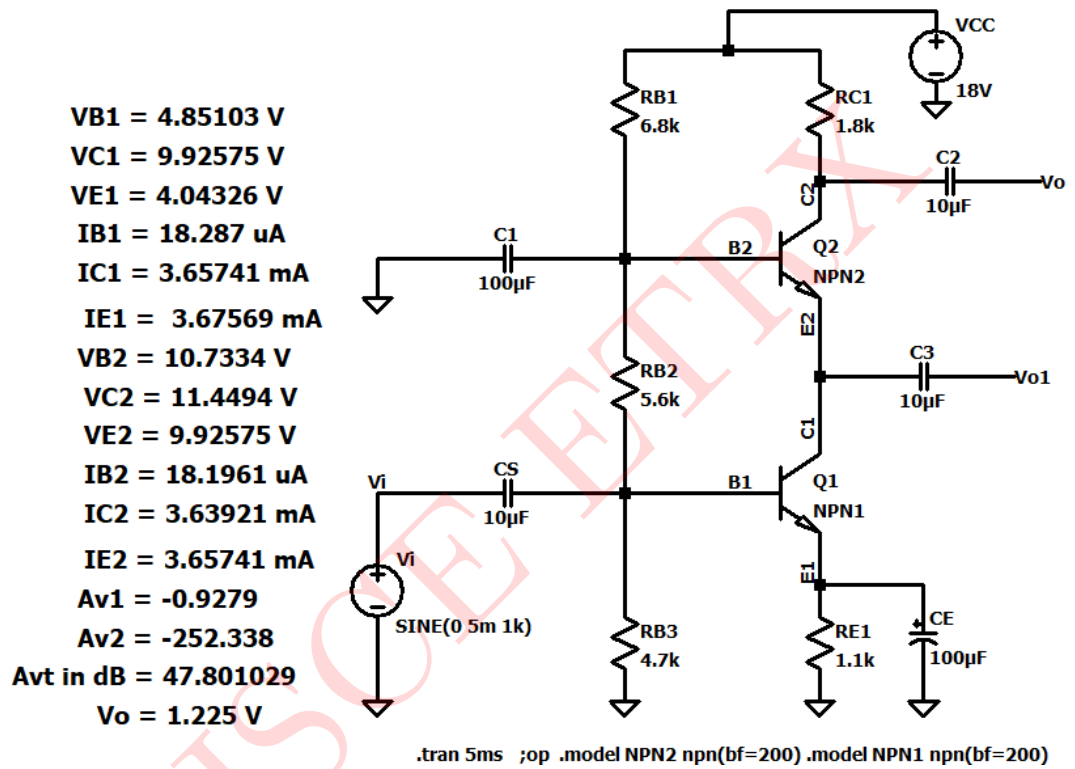


Figure 4: Circuit Schematic 1: Results

 


Figure 5: Input & Output waveforms for stage 1

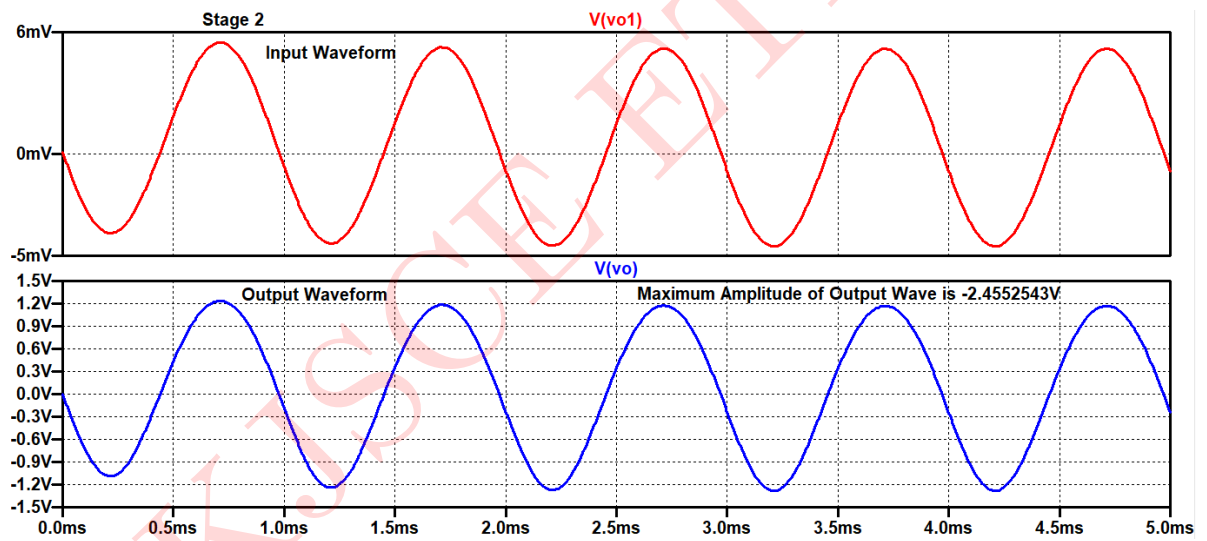


Figure 6: Input & Output waveforms for stage 2

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_{B_1}	19.2 μA	18.287 μA
I_{C_1}	3.84 mA	3.6574 μA
I_{E_1}	3.86 mA	3.6756 μA
I_{B_2}	19.1 μA	18.1961 μA
I_{C_2}	3.82 mA	3.6392 μA
I_{E_2}	3.84 mA	3.6571 μA
V_{C_1}	10.142 V	9.9257 V
V_{C_2}	11.124 V	11.4494 V
V_{E_1}	4.247 V	4.0432 V
V_{E_2}	10.142 V	9.9257 V
V_{B_1}	4.947 V	4.8510 V
V_{B_2}	10.842 V	10.7334 V
Voltage gain of stage 1: A_{V_1}	-0.994	-0.9279
Voltage gain of stage 2: A_{V_2}	-264.456	-252.338
Overall voltage gain: A_{VT} in dB	48.3947 dB	47.8010 dB
Input impedance of stage 1	882.045 Ω	—
Output impedance of stage 2	1.8 k Ω	—
Output Voltage	1.314 V	1.225 V

Table 1: Numerical 1

Numerical 2: The transistor parameters of the NMOS cascade circuit shown in figure 7 are, $V_{TN_1} = V_{TN_2} = 0.8$ V, $k_{n_1} = k_{n_2} = 3$ mA/V² and $\lambda_1 = \lambda_2 = 0$. Determine 1st and 2nd stage DC parameters. Determine 1st and 2nd stage voltage gain and overall voltage gain in dB. Calculate 1st stage input impedance, 2nd stage output impedance and output voltage.

 


Figure 7: Circuit 2

Solution:

The given circuit 2 is a CS-CG cascade amplifier employing NMOS. For DC biasing, the capacitors acts as an open source.

DC Analysis:

$$V_{G_1} = \frac{R_3}{R_1 + R_2 + R_3} V_{DD} \quad \dots (\text{Voltage divider})$$

$$V_{G_1} = \frac{54.6 \times 10^3 \times 5}{95.4 \times 10^3 + 150 \times 10^3 + 54.6 \times 10^3} = 0.91 \text{ V}$$

 


Figure 8: DC Equivalent circuit

$$V_{G_2} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} V_{DD}$$

$$V_{G_1} = \frac{150 \times 10^3 + 54.6 \times 10^3}{95.4 \times 10^3 + 150 \times 10^3 + 54.6 \times 10^3} \times 5 = \mathbf{3.41 \text{ V}}$$

Applying KVL to the gate source loop of the 1st transistor,

$$V_G - V_{GS} - I_{D_1} R_S - V_{SS} = 0$$

$$I_{D_1} R_{S_1} = V_{G_1} - V_{GS_1} - V_{SS}$$

$$I_{D_1} = \frac{V_{G_1} - V_{GS_1} - V_{SS}}{R_{S_1}}$$

$$I_{D_1} = \frac{0.91 - V_{GS_1} + 5}{10 \times 10^3}$$

$$I_{D_1} = \frac{5.91 - V_{GS_1}}{10 \times 10^3}$$

From current equation,

$$I_{D_1} = k_{n_1}(V_{GS_1} - V_{TN_1})^2$$

$$\frac{5.91 - V_{GS_1}}{10 \times 10^3} = 3 \times 10^{-3}(V_{GS_1} - 0.8)^2$$

$$5.91 - V_{GS_1} = 30(V_{GS_1}^2 - 1.6V_{GS_1} + 0.64)$$

$$5.91 - V_{GS_1} = 20V_{GS_1}^2 - 48V_{GS_1} + 19.2$$

$$30V_{GS_1}^2 - 47V_{GS_1} + 13.29 = 0$$

$$V_{GS_1} = \mathbf{1.196 \text{ V}} \text{ or } V_{GS_1} = \mathbf{0.37 \text{ V}}$$

Let, $V_{GS_1} = 1.196 \text{ V}$

$$I_{D_1} = \frac{5.91 - 1.196}{10 \times 10^3} = \mathbf{0.471 \text{ mA}}$$

Let, $V_{GS_1} = 0.37 \text{ V}$

$$I_{D_1} = \frac{5.91 - 0.37}{10 \times 10^3} = \mathbf{0.554 \text{ mA}}$$

V_{GS_1} cannot be less than V_{TN} for NMOS,

$$V_{GS_1} = \mathbf{1.196 \text{ V}}$$

$$I_{D_1} = \mathbf{0.471 \text{ mA}}$$

As both the NMOS are identical,

$$V_{GS_1} = V_{GS_2} = \mathbf{1.96 \text{ V}}$$

Terminal D_1 is connected to S_2 ,

$$I_{D_1} = I_{D_2} = \mathbf{0.471 \text{ mA}}$$

Voltage across terminal S_2 can be given as,

$$V_{S_2} = V_{G_2} - V_{GS_2}$$

$$V_{S_2} = 3.41 - 1.196 = \mathbf{2.214 \text{ V}}$$

$$V_{S_2} = V_{D_1} = \mathbf{2.214 \text{ V}}$$

Voltage across terminal D_2 is given as,

$$V_{D_2} = V_{DD} - I_{D_2}R_{D_2}$$

$$V_{D_2} = 5 - 0.471 \times 10^{-3} \times 2.5 \times 10^3 = \mathbf{3.822 \text{ V}}$$

Voltage across terminal S_1 can be given as,

$$V_{S_1} = V_{G_1} - V_{GS_1}$$

$$V_{S_1} = 0.91 - 1.196 = \mathbf{-0.286 \text{ V}}$$

AC Analysis:

Small signal parameters:

$$g_{m1} = 2k_{n1}(V_{GS1} - V_{TN1})$$

$$g_{m1} = 2 \times 3 \times 10^{-3}(1.196 - 0.8) = \mathbf{2.376 \text{ mA/V}}$$

$$g_{m2} = 2k_{n2}(V_{GS2} - V_{TN2})$$

$$g_m = 2 \times 3 \times 10^{-3}(1.196 - 0.8) = \mathbf{2.376 \text{ mA/V}}$$

Small Signal Equivalent Circuit is shown in figure 9:

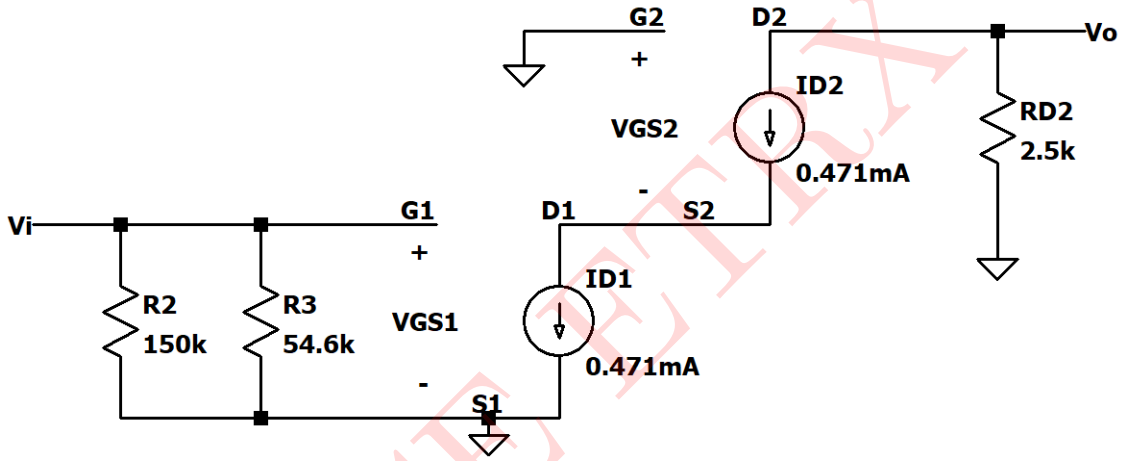


Figure 9: Small Signal Equivalent Circuit

Input impedance of stage 1:

$$Z_i = R_G = (R_2 \parallel R_3)$$

$$Z_i = (150 \times 10^3 \parallel 54.6 \times 10^3) = \mathbf{40.029 \text{ k}\Omega}$$

Output impedance of stage 2:

$$Z_o = R_{D2} = \mathbf{2.5 \text{ k}\Omega}$$

Stage 2 Voltage gain:

$$A_{V2} = \frac{-g_{m2}V_{gs2}(R_{D2})}{-V_{gs2}}$$

$$A_{V2} = g_{m2}R_{D2}$$

$$A_{V2} = 2.376 \times 10^{-3} \times 2.5 \times 10^3 = \mathbf{5.94}$$

Stage 1 voltage gain:

$$A_{V1} = \frac{-g_{m1}V_{gs1} \left(\frac{1}{g_{m2}} \right)}{V_{gs1}} = -1 \quad \dots (\because g_{m1} = g_{m2})$$

Overall voltage gain:

$$A_{VT} = A_{V_1} \times A_{V_2}$$

$$A_{VT} = (-1) \times (5.94) = -5.94$$

$$A_{VT} \text{ in dB} = 20\log_{10}(|A_{VT}|)$$

$$A_{VT} \text{ in dB} = 20\log_{10}(5.94) = 15.4757 \text{ dB}$$

Output Voltage:

$$V_o = A_{VT}V_i$$

$$V_o = -5.94 \times 10 \times 10^{-3} = -0.0594 \text{ V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

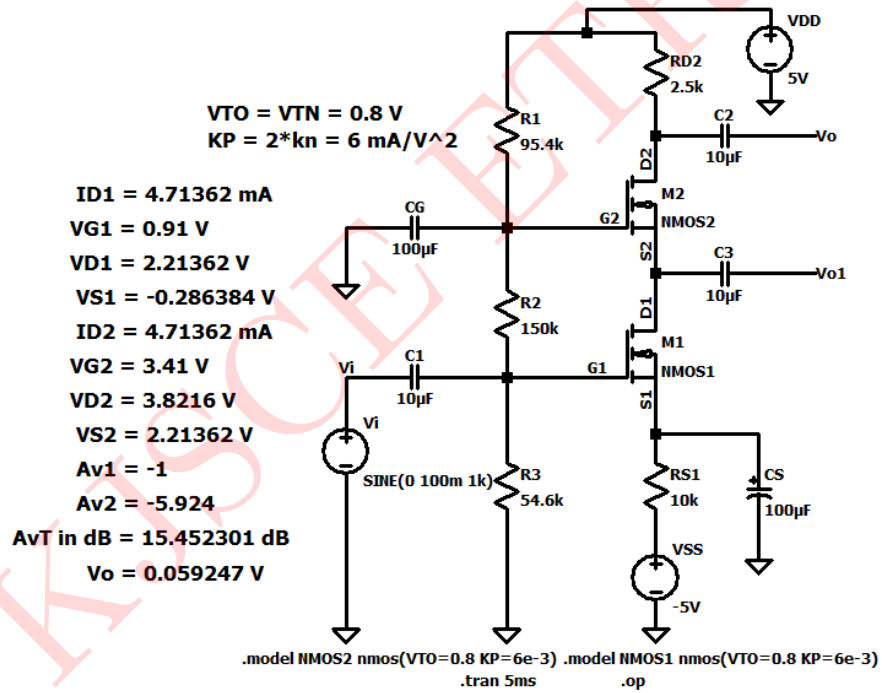


Figure 10: Circuit Schematic 2: Results

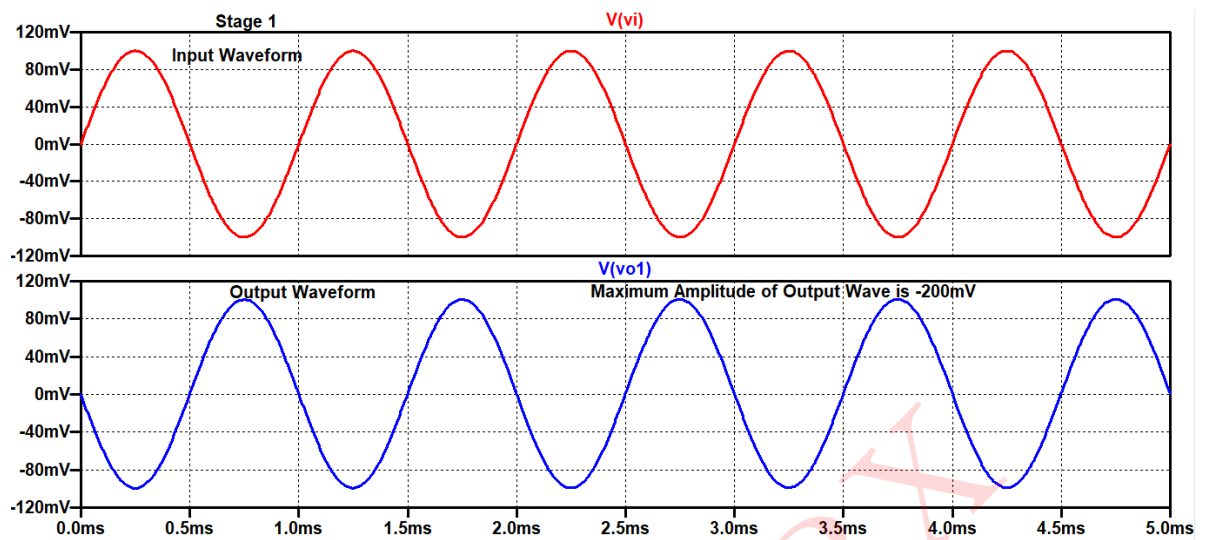


Figure 11: Input & Output waveforms for stage 1

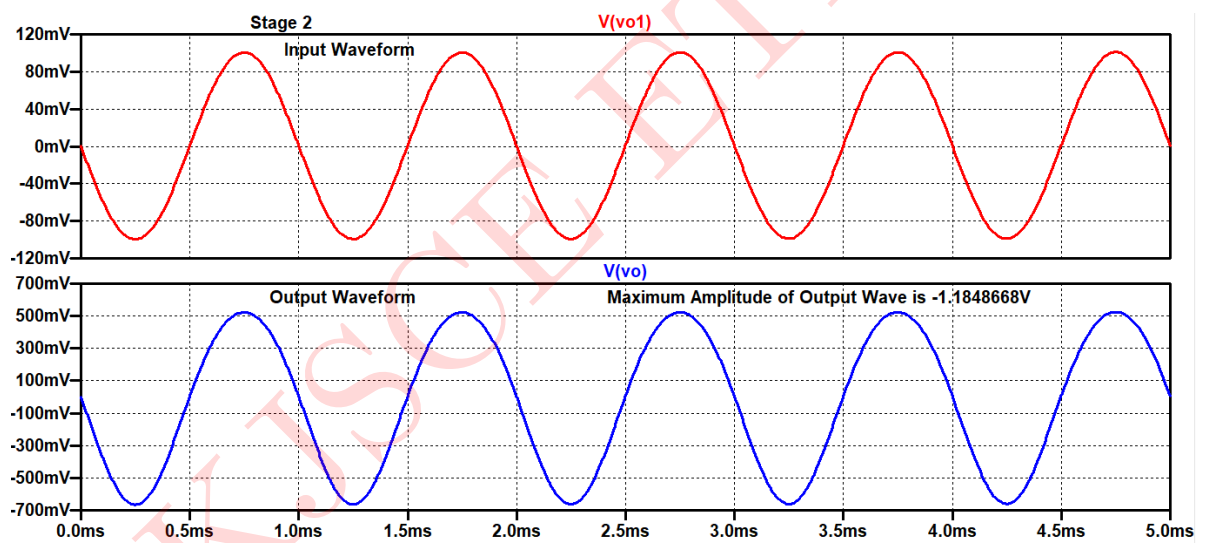


Figure 12: Input & Output waveforms for stage 2

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_{D_1}	0.471 mA	0.4713 mA
V_{G_1}	0.91 V	0.91 V
V_{D_1}	2.214 V	2.2136 V
V_{S_1}	-0.286 V	-0.2863 V
I_{D_2}	0.471 mA	0.4713 mA
V_{G_2}	3.41 V	3.41 V
V_{D_2}	3.822 V	3.8216 V
V_{S_2}	2.214 V	2.2136 V
Voltage gain of stage 1: A_{V_1}	-1	-1
Voltage gain of stage 2: A_{V_2}	5.94	5.924
Overall voltage gain: A_{VT} in dB	15.4757 dB	15.4523 dB
Input impedance of stage 1	40.029 k Ω	-
Output impedance of stage 2	2.5 k Ω	-
Output Voltage	-0.0594 V	-0.05924 V

Table 2: Numerical 2
