

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Multi-transistor circuits**

12<sup>st</sup> July, 2020

Numericals

**Numerical 1:** Calculate voltage gain of each stage and overall AC Voltage gain for the BJT Cascade amplifier circuit shown in figure 1. Here,  $V_A = 100V$  and load resistance  $R_L = 12k\Omega$

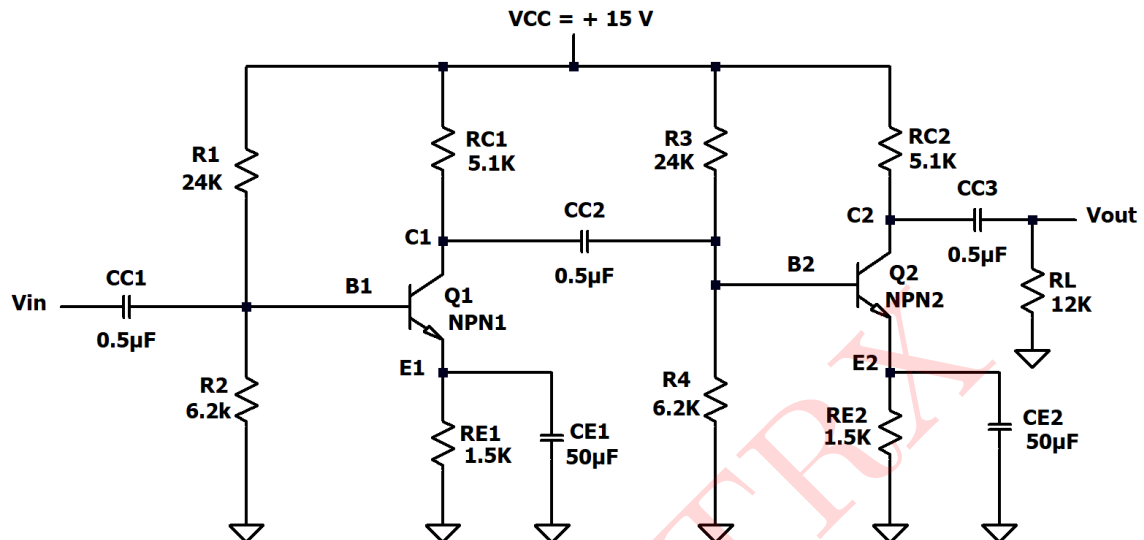


Figure 1: Circuit 1

**Solution:**

**DC ANALYSIS:**

$f = 0$ , thus  $X_C = \infty$ , So we replace each capacitor with short circuit,

Also due to RC coupling both the stages Q points are isolated.

Since, both stages are symmetric in parameters and resistors values, DC analysis of one stage is enough.

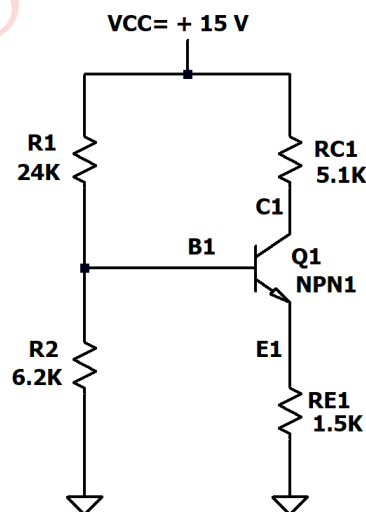


Figure 2: DC Equivalent Circuit

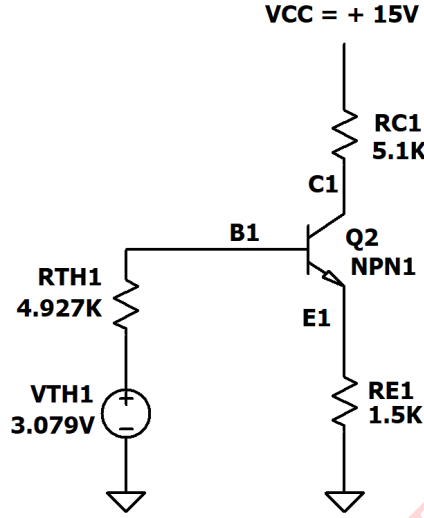


Figure 3: Thevenin equivalent circuit

Here,  $R_{TH1} = R_1 \parallel R_2 = 24k \parallel 6.2k = 4.927k\Omega$

$$\text{and } V_{TH1} = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{15 \times 6.2 \times 10^3}{24k + 6.2k} = 3.079V$$

Applying KVL to Base- Emitter loop;

$$V_{TH1} - I_{B1}R_{TH1} - V_{BE1} - I_{E1}R_{E1} = 0$$

But,  $I_{E1} = (\beta_1 + 1)I_{B1}$

$$\therefore V_{TH1} - I_{B1}R_{TH1} - V_{BE1} - I_{B1}(1 + \beta_1)R_{E1} = 0$$

$$\therefore V_{TH1} - V_{BE1} = I_{B1}(R_{TH1} + (1 + \beta_1)R_{E1})$$

$$\begin{aligned} \therefore I_{B1} &= \frac{V_{TH1} - V_{BE1}}{R_{TH1} + (1 + \beta_1)R_{E1}} = \frac{3.079 - 0.7}{4.927k + (151)1.5 \times 10^3} = \frac{2.379 \times 10^{-3}}{231.427} = 10.27 \times 10^{-6} \\ &= 10.27\mu A \end{aligned}$$

$$\text{But } I_{C1} = \beta I_{B1} = 150 \times 10.27 \times 10^{-6} = 1.54mA$$

Applying KVL to Common - Emitter loop;

$$V_{CC} - I_{C1}R_{C1} - V_{CE1} - I_{E1}R_{E1} = 0$$

$$I_{E1} = (\beta_1 + 1)I_{B1}$$

$$\begin{aligned} V_{CE1} &= V_{CC} - I_{C1}R_{C1} - (1 + \beta_1)I_{B1}R_{E1} \\ &= 15 - (1.54 \times 10^{-3})(5.1)(10^3) - 151(10.27 \times 10^{-6})(1.5 \times 10^3) = 15 - 7.854 - 2.326 \\ &= 4.8198V \end{aligned}$$

Since both the stages are identical,

$$I_{CQ1} = I_{CQ2} = \mathbf{1.54mA}$$

$$V_{CE1Q} = V_{CE2Q} = \mathbf{4.8198V}$$

**Small signal parameters:**

$$r_{\pi} = \frac{\beta_1 V_T}{I_{C1Q}} = \frac{150 \times 26 \times 10^{-3}}{1.54 \times 10^{-3}} = \mathbf{2.532k\Omega}$$

$$g_{m1} = \frac{I_{C1Q}}{V_T} = \frac{1.54 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{59.23mA/V}$$

Since, both stages are identical we have,

$$r_{\pi1} = r_{\pi2} = \mathbf{2.532k\Omega}$$

$$g_{m1} = g_{m2} = \mathbf{59.23mA/V}$$

$$r_{d1} = \frac{V_A}{I_{CQ1}} = \frac{100}{1.54 \times 10^{-3}} = \mathbf{64.935k\Omega}$$

$$r_{d1} = r_{d2} = \mathbf{64.935k\Omega}$$

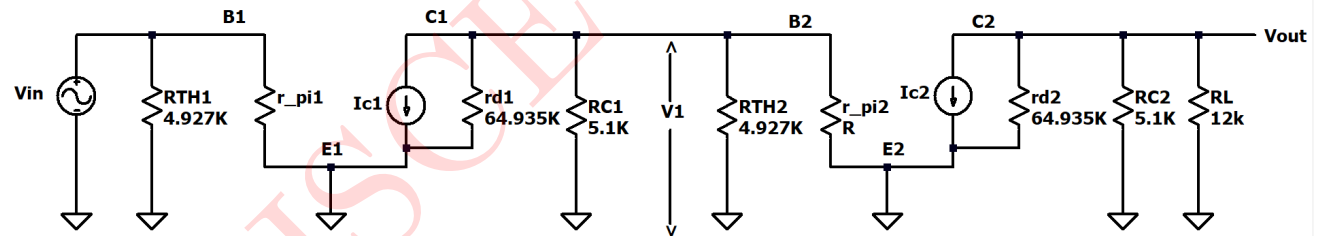


Figure 4: AC (mid band) equivalent circuit

$$A_{V1} = \frac{V_1}{V_{in}} \text{ and } A_{V2} = \frac{V_{out}}{V_1}$$

$$A_{VT} = A_{V1} A_{V2}$$

**Input impedance of first stage:**

$$Z_i = R_{TH1} \parallel r_{\pi1} = 4.927k\Omega \parallel 2.532k\Omega = \mathbf{1.672k\Omega}$$

**Output impedance of second stage:**

$$Z_o = R_2 \parallel r_{d2} \parallel R_{C2} = 64.935k \parallel 12k \parallel 5.1k = 3578.947 \parallel 64.93k = \mathbf{3.392k\Omega}$$

**Finding  $A_{V1}$ :**

$$\begin{aligned} A_{V1} &= \frac{V_1}{V_{in}} = \frac{-g_m V_{\pi1} (R_{C1} \parallel R_{TH1} \parallel r_{d1} \parallel r_{\pi2})}{V_{\pi1}} = -g_m V_{\pi1} (R_{C1} \parallel R_{TH1} \parallel r_{d1} \parallel r_{\pi2}) \\ &= -(59.23 \times 10^{-3})(95.1k \parallel 4.927k \parallel 64.935k \parallel 2.532k) \\ &= -(59.23 \times 10^{-3})(2506.003 \parallel 2436.97) \\ &= -(59.23 \times 10^{-3})(1235.5) = \mathbf{73.178} \end{aligned}$$

$$A_{V1} \text{ in dB} = 20 \log_{10}(73.178) = \mathbf{37.287dB}$$

**Finding  $A_{V2}$ :**

$$\begin{aligned} A_{V2} &= \frac{V_{out}}{V_1} = \frac{-g_m V_{\pi2} (R_{C2} \parallel r_{d2} \parallel R_L)}{V_{\pi2}} = -g_m (R_{C2} \parallel r_{d2} \parallel R_L) \\ &= -(59.23 \times 10^{-3})(12k \parallel 5.1k \parallel 64.935k) = -(59.23 \times 10^{-3})(3578.9 \parallel 64.935k) \\ &= -(59.23 \times 10^{-3})(3391.99) = \mathbf{-200.907} \end{aligned}$$

$$A_{V2} \text{ in dB} = 20 \log_{10}(200.907) = \mathbf{46.059dB}$$

**Finding  $A_{VT}$ :**

$$A_{VT} = A_{V1} A_{V2} = (-73.178) \times (-200.9.7) = \mathbf{14701.97}$$

$$A_{VT} \text{ in dB} = 20 \log_{10}(14701.97) = \mathbf{83.346dB}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

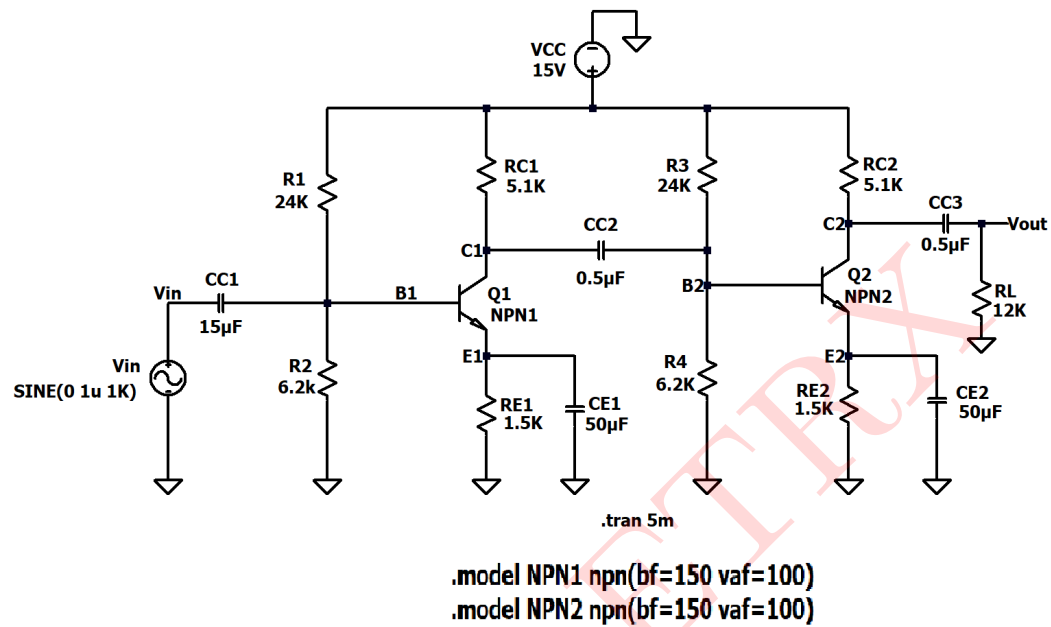


Figure 5: Circuit Schematic

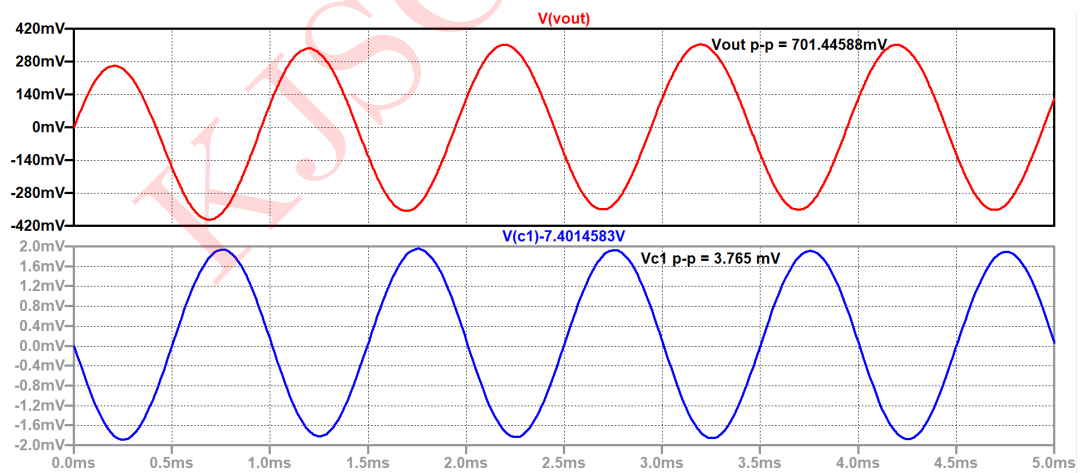


Figure 6: Input output waveform of stage 1

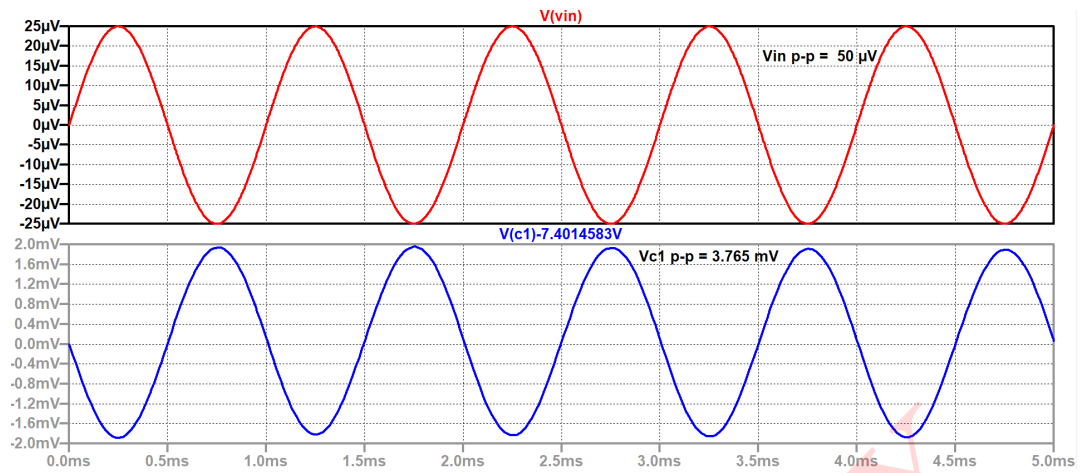


Figure 7: Input output waveform of stage 2

#### Comparison between Theoretical and Simulated values :-

Parameter	Simulated	Theoretical
$I_{C1Q}$	1.54mA	1.487mA
$V_{CE1Q}$	4.8198V	5.167V
$I_{C2Q}$	1.54mA	1.487mA
$V_{CE2Q}$	4.8198V	5.167V
Voltage gain of 2 <sup>nd</sup> stage ( $A_{V1}$ )	37.287dB	37.53dB
Voltage gain of 2 <sup>nd</sup> stage ( $A_{V2}$ )	46.049dB	45.4B
Overall Voltage gain	83.346dB	82.9dB
1 <sup>st</sup> stage input impedance ( $Z_i$ )	1.672k $\Omega$	—
2 <sup>nd</sup> stage input impedance ( $Z_i$ )	3.392k $\Omega$	—

Table 1: Numerical 1

**Numerical 2:** For the figure 8, calculate input impedance, output impedance, voltage gain and resulting output voltage.

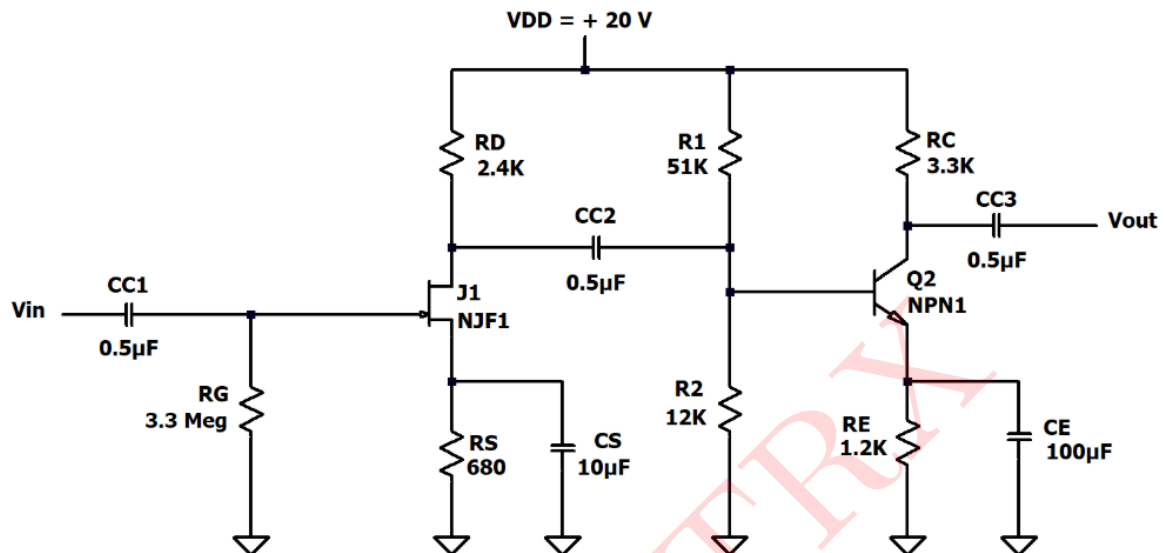


Figure 8: Circuit 2

**Solution:**

**DC ANALYSIS:**

$f = 0$ , thus  $X_C = \infty$ , So we replace each capacitor with short circuit, Also due to RC coupling both the stages Q points are isolated.

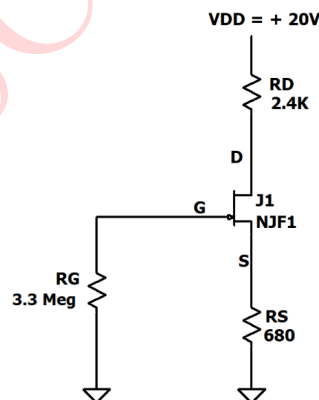


Figure 9: DC Equivalent Circuit for stage 1

DC analysis for 1<sup>st</sup> stage:

Applying KVL to gate - source loop;

$$\therefore -I_G R_G - V_{GS} - I_S R_S = 0$$

For mosfet,  $I_G = 0$  and  $I_S = I_D$

$$\therefore V_{GS} = -I_D R_S = -680 I_D \quad \text{.....1}$$

$$\text{Also, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 10 \times 10^{-3} \left(1 + \frac{V_{GS}}{4}\right)^2 \quad \text{.....2}$$

From 1 and 2, we get;

$$\therefore \frac{-V_{GS}}{680} = 10 \times 10^{-3} \left(1 + \frac{V_{GS}}{4}\right)^2$$

$$\therefore -V_{GS} = 6.8 \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16}\right)$$

$$\therefore 6.8 + 3.4 V_{GS} + 0.425 V_{GS}^2 + V_{GS} = 0$$

$$\therefore 0.425 V_{GS}^2 + 4.4 V_{GS} + 6.8 = 0$$

$$V_{GS} = -1.89V \text{ or } -8.462V$$

But  $V_{GS} > V_P$

$$\therefore V_{GSQ} = -1.89V$$

Substituting value of  $V_{GS}$  in 1;

$$I_D = \frac{V_{GS}}{-680} = \frac{1.89}{680} = 2.8mA$$



DC analysis for 2<sup>nd</sup> stage:

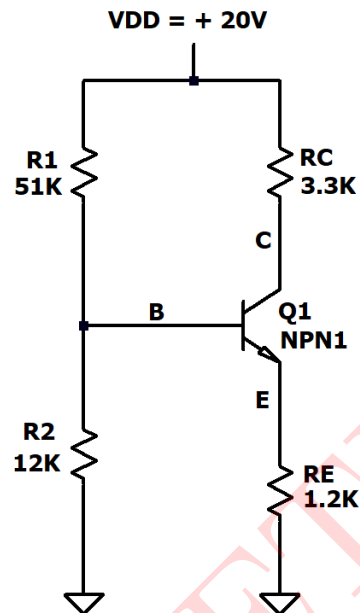


Figure 10: DC Equivalent Circuit for stage 2

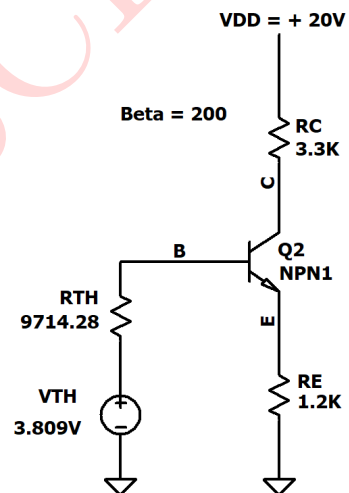


Figure 11: Thevenin equivalent circuit

Where,  $V_{TH} = \frac{V_{DD} \times R_2}{R_1 + R_2} = \frac{20 \times 12k}{51k + 12k} = \mathbf{3.809V}$

Also,  $R_{TH} = R_1 \parallel R_2 = 51k \parallel 12k = \mathbf{9714.28\Omega}$

Applying KVL to base - emitter loop;

$$V_{TH} - I_B R_{TH} - I_E R_E - V_{BE} = 0$$

But  $I_E = (\beta + 1)I_B$

$$\therefore 3.809 - 0.7 = I_B(R_{TH} + (\beta + 1)R_E)$$

$$I_B = \frac{3.809 - 0.7}{9714.28 + (201)(1.2 \times 10^3)} = \mathbf{12.39\mu A}$$

$$I_C = \beta I_B = 200 \times 12.39 \times 10^{-6} = \mathbf{2.478mA}$$

Applying KVL to common - emitter loop;

$$V_{DD} - I_C R_C - V_{CE} - I_E R_E = 0$$

But,  $I_E = (1 + \beta)I_B$

$$\begin{aligned} \therefore V_{CE} &= V_{DD} - I_C R_C - (1 + \beta)I_B R_E \\ &= 20 - (2.478 \times 10^{-3})(3.3 \times 10^3) - (201)(12.39 \times 10^{-6})(1200) = 20 - 8.1774 - 2.988 \\ &= \mathbf{8.834V} \end{aligned}$$

**Small Signal Parameters:**

$$g_{m1} = \frac{2I_{DSS}}{|V_P|} \left( 1 - \frac{V_{GS}}{V_P} \right) \quad (\text{where } g_{m1} \text{ is the trans conductance of first stage})$$

$$g_{m1} = \frac{2 \times 10^{-3} \times 10}{4} \left( 1 + \frac{(-1.89)}{4} \right) = \frac{10^{-3}}{2} (0.5275) \times 10 = 0.26 \times 10^{-2} = \mathbf{2.6mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{200 \times 26 \times 10^{-3}}{2.478 \times 10^{-3}} = \mathbf{2098.46\Omega}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{2.478 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{95.3mA/V}$$

(where  $g_{m2}$  is the trans conductances of second stage)

### Mid Band AC Equivalent circuit:

All the capacitors are short circuited and DC sources are open circuited.

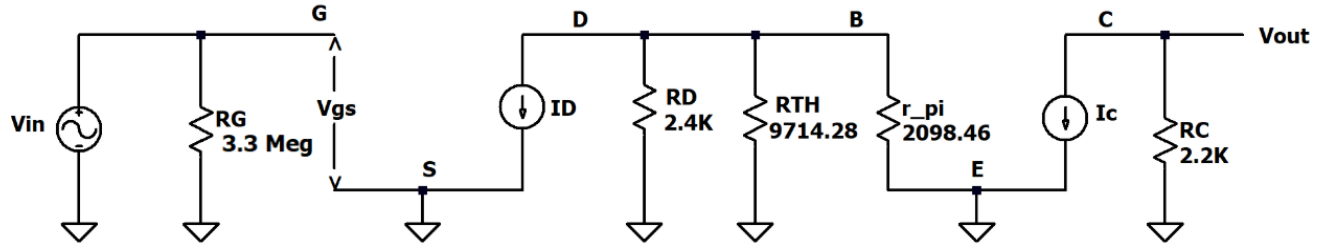


Figure 12: mid band AC equivalent circuit

### Input impedance:

$$Z_i = R_G = 3.3\text{M}\Omega$$

### Output Impedance:

$$Z_o = R_C = 2.2\text{k}\Omega$$

### Finding out $A_{V1}$ :

$$A_{V1} = \frac{V_1}{V_{in}} = \frac{-g_{m1}V_{\pi}(R_D \parallel R_{TH} \parallel r_{\pi2})}{V_{\pi}} = -g_{m1}(R_D \parallel R_{TH} \parallel r_{\pi2})$$

$$= -2.6 \times 10^{-3}(2.4\text{k} \parallel 9714.28 \parallel 2098.46) = -(2.6 \times 10^{-3})(2.4\text{k} \parallel 1725.68) = -2.61$$

$$A_{V1} \text{ in dB} = 20\log_{10}(2.61) = 8.332\text{dB}$$

### Finding $A_{V2}$ :

$$A_{V2} = \frac{V_{out}}{V_1} = \frac{-g_{m2}V_{\pi2}R_C}{V_{\pi2}} = -g_{m2}R_C = -95.3 \times 10^{-3}(3.3 \times 10^3) = (-314.49)$$

$$A_{V2} \text{ in dB} = 20\log_{10}(314.49) = 49.95\text{dB}$$

### Overall AC voltage gain:

$$A_{VT} = A_{V1} \times A_{V2} = (-2.61)(-314.49) = 820.8189$$

$$A_{VT} \text{ in dB} = 20\log_{10}(820.8189) = 58.2849\text{dB}$$

$$\text{Also, } A_{VT} = \frac{V_{out}}{V_{in}}$$

$$V_{out} = A_{VT} \times V_{in} = 10^{-3} \times 820.8189 = 0.82\text{mV}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

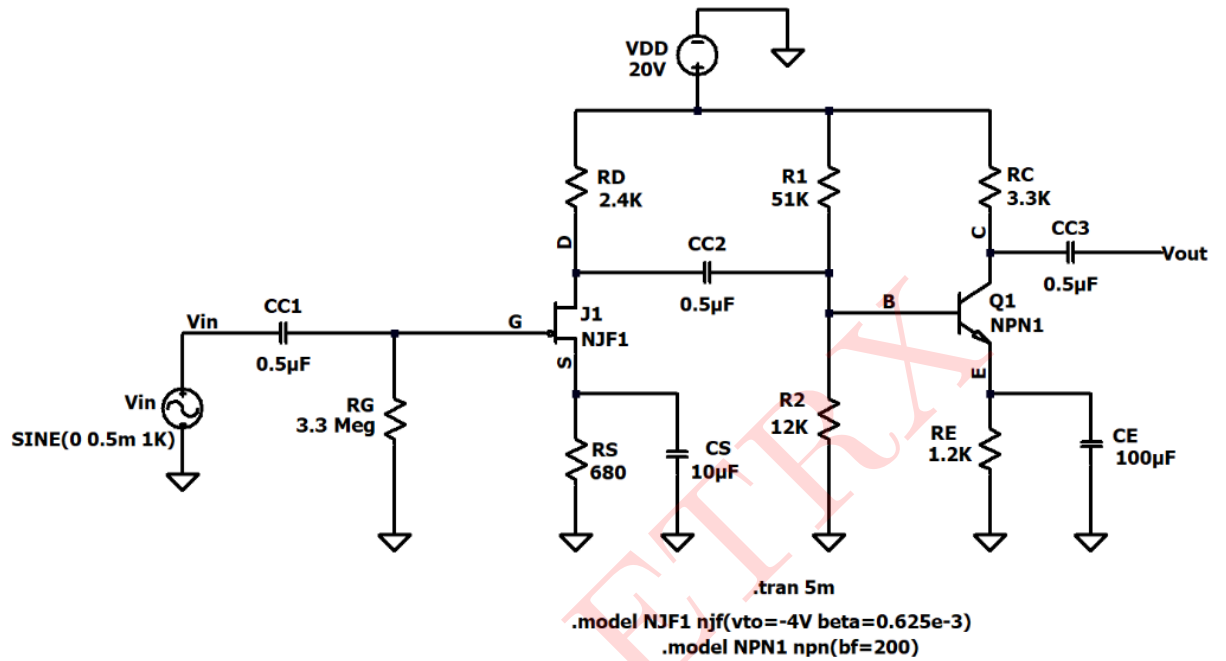


Figure 13: Circuit Schematic

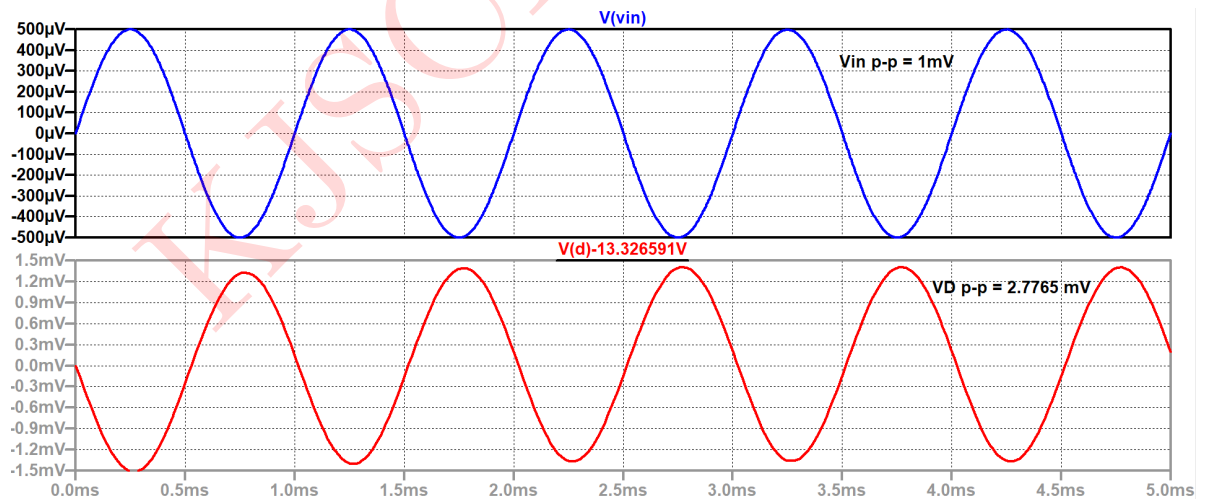


Figure 14: Input output waveform of stage 1

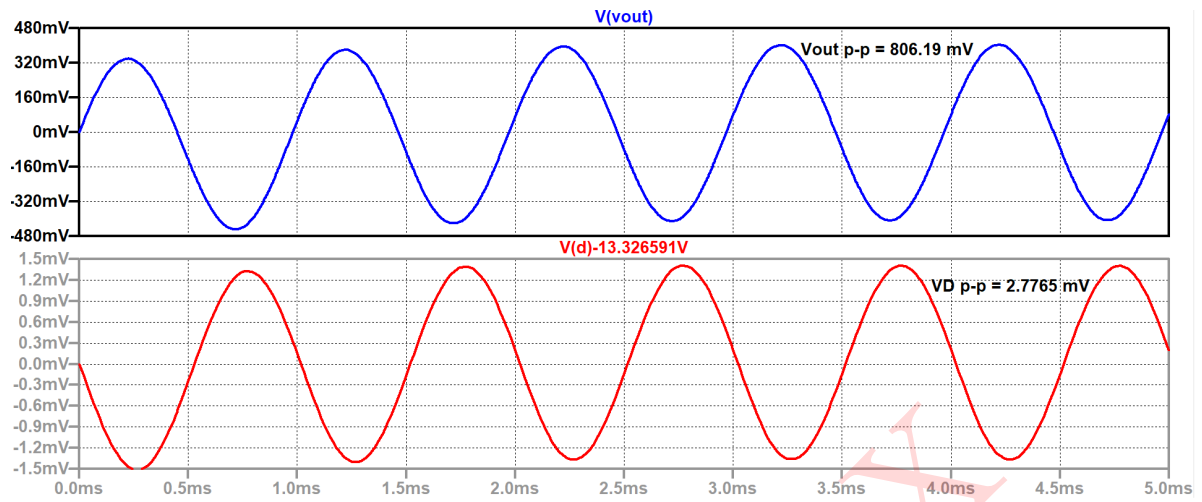


Figure 15: Input output waveform of stage 2

#### Comparison between Theoretical and Simulated values :-

Parameters	Simulated	Theoretical
$I_{DQ}$	2.8mA	2.8mA
$V_{GSQ}$	-1.89V	-1.89V
$I_{CQ}$	2.4mA	2.478mA
$V_{CEQ}$	9.17V	8.834V
Voltage gain of 1 <sup>st</sup> stage ( $A_{V1}$ )	-2.27	-2.61
Voltage gain of 2 <sup>nd</sup> stage ( $A_{V2}$ )	-291	-314.49
Overall Voltage gain	58.127dB	58.2849dB
Output Voltage	0.806V	0.82V
input impedance	—	3.3M $\Omega$
output impedance	—	2.2k $\Omega$

Table 2: Numerical 2

**Numerical 3:** A two stage circuit is shown in figure 16. Its BJT parameters are  $\beta_1 = \beta_2 = 20$  and  $V_{BE1} = V_{BE2} = 0.6$

- Determine all node voltages and terminal currents under DC analysis.
- Determine overall voltage gain of the circuit.

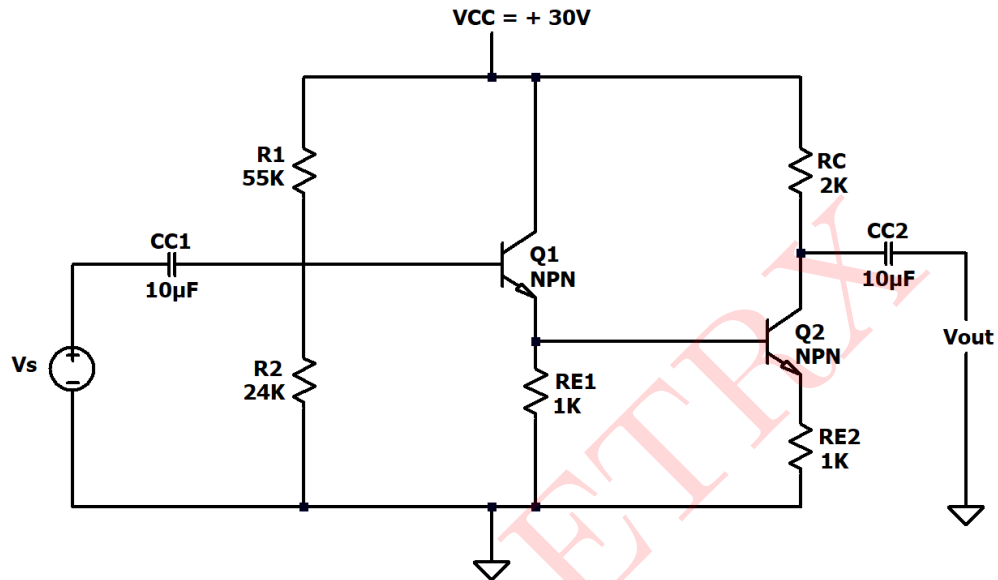


Figure 16: Circuit 1

**Solution:**

**DC ANALYSIS:**

$f = 0$ , thus  $X_C = \infty$ , So we replace each capacitor with short circuit,

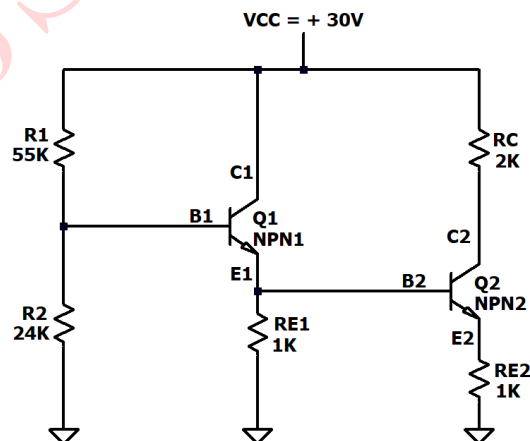


Figure 17: DC Equivalent Circuit

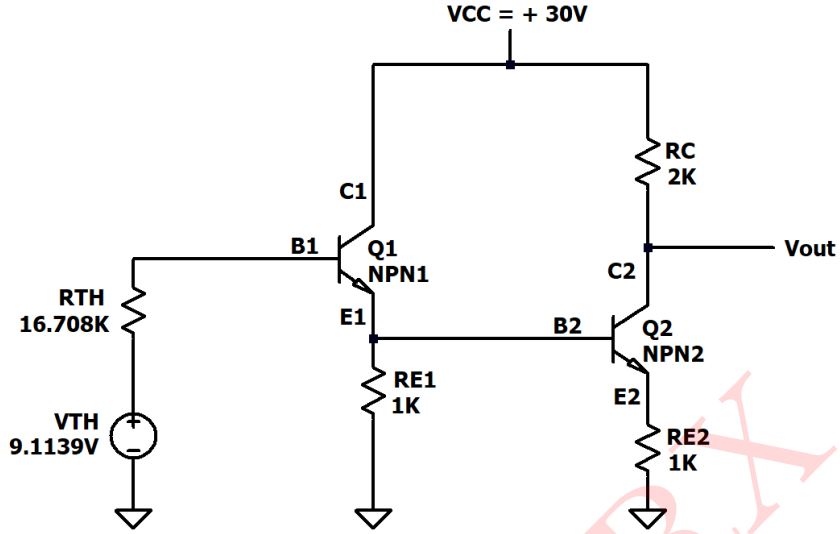


Figure 18: Thevenin Equivalent Circuit

Where,  $R_{TH} = R_1 \parallel R_2 = 55k \parallel 24k = 16.708k\Omega$

And  $V_{TH} = \frac{V_{CC} \times R_2}{R_1 + R_2} = 9.1139V$

Applying KVL to base - emitter loop;

Assuming  $I_{E1} = I_{RE1}$ ,  $I_{B2}$  is negligible

$$V_{TH} - I_{B1}R_{TH} - V_{BE1} - I_{E1}R_{E1} = 0$$

But  $I_{E1} = (\beta_1 + 1)I_{B1}$

$$\therefore V_{TH} - V_{BE1} = I_{B1}R_{TH} + (\beta_1 + 1)I_{B1}R_{E1}$$

$$I_{B1} = \frac{V_{TH} - V_{BE1}}{R_{TH} + (\beta_1 + 1)R_{E1}} = \frac{9.1139 - 0.6}{16.708k + (21)(1k)} = 0.225mA$$

$$I_{C1} = \beta_1 I_{B1} = 20 \times 0.225 \times 10^{-3} = 4.5mA$$

$$I_{E1} = I_{C1} + I_{B1} = 4.5mA + 0.225mA = 4.74mA$$

$$V_{B1} = V_{BE1} + V_{E1}$$

Where  $V_{E1} = I_{RE1}R_{E1}$

.....1

$$V_{E1} = 4.74 \times 10^{-3}(1 \times 10^3) = 4.74V \quad (\text{since } I_{RE1} \approx I_{E1})$$

$$V_{B1} = 4.74 + 0.6 = 5.34V$$

From the circuit we can see that

$$V_{B2} = V_{E1} = 4.74V$$

Also,  $V_{B2} = V_{E2} + V_{BE2}$

$$V_{E2} = V_{B2} - V_{BE2} = 4.74 - 0.6 = \mathbf{4.14V}$$

$$I_{E2} = \frac{V_{E2}}{R_{E2}} = \frac{4.14}{1k} = \mathbf{4.14mA}$$

$$I_{B2} = \frac{I_{E2}}{\beta_2 + 1} = \frac{4.14 \times 10^{-3}}{21} = \mathbf{197\mu A}$$

$$I_{C2} = \beta_2 I_{B2} = 20 \times 197 \times 10^{-6} = \mathbf{3.94mA}$$

Rewriting the exact expression of equation 1,

$$V_{E1(new)} = I_{RE1} R_{E1}$$

$$I_{RE1} = I_{E1} - I_{B2} = 4.74mA - 0.197mA = \mathbf{4.543mA}$$

$$V_{E1(new)} = 4.53 \times 10^{-3} \times 1 \times 10^3 = \mathbf{4.53V}$$

$$V_{B2(new)} = V_{E1(new)} = 4.53V$$

$$V_{B2(new)} = V_{BE2} + V_{E2(new)}$$

$$V_{E2(new)} = V_{B2(new)} - V_{BE2} = 4.53 - 0.6 = \mathbf{3.943V}$$

$$I_{E2(new)} = \frac{V_{E2(new)}}{R_{E2}} = \frac{3.943}{1 \times 10^3} = \mathbf{3.943mA}$$

$$I_{B2(new)} = \frac{I_{E2(new)}}{\beta_2 + 1} = \frac{3.943 \times 10^{-3}}{21} = \mathbf{187\mu A}$$

$$I_{C2(new)} = \beta_2 (I_{B2(new)}) = 20 \times 187 \times 10^{-6} = \mathbf{3.755mA}$$

$$V_{C2} = V_{CC} - I_{C2} R_C = 30 - (3.755 \times 10^{-3} \times 2 \times 10^3) = \mathbf{22.49V}$$

$$V_{C1} = \mathbf{30V}$$

**Node Voltage:**

$$V_{B1} = 5.34V, \quad V_{B2} = 4.53V$$

$$V_{C1} = 30V, \quad V_{B2} = 22.49V$$

$$V_{E1} = 4.53V, \quad V_{E2} = 3.943$$

**Terminal currents:**

$$I_{B1} = 225\mu A, \quad I_{B2} = 187\mu A$$

$$I_{C1} = 4.5mA, \quad I_{B2} = 3.755mA$$

$$I_{E1} = 4.74mA, \quad I_{E2} = 3.943mA$$



**Small signal parameters:**

$$r_{\pi 1} = \frac{\beta_1 V_T}{I_{C1}} = \frac{20 \times 26 \times 10^{-3}}{4.5 \times 10^{-3}} = \mathbf{115.55\Omega}$$

$$r_{\pi 2} = \frac{\beta_2 V_T}{I_{C2}} = \frac{20 \times 26 \times 10^{-3}}{26 \times 10^{-3}} = 138.48\Omega$$

$$g_{m1} = \frac{I_{CQ1}}{V_T} = \frac{4.5 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{173\text{mA/V}}$$

$$g_{m2} = \frac{I_{CQ2}}{V_T} = \frac{3.755 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{144\text{mA/V}}$$

**AC equivalent circuit:**

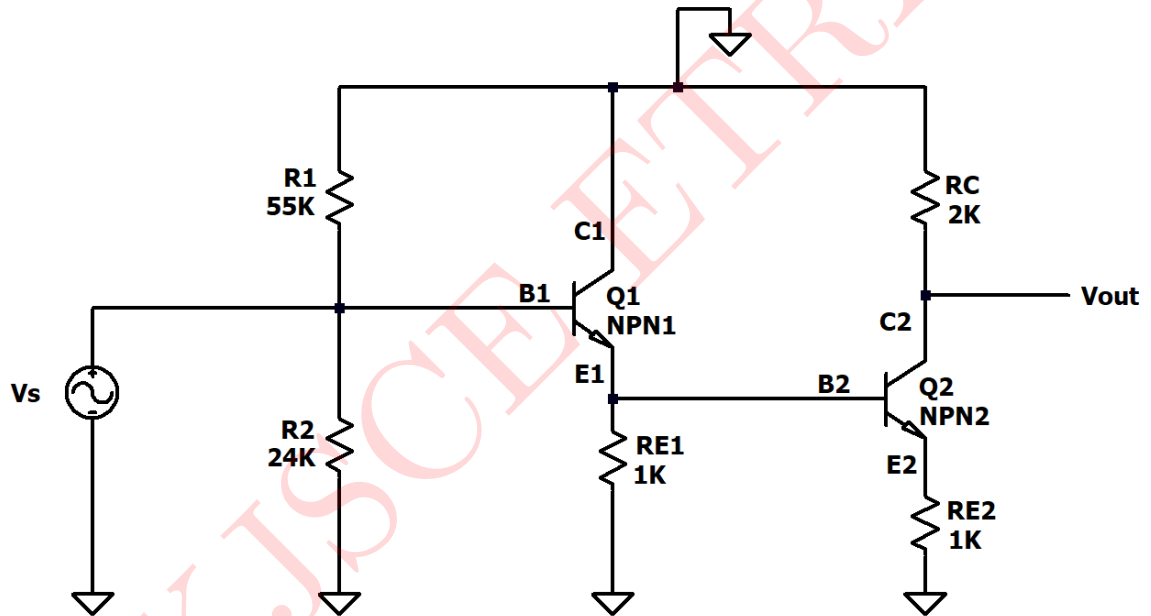


Figure 19: AC equivalent circuit

AC (mid frequency) equivalent circuit:

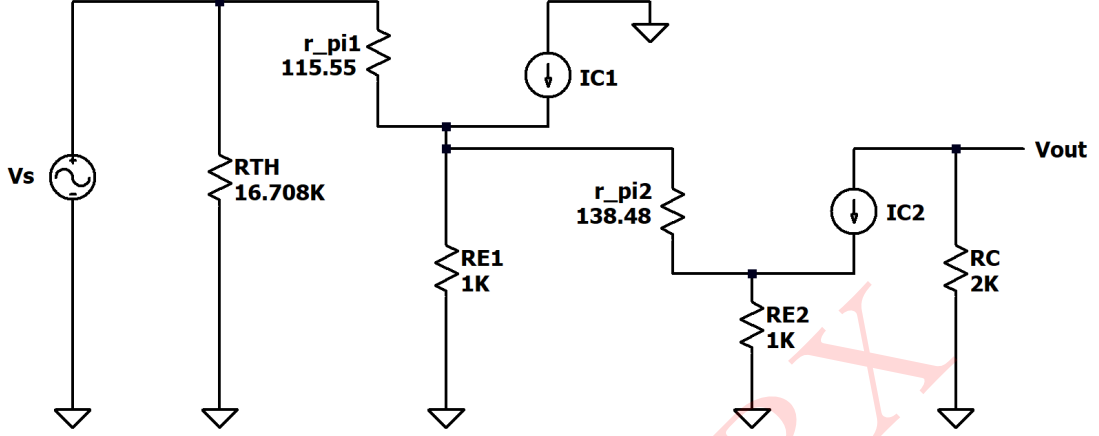


Figure 20: AC (mid band) equivalent circuit

Finding out overall voltage gain:

$$A_{VT} = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_1} \times \frac{V_1}{V_S}$$

$$i_{c2} = g_{m2}V_{\pi2} = \beta_2 i_{b2}$$

$$\begin{aligned} \text{Now, } A_{V2} = \frac{V_{out}}{V_1} &= -\frac{g_{m2}V_{\pi2}R_S}{i_{b2}(r_{\pi2} + (1 + \beta_2)R_{E2})} = \frac{-\beta_2(i_{b2})R_S}{i_{b2}(r_{\pi2} + (1 + \beta_2)R_{E2})} \\ &= \frac{-\beta_2)R_C}{(r_{\pi2} + (1 + \beta_2)R_{E2})} = \frac{-20 \times 2 \times 10^3}{138.48 + (21)(1 \times 10^3)} = -1.892 \end{aligned}$$

$$i_{C1} = g_{m1}V_{\pi1} = \beta_1(i_{b1})$$

$$\begin{aligned} A_{V1} = \frac{V_1}{V_S} &= \frac{g_{m1}V_{\pi1}R_{E1}}{i_{b1}(r_{\pi1} + (1 + \beta_1)R_{E1})} = \frac{\beta_1 i_{b1}R_{E1}}{i_{b1}(r_{\pi1} + (1 + \beta_1)R_{E1})} = \frac{\beta_1 R_{E1}}{(r_{\pi1} + (1 + \beta_1)R_{E1})} \\ &= \frac{20 \times 1 \times 10^3}{115.55 + (21)(1 \times 10^3)} = 0.947 \end{aligned}$$

$$\text{Overall voltage gain} = A_{VT} = A_{V1} \times A_{V2} = 0.947 \times (-1.892) = -1.792$$

Finding out output voltage:

$$A_{VT} = \frac{V_{out}}{V_S}$$

$$\text{let } V_S = 2V(p - p)$$

$$V_{out} = V_S \times A_{VT} = 2 \times 1.79 = 3.58V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

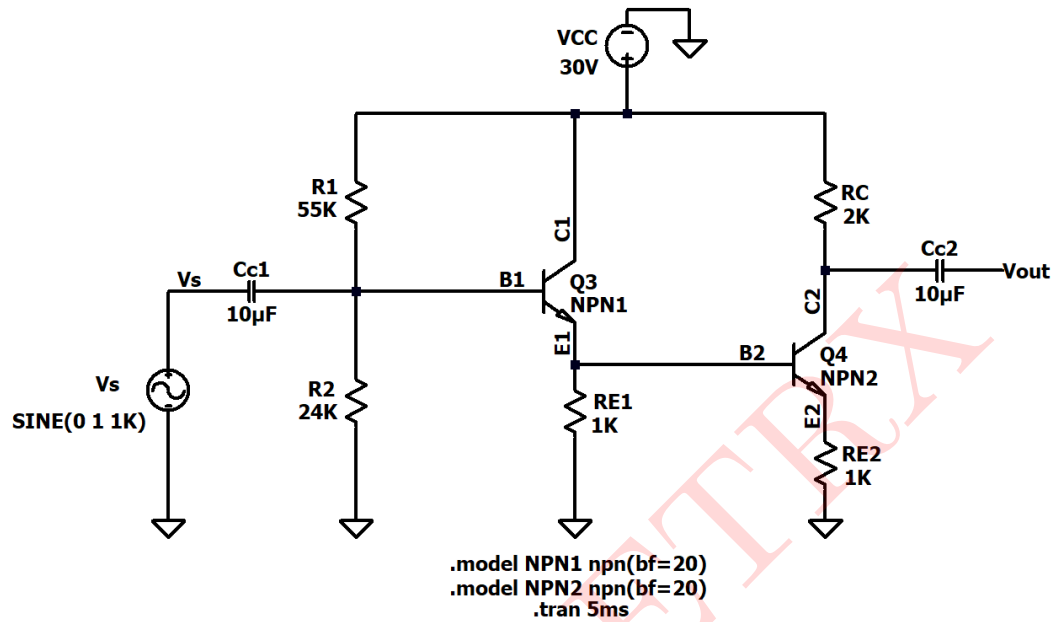


Figure 21: Circuit Schematic

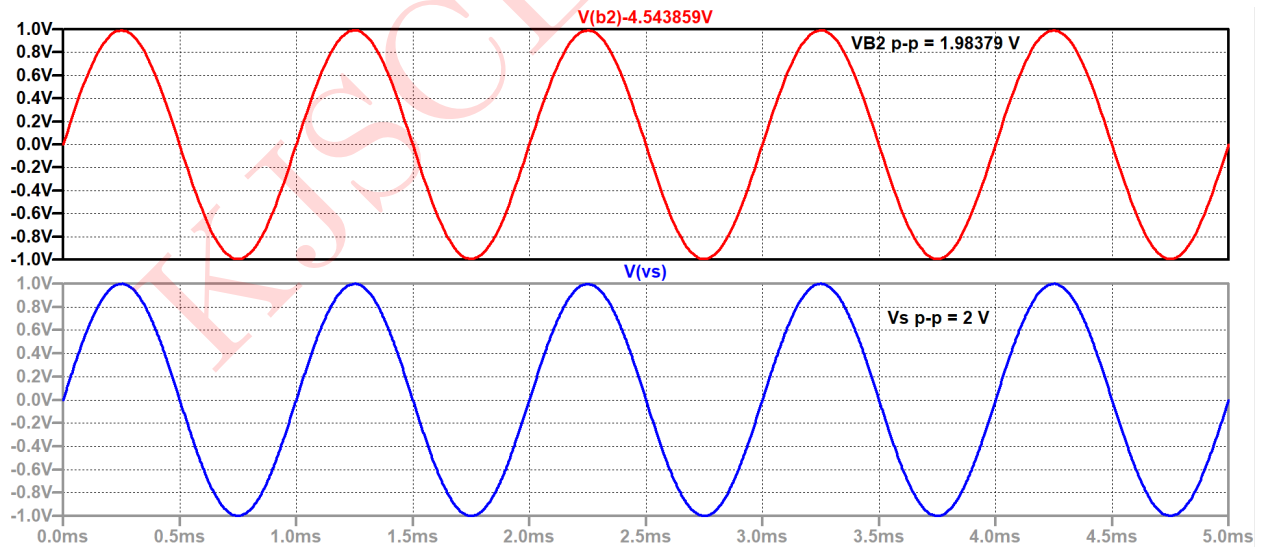


Figure 22: Input output waveform for stage 1

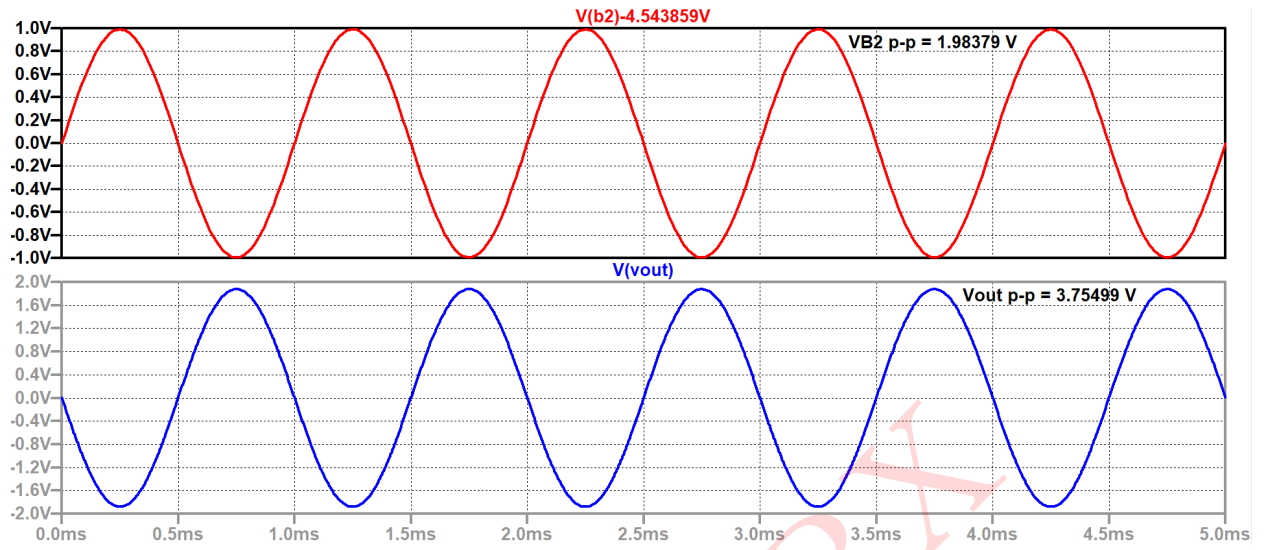


Figure 23: Input output waveform for stage 2

#### Comparison between Theoretical and Simulated values :-

Parameter	Simulated	Theoretical
$I_{B1}$	0.22mA	0.225mA
$I_{C1}, I_{E1}$	4.4mA, 4.62mA	4.5mA , 4.74mA
$I_{B2}$	117 $\mu$ A	1.87 $\mu$ A
$I_{C2}$	3.55mA	3.755 mA
$I_{E2}$	3.73 mA	3.943mA
$V_{C1}$	30V	30V
$V_{C2}$	22.8V	22.49V
$V_{E1}$	4.54V	4.53V
$V_{E2}$	3.736V	3.943V
$V_{B1}$	5.35V	5.34V
$V_{B2}$	4.54V	4.53V
$A_{VT}$	-1.87	-1.79
$V_{out}$	3.7549V	3.58V

Table 3: Numerical 3

\*\*\*\*\*