

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Design of single-stage Amplifier

11th July, 2020

Numericals

Design 1: Design a single stage RC coupled BJT Amplifier for following specification:

$$V_{orms} = 5V, V_{CC} = 20V, f_L \leq 20Hz, S \leq 10 \text{ and } |A_V| \geq 150$$

Select transistor BC 147A from datasheet

Solution:

1. Data given:

$$V_{orms} = 5V, V_{CC} = 20V, f_L \leq 20Hz, S \leq 10 \text{ and } |A_V| \geq 150$$

2. Selection of transistor:

The transistor selected is BC 147A and its specification are:

$$h_{ie} = 2.7k\Omega, V_{CE(sat)} = 0.25V$$

$$h_{FE(min)} = 115, h_{FE(typ)} = 180, h_{FE(max)} = 220$$

$$h_{fe(min)} = 125, h_{fe(typ)} = 220, h_{fe(max)} = 260$$

3. Selection of the biasing network:

Voltage divider biasing network is selected to keep Q point independent of variation in β or temperature.

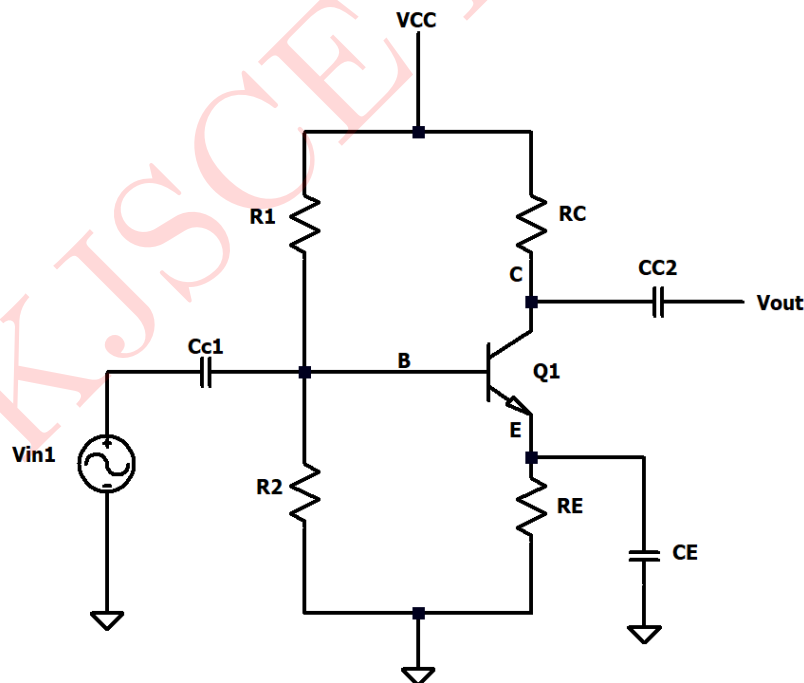


Figure 1: Circuit 1

4. Selection of R_C :

$$A_V = \frac{h_{fe(min)} R_C}{h_{ie}}$$

$$150 = \frac{125 R_C}{2.7 \times 10^3}$$

$$R_C = \frac{150 \times 2.7 \times 10^3}{125} = \mathbf{3.24k\Omega}$$

Selecting higher standard value of R_C to increase the gain

$$\therefore R_C = \mathbf{3.3k\Omega, 1/4W}$$

5. Selection of Q point:

$$V_{CC} = 20V \quad (\text{given})$$

$$V_{CE} = \frac{V_{CC}}{2} = \frac{20}{2} = \mathbf{10V}$$

$$I_C = \frac{V_{CC} - V_{CE} - V_E}{R_C}$$

$$V_E = 10\% \text{ of } V_{CC} = \frac{10}{10} \times 20 = \mathbf{2V}$$

.....1

$$I_C = \frac{20 - 10 - 2}{3.3 \times 10^3} = \mathbf{2.424mA}$$

Q point is (V_{CEQ}, I_{CQ}) which is $(10V, 2.424mA)$

6. Calculations of R_E

$$V_E = V_{RE} = 2V \quad (\text{from 1})$$

$$\text{Now, } V_E = V_{RE} = I_{EQ} \times R_E$$

$$R_E = \frac{V_E}{I_{EQ}}$$

$$I_{EQ} \approx I_{CQ}$$

$$\therefore I_{EQ} = 2.424mA$$

$$R_E = \frac{2}{2.424 \times 10^{-3}} = \mathbf{825\Omega}$$

Selecting lower standard value of R_E

$$\therefore R_e = \mathbf{820\Omega, 1/4W}$$

7. Calculations of biasing resistors (R_1 & R_2):

$$S \leq 10$$

$$\beta = h_{fe(max)} = 220$$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_E + R_B} \right)}$$

$$10 = \frac{1 + 220}{1 + (220) \left(\frac{820}{820 + R_B} \right)}$$

$$1220 = 10 + (2200) \left(\frac{820}{820 + R_B} \right)$$

$$\frac{221}{2200} = \frac{820}{820 + R_B}$$

$$820 + R_B = \frac{820 \times 2200}{211}$$

$$R_B = 8549.76 - 820 = 7729.76$$

$$R_{TH} = R_B = \frac{R_1 R_2}{R_1 + R_2}$$

.....2

From the Thevenin equivalent circuit shown in figure 2 we get to know that,

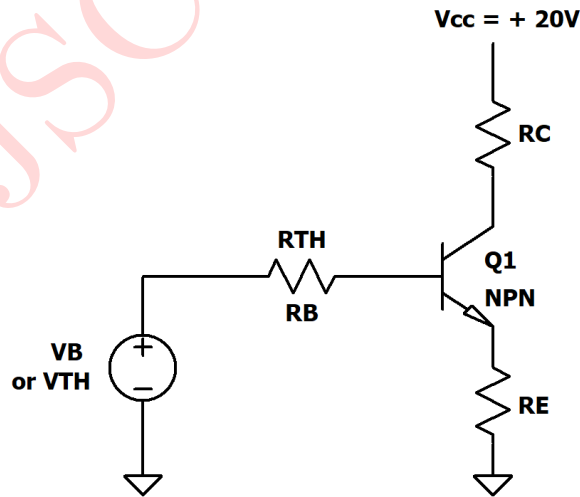


Figure 2: Thevenin Equivalent Circuit

$$V_B - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$\therefore V_B - \frac{I_C}{\beta} R_{TH} - V_{BE} - I_C R_E = 0$$

$$\therefore V_B = V_{BE} + I_C R_E + \frac{I_C}{\beta} R_{TH} = 0.7 + (2.424 \times 10^{-3})(825) + \frac{2.424 \times 10^{-3}}{180}(7729.76)$$

$$= 0.7 + 1.9998 + 0.1041 = \mathbf{2.803V}$$

$$V_{TH} = V_B = 2.803V$$

$$\text{From 2, } V_B = 2.803 = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$\therefore \frac{R_2}{R_1 + R_2} = \frac{2.803}{20} = 0.14019$$

.....3

From 2 and 3 we get;

$$7729.76 = R_B = R_{TH} = R_1(0.14019)$$

$$R_1 = \frac{7729.76}{0.14019} = \mathbf{55.135k\Omega}$$

Selecting higher standard value of R_1 :

$$R_1 = \mathbf{56k\Omega, 1/4W}$$

$$\text{Also, } \frac{R_2}{R_2 + 56k} = 0.14019$$

$$\therefore R_2 = 0.14019R_2 + (56 \times 10^3)(0.14019) = \frac{56 \times 10^3 \times 0.14019}{0.8589} = \mathbf{9.1307k\Omega}$$

Selecting lower standard value of R_2 :

$$R_2 = \mathbf{9.1k\Omega, 1/4W}$$

8. Calculation of coupling capacitors:

a. Finding out C_{C_1} :

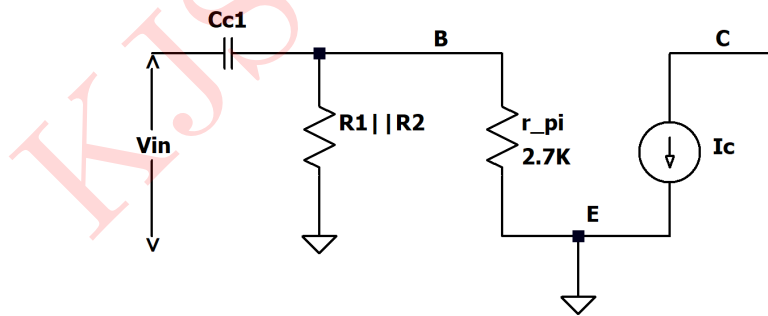


Figure 3: Small signal low frequency equivalent circuit for C_{C_1}

$$C_{C_1} = \frac{1}{2\pi R_{eq} f_L}$$

$$\text{here, } R_{eq} = R_1 \parallel R_2 \parallel h_{ie} = 56k \parallel 9.1k \parallel 2.7k = 7827.95 \parallel 2.7k = 2.0075$$

$$C_{C_1} = \frac{1}{2\pi(2.0075 \times 10^3)(20)} = \mathbf{3.964\mu F}$$

Selecting higher standard value for C_{C_1}

$$C_{C_1} = \mathbf{4.2\mu F/25V}$$

b. Finding out C_{C_2} :

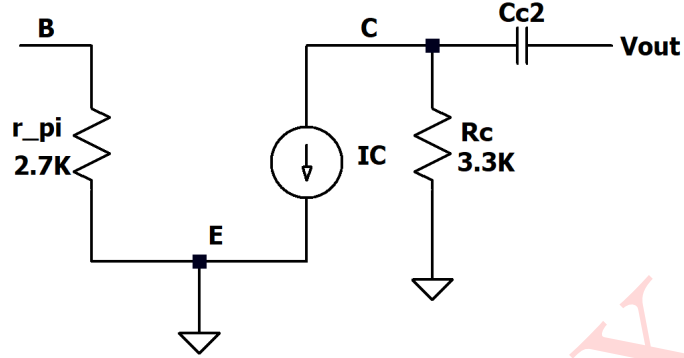


Figure 4: Small signal low frequency equivalent circuit for C_{C_2}

$$C_{C_2} = \frac{1}{2\pi R_C f_L} = \frac{1}{2\pi (3.3 \times 10^3) 20} = \mathbf{2.411 \mu F}$$

Selecting $C_{C_2} = \mathbf{2.7 \mu F / 25 V}$

9. Selecting C_E :

$$X_{C_E} = \frac{R_E}{10} = 0.1 R_E = \frac{820}{10} = \mathbf{82}$$

$$C_E = \frac{1}{2\pi f_L (X_{C_E})} = \frac{1}{2\pi \times 20 \times 82} = \mathbf{97.04 \mu F}$$

Selecting higher standard value for C_E

$C_E = \mathbf{100 \mu F / 25 V}$

10. Verification of overall gain A_V :

$$A_V = -g_m R_C$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.424 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{93.2 \text{ mA/V}}$$

$$|A_V| = -(93.2 \times 10^{-3} \times 3.3 \times 10^3) = \mathbf{-304}$$

FINAL DESIGN:

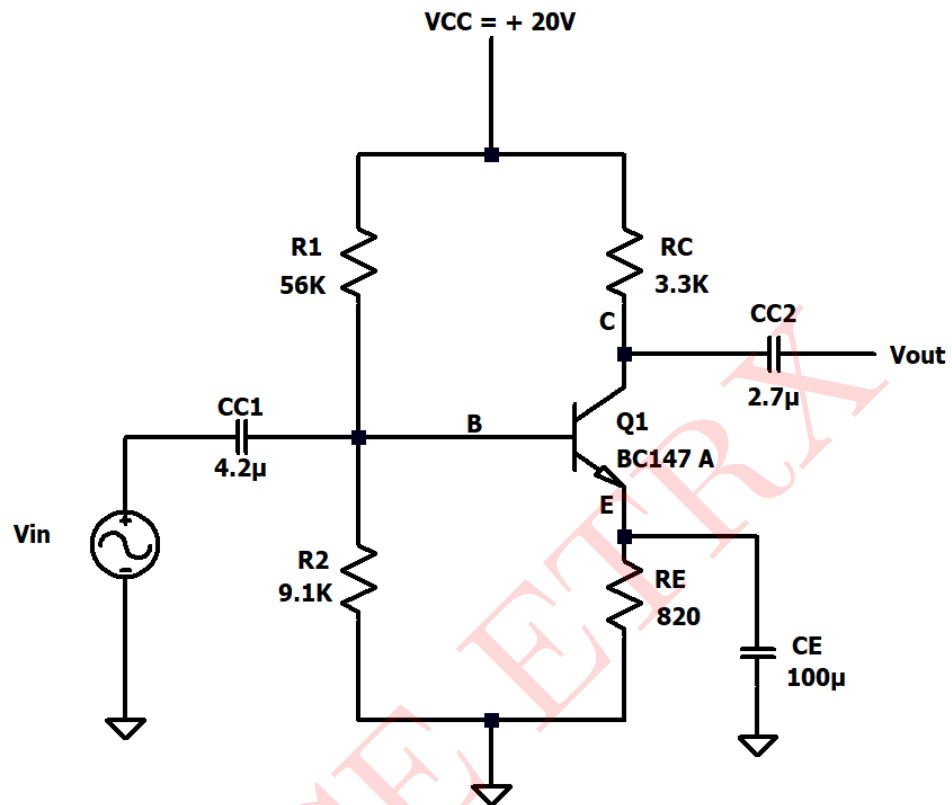


Figure 5: Designed Circuit

SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

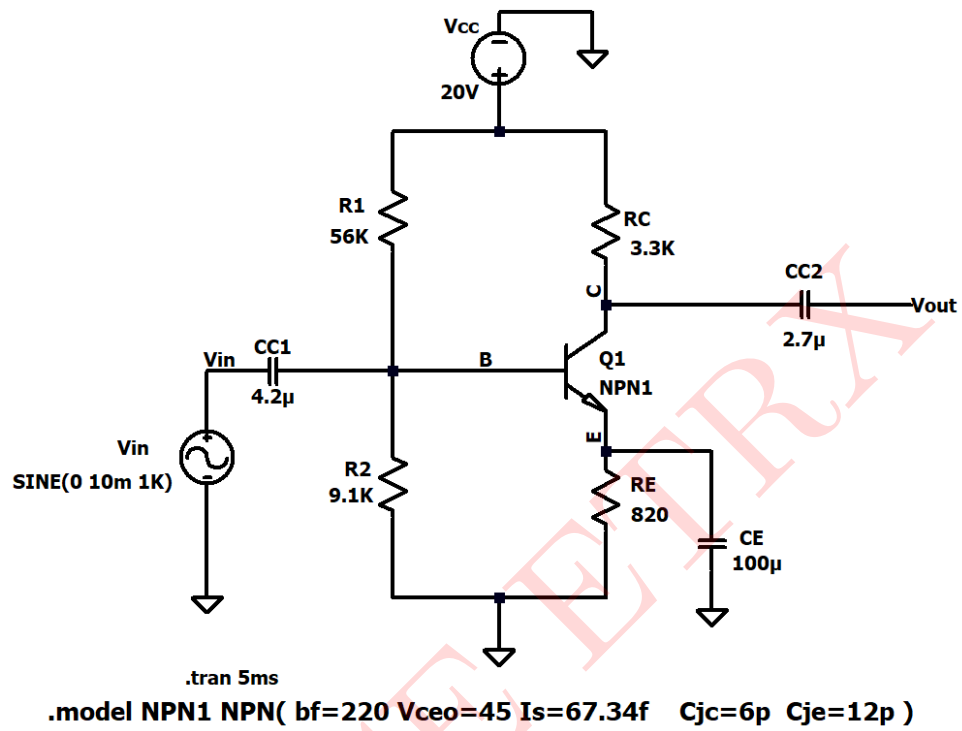


Figure 6: Circuit Schematic

The input and output waveforms are shown in figure 7.

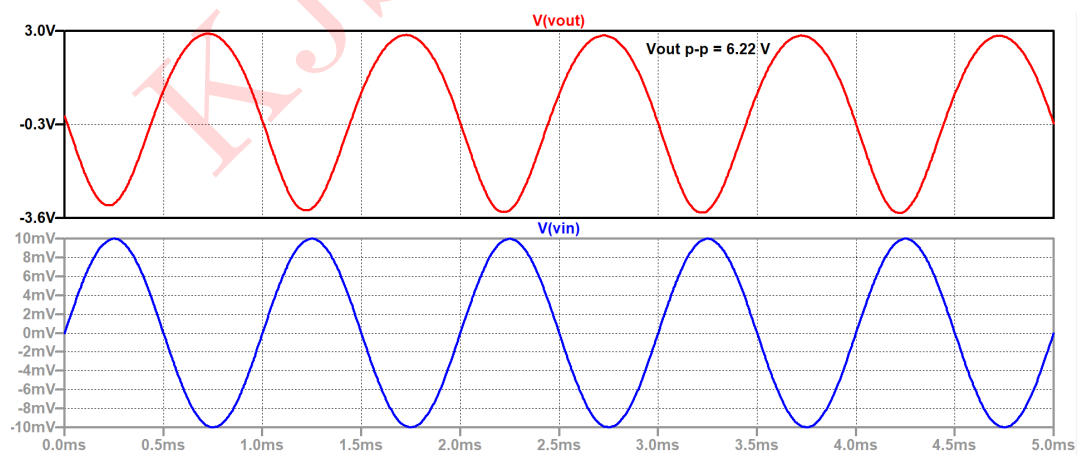


Figure 7: Input and Output Waveforms

Comparison between Theoretical and Simulated values :-

Parameter	Simulated	Theoretical
I_{CQ}	2.424mA	2.5mA
V_{CEQ}	10V	9.61V
A_V	-304	-311

Table 1: Design 1

KJSCE ETRX