

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Diode Application

Numerical 1:

For the circuit shown in figure 1, Plot

a) Input $V_{in}(t)$ and output $V_{out}(t)$ waveform

b) VTC Curve

Given: $V_{in} = 10$ Vp-p sinusoidal signal with frequency of 500Hz.

Use constant voltage model i.e. $V_{D_{on}} = 0.7V$, $V_B = 1V$ and $R_1 = 1k\Omega$

 


Figure 1: Circuit 1

Solution:

Assuming constant voltage model ($V_{D_{on}} = 0.7V$) for the diode D_1 , bias voltage V_B forward biases the diode D_1

→ If $V_{in} < (-V_{D_{on}} + V_B)$, diode D_1 is ON (as cathode voltage is greater than anode voltage) and hence circuit reduces to the circuit shown in figure 2

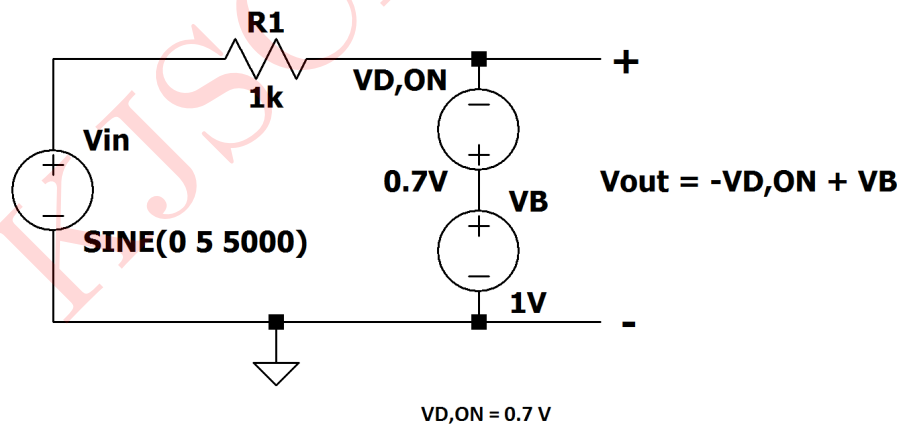


Figure 2: When diode is ON

$$V_{out} = -V_{D_{on}} + V_B = -0.7 + 1 = 0.3V$$

$$V_{out} = 0.3V$$

→ If $V_{in} > (-V_{D1_{on}} + V_B)$, diode D_1 is OFF (as anode voltage is greater than cathode voltage) and hence circuit reduces to the circuit shown in figure 3

 


Figure 3: When diode is OFF

∴ $V_{out} = V_{in}$ [i.e. output follows the input]

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

 


Figure 4: Circuit Schematic 1

 


Figure 5: Input & Output waveform

 


Figure 6: VTC Curve

From the above waveforms, we could conclude that the clipper circuit was a negative biased shunt (parallel) clipper.

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
level of clipped voltage	0.3V	0.33V

Table 1: Question 1

Numerical 2:

For the circuit shown in figure 8, Plot: Input $V_{in}(t)$ and output $V_{out}(t)$ waveforms
Given: $V_{in}(t) = 16 \text{ Vp-p}$ sinusoidal signal with frequency of 1000Hz .

 


Figure 7: Input

 


Figure 8: Circuit 2

Solution:

The given diode D_1 is silicon diode, hence $V_{D1_{on}} = 0.7V$

→ If $V_{in} > (V_{D1_{on}} + V_B)$, i.e. $V_{in} > 4.7V$ diode D_1 is ON (as anode voltage is greater than cathode voltage) and hence circuit reduces to the circuit shown in figure 9

 


Figure 9: When diode is ON

$$V_{out} = V_{D1_{on}} = 0.7V$$

$$V_{out} = 0.7V$$

→ If $V_{in} < (V_{D1_{on}} + V_B)$, i.e. $V_{in} < 4.7V$ diode D_1 is OFF and hence circuit reduces to the circuit shown in figure 10

 


Figure 10: When diode is OFF

Applying KVL to the input loop:

$$V_{in} - IR_1 - V_B - V_{out} = 0$$

$$V_{out} = V_{in} - V_B$$

$$V_{out} = V_{in} - 4$$

Minimum value of V_{out} is when $V_{in} = -8V$

$$V_{out} = -8 - 4 = -12V$$

$$\therefore V_{out} = -12V$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

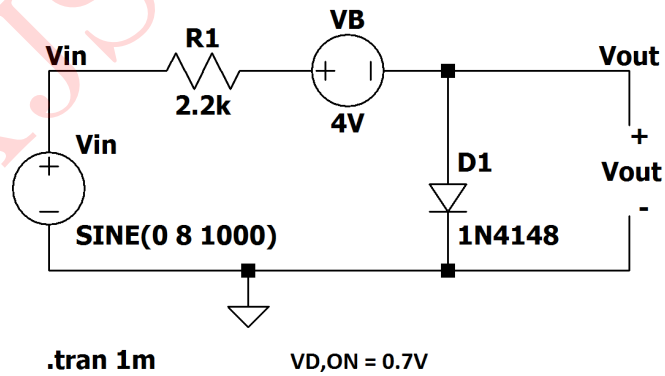


Figure 11: Circuit Schematic 2

 


Figure 12: Input & Output waveform

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
Minimum level of clipped voltage	0.7V	0.604V

Table 2: Question 2

Numerical 3:

For the circuit shown in figure 14, Plot: Input $V_{in}(t)$ and output $V_{out}(t)$ waveforms

Given: $V_{in}(t) = 16$ Vp-p square wave with frequency of 1000Hz. $C_1 = 10\mu\text{F}$, $R_1 = 10k\Omega$, diode D_1 is Silicon diode hence, $V_{D1ON} = 0.7V$ & $V_B = 2.7V$

 


Figure 13: Input waveform

 


Figure 14: Circuit 3

Solution:

The given diode D_1 is silicon diode, hence $V_{D1ON} = 0.7V$

Also, $V_{in} = 10$ Vp-p i.e. $V_{max} = 5V$

Assumptions:-

$$RC = 10 \times 10^3 \times 10 \times 10^{-6} = 0.1s = 100ms$$

Time period of input signal = 1ms

RC time constant is large enough (than time period of input signal) so that voltage across capacitor does not discharge significantly during the period, The diode is OFF

→ If $V_{in} > (V_{D1_{ON}} - V_B)$, i.e. $V_{in} > -2V$ diode D_1 is ON(as anode voltage is greater than cathode voltage) and hence circuit reduces to the circuit shown in figure 15

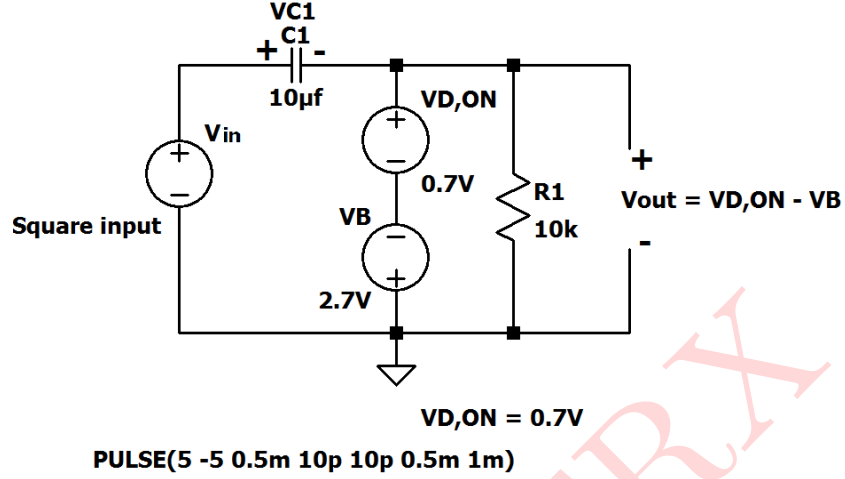


Figure 15: When diode is ON

$$V_{out} = V_{D1_{ON}} - V_B = 0.7V - 2.7V = -2V$$

$$V_{out} = -2V$$

At the same time, C_1 charges and voltage across capacitor V_{C1} reaches upto V_{max}

Applying KVL to the input loop:-

$$V_{in} - V_{C1} - V_{D1_{on}} + V_B = 0$$

$$V_{C1} = V_{in} - 0.7 + 2.7 = V_{max} + 2 = 5 + 2 = 7V$$

i.e. Voltage across capacitor during positive half cycle

→ If $V_{in} < (V_{D1_{ON}} - V_B)$, i.e. $V_{in} < -2V$ diode D_1 is OFF and hence circuit reduces to the circuit shown in figure 16

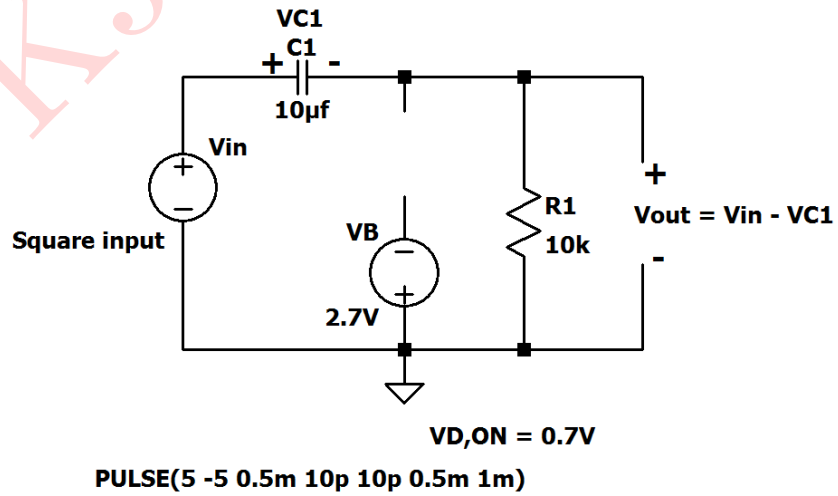


Figure 16: When diode is OFF

During negative half cycle, capacitor holds the charges, $V_{C_1} = 7V$ and act as battery

Applying KVL to the input loop:

$$-V_{in} - V_{C_1} - V_{out} = 0$$

$$V_{out} = -V_{in} - V_{C_1}$$

$$V_{out} = -V_{in} - 7$$

Minimum value of V_{out} is when $V_{in} = -5V$

$$V_{out} = -5 - 7 = -12V$$

$$\therefore V_{out} = -12V$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

 


Figure 17: Circuit Schematic 3

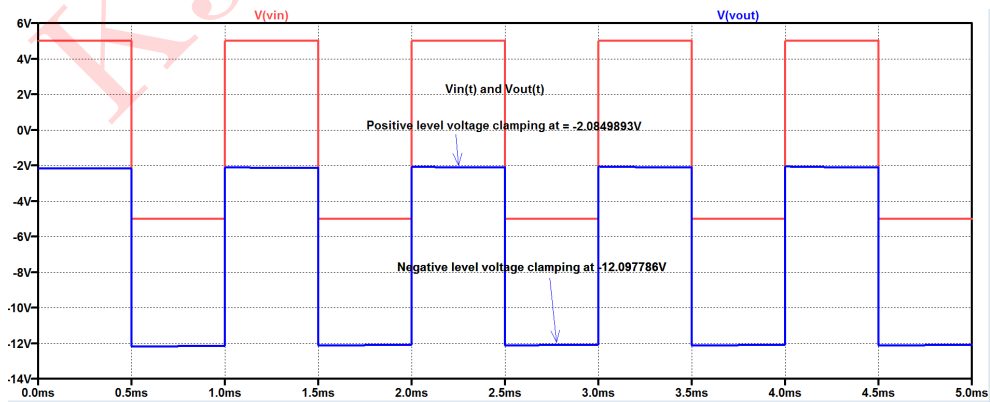


Figure 18: Input & Output waveform

Since, the output waveform is shifted down of the x-axis, the given circuit is negative clamper.

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
Positive level voltage clamping	$-2V$	$-2.084V$
Negative level voltage clamping	$-12V$	$-12.09V$

Table 3: Question 3

KJSCE ETRX