

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Multi-transistor Circuits

Numerical 1:

Calculate the voltage gain of each stage and the overall AC voltage gain for the BJT cascade amplifier circuit shown in figure 1. Given $\beta_1 = 150$ & $\beta_2 = 150$

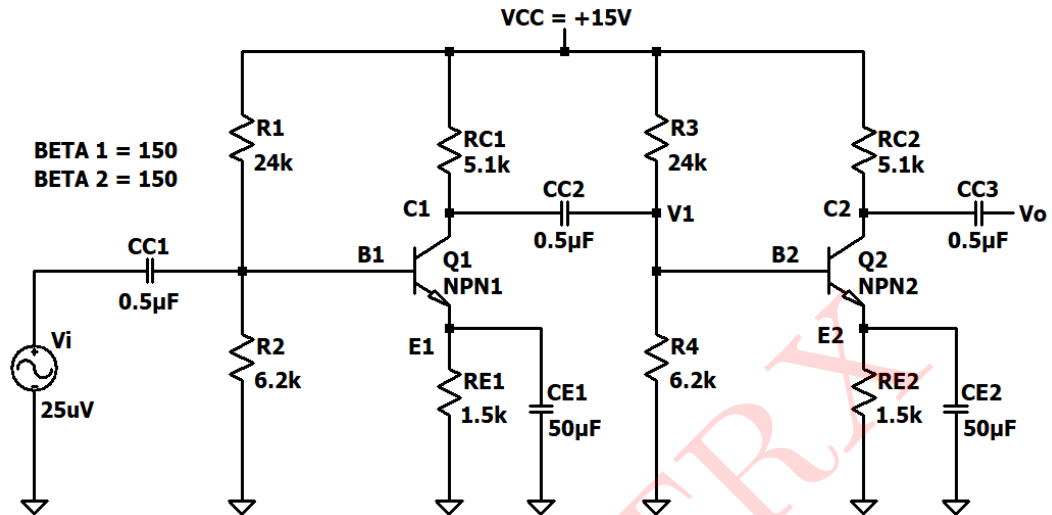


Figure 1: Circuit 1

Solution:

DC Analysis:

Due to R-C coupling, both the stages Q point are isolated.

Since both stages are symmetric in parameters & resistor values, DC analysis of one stage is sufficient

For DC analysis all the capacitors are open circuited, since $f = 0Hz$

Hence the circuit becomes,

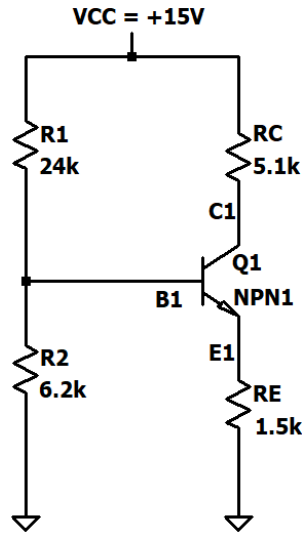


Figure 2: DC Equivalent Circuit

Applying Thevenin's theorem at the base of the transistor,

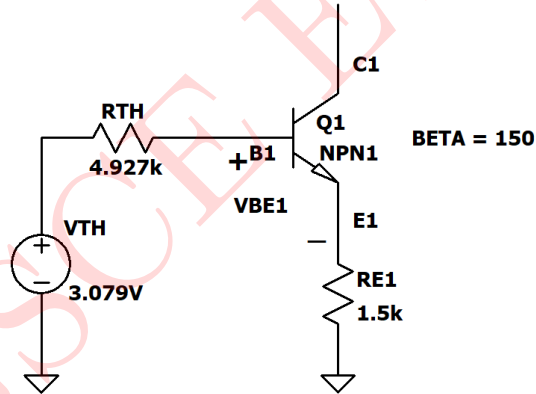


Figure 3: Thevenin's Equivalent Circuit

$$\begin{aligned}
 V_{TH} &= \frac{R_2 \times V_{CC}}{R_1 + R_2} \\
 &= \frac{6.2k\Omega \times 15V}{24k\Omega + 6.2k\Omega} \\
 &= \mathbf{3.079V}
 \end{aligned}$$

$$\begin{aligned}
 R_{TH} &= R_1 \parallel R_2 \\
 &= 24k\Omega \parallel 6.2k\Omega \\
 &= \mathbf{4.927k\Omega}
 \end{aligned}$$

Applying KVL to input Base Emitter loop,

$$V_{TH} - I_{B1Q}R_{TH} - V_{BE1} - I_{E1Q}R_{E1} = 0$$

$$V_{TH} - I_{B1Q}R_{TH} - V_{BE1} - (1 + \beta_1)I_{B1Q}R_{E1} = 0$$

[Since, $I_E = (1 + \beta)I_B$]

$$\begin{aligned}
I_{B1Q} &= \frac{V_{TH} - V_{BE1}}{R_{TH} + (1 + \beta_1)R_{E1}} \\
&= \frac{3.079 - 0.7}{4.927k\Omega + (151) \times 1.5k\Omega} \\
&= \mathbf{10.279\mu A}
\end{aligned}$$

$$I_{C1Q} = \beta_1 I_{B1Q} = 150 \times 10.279\mu A = \mathbf{1.54mA}$$

Applying KVL to output Collector Emitter loop,

$$V_{CC} - I_{C1Q}R_{C1} - V_{CE1Q} - I_{C1Q}R_{E1} = 0$$

$$\begin{aligned}
V_{CE1Q} &= V_{CC} - I_{C1Q}(R_{C1} + R_{E1}) \\
&= 15V - (1.54mA)(5.1k\Omega + 1.5k\Omega) \\
&= 15V - 10.225V \\
&= \mathbf{4.775V}
\end{aligned}$$

Small Signal Parameters:

$$r_{o1} = r_{o2} = \infty$$

[Assumption]

$$\begin{aligned}
r_{\pi1} &= \frac{\beta_1 V_T}{I_{C1Q}} \\
&= \frac{150 \times 0.026V}{1.54mA} \\
&= \mathbf{2.532k\Omega}
\end{aligned}$$

$$\begin{aligned}
g_{m1} &= \frac{I_{C1Q}}{V_T} \\
&= \frac{1.54mA}{26mV} \\
&= \mathbf{59.23mA/V}
\end{aligned}$$

Since both stages are identical,

$$r_{\pi1} = r_{\pi2} = \mathbf{2.532k\Omega} \quad \& \quad g_{m1} = g_{m2} = \mathbf{59.23mA/V}$$

Mid Band AC Equivalent Circuit:

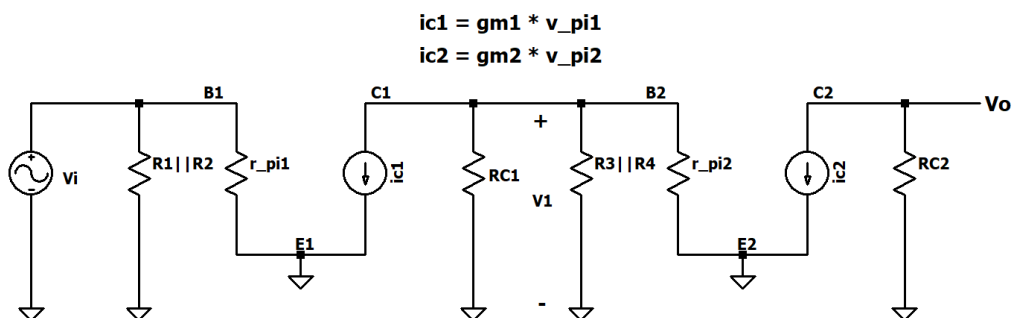


Figure 4: Small Signal Equivalent Circuit

Voltage gain of first stage: $Av_1 = \frac{V_1}{V_i}$

$$Av_1 = \frac{V_1}{V_i} = \frac{-g_{m1}V_{\pi_1}(R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi_2})}{V_{\pi_1}}$$

$$\begin{aligned} Av_1 &= -g_{m1}(R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi_2}) \\ &= -(59.23mA/V)(5.1k\Omega \parallel 24k\Omega \parallel 6.2k\Omega \parallel 2.532k\Omega) \\ &= -(59.23mA/V)(1259.477\Omega) \\ &= \mathbf{-74.59} \end{aligned}$$

Voltage gain of second stage: $Av_2 = \frac{V_o}{V_1}$

$$Av_2 = \frac{V_o}{V_1} = \frac{-g_{m2}V_{\pi_2}(R_{C2})}{V_{\pi_2}}$$

$$\begin{aligned} Av_2 &= -g_{m2}(R_{C2}) \\ &= -(59.23mA/V)(5.1k\Omega) \\ &= \mathbf{-302} \end{aligned}$$

Input Impedance of first stage (Z_i):

$$\begin{aligned} Z_i &= R_1 \parallel R_2 \parallel r_{\pi_1} \\ &= 24k\Omega \parallel 6.2k\Omega \parallel 2.532k\Omega \\ &= \mathbf{1.672k\Omega} \end{aligned}$$

Output Impedance of second stage (Z_o):

$$\begin{aligned} Z_o &= R_{C2} \\ &= \mathbf{5.1k\Omega} \end{aligned}$$

Overall Voltage Gain: $A_{V_T} = \frac{V_o}{V_i}$

$$A_{V_T} = \frac{V_o}{V_i} = \frac{V_1}{V_i} \times \frac{V_o}{V_1}$$

$$\begin{aligned} \therefore A_{V_T} &= A_{V_1} \times A_{V_2} \\ &= (-74.59) \times (-302) \\ &= \mathbf{22526.18} \end{aligned}$$

$$\begin{aligned} |A_{V_T}| \text{ in dB} &= 20 \log_{10}(A_{V_T}) \\ &= 20 \log_{10}(22526.18) \\ &= \mathbf{87.05dB} \end{aligned}$$

Output Voltage (V_o):

$$A_{V_T} = \frac{V_o}{V_i} \implies V_o = A_{V_T} \times V_i$$

$$V_i = 25\mu V \quad [\text{peak to peak}]$$

$$\begin{aligned} \therefore V_o &= A_{V_T} \times V_i \\ &= 22526.18 \times 25\mu V \\ &= 0.563V \end{aligned}$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

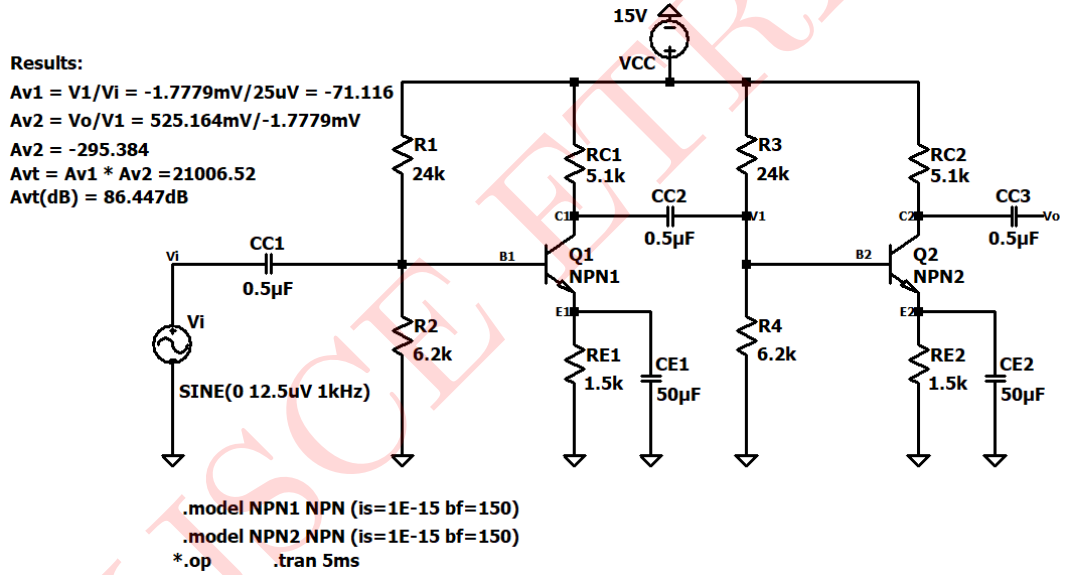


Figure 5: Circuit Schematic

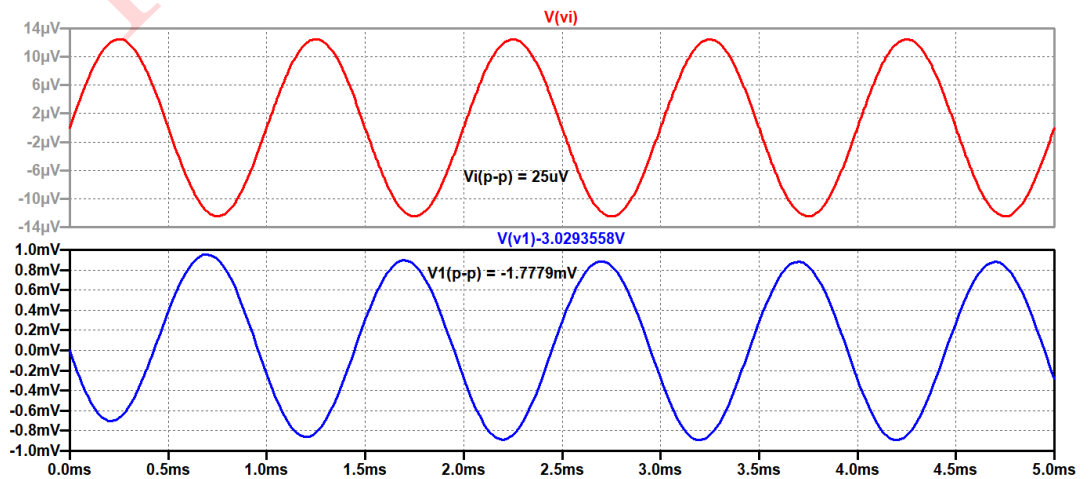


Figure 6: Input Output waveforms of 1st stage

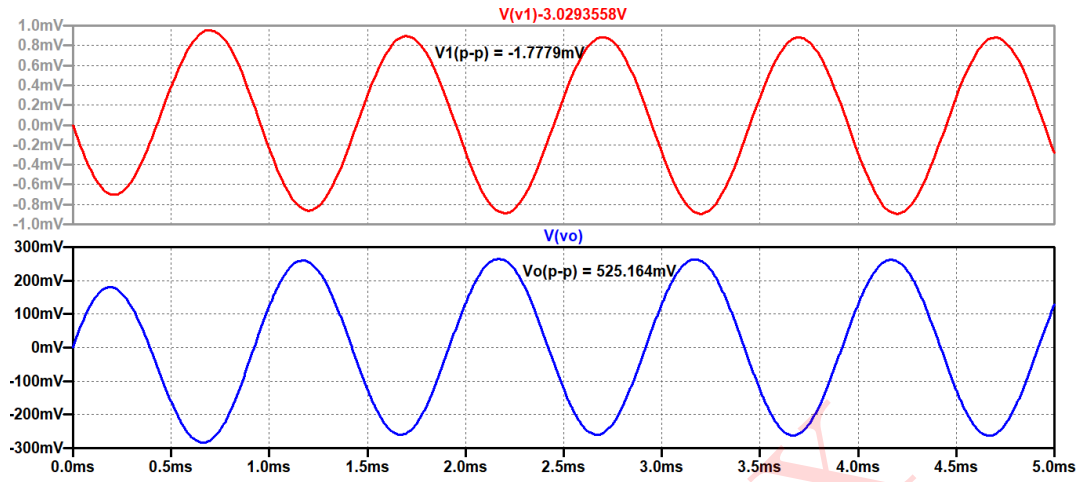


Figure 7: Input Output waveforms of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
Q point: I_{C1Q}, V_{CE1Q}	1.54mA, 4.775V	1.525mA, 4.916V
Q point: I_{C2Q}, V_{CE2Q}	1.54mA, 4.775V	1.525mA, 4.916V
Voltage gain of 1st stage: Av_1	-74.59	-71.116
Voltage gain of 2nd stage: Av_2	-302	-295.384
Overall Voltage gain: Av_T	22526.18	21006.52
Input Impedance of 1st stage: Z_i	1.672k Ω	—
Output Impedance of 2nd stage: Z_o	5.1k Ω	—
Output Voltage	0.563V	0.525V
Overall voltage gain Av_T in dB	87.05dB	86.447dB

Table 1: Numerical 1

Numerical 2:

For the JFET cascade amplifier given in figure 8, using identical JFET's with $I_{DSS} = 8mA$ & $V_p = -4.5V$, calculate the voltage gain of each stage, the overall gain of the amplifier & the output voltage V_o .

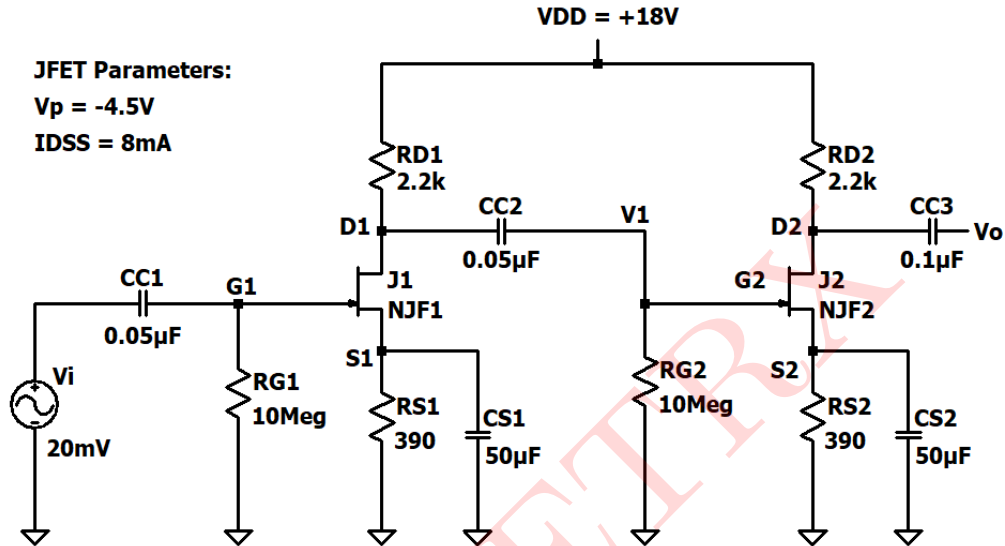


Figure 8: Circuit 2

Solution: Since both stages of given amplifier are symmetric, DC analysis of single stage is sufficient

DC Analysis:

For DC analysis all the capacitors will get open circuited as $f = 0Hz$

Thus the circuit becomes,

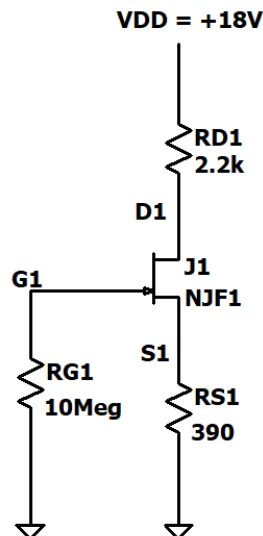


Figure 9: DC Equivalent Circuit

$$\begin{aligned}
V_{GS_1} &= V_{G_1} - V_{S_1} \\
&= 0 - I_{D_1} R_{S_1} & [\because I_G = 0] \\
&= -I_{D_1} (390) \\
&= -390 I_{D_1} & \dots(1)
\end{aligned}$$

$$\begin{aligned}
I_{D_1} &= I_{DSS} \left(1 - \frac{V_{GS_1}}{V_p} \right)^2 \\
&= (8mA) \left(1 + \frac{V_{GS_1}}{4.5} \right)^2 & \dots(2)
\end{aligned}$$

Substituting equation (2) in equation (1),

$$\begin{aligned}
V_{GS_1} &= -3.12 \left(1 + \frac{V_{GS_1}}{4.5} \right)^2 \\
&= -3.12 (1 + 0.44 V_{GS_1} + 0.0493 V_{GS_1}^2) \\
&= -3.12 - 1.3728 V_{GS_1} - 0.1538 V_{GS_1}^2
\end{aligned}$$

$$0.1538 V_{GS_1}^2 + 2.3728 V_{GS_1} + 3.12 = 0$$

$$V_{GS_1} = -1.45V \quad \text{or} \quad V_{GS_1} = -13.976V$$

$$\because V_{GS} > V_p, \therefore V_{GSQ_1} = -1.45V$$

$$\begin{aligned}
I_{DQ_1} &= I_{DSS} \left(1 - \frac{V_{GSQ_1}}{V_p} \right)^2 \\
&= (8mA) \left(1 - \frac{(-1.45V)}{-4.5V} \right)^2 \\
&= \mathbf{3.675mA}
\end{aligned}$$

Since both stages are identical

$$\therefore V_{GSQ_1} = V_{GSQ_2} \quad \& \quad I_{DQ_1} = I_{DQ_2}$$

Small Signal Parameter:

$$\begin{aligned}
g_{m_1} &= \frac{2I_{DSS}}{|V_p|} \left(1 - \frac{V_{GSQ_1}}{V_p} \right) \\
&= \frac{2 \times 8mA}{4.5} \left(1 - \frac{(-1.45V)}{-4.5V} \right) \\
&= \mathbf{2.4mA/V}
\end{aligned}$$

\therefore Both stages are identical,

$$\therefore g_{m_1} = g_{m_2}$$

Mid frequency AC Equivalent Circuit:

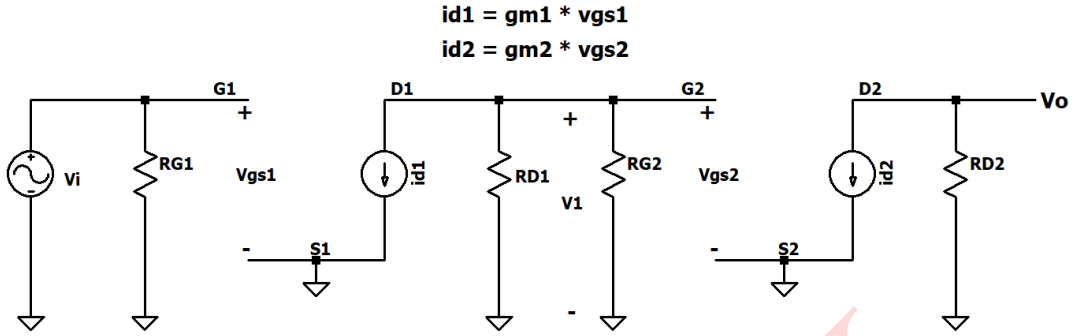


Figure 10: Small Signal Equivalent Circuit

Gain of 1st stage: $Av_1 = \frac{V_1}{V_i}$

$$Av_1 = \frac{V_1}{V_i} = \frac{(-g_{m1} V_{gs1})(R_{D1} \parallel R_{G2})}{V_{gs1}}$$

$$\begin{aligned} Av_1 &= -g_{m1}(R_{D1} \parallel R_{G2}) \\ &= -(2.4mA/V)(2.2k\Omega \parallel 10M\Omega) \\ &= -(2.4mA/V)(2.199k\Omega) \\ &= \mathbf{-5.28} \end{aligned}$$

Gain of 2nd stage: $Av_2 = \frac{V_o}{V_1}$

$$\begin{aligned} Av_2 &= \frac{(-g_{m2} V_{gs2})(R_{D2})}{V_{gs2}} \\ &= -g_{m2} R_{D2} \\ &= -(2.4mA/V)(2.2k\Omega) \\ &= \mathbf{-5.28} \end{aligned}$$

Overall Voltage Gain: $Av_T = \frac{V_o}{V_i}$

$$Av_T = \frac{V_1}{V_i} \times \frac{V_o}{V_1}$$

$$\begin{aligned} \therefore Av_T &= Av_1 \times Av_2 \\ &= (-5.28) \times (-5.28) \\ &= \mathbf{27.8784} \end{aligned}$$

$$\begin{aligned} |Av_T| \text{ in dB} &= 20 \log_{10}(Av_T) \\ &= \mathbf{28.9dB} \end{aligned}$$

Input Impedance of 1st stage (Z_i):

$$Z_i = R_{G1} = 10M\Omega$$

$$\therefore Z_i = 10M\Omega$$

Output Impedance of 2nd stage (Z_o):

$$Z_o = R_{o2}$$

$$\therefore Z_o = 2.2k\Omega$$

Output Voltage (V_o):

$$A_{V_T} = \frac{V_o}{V_i} \implies V_o = A_{V_T} \times V_i$$

$$\therefore V_o = 27.8784 \times (20mV) = 0.5575V$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

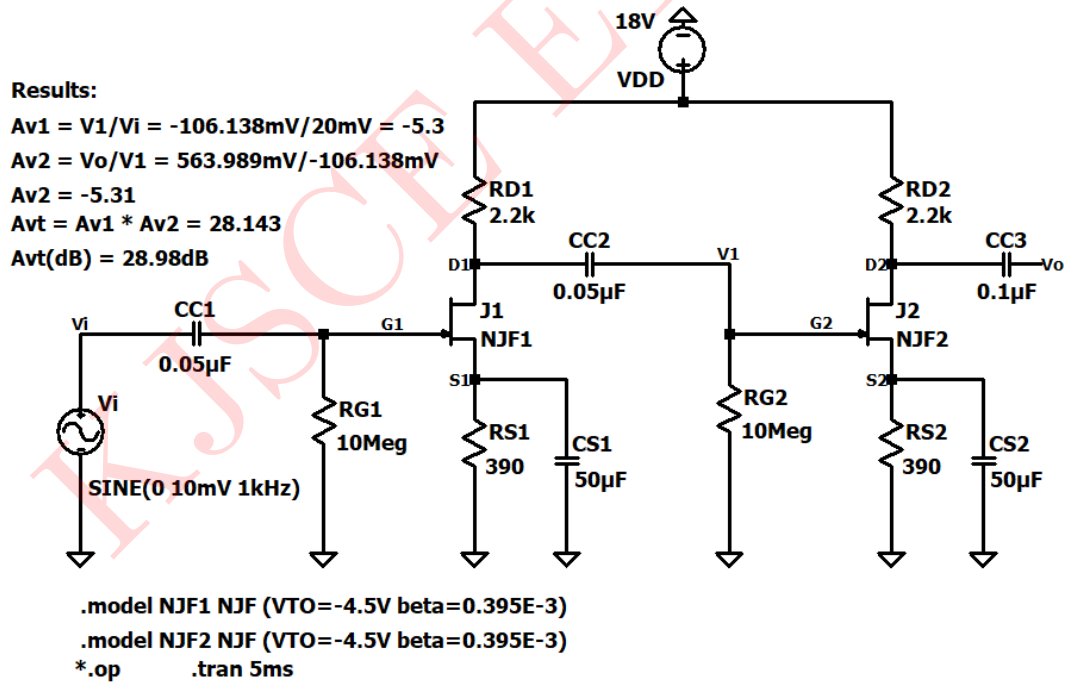


Figure 11: Circuit Schematic

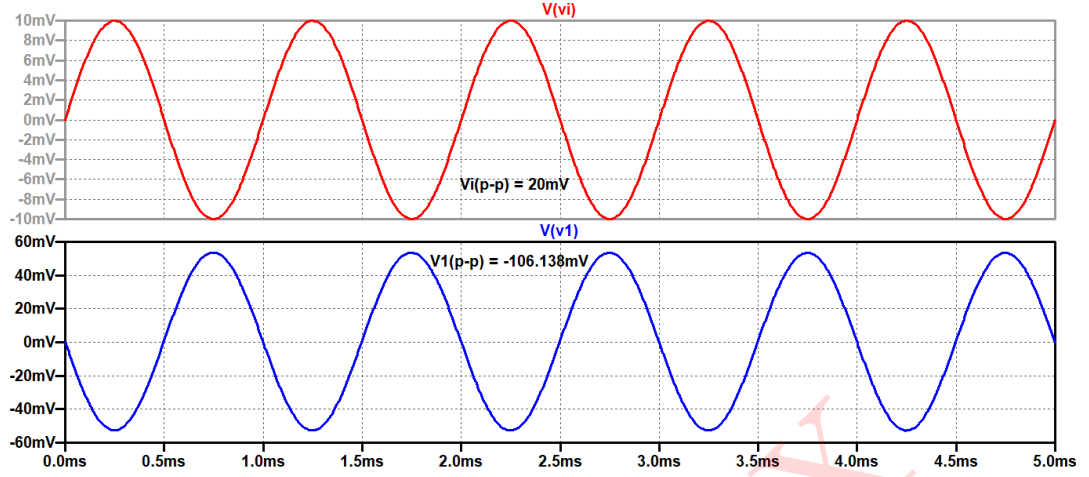


Figure 12: Input Output waveforms of 1st stage

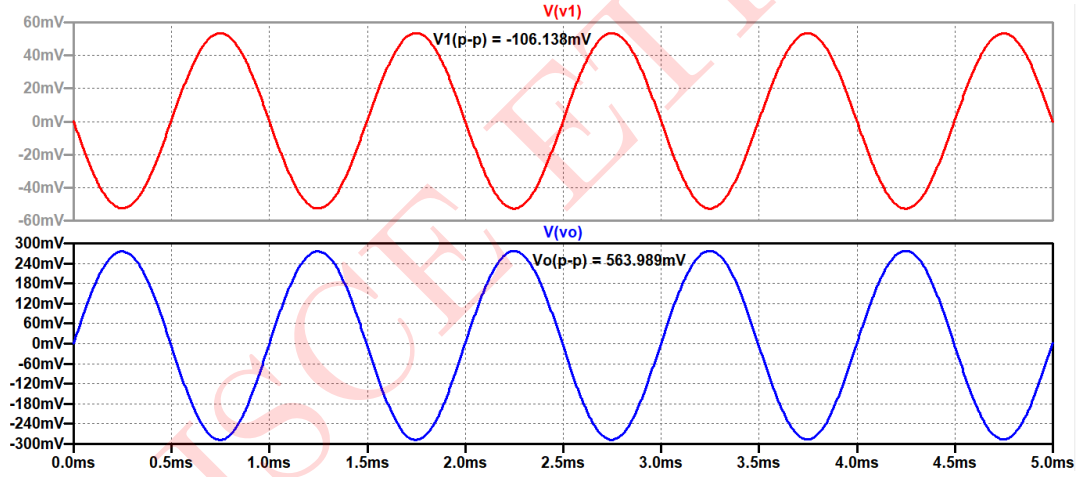


Figure 13: Input Output waveforms of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
Q point: I_{DQ1}, V_{GSQ1}	$3.675mA, -1.45V$	$3.69mA, -1.44V$
Q point: I_{DQ2}, V_{GSQ2}	$3.675mA, -1.45V$	$3.69mA, -1.44V$
Voltage gain of 1st stage: Av_1	-5.28	-5.3
Voltage gain of 2nd stage: Av_2	-5.28	-5.31
Overall Voltage gain: Av_T in dB	28.9dB	28.98dB
Input Impedance of 1st stage: Z_i	10M Ω	—
Output Impedance of 2nd stage: Z_o	2.2k Ω	—
Output Voltage: V_o	0.5575V	0.5639V

Table 2: Numerical 2

Numerical 3:

Determine the small signal voltage gain of the multitransistor circuit shown in figure 14.
Given $\beta_1 = 150$ & $\beta_2 = 200$

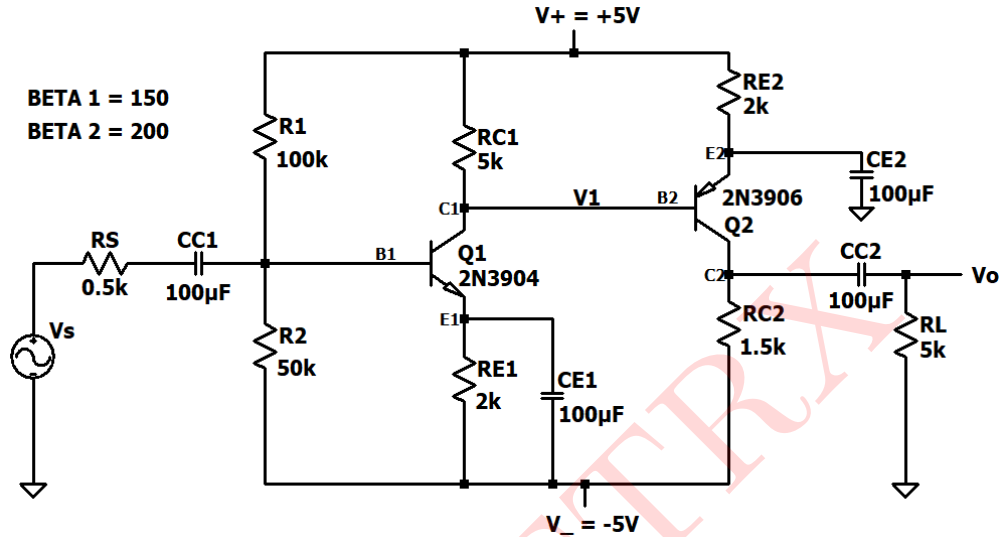


Figure 14: Circuit 3

Solution:

From datasheet,

For 2N3904, $\beta_1 = 150$, $V_{BE} = 0.7V$ & For 2N3906, $\beta_2 = 200$, $V_{EB} = 0.7V$

DC Analysis:

For DC analysis we will short circuit all the capacitors, since frequency is $0Hz$

Thus the circuit becomes,

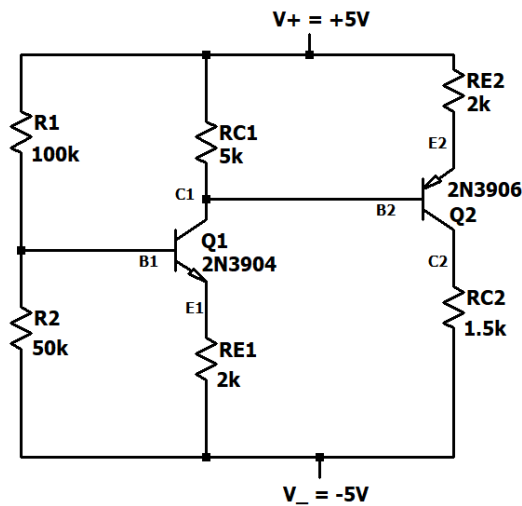


Figure 15: DC Equivalent Circuit

Considering the Thevenin's Equivalent of base circuit of transistor Q_1

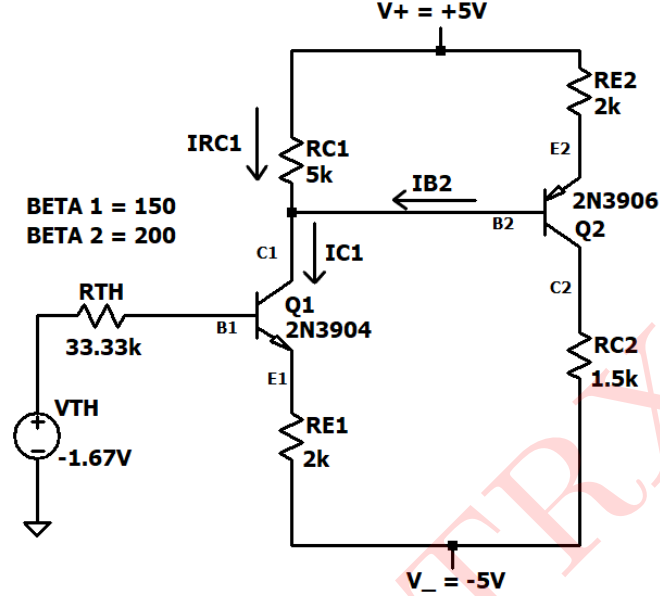


Figure 16: DC Equivalent Circuit with Thevenin's Equivalent Circuit

$$\begin{aligned}
 V_{TH} &= \frac{R_2}{R_1 + R_2}(V_+ - V_-) - V_- \\
 &= \frac{50k\Omega}{100k\Omega + 50k\Omega} \times (10V - 5V) \\
 &= \mathbf{-1.67V}
 \end{aligned}$$

$$\begin{aligned}
 R_{TH} &= R_1 \parallel R_2 \\
 &= 100k\Omega \parallel 50k\Omega \\
 &= \mathbf{33.33k\Omega}
 \end{aligned}$$

Applying KVL to Base Emitter loop of Q_1 ,

$$V_{TH} - I_{B1}R_{TH} - V_{BE1} - I_{E1}R_{E1} = V_-$$

$$V_{TH} - I_{B1}R_{TH} - V_{BE1} - (1 + \beta_1)I_{B1}R_{E1} - V_- = 0 \quad [\text{Since, } I_E = (1 + \beta)I_B]$$

$$\begin{aligned}
 I_{B1} &= \frac{V_{TH} - V_{BE1} - V_-}{R_{TH} + (1 + \beta_1)R_{E1}} \\
 &= \frac{-1.67 - 0.7 + 5}{33.33k\Omega + (151) \times 2k\Omega} \\
 &= \mathbf{7.84\mu A}
 \end{aligned}$$

$$I_{C1} = \beta_1 I_{B1} = 150 \times 7.84\mu A = \mathbf{1.176mA}$$

$$I_{E1} = I_{C1} + I_{B1} = 1.176 + 7.84 = \mathbf{1.183mA}$$

$$\begin{aligned}
 V_{C1} &= V_{CC} - I_{C1}R_{C1} \quad [\text{Ignoring } I_{B2} \text{ \& } I_{RC1} \cong I_{C1}] \\
 &= 5 - (1.176mA \times 5k\Omega) \\
 &= \mathbf{-0.88V}
 \end{aligned}$$

$$\begin{aligned}
V_{E_2} &= V_{B_2} + V_{EB_2} \\
&= V_{C_1} + V_{EB_2} & [\because V_{C_1} = I_{B_2}] \\
&= -0.88 + 0.7 \\
&= \mathbf{-0.18V}
\end{aligned}$$

$$\begin{aligned}
I_{E_2} &= \frac{V_+ - V_{E_2}}{R_{E_2}} \\
&= \frac{5 - (-0.18)}{2k\Omega} \\
&= \mathbf{2.59mA}
\end{aligned}$$

$$\begin{aligned}
I_{C_2} &= \frac{\beta_2}{1 + \beta_2} I_{E_2} \\
&= \frac{200}{1 + 200} \times 2.59mA \\
&= \mathbf{2.577mA}
\end{aligned}$$

$$\begin{aligned}
I_{B_2} &= \frac{I_{E_2}}{1 + \beta_2} \\
&= \frac{2.59}{1 + 200} \\
&= \mathbf{12.88\mu A}
\end{aligned}$$

Now, rewriting the exact expression for equation (1),

$$V_{C_1} = V_{CC} - I_{RC_1} R_{C_1}$$

$$I_{RC_1} = I_{C_1} - I_{B_2} = 1.176mA - 12.88\mu A = \mathbf{1.163mA}$$

$$\begin{aligned}
V_{C_1} &= V_+ - I_{RC_1} R_{C_1} \\
&= 5 - (1.163mA \times 5k\Omega) \\
&= \mathbf{-0.815V}
\end{aligned}$$

$$\begin{aligned}
V_{E_2} &= V_{B_2} + V_{EB_2} \\
&= V_{C_1} + V_{EB_2} & [\because V_{C_1} = V_{B_2}] \\
&= -0.815 + 0.7 \\
&= \mathbf{-0.115V}
\end{aligned}$$

$$\begin{aligned}
I_{E_2} &= \frac{V_+ - V_{E_2}}{R_{C_2}} \\
&= \frac{5 - (-0.115)}{2k\Omega} \\
&= \mathbf{2.5575mA}
\end{aligned}$$

$$\begin{aligned}
I_{C_2} &= \frac{\beta_2}{1 + \beta_2} I_{E_2} \\
&= \frac{200}{1 + 200} \times 2.5575mA = \mathbf{2.544mA}
\end{aligned}$$

$$\begin{aligned}
I_{B_2} &= \frac{I_{E_2}}{1 + \beta_2} \\
&= \frac{2.5575}{1 + 200} \\
&= \mathbf{12.72\mu A}
\end{aligned}$$

$$\begin{aligned}
V_{E_1} &= I_{E_1} R_{E_1} + V_- \\
&= (1.183mA \times 2k\Omega) - 5 \\
&= \mathbf{-2.634V}
\end{aligned}$$

$$\begin{aligned}
V_{CE_1} &= I_{C_1} - V_{E_1} \\
&= -0.815 - (-2.634) \\
&= \mathbf{1.819V}
\end{aligned}$$

$$\begin{aligned}
V_{C_2} &= I_{C_2} R_{C_2} - V_- \\
&= (2.544mA \times 1.5k\Omega) - 5 \\
&= \mathbf{-1.184V}
\end{aligned}$$

$$\begin{aligned}
V_{EC_2} &= V_{E_2} - V_{C_2} \\
&= -0.115 - (-1.184) \\
&= \mathbf{1.069V}
\end{aligned}$$

Node Voltages:

$$\begin{aligned}
V_{B_1} &= -1.934V, V_{C_1} = -0.815V, V_{E_1} = -2.634V \\
V_{C_2} &= -1.184V, V_{E_1} = -0.115V, V_{B_1} = -0.815V
\end{aligned}$$

Terminal Currents:

$$\begin{aligned}
I_{B_1} &= 7.84\mu A, I_{C_1} = 1.176mA, I_{E_1} = 1.183mA \\
I_{B_2} &= 12.72\mu A, I_{C_2} = 2.544mA, I_{E_2} = 2.5575mA
\end{aligned}$$

AC Equivalent Circuit:

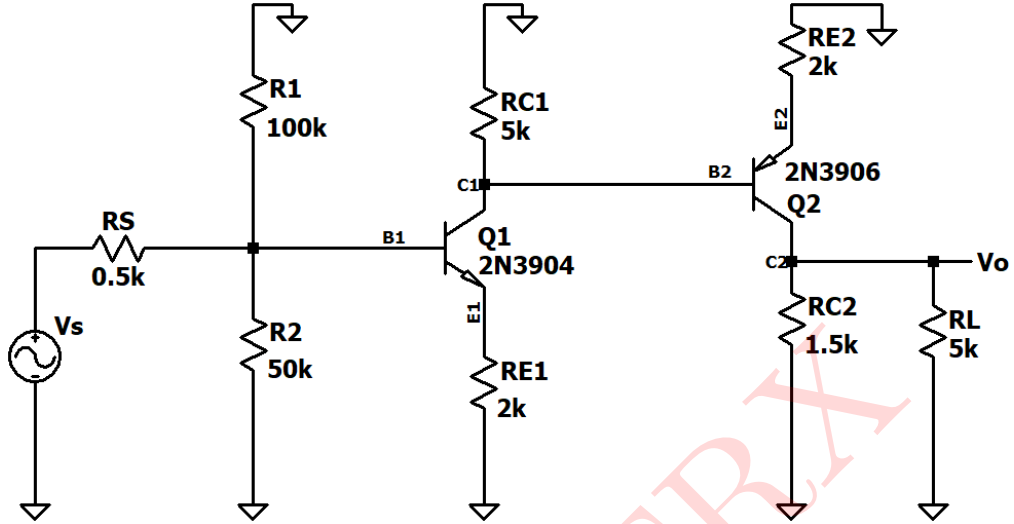


Figure 17: AC Equivalent Circuit

Small Signal Parameters:

$$\begin{aligned}
 g_{m1} &= \frac{I_{C1}}{V_T} \\
 &= \frac{1.176mA}{26mV} \\
 &= \mathbf{45.23mA/V}
 \end{aligned}$$

$$\begin{aligned}
 r_{\pi1} &= \frac{\beta_1 V_T}{I_{C1}} \\
 &= \frac{150 \times 26mV}{1.176mA} \\
 &= \mathbf{3.316k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 g_{m2} &= \frac{I_{C2}}{V_T} \\
 &= \frac{2.544mA}{26mV} \\
 &= \mathbf{97.846mA/V}
 \end{aligned}$$

$$\begin{aligned}
 r_{\pi2} &= \frac{\beta_2 V_T}{I_{C2}} \\
 &= \frac{200 \times 0.026V}{2.544mA} \\
 &= \mathbf{2.044k\Omega}
 \end{aligned}$$

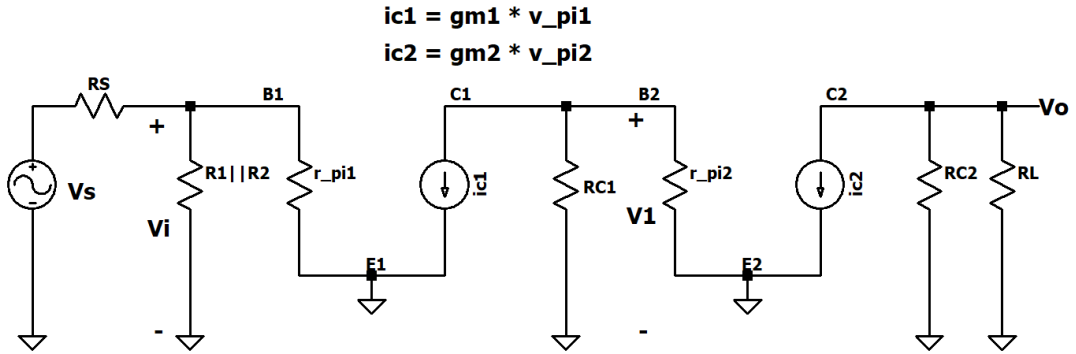


Figure 18: Small Signal Equivalent Circuit

$$A_{V_T} = \frac{V_o}{V_s} = \frac{V_o}{V_1} \times \frac{V_1}{V_s}$$

$$A_{v1} = \frac{V_1}{V_s} = \frac{V_1}{V_i} \times \frac{V_i}{V_s}$$

$$V_i = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} V_s$$

$$\frac{V_i}{V_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S}$$

$$\begin{aligned}
 A_{v1} &= \frac{-g_{m1} V_{\pi1} (R_{C1} \parallel r_{\pi2})}{V_{\pi1}} \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} \\
 &= -g_{m1} (R_{C1} \parallel r_{\pi2}) \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_S} \\
 &= -(45.23 \text{ mA/V}) \times (5 \text{ k}\Omega \parallel 2.044 \text{ k}\Omega) \times \frac{33.33 \text{ k}\Omega}{33.33 \text{ k}\Omega + 0.5 \text{ k}\Omega} \\
 &= -(45.23 \text{ mA/V}) \times (1.45 \text{ k}\Omega) \times (0.985) \\
 &= \mathbf{-64.599}
 \end{aligned}$$

$$\begin{aligned}
 A_{v2} &= \frac{V_o}{V_1} = \frac{-g_{m2} V_{\pi2} (R_{C2} \parallel R_L)}{V_{\pi2}} \\
 &= -g_{m2} (R_{C2} \parallel R_L) \\
 &= -(97.846 \text{ mA/V}) \times (1.5 \text{ k}\Omega \parallel 5 \text{ k}\Omega) \\
 &= -(97.846 \text{ mA/V}) \times (1.153 \text{ k}\Omega) \\
 &= \mathbf{-112.816}
 \end{aligned}$$

Overall Volatge Gain (A_{V_T}):

$$\begin{aligned}
 A_{V_T} &= A_{v1} \times A_{v2} \\
 &= (-64.599) \times (-112.816) \\
 &= \mathbf{7287.8}
 \end{aligned}$$

$$\begin{aligned}
A_{V_T} \text{ in dB} &= 20 \log_{10} (A_{V_T}) \\
&= 20 \log_{10} (7287.8) \\
&= \mathbf{77.251 \text{ dB}}
\end{aligned}$$

Output Voltage (V_o):

$$A_{V_T} = \frac{V_o}{V_i} \implies V_o = A_{V_T} \times V_i$$

$$V_i = 1 \mu V \quad [\text{peak to peak}]$$

$$\begin{aligned}
\therefore V_o &= A_{V_T} \times V_i \\
&= 7287.8 \times 1 \mu V \\
&= \mathbf{7.287 \text{ mV}} \quad [\text{peak to peak}]
\end{aligned}$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

Results:

$$Av1 = V1/Vi = -56.9 \mu V / 1 \mu V = -56.9$$

$$Av2 = V_o/V1 = 6.281 \text{ mV} / -56.9 \mu V = -110.38$$

$$Avt = Av1 \times Av2 = 6280.622$$

$$Avt(\text{dB}) = 75.96 \text{ dB}$$

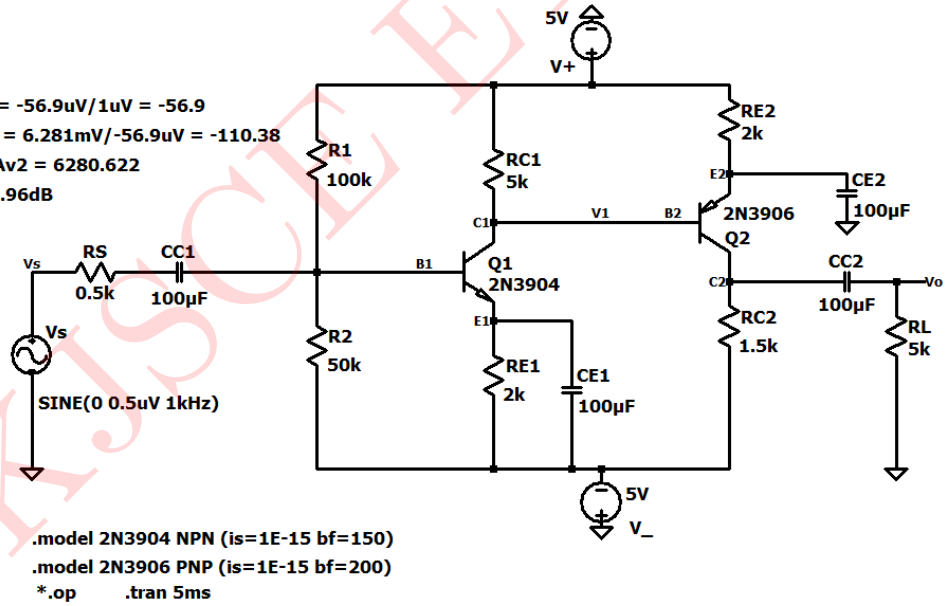


Figure 19: Circuit Schematic

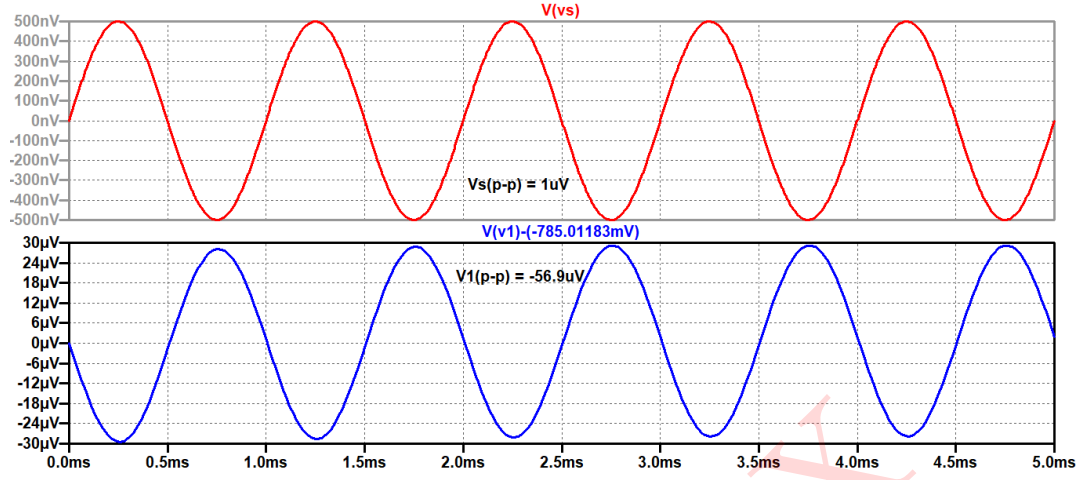


Figure 20: Input Output waveforms of 1st stage

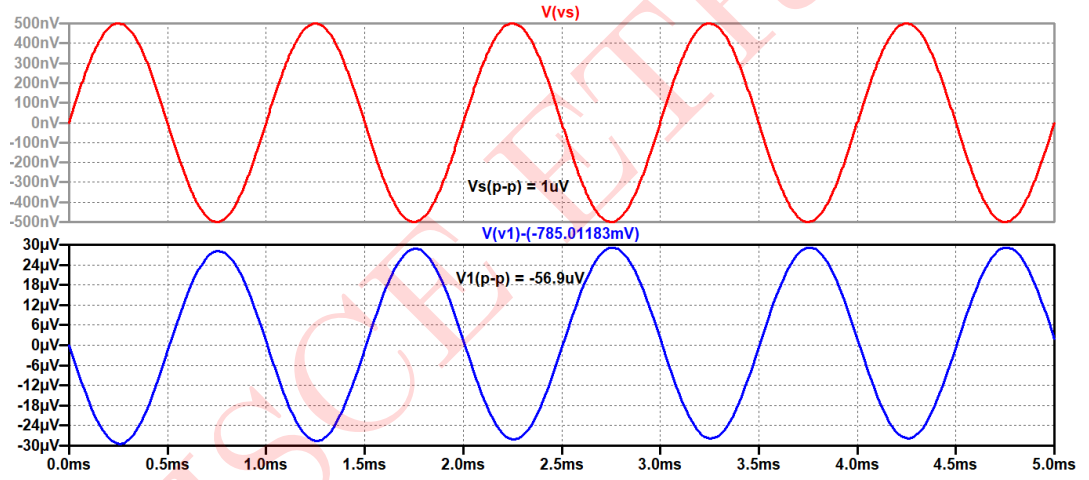


Figure 21: Input Output waveforms of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
I_{B1}	$7.84\mu A$	$7.797\mu A$
I_{C1}, I_{E1}	$1.176mA, 1.183mA$	$1.169mA, 1.177mA$
I_{B2}	$12.72\mu A$	$12.553\mu A$
I_{C2}, I_{E2}	$2.544mA, 2.5575mA$	$2.51mA, 2.523mA$
V_{C1}	$-0.815V$	$-0.785V$
V_{C2}	$-1.184V$	$-1.2339V$
V_{E1}	$-2.634V$	$-2.645V$
V_{E2}	$-0.115V$	$-0.0465V$
V_{B1}	$-1.934V$	$-1.9265V$
V_{B2}	$-0.815V$	$-0.785V$
A_{VT} in dB	77.25dB	75.96dB
V_o [peak to peak]	$7.287mV$	$6.281mV$

Table 3: Numerical 3
