

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELEMENTS OF ELECTRICAL AND ELECTRONICS ENGINEERING
DIODE APPLICATION

Numerical 1: Simulate a half wave rectifier circuit with input amplitude = $150V_{peak}$, $f = 50\text{Hz}$ and $R_L = 110\Omega$ using LTspice. Select diode as 1N4148. Use 10:1 step down transformer. Find output peak value(V_m), output peak current(I_m), AC power, DC power, efficiency, PIV rating.

Plot the following using LTspice,

- Primary peak voltage.
- Secondary peak voltage.
- Output voltage across resistor.
- Output voltage across diode.
- Current flowing through the circuit.

Solution:

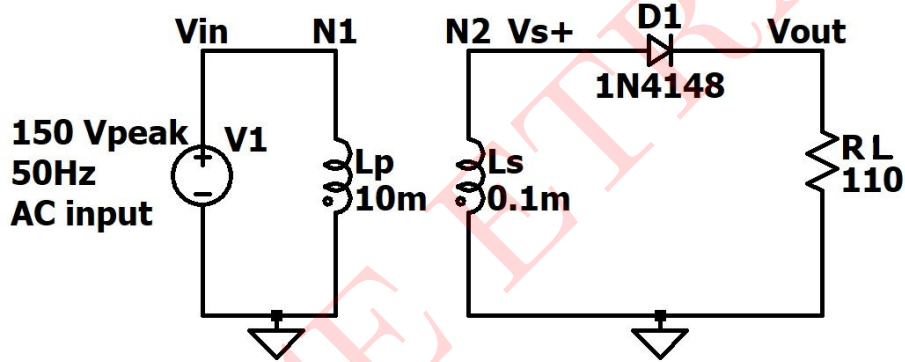


Figure 1: Circuit 1

i] We know that,

$$\frac{N_1}{N_2} = \frac{10}{1}$$

$$\therefore \frac{V_P}{V_S} = \frac{10}{1}$$

$$\therefore V_S = 150 \times \frac{1}{10}$$

$$\therefore V_S = 15V$$

ii] By KVL we get,

$$V_{in} - V_{DON} - V_{out} = 0$$

$$\therefore V_{out} = V_{in} - V_{DON} = 15 - 0.7$$

$$\therefore V_{out} = 14.3V$$

$$\text{i.e } V_m = 14.3V$$

$$\text{iii] } I_m = \frac{V_m}{R_S + R_L}$$

Since, $R_S \ll R_L$

$$\therefore I_m = \frac{V_m}{R_L}$$

$$\therefore I_m = \frac{14.3}{110}$$

$$\therefore I_m = 0.13\text{A} = 130\text{mA}$$

$$\text{iv] DC power} = \frac{V_m^2}{\pi^2 \times R_L}$$

$$\therefore \text{DC power} = \frac{14.3^2}{\pi^2 \times 110}$$

$$\therefore \text{DC power} = 0.1884\text{W}$$

$$\text{v] AC power} = \frac{V_m^2}{4 \times (R_S + R_L)}$$

$$\therefore \text{AC power} = \frac{14.3^2}{4 \times 110}$$

$$\therefore \text{AC power} = 0.46475\text{W}$$

$$\text{vi] Efficiency} = \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.1884}{0.46475} \times 100$$

$$\therefore \text{Efficiency} = \eta = 40\%$$

$$\text{vii] Peak inverse voltage(PIV) rating} = -V_m = -14.3\text{V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice. The results are presented below.

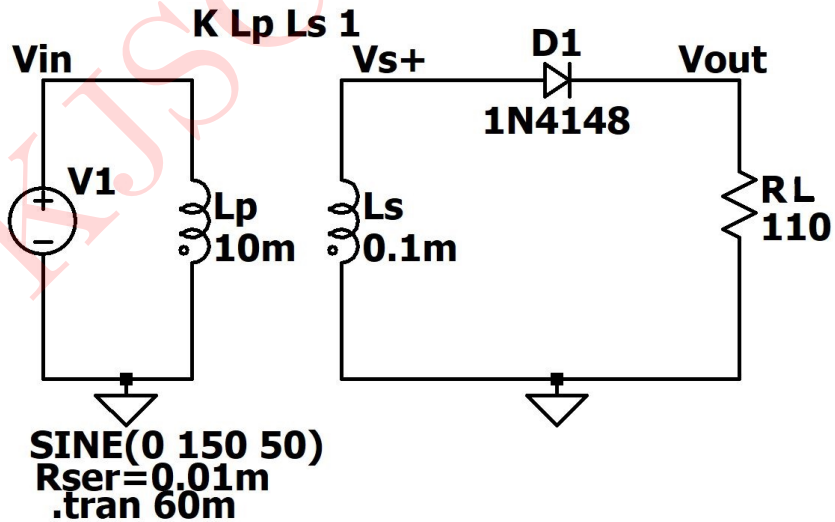


Figure 2: Circuit schematic

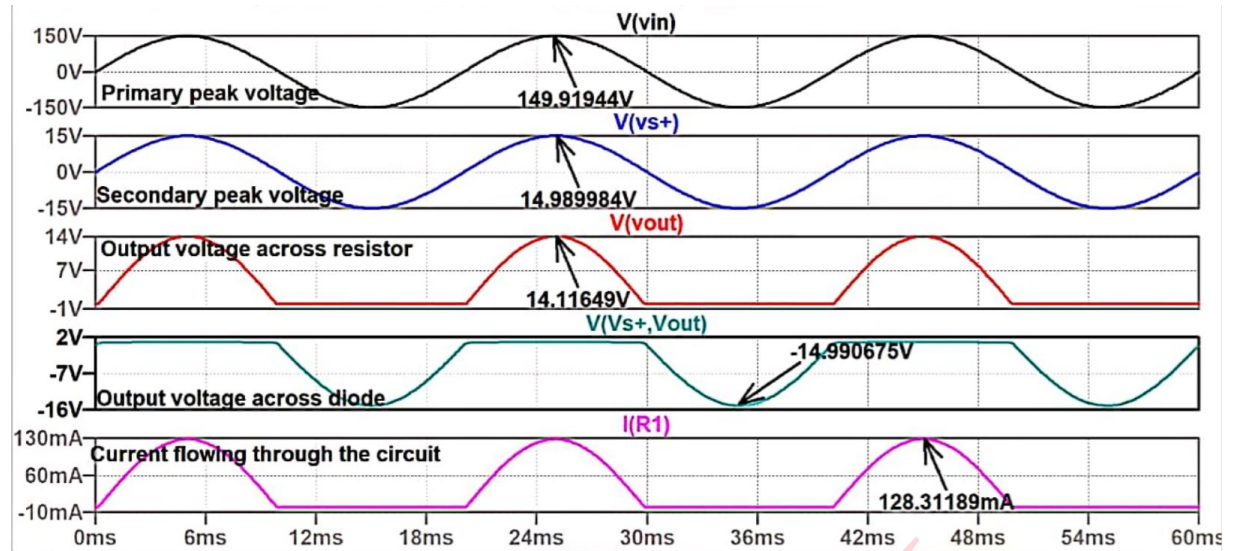


Figure 3: Simulated results

From graph we get,

Output peak voltage = 14.116V

Output peak current = 128.312mA

$$P_{AC} = \frac{V_m^2}{4 \times (R_S + R_L)}$$

$$\therefore P_{AC} = \frac{14.116^2}{4 \times (110)}$$

$$\therefore P_{AC} = 0.4528W$$

$$P_{DC} = \frac{V_m^2}{\pi^2 \times R_L}$$

$$\therefore P_{DC} = \frac{14.116^2}{\pi^2 \times 110}$$

$$\therefore P_{DC} = 0.4528W$$

$$\text{Efficiency} = \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.1835}{0.4528} \times 100$$

$$\text{Efficiency} = 40\%$$

$$\text{Peak inverse voltage(PIV) rating} = -V_m = -14.116V$$

Comparison table between theoretical and simulated values:

Parameter	Theoretical value	Simulated values
V_m	14.3V	14.116V
I_m	130mA	128.312mA
AC power	0.46475W	0.4528W
DC power	0.1884W	0.1835W
Efficiency	40.537%	40.52%
PIV rating	-14.3V	-14.115V

Table 1: Numerical 1

Numerical 2: Simulate a full wave rectifier circuit with input amplitude = $140V_{peak}$, $f = 50\text{Hz}$ and $R_L = 110\Omega$ using LTspice. Select diode as 1N4148. Use 10:1 step down center tap transformer. Find output peak value(V_m), output peak current(I_M), AC power, DC power, efficiency, PIV rating.

Plot the following using LTspice,

- Primary peak voltage.
- Secondary peak voltage.
- Output voltage across resistor.
- Output voltage across diode.
- Current flowing through the diode.
- Current flowing through the circuit.

Solution:

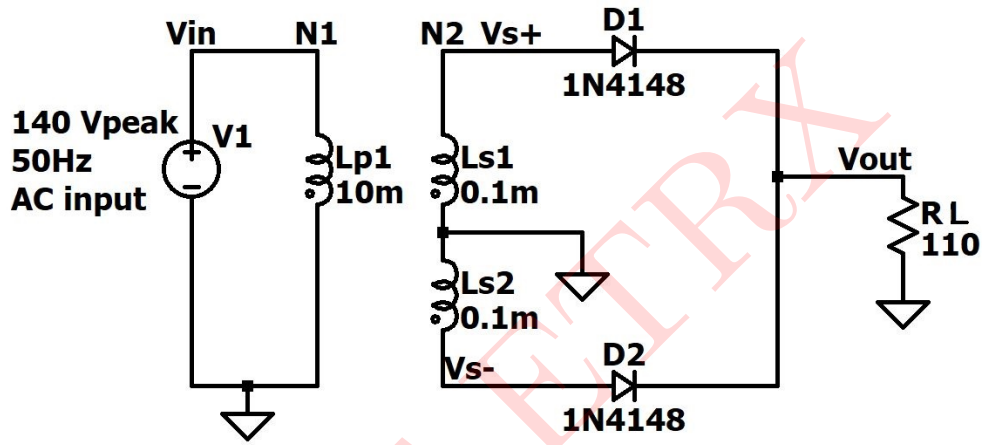


Figure 4: Circuit 2

i] We know that,

$$\frac{V_P}{V_S} = \frac{N_1}{N_2} = \frac{10}{1}$$

$$\therefore \frac{V_P}{V_S} = \frac{10}{1}$$

$$\therefore V_S = 140 \times \frac{1}{10}$$

$$\therefore V_S = 14V$$

ii] By KVL we get,

$$V_{in} - V_{DON} - V_{out} = 0$$

$$\therefore V_{out} = V_{in} - V_{DON} = 14 - 0.7$$

$$\therefore V_{out} = 13.3V$$

i.e $V_m = 13.3V$

$$\text{iii] } I_m = \frac{V_m}{R_S + R_L}$$

Since, $R_S \ll R_L$

$$\therefore I_m = \frac{V_m}{R_L}$$

$$\therefore I_m = \frac{13.3}{110}$$

$$\therefore I_m = 0.1209\text{A} = 120.9\text{mA}$$

$$\text{iv] DC power} = \frac{4 \times V_m^2}{\pi^2 \times R_L}$$

$$\therefore \text{DC power} = \frac{4 \times 13.3^2}{\pi^2 \times 110}$$

$$\therefore \text{DC power} = 0.6517\text{W}$$

$$\text{v] AC power} = \frac{V_m^2}{2 \times (R_S + R_L)}$$

$$\therefore \text{AC power} = \frac{13.3^2}{2 \times 110}$$

$$\therefore \text{AC power} = 0.8040\text{W}$$

$$\text{vi] Efficiency} = \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.6517}{0.8040} \times 100$$

$$\therefore \text{Efficiency} = \eta = 81.06\%$$

$$\text{vii] Peak inverse voltage(PIV) rating} = -2V_m = -26.6\text{V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice. The results are presented below.

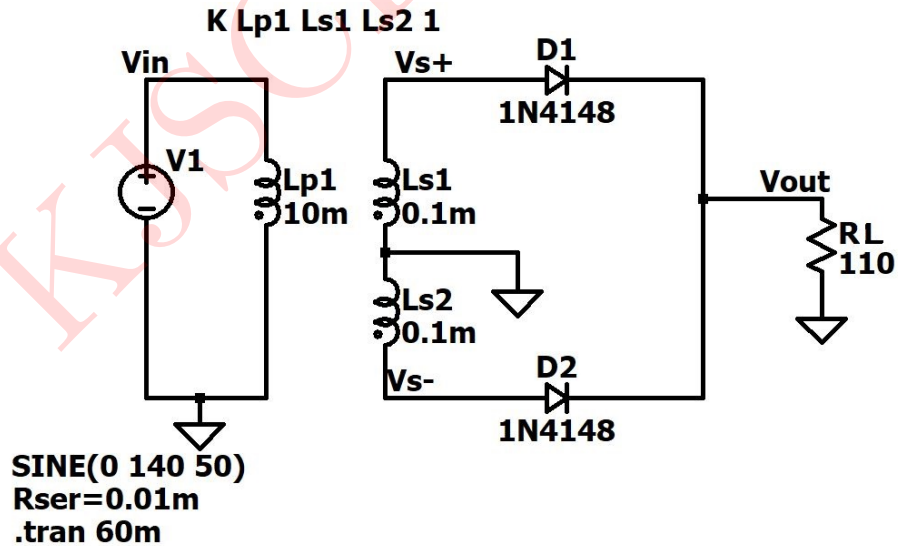


Figure 5: Circuit schematic

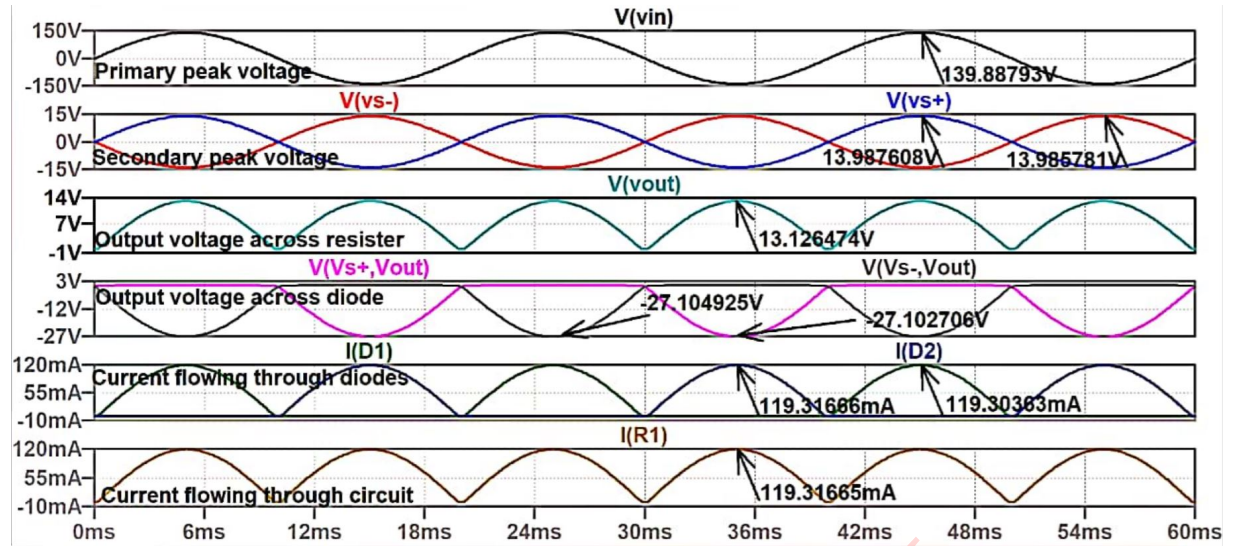


Figure 6: Simulated results

From graph we get,

Output peak voltage = 13.1264V

Output peak current = 119.3165mA

$$P_{AC} = \frac{V_m^2}{2 \times (R_S + R_L)}$$

$$\therefore P_{AC} = \frac{13.1264^2}{2 \times (110)}$$

$$\therefore P_{AC} = 0.7832W$$

$$P_{DC} = \frac{4 \times V_m^2}{\pi^2 \times R_L}$$

$$\therefore P_{DC} = \frac{4 \times 13.1264^2}{\pi^2 \times 110}$$

$$\therefore P_{DC} = 0.6348W$$

$$\text{Efficiency} = \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.6348}{0.7832} \times 100$$

$$\text{Efficiency} = 81.052\%$$

$$\text{Peak inverse voltage(PIV) rating} = -2V_m = -26.2528V$$

Comparison table between theoretical and simulated values:

Parameter	Theoretical value	Simulated values
V_m	13.3V	13.1264V
I_m	120.91mA	119.3165mA
AC power	0.8040W	0.7832W
DC power	0.6517W	0.6348W
Efficiency	81.057%	81.052%
PIV rating	-26.6V	-26.2528V

Table 2: Numerical 2