

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DIODE APPLICATION**

29<sup>th</sup> June, 2020

Numericals

1. For the circuit shown in Figure 1, plot
  - a) Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms
  - b) VTC curve

Given:  $V_{in}(t) = 10V_{p-p}$  sinusoidal signal with frequency 5000 Hz

Use constant voltage model i.e.  $V_{D,on} = 0.7$  V,  $V_B = 1$  V,  $R_1 = 1k\Omega$

 


Figure 1: Clipper circuit

**Solution:**

$$V_{in} = V_m \sin \omega t = 5 \sin(2\pi 5000t) = 5 \sin(10000\pi t)$$

Assuming a constant voltage model for  $D_1$

**Case 1:** If  $V_{in} > (V_{D,on} - V_B)$

$$\text{i.e. } V_{in} > (0.7 - 1)$$

$$\text{i.e. } V_{in} > (-0.3)$$

The diode  $D_1$  is ON, hence Circuit 1 reduces to Circuit 2.

 


Figure 2: Circuit 2

Applying KVL,

$$V_{in} - V_{D,on} + V_B - V_{out} = 0$$

$$\therefore V_{out} = V_{in} - (V_{D,on} - V_B)$$

$$\therefore V_{out} = 5 - (0.7 - 1) = 5.3 \text{ V}$$

$\therefore$  Output tracks input, but with a shift  $(V_{D,on} - V_B)$

**Case 2:** If  $V_{in} < (V_{D,on} - V_B)$

$$\text{i.e } V_{in} < (0.7 - 1)$$

$$\text{i.e } V_{in} < (-0.3)$$

The diode  $D_1$  is OFF, hence the circuit reduces to Circuit 3.

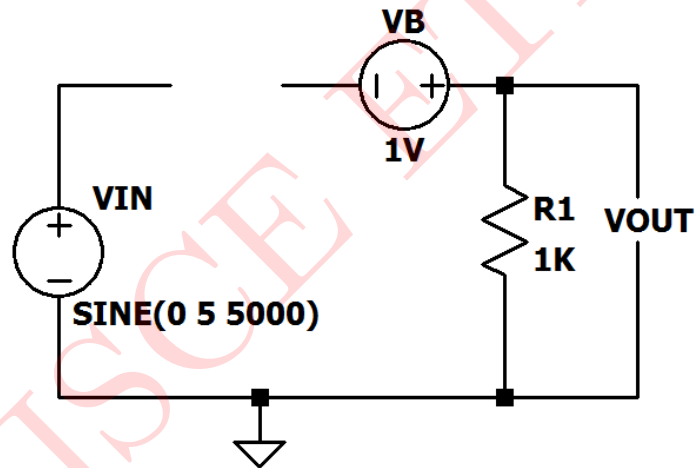


Figure 3: Circuit 3

In Circuit 3, we can observe that  $V_{out} = 0 \text{ V}$

### SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

 


Figure 4: Circuit schematic

The input and output waveforms are shown in Figure 5.

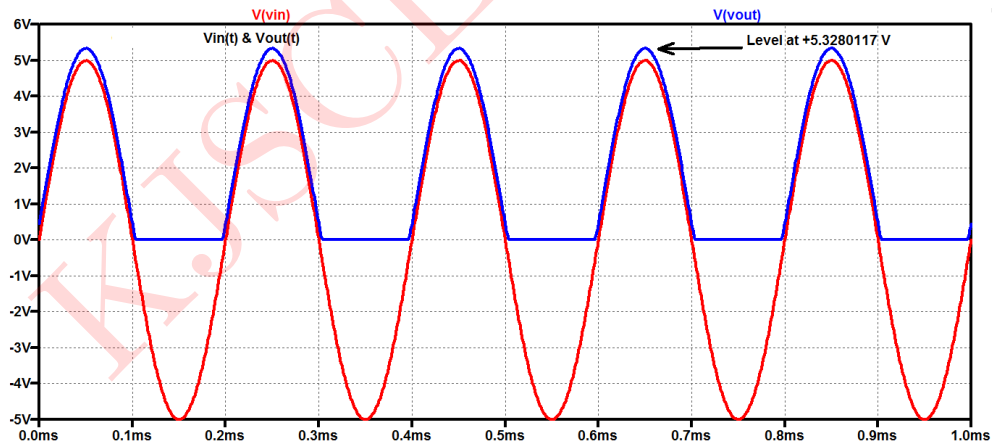


Figure 5: Input and output waveforms

The VTC curve is given below in Figure 6.

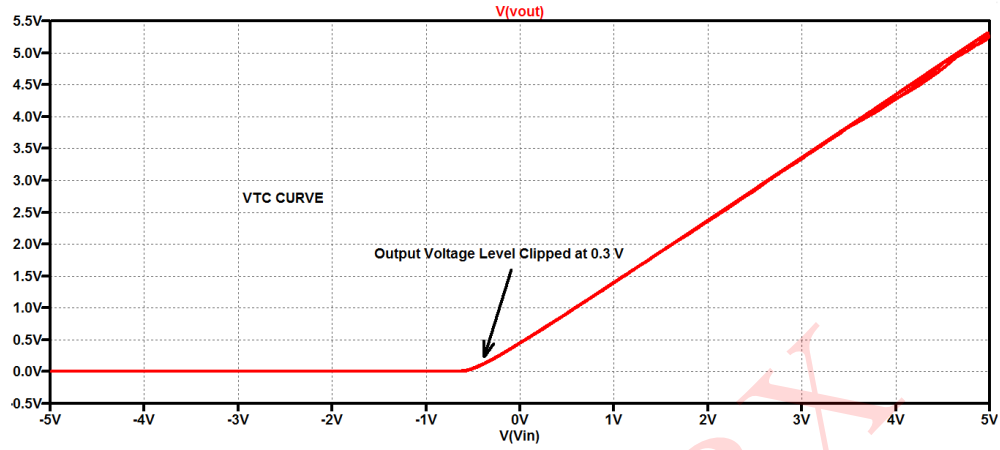


Figure 6: VTC curve

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
Level of clipped voltage	0.3 V	0.3280 V

Table 1: Table 1

2. For the circuit shown in Figure 7, plot input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms  
 Given:  $V_{in}(t) = 20V_{p-p}$  square wave signal with frequency 1000 Hz and  $D_1$  is a silicon diode

 


Figure 7: Clipper circuit

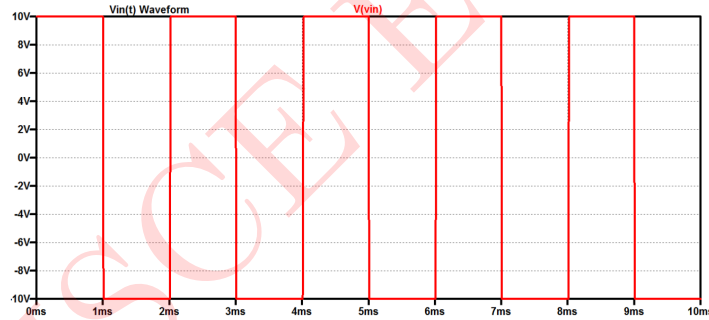


Figure 8: Input signal

**Solution:**

The given diode  $D_1$  is a silicon diode,  $\therefore V_{D,on} = 0.7 \text{ V}$

$$V_{in} = 20V_{p-p}, \therefore V_m = 10 \text{ V}$$

**Case 1:** When  $V_{in} > (V_{D,on} - V_B)$

i.e. when  $V_{in} > (0.7V)$ , the diode  $D_1$  is ON(because the anode voltage of the diode which is connected to  $V_{in}$  is greater than cathode voltage by 0.7, hence the diode will turn on)

$\therefore$  When  $V_{in} > 0.7 \text{ V}$ ,  $D_1$  turns ON and the clipper circuit reduces to Circuit 4.

Applying KVL,

$$V_{in} - V_{D,on} - (I \times R_1) - (I \times R_2) = 0$$

$$\therefore I = \frac{V_{in} - V_{D,on}}{R_1 + R_2}$$

 


Figure 9: Circuit 4

$$\therefore I \times R_2 = V_{out} = \frac{V_{in} - V_{D,on}}{R_1 + R_2} \times R_2$$

$$\therefore V_{out} = \frac{10 - 0.7}{1.2k + 2.2k} \times 1.2k$$

$$\therefore V_{out} = 3.283 \text{ V}$$

**Case 2:** When  $V_{in} < V_{D,on}$

i.e. when  $V_{in} < 0.7$ , the diode  $D_1$  will be OFF

Hence the clipper circuit reduces to Circuit 5.

 


Figure 10: Circuit 5

In Circuit 5, we can observe that  $V_{out} = 0 \text{ V}$

### SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

 


Figure 11: Circuit schematic

The input and output waveforms are shown in Figure 12.

 


Figure 12: Input and output waveforms

### Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
Level of clipped voltage	3.283 V	3.30647 V

Table 2: Table 2

3. For the circuit shown in Figure 1, plot input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms  
 Given:  $V_{in}(t) = 40V_{p-p}$  sinusoidal wave of frequency 1000 Hz  
 $C_1 = 10\mu F$  and  $R_1 = 10k\Omega$   
 Diode  $D_1$  is silicon diode, i.e.  $V_{D,on} = 0.7$  V,  $V_B = 10$  V DC

 


Figure 13: Clamper circuit

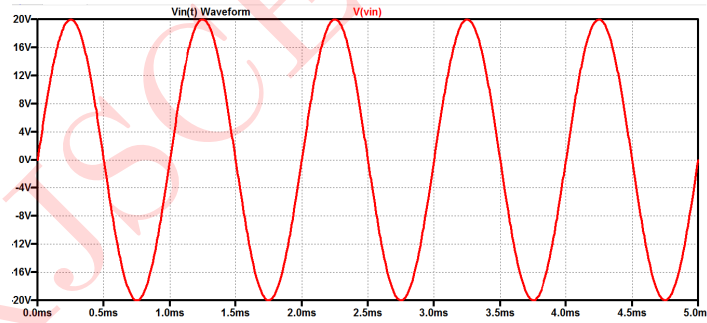


Figure 14: Input signal

**Solution:**

Since the given diode  $D_1$  is a silicon diode,  $\therefore V_{D,on} = 0.7$  V

Given:  $V_{in} = 40V_{p-p}$ ,  $\therefore V_m = 20$  V

Operation:

a) During negative half cycle,  $D_1$  is ON.

When  $V_{in} < (-V_{D,on} + V_B)$ , i.e.  $(-0.7 + 10)$  V, i.e. 9.3 V,  
 Figure 13 reduces to Figure 15.



 


Figure 15: When diode  $D_1$  is ON

Here,  $V_{out} = -V_{D,on} - V_B = -0.7 - 10$

$$\therefore V_{out} = -10.7 \text{ V}$$

b) At the same time, voltage across capacitor  $V_C$  changes to  $-V_m$

Applying KVL,

$$V_{in} - V_C - V_{D,on} + V_B = 0$$

$$\therefore V_C = V_{in} + V_{D,on} + V_B \quad (\text{for negative half cycle})$$

$$\therefore V_C = -V_m + V_{D,on} + V_B = -9.3 \text{ V}$$

c) During positive half cycle, diode  $D_1$  is OFF for the entire positive half cycle, hence Figure 13 reduces to Figure 16.

 


Figure 16: When diode  $D_1$  is OFF

During positive half cycle, capacitor  $C_1$  holds the charge  $V_C = -9.3$  V and acts as a battery.

Applying KVL,

$$V_{in} - V_C - V_{out} = 0$$

$$\therefore V_{out} = V_{in} - V_C$$

$$\therefore V_{out} = 20 - (-9.3) = 29.3 \text{ V} \quad (\text{for positive half cycle})$$

### SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

 


Figure 17: Circuit schematic

The input and output waveforms are shown in Figure 18.

 


Figure 18: Input and output waveforms

The output waveform is shifted above the axis, hence the circuit is a biased positive clamper.

### Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
Positive clamping voltage level	29.3 V	29.18114 V
Negative clamping voltage level	-10.7 V	-10.76083 V

Table 3: Table 3